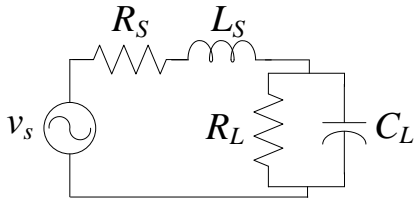


GRAPHICAL EXAMPLES OF UNCONSTRAINED AND CONSTRAINED OPTIMIZATION PROBLEMS

1. Maximizing Power Transfer in a Simple AC Circuit – Unconstrained Problem

Consider the following AC circuit. Assuming that  $R_S = 50 \Omega$ ,  $L_S = 5 \text{ nH}$ ,  $v_s = (1V)\sin 2\pi ft$ , with  $f = 1\text{GHz}$ , we want to find the optimal values of  $R_L$  and  $C_L$  that maximize the power delivered to the load.



From basic circuit theory we know that this problem has a closed form solution. The power delivered to the load is maximum when  $Z_S = Z_L^*$  (load impedance equal to the complex conjugate of the source impedance). Using this fact, the optimal values of  $R_L$  and  $C_L$  at 1GHz are

$$R_L \text{ optimum} = 69.7392 \Omega$$

$$C_L \text{ optimum} = 1.4339 \text{ pF}$$

For which the corresponding impedances are

$$Z_S = 50 + j31.4159 \Omega$$

$$Z_L = 50 - j31.4159 \Omega$$



and the average real power delivered to the load is

$$P_{L\text{max}} = 2.5 \text{ mW}$$

The corresponding optimization problem is  $\mathbf{x}^* = \arg \min u(\mathbf{x})$ . The optimization variables are

$\mathbf{x} = [R_L \ C_L]^T$ . Since we want to maximize the power at the load,  $u(\mathbf{x}) = -P_L$ , where  $P_L = \frac{1}{2} \text{Re}\{V_L I_L^*\}$

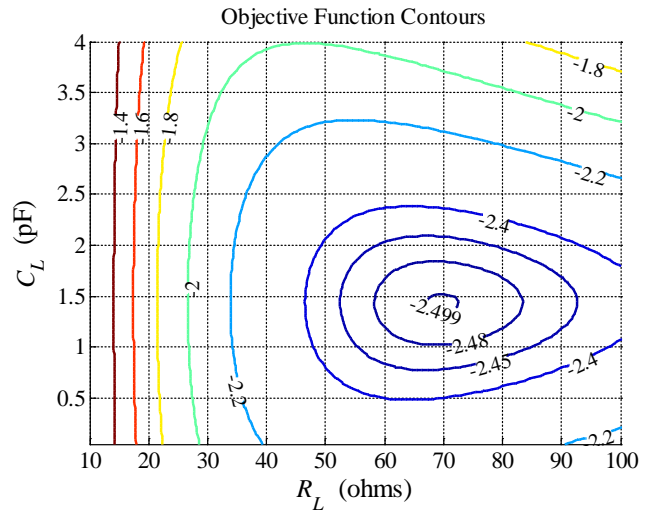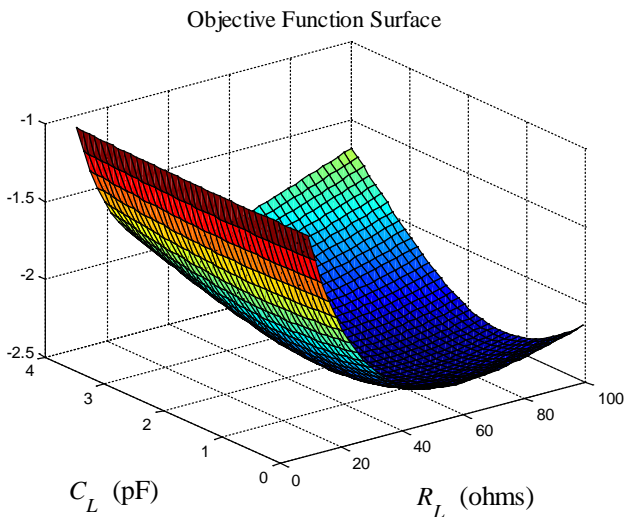and  $V_L(\mathbf{x}) = I_L Z_L$ ,  $I_L(\mathbf{x}) = \frac{V_S}{Z_S + Z_L}$ ,  $Z_S = R_S + j2\pi f L_S$ ,  $Z_L = \frac{R_L}{1 + j2\pi f R_L C_L}$ .




It is seen that the graphical solution of the optimization problem agrees with the theoretical solution.
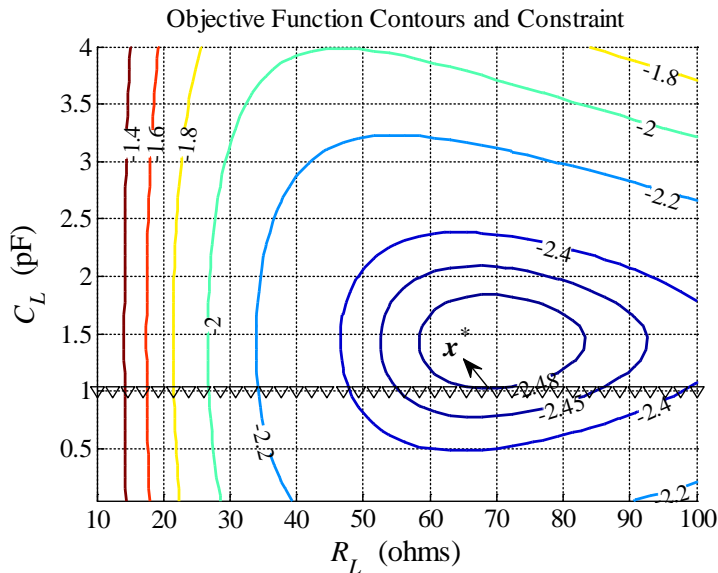
## 2. Maximizing Power Transfer in a Simple AC Circuit – Adding Box Constraints

Let us assume that we want to solve the same problem but now considering a maximum load capacitance  $C_{L\max} = 1$  pF. The new optimization problem is

$$\begin{aligned} \mathbf{x}^* &= \arg \min_{\mathbf{x}} u(\mathbf{x}) && \text{with } u(\mathbf{x}) = -P_L, \quad \mathbf{x} = [R_L \quad C_L]^T, \quad P_L = \frac{1}{2} \text{Re}\{V_L I_L^*\}, \quad V_L(\mathbf{x}) = I_L Z_L, \\ &\text{subject to} && I_L(\mathbf{x}) = \frac{V_S}{Z_S + Z_L}, \quad Z_S = R_S + j2\pi f L_S, \quad \text{and } Z_L(\mathbf{x}) = \frac{R_L}{1 + j2\pi f R_L C_L}. \\ &x_2 \leq C_{L\max} \end{aligned}$$




Zooming in the graphical solution it is seen that  $\mathbf{x}^* \approx [68.5\Omega \quad 1\text{pF}]^T$ .

We can remove the box constraints through variable transformations, as follows,

$$\mathbf{z}^* = \arg \min_{\mathbf{z}} u(\mathbf{z}) \quad \text{where } u(\mathbf{z}) = u(\mathbf{x}) \text{ with } x_1 = z_1 \text{ and } x_2 = C_{L\max} - z_2^2.$$

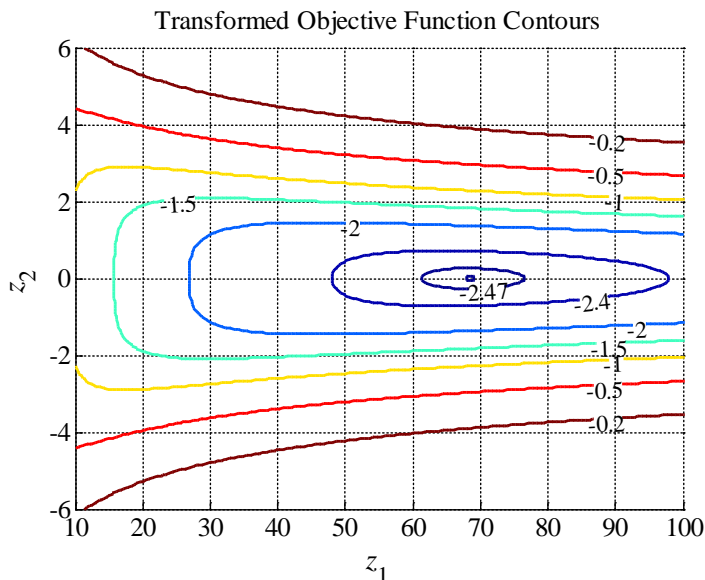The contours of the new unconstrained objective are:




Zooming in the graphical solution it is seen that  $\mathbf{z}^* \approx [68.5\Omega \quad 0]^T$ , which corresponds to  $\mathbf{x}^* \approx [68.5\Omega \quad 1\text{pF}]^T$ .

The optimal response at the constrained solution is  $P_{L\max} = 2.4778$  mW.

### 3. Maximizing Power Transfer in a Simple AC Circuit – Adding Inequality Constraints

Let us assume that we want to solve the same problem but now restricted to a magnitude of the load admittance larger than  $25\text{m}\Omega^{-1}$ , that is,  $|Y_L| \geq Y_{L\min} = 25\text{m}\Omega^{-1}$ . The new optimization problem is

$$\begin{aligned} \mathbf{x}^* &= \arg \min_{\mathbf{x}} u(\mathbf{x}) && \text{with } u(\mathbf{x}) = -P_L, \quad \mathbf{x} = [R_L \quad C_L]^T, \quad P_L = \frac{1}{2} \text{Re}\{V_L I_L^*\}, \quad V_L(\mathbf{x}) = I_L Z_L, \\ &\text{subject to} && I_L(\mathbf{x}) = \frac{V_S}{Z_S + Z_L}, \quad Z_S = R_S + j2\pi f L_S, \quad Z_L(\mathbf{x}) = \frac{R_L}{1 + j2\pi f R_L C_L}, \text{ and} \\ &g(\mathbf{x}) \leq 0 && g(\mathbf{x}) = Y_{L\min} - |1/Z_L(\mathbf{x})|, \quad Y_{L\min} = 25\text{m}\Omega^{-1}. \end{aligned}$$

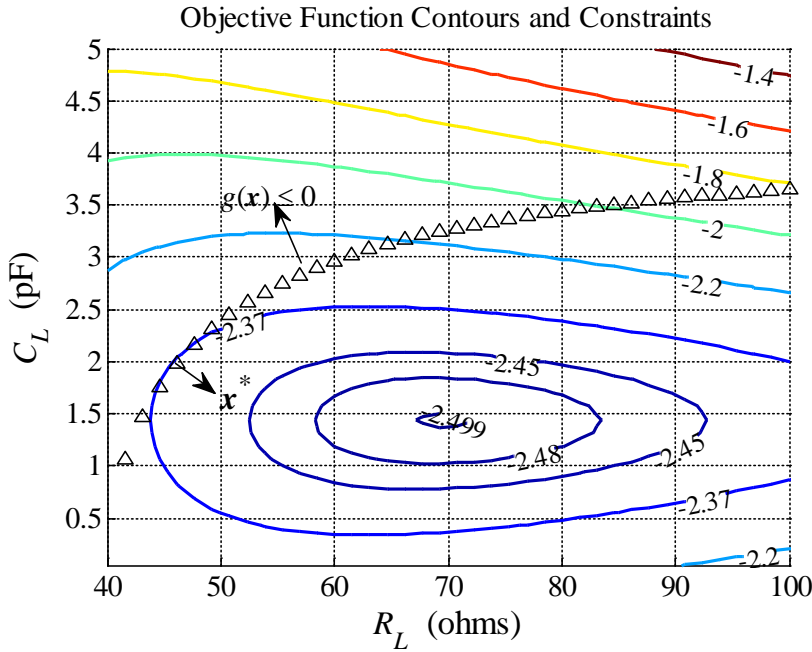


Zooming in the graphical solution it is seen that  $\mathbf{x}^* \approx [46.1\Omega \quad 1.97\text{pF}]^T$ .

The above problem can be solved as an unconstrained optimization problem using penalty functions. The new objective function is

$$\begin{aligned} U(\mathbf{x}) &= u(\mathbf{x}) + r^g (G(\mathbf{x}))^2 && \text{with } u(\mathbf{x}) = -P_L, \quad \mathbf{x} = [R_L \quad C_L]^T, \quad P_L = \frac{1}{2} \text{Re}\{V_L I_L^*\}, \quad V_L(\mathbf{x}) = I_L Z_L, \\ &&& I_L(\mathbf{x}) = \frac{V_S}{Z_S + Z_L}, \quad Z_S = R_S + j2\pi f L_S, \quad Z_L(\mathbf{x}) = \frac{R_L}{1 + j2\pi f R_L C_L}, \text{ and} \\ &&& G = \max\{0, g(\mathbf{x})\}, \\ &&& g(\mathbf{x}) = Y_{L\min} - |1/Z_L(\mathbf{x})|, \\ &&& Y_{L\min} = 25\text{m}\Omega^{-1}. \end{aligned}$$

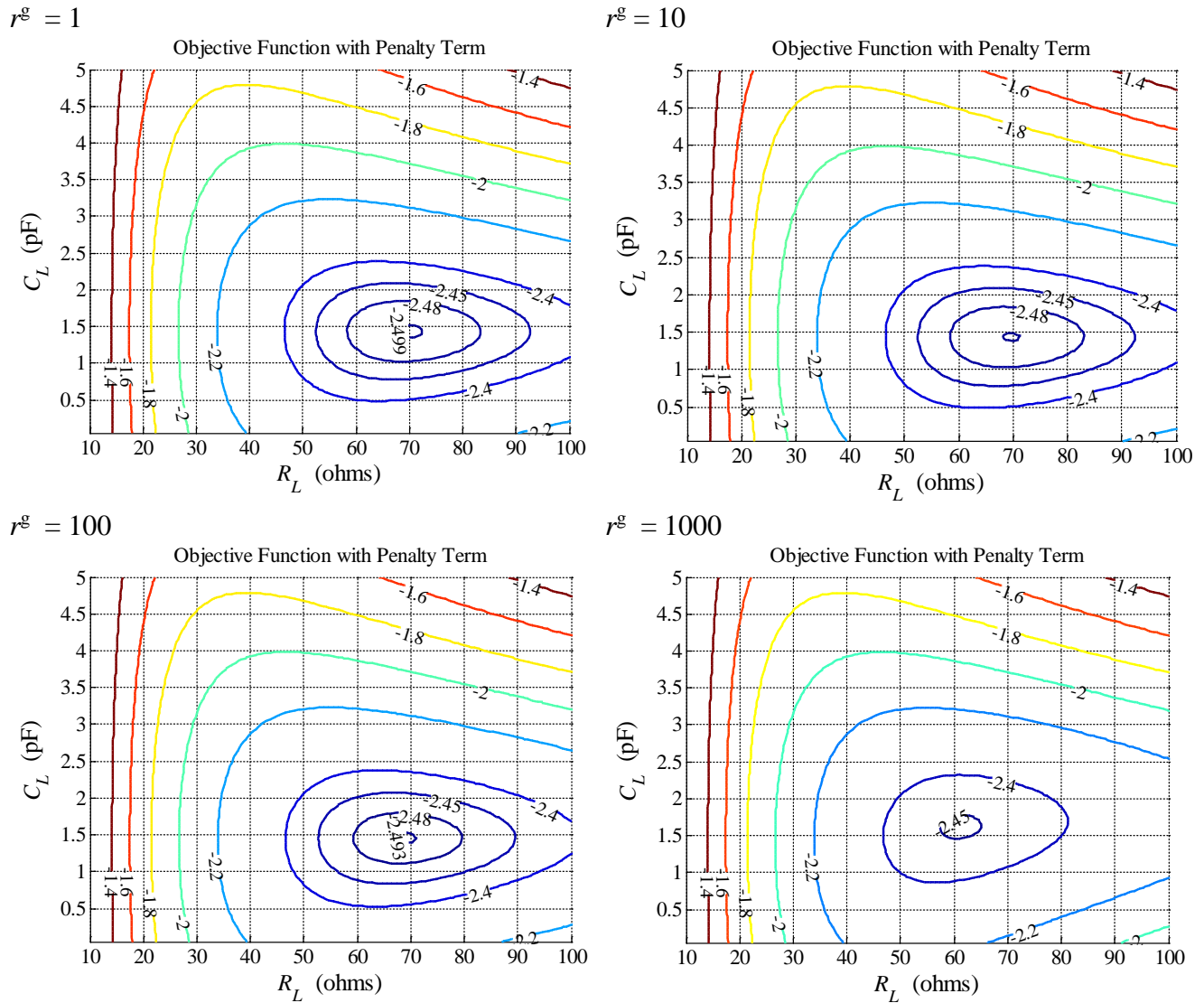The optimal solution found,  $\mathbf{x}^*$ , depends on the value of the penalty term  $r^g$ , as illustrated in the following contours of  $U(\mathbf{x})$ :



The values used above for the penalty coefficient  $r^g$  are too small. This makes that the overall objective function  $U(\mathbf{x})$  does not “see” the effects of the inequality constraint  $g(\mathbf{x})$ .


This problem illustrates how an arbitrary selection of the initial penalty coefficient  $r^g$  can yield an important amount of unnecessary unconstrained optimizations before we reach the solution.

The effect of selecting a better initial penalty coefficient  $r^g$  is now illustrated with two starting points.

a) Let us assume that the starting point is  $\mathbf{x}_0 \approx [90\Omega \quad 4.5\text{pF}]^T$  (an interior point). Then  $u(\mathbf{x}_0) = -1.5638$ ,  $g(\mathbf{x}_0) = -0.0054$ . A better way to choose the initial  $r^g$  is

$$r_0^g = \frac{|u(\mathbf{x}_0)|}{\|g(\mathbf{x}_0)\|_2^2} = \frac{1.5638}{(0.0054)^2} = 53,628$$

Using  $r^g = 53,628$

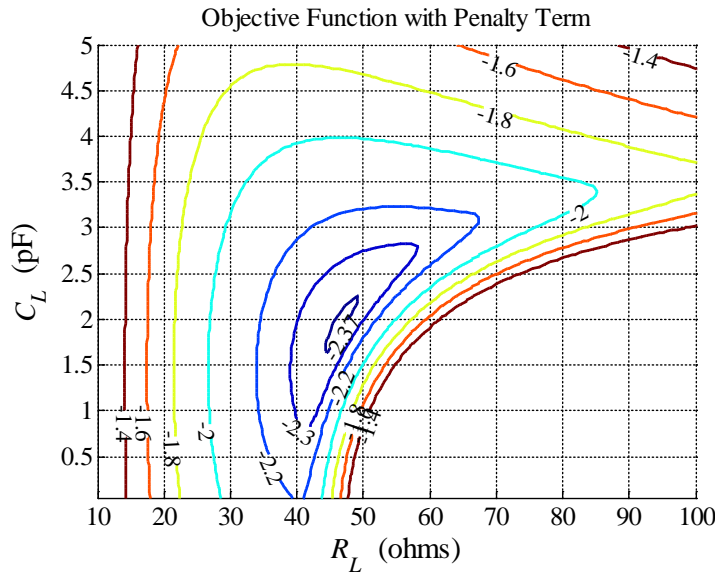


Zooming in the graphical solution it is seen that  $\mathbf{x}^* \approx [46.1\Omega \quad 1.97\text{pF}]^T$ .

b) Let us assume that the starting point is  $\mathbf{x}_0 \approx [70\Omega \quad 1\text{pF}]^T$  (an exterior point). Then  $u(\mathbf{x}_0) = -2.2546$ ,  $g(\mathbf{x}_0) = 0.0094$ . Recalculating the initial  $r^g$ ,

$$r_0^g = \frac{|u(\mathbf{x}_0)|}{\|g(\mathbf{x}_0)\|_2^2} = \frac{2.2546}{(0.0094)^2} = 25,516.$$

Using  $r^g = 25,516$

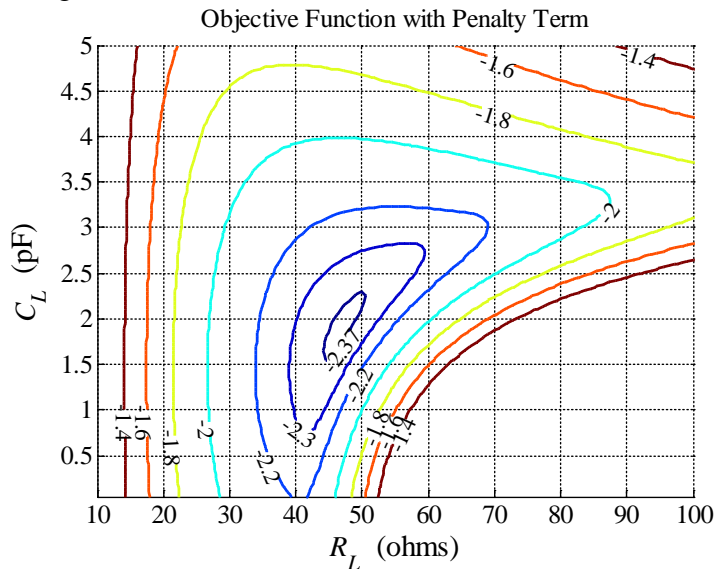

Zooming in the graphical solution it is seen that  $\mathbf{x}^* \approx [46.1\Omega \quad 1.97\text{pF}]^T$ .