
Frequency Response

(Part 1)

A diagram of this presentation was taken from the web site of the author of the book:

A.R. Hambley, *Electronics: A Top-Down Approach to Computer-Aided Circuit Design*. Englewood Cliffs, NJ: Prentice Hall, 2000.

s-Domain Analysis

Voltage gain as a transfer function of the complex frequency $s = j\omega$

$$T(s) \equiv \frac{v_o(s)}{v_i(s)}$$

$$T(s) = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_1 s + a_0}{s^n + b_{n-1} s^{n-1} + \dots + b_1 s + b_0}$$

n is the order of the circuit ($m < n$)

for a stable circuit, all the roots of the denominator polynomial must have negative real parts

s -Domain Analysis (cont.)


Poles and Zeros

$$T(s) = a_m \frac{(s - Z_1)(s - Z_2) \cdots (s - Z_m)}{(s - P_1)(s - P_2) \cdots (s - P_n)}$$

Z_1, \dots, Z_m are the transfer function zeros, or transmission zeros

P_1, \dots, P_m are the transfer function poles, transmission poles or natural modes

The Amplifier Transfer Function

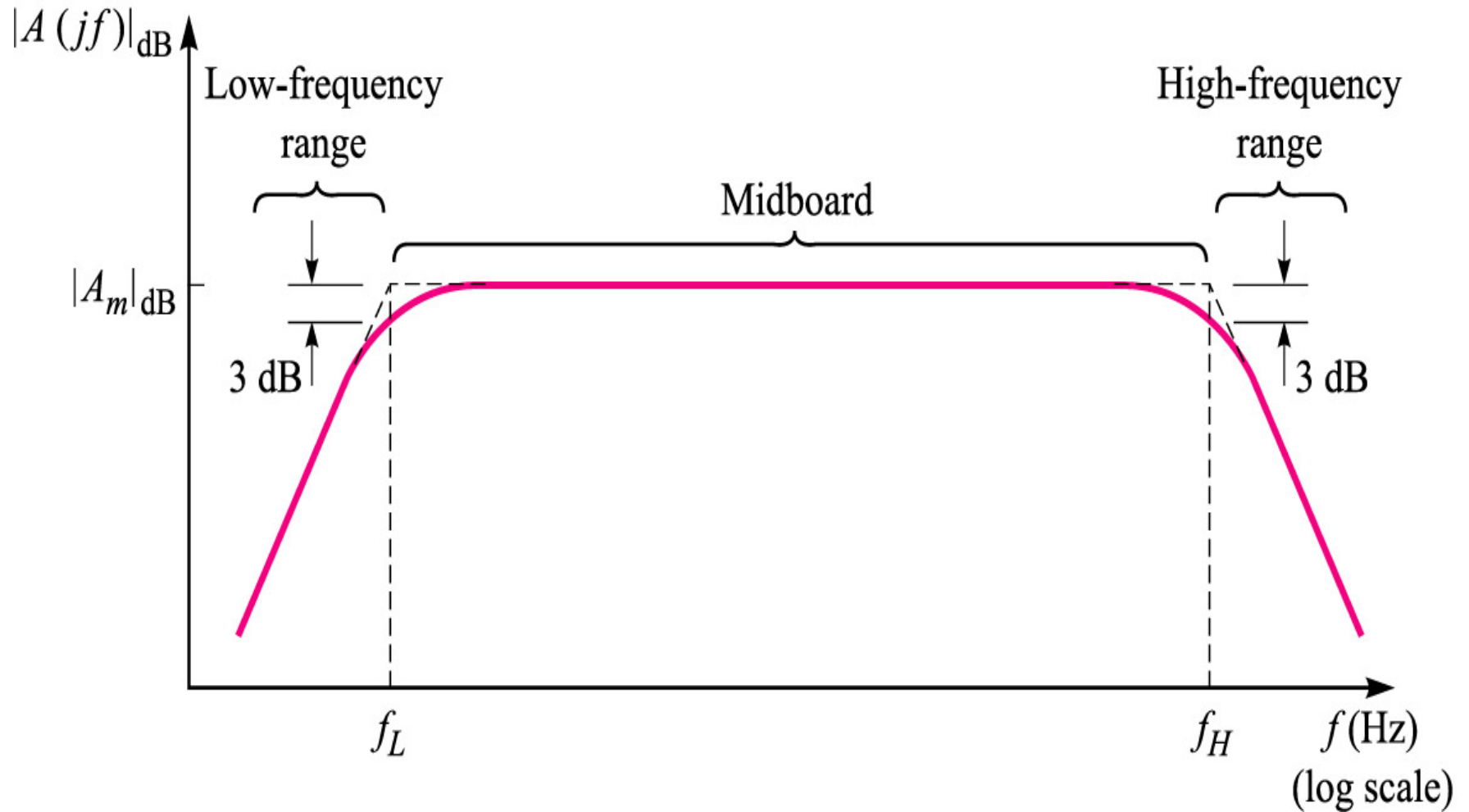

The Amplifier Transfer Function (continue)

A_M midband gain

ω_L cutoff low frequency, 3-dB low frequency

ω_H cutoff high frequency, 3-dB high frequency

Bandwidth (BW)

$$BW = f_H - f_L \quad (\text{Hz})$$

$$BW = \omega_H - \omega_L \quad (\text{rad/sec})$$

usually $\omega_H \gg \omega_L$, $BW \approx \omega_H$

Gain-Bandwidth Product (GB)

$$GB = A_M \omega_H$$

The Gain Function

$$A(s) = \frac{v_o(s)}{v_i(s)} = A_M F_L(s) F_H(s)$$

A_M midband gain

$F_L(s)$ low frequency response

$F_H(s)$ high frequency response

When $\omega_H \gg \omega \gg \omega_L$, $A(s) \approx A_M$

When $\omega \gg \omega_L$, $F_L(s) \approx 1$

When $\omega \ll \omega_H$, $F_H(s) \approx 1$

Low Frequency Response

$$F_L(s) = \frac{(s + \omega_{Z1})(s + \omega_{Z2}) \cdots (s + \omega_{Zn_L})}{(s + \omega_{P1})(s + \omega_{P2}) \cdots (s + \omega_{Pn_L})}$$

n_L number of poles (or zeros) of $F_L(s)$

$$|F_L(j\omega)|^2 = \frac{(\omega^2 + \omega_{Z1}^2)(\omega^2 + \omega_{Z2}^2) \cdots (\omega^2 + \omega_{Zn_L}^2)}{(\omega^2 + \omega_{P1}^2)(\omega^2 + \omega_{P2}^2) \cdots (\omega^2 + \omega_{Pn_L}^2)}$$

$$\lim_{\omega \rightarrow \infty} |F_L(j\omega)| = 1$$

$$\lim_{\omega \rightarrow 0} |F_L(j\omega)| = \sqrt{\frac{\omega_{Z1}^2 \omega_{Z2}^2 \cdots \omega_{Zn_L}^2}{\omega_{P1}^2 \omega_{P2}^2 \cdots \omega_{Pn_L}^2}} \quad \exists i \ni \omega_{Zi} = 0, \lim_{\omega \rightarrow 0} |F_L(j\omega)| = 0$$

Low Frequency Response (cont)

$$F_L(s) = \frac{(s + \omega_{Z1})(s + \omega_{Z2}) \cdots (s + \omega_{Zn_L})}{(s + \omega_{P1})(s + \omega_{P2}) \cdots (s + \omega_{Pn_L})}$$

$$\omega_{P1}, \dots, \omega_{Pn_L} > 0$$

if $\omega_{P1} \gg \omega_{P2}, \dots, \omega_{Pn_L}, \omega_{Z1}, \dots, \omega_{Zn_L}$ then

$$F_L(s) \approx \frac{s}{(s + \omega_{P1})} \quad \text{and} \quad \omega_L \approx \omega_{P1} \quad (\omega_{P1} \text{ is a dominant pole})$$

What if there is no dominant pole?

Low Frequency Response - No Dominant Pole

$$F_L(s) = \frac{(s + \omega_{Z1})(s + \omega_{Z2})}{(s + \omega_{P1})(s + \omega_{P2})} \quad |F_L(j\omega)|^2 = \frac{(\omega^2 + \omega_{Z1}^2)(\omega^2 + \omega_{Z2}^2)}{(\omega^2 + \omega_{P1}^2)(\omega^2 + \omega_{P2}^2)}$$

$$\text{Como } |F_L(j\omega_L)|^2 = \frac{1}{2} \quad \frac{(\omega_L^2 + \omega_{Z1}^2)(\omega_L^2 + \omega_{Z2}^2)}{(\omega_L^2 + \omega_{P1}^2)(\omega_L^2 + \omega_{P2}^2)} = \frac{1}{2}$$

$$\frac{\omega_L^4 + \omega_L^2(\omega_{Z1}^2 + \omega_{Z2}^2) + \omega_{Z1}^2\omega_{Z2}^2}{\omega_L^4 + \omega_L^2(\omega_{P1}^2 + \omega_{P2}^2) + \omega_{P1}^2\omega_{P2}^2} = \frac{1}{2}$$

$$\frac{1 + (1/\omega_L^2)(\omega_{Z1}^2 + \omega_{Z2}^2) + (1/\omega_L^4)\omega_{Z1}^2\omega_{Z2}^2}{1 + (1/\omega_L^2)(\omega_{P1}^2 + \omega_{P2}^2) + (1/\omega_L^4)\omega_{P1}^2\omega_{P2}^2} = \frac{1}{2} \approx \frac{1 + (1/\omega_L^2)(\omega_{Z1}^2 + \omega_{Z2}^2)}{1 + (1/\omega_L^2)(\omega_{P1}^2 + \omega_{P2}^2)}$$

$$(1/\omega_L^2)[\omega_{P1}^2 + \omega_{P2}^2 - 2(\omega_{Z1}^2 + \omega_{Z2}^2)] = 1$$

$$\omega_L \approx \sqrt{\omega_{P1}^2 + \omega_{P2}^2 - 2(\omega_{Z1}^2 + \omega_{Z2}^2)}$$

Low Frequency Response - No Dominant Pole

$$F_L(s) = \frac{(s + \omega_{Z1})(s + \omega_{Z2}) \cdots (s + \omega_{Zn_L})}{(s + \omega_{P1})(s + \omega_{P2}) \cdots (s + \omega_{Pn_L})}$$

If there is no dominant pole

$$\omega_L \approx \sqrt{\omega_{P1}^2 + \omega_{P2}^2 + \dots + \omega_{Pn_L}^2 - 2(\omega_{Z1}^2 + \omega_{Z2}^2 + \dots + \omega_{Zn_L}^2)}$$

High Frequency Response

$$F_H(s) = \frac{(1 + s/\omega_{Z1})(1 + s/\omega_{Z2}) \cdots (1 + s/\omega_{Zn_H})}{(1 + s/\omega_{P1})(1 + s/\omega_{P2}) \cdots (1 + s/\omega_{Pn_H})}$$

n_H number of poles (or zeros) of $F_H(s)$

$$|F_H(j\omega)|^2 = \frac{[1 + (\omega/\omega_{Z1})^2][1 + (\omega/\omega_{Z2})^2] \cdots [1 + (\omega/\omega_{Zn_H})^2]}{[1 + (\omega/\omega_{P1})^2][1 + (\omega/\omega_{P2})^2] \cdots [1 + (\omega/\omega_{Pn_H})^2]}$$

$$\lim_{\omega \rightarrow 0} |F_H(j\omega)| = 1$$

$$\lim_{\omega \rightarrow \infty} |F_H(j\omega)| = \sqrt{\frac{\omega_{P1}^2 \omega_{P2}^2 \cdots \omega_{Pn_L}^2}{\omega_{Z1}^2 \omega_{Z2}^2 \cdots \omega_{Zn_L}^2}} \quad \exists i \ni \omega_{Zi} = \infty, \lim_{\omega \rightarrow \infty} |F_H(j\omega)| = 0$$

High Frequency Response (cont)

$$F_H(s) = \frac{(1 + s/\omega_{Z1})(1 + s/\omega_{Z2}) \cdots (1 + s/\omega_{Zn_H})}{(1 + s/\omega_{P1})(1 + s/\omega_{P2}) \cdots (1 + s/\omega_{Pn_H})}$$



if $\omega_{P1} \ll \omega_{P2}, \dots, \omega_{Pn_L}, \omega_{Z1}, \dots, \omega_{Zn_L}$ then

$$F_H(s) \approx \frac{1}{(1 + s/\omega_{P1})} \quad \text{and} \quad \omega_H \approx \omega_{P1} \quad (\omega_{P1} \text{ is a dominant pole})$$

If there is no dominant pole

$$\omega_H \approx \frac{1}{\sqrt{1/\omega_{P1}^2 + 1/\omega_{P2}^2 + \dots + 1/\omega_{Pn_H}^2 - 2(1/\omega_{Z1}^2 + 1/\omega_{Z2}^2 + \dots + 1/\omega_{Zn_H}^2)}}$$


Example: Common Source Low Frequency

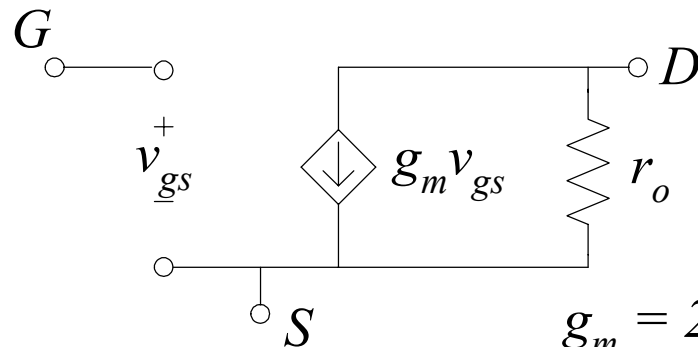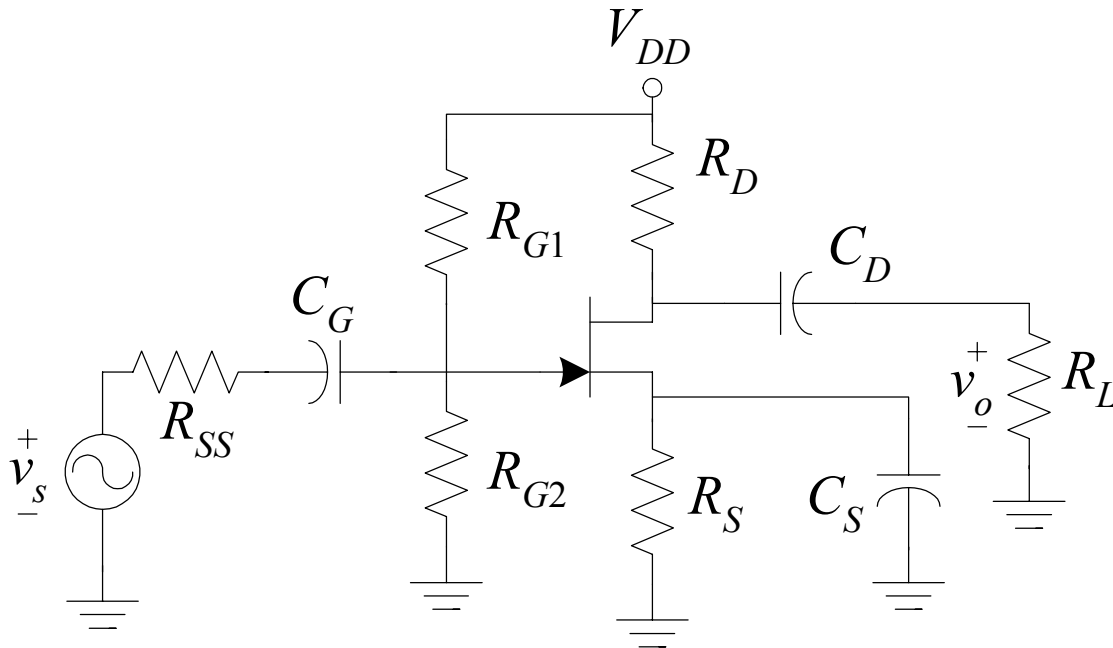

$$g_m = 2K(V_{GS} - V_t)$$

$$r_o = V_A/I_D = 1/\lambda I_D$$

Example (cont)

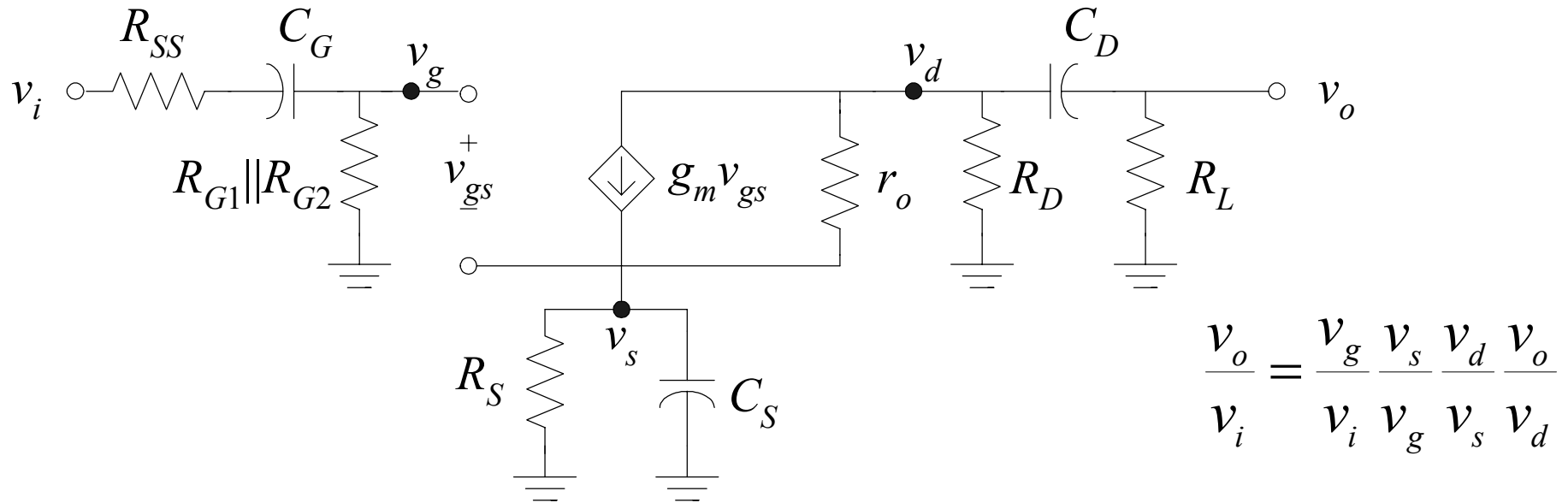


$$\frac{v_o}{v_i} = \frac{v_g}{v_i} \frac{v_s}{v_g} \frac{v_d}{v_s} \frac{v_o}{v_d}$$

$$v_g = \frac{(R_{G1} \parallel R_{G2})v_i}{R_{SS} + (R_{G1} \parallel R_{G2}) + 1/sC_G}$$

$$\frac{v_g}{v_i} = \frac{(R_{G1} \parallel R_{G2})C_G s}{1 + [R_{SS} + (R_{G1} \parallel R_{G2})]C_G s}$$

Example (cont)

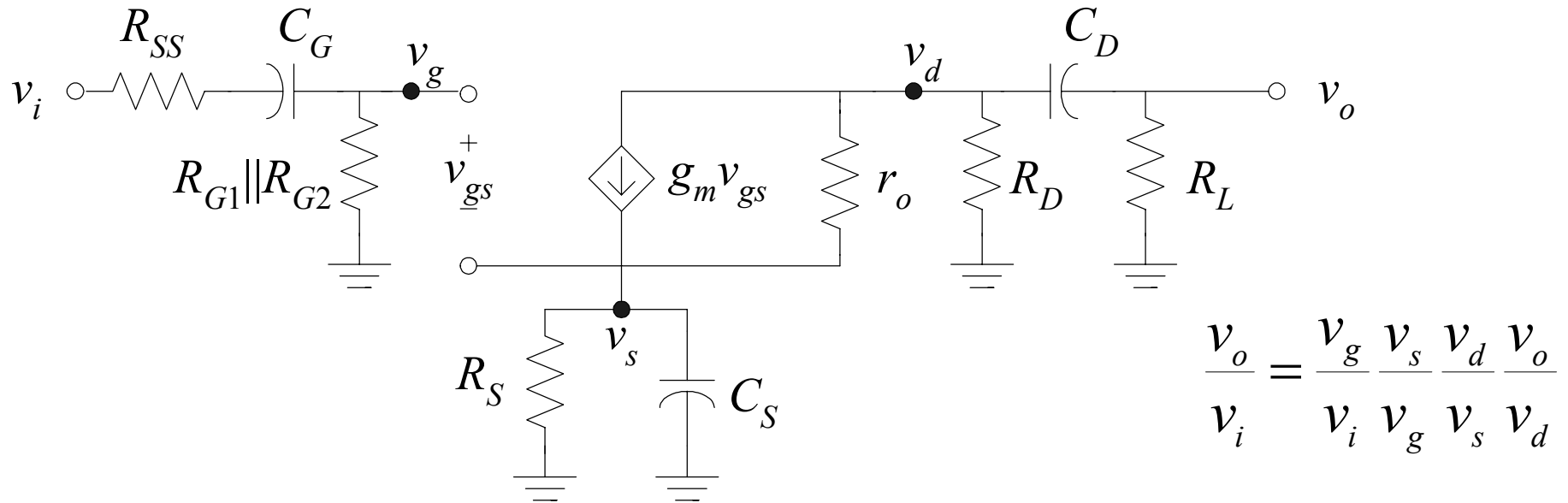


$$\frac{v_o}{v_i} = \frac{v_g}{v_i} \frac{v_s}{v_g} \frac{v_d}{v_s} \frac{v_o}{v_d}$$

$$v_o = \frac{R_L v_d}{R_L + 1/sC_D}$$

$$\frac{v_o}{v_d} = \frac{R_L C_D s}{1 + R_L C_D s}$$

Example (cont)

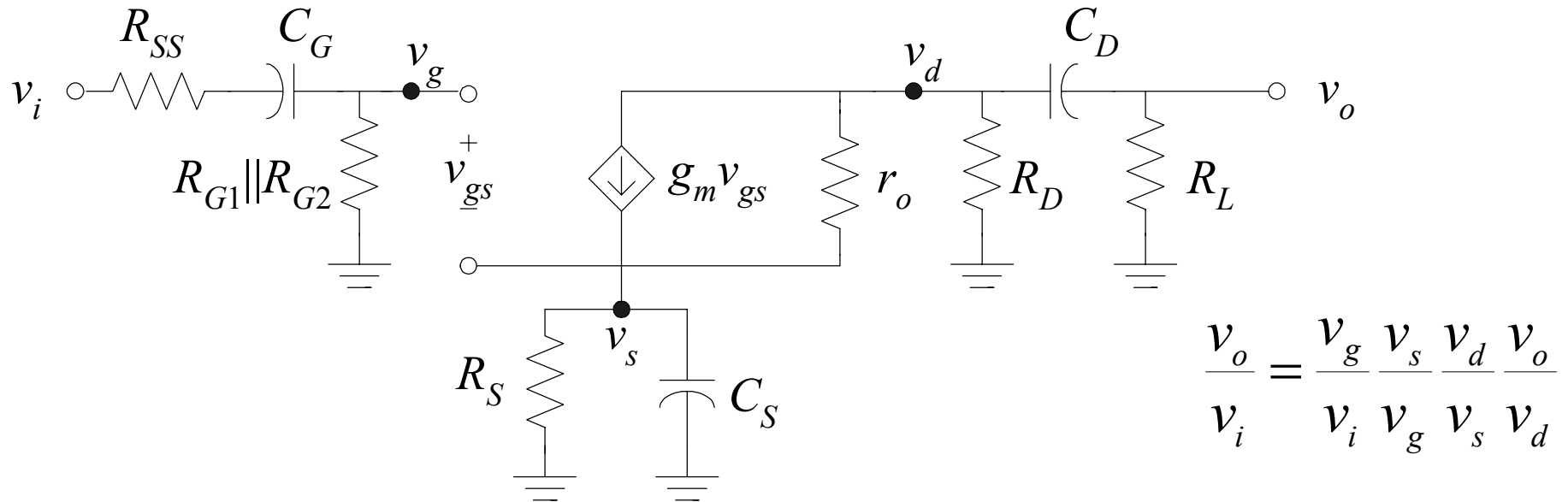


$$\frac{v_o}{v_i} = \frac{v_g}{v_i} \frac{v_s}{v_g} \frac{v_d}{v_s} \frac{v_o}{v_d}$$

$$v_s = i_s Z_s \quad Z_s = R_S \parallel \frac{1}{sC_S} = \frac{(R_S)(1/sC_S)}{R_S + 1/sC_S} \quad Z_s = \frac{R_S}{1 + R_S C_S s}$$

$$v_d = -i_s Z_d \quad Z_d = R_D \parallel \left(\frac{1}{sC_D} + R_L \right) \quad Z_d = \frac{R_D (1 + R_L C_D s)}{1 + (R_D + R_L) C_D s} \quad \frac{v_d}{v_s} = \frac{-Z_d}{Z_s}$$

Example (cont)

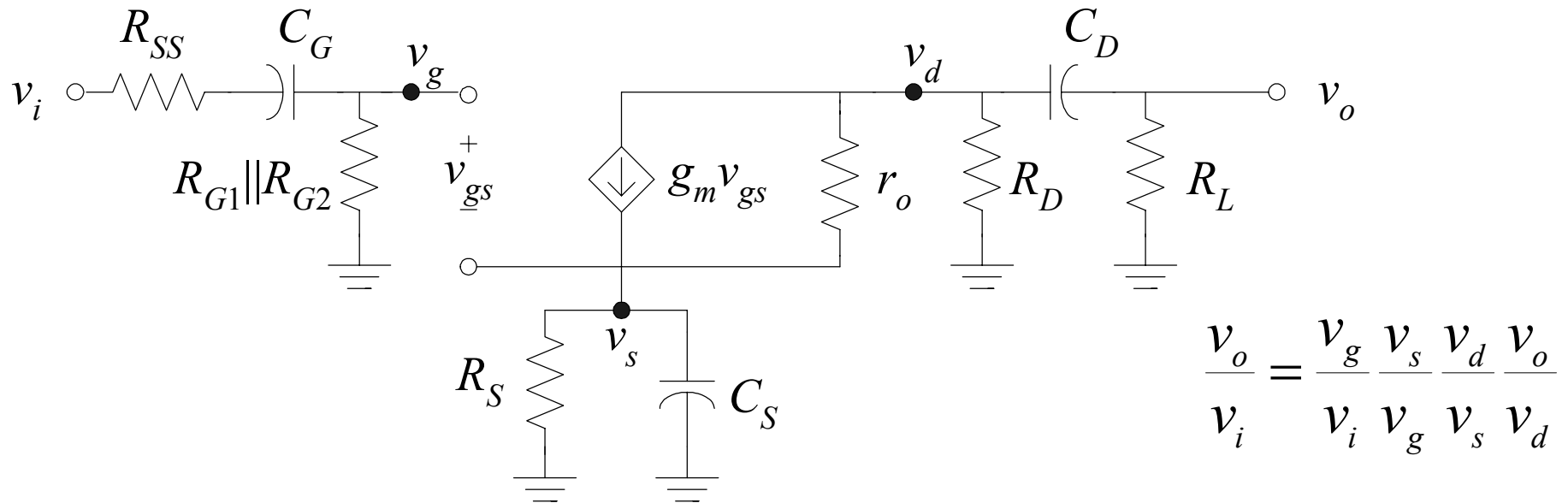

$$\frac{v_o}{v_i} = \frac{v_g}{v_i} \frac{v_s}{v_g} \frac{v_d}{v_s} \frac{v_o}{v_d}$$


$$\frac{v_d}{v_s} = \frac{-Z_d}{Z_s}$$

$$Z_s = \frac{R_S}{1 + R_S C_S s}$$

$$Z_d = \frac{R_D (1 + R_L C_D s)}{1 + (R_D + R_L) C_D s}$$

$$\frac{v_d}{v_s} = \frac{-R_D (1 + R_S C_S s)(1 + R_L C_D s)}{R_S (1 + (R_D + R_L) C_D s)}$$

Example (cont)

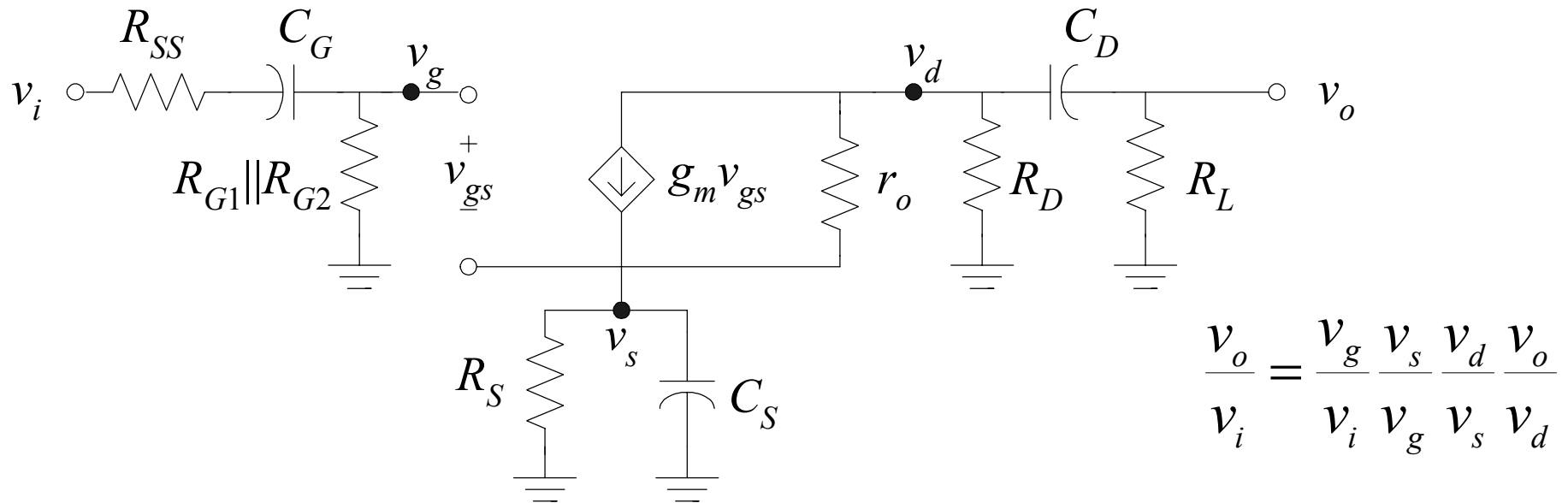


$$v_s = i_s Z_s = [g_m v_{gs} + (v_d - v_s)/r_o] Z_s = [g_m v_g + v_d/r_o - v_s(g_m + 1/r_o)] Z_s$$

$$\text{Como } r_o \gg \frac{1}{g_m}, \quad v_s \approx [g_m v_g + v_d/r_o - v_s g_m] Z_s$$

$$\text{Como } \frac{v_d}{v_s} = \frac{-Z_d}{Z_s}, \quad v_s (1 + g_m Z_s + Z_d/r_o) \approx g_m Z_s v_g$$

Example (cont)

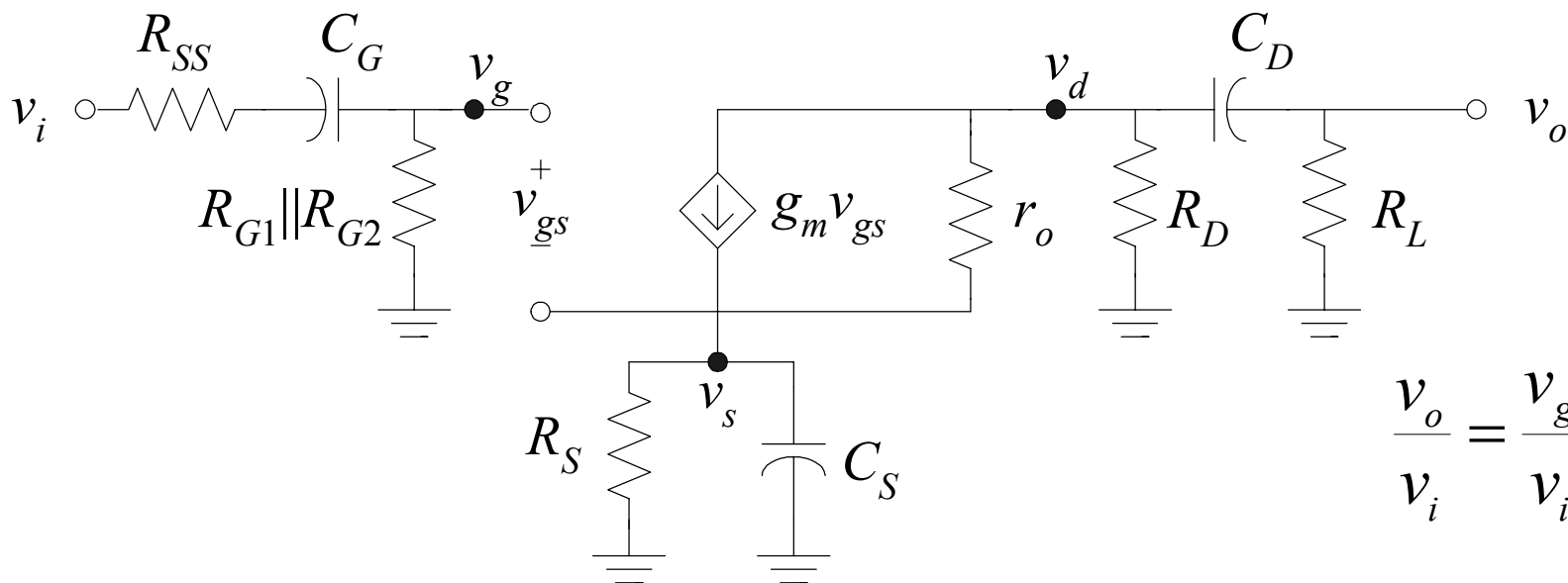

$$\frac{v_o}{v_i} = \frac{v_g}{v_i} \frac{v_s}{v_g} \frac{v_d}{v_s} \frac{v_o}{v_d}$$

$$v_s (1 + g_m Z_s + Z_d / r_o) \approx g_m Z_s v_g$$

Si $g_m Z_s \gg Z_d / r_o$,

$$\frac{v_s}{v_g} \approx \frac{g_m Z_s}{1 + g_m Z_s + Z_d / r_o}$$

$$\frac{v_s}{v_g} \approx \frac{g_m Z_s}{1 + g_m Z_s} = \frac{g_m R_S}{1 + g_m R_S + R_S C_S s} = \frac{g_m R_S}{1 + g_m R_S} = \frac{g_m R_S}{1 + (R_S || 1/g_m) C_S s}$$

Example (cont)

$$\frac{v_o}{v_i} = \frac{v_g}{v_i} \frac{v_s}{v_g} \frac{v_d}{v_s} \frac{v_o}{v_d}$$

$$\frac{v_g}{v_i} = \frac{(R_{G1} \parallel R_{G2})C_G s}{1 + [R_{SS} + (R_{G1} \parallel R_{G2})]C_G s}$$

$$\frac{v_s}{v_g} = \frac{g_m R_S / (1 + g_m R_S)}{1 + (R_S \parallel 1/g_m)C_S s}$$

$$\frac{v_d}{v_s} = \frac{-R_D (1 + R_S C_S s)(1 + R_L C_D s)}{R_S [1 + (R_D + R_L)C_D s]}$$

$$\frac{v_o}{v_d} = \frac{R_L C_D s}{1 + R_L C_D s}$$

$$\omega_{Z1} = \frac{1}{R_S C_S}$$


$$\omega_{P1} = \frac{1}{[R_{SS} + (R_{G1} \parallel R_{G2})]C_G}$$

$$\omega_{P2} = \frac{1}{(R_S \parallel 1/g_m)C_S}$$

$$\omega_{P3} = \frac{1}{(R_D + R_L)C_D}$$

$$\omega_L \approx \sqrt{\omega_{P1}^2 + \omega_{P2}^2 + \omega_{P3}^2 - 2\omega_{Z1}^2}$$

Example (cont)

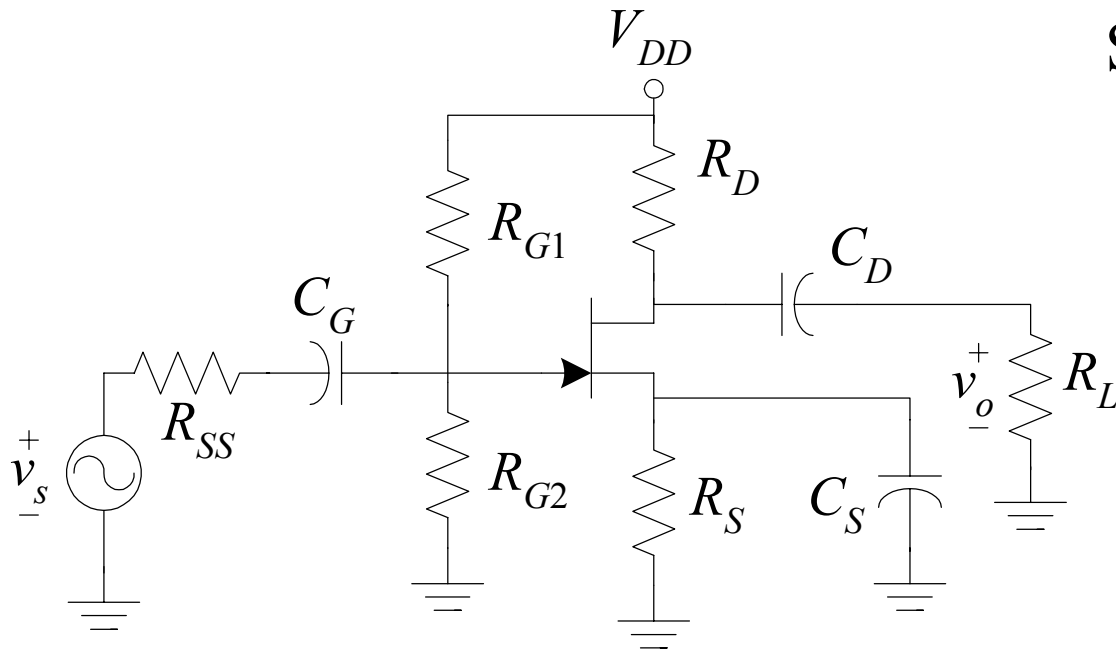

$$\text{Si } r_o \gg \frac{1}{g_m}, \quad g_m Z_s \gg Z_d / r_o$$

$$Z_s = R_S \parallel \frac{1}{sC_S}$$

$$Z_d = R_D \parallel \left(\frac{1}{sC_D} + R_L \right)$$

$$\omega_{Z1} = \frac{1}{R_S C_S}$$

$$\omega_{P1} = \frac{1}{[R_{SS} + (R_{G1} \parallel R_{G2})]C_G}$$

$$\omega_{P2} = \frac{1}{(R_S \parallel 1/g_m)C_S}$$

$$\omega_{P3} = \frac{1}{(R_D + R_L)C_D}$$

$$\omega_L \approx \sqrt{\omega_{P1}^2 + \omega_{P2}^2 + \omega_{P3}^2 - 2\omega_{Z1}^2}$$

The Time Constant Method

- It is an approximate method to calculate ω_L and ω_H
- Works well for most amplifiers
- Assumes that all the poles are real, that there is a dominant pole and no dominant zero
- No poles and zeros calculations required
- Very suitable for deriving design formulas

The Short-Circuit Time Constant Method (LF)

- 1) Replace the amplifier by its low frequency model
- 2) Calculate the resistance R_i in parallel with the capacitor C_i , considering all the remaining capacitors as short circuits
- 3) Repeat step 2) for each capacitor ($i = 1, 2, \dots, n_L$)
- 4) Calculate ω_L using

$$\omega_L \approx \sum_{i=1}^{n_L} \frac{1}{R_i C_i}$$



The Open-Circuit Time Constant Method (HF)

- 1) Replace the amplifier by its high frequency model
- 2) Calculate the resistance R_i in parallel with the capacitor C_i , considering all the remaining capacitors as open circuits
- 3) Repeat step 2) for each capacitor ($i = 1, 2, \dots, n_H$)
- 4) Calculate ω_H using

$$\omega_H \approx \frac{1}{\sum_{i=1}^{n_H} R_i C_i}$$

Low-Frequency Response of FET Amplifiers

Common Source

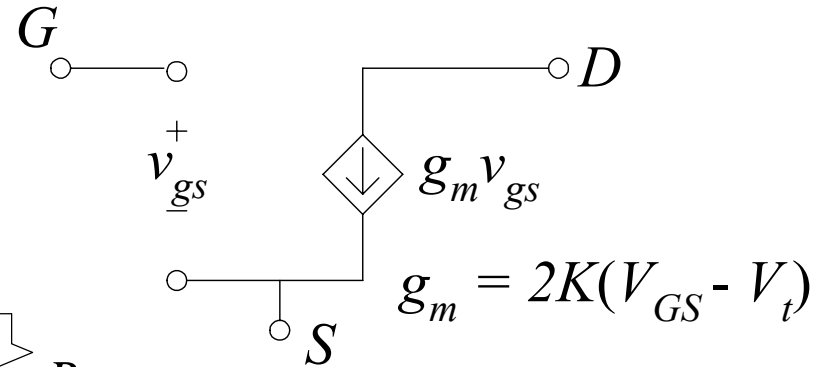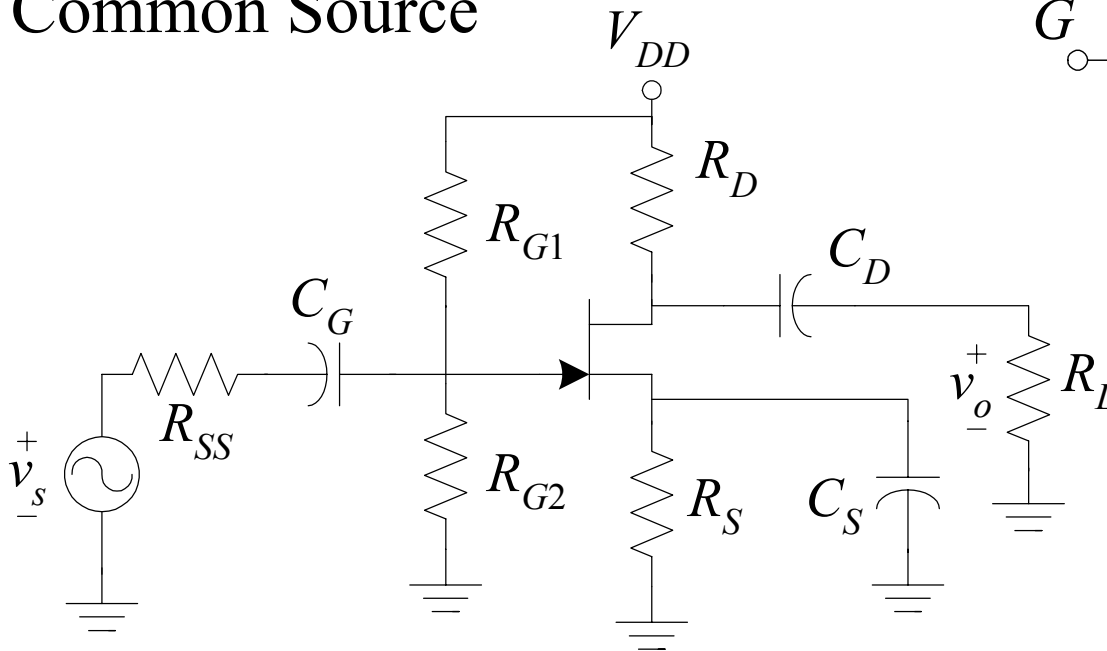

$$\omega_L \approx \frac{1}{R_{C_G} C_G} + \frac{1}{R_{C_S} C_S} + \frac{1}{R_{C_D} C_D}$$

$$R_{C_G} = R_{SS} + R_{G1} \parallel R_{G2}$$



$$R_{C_S} = R_S \parallel \frac{1}{g_m}$$

$$R_{C_D} = R_L + R_D$$

usually $1/(R_{C_S} C_S)$ is the dominant pole

Low-Frequency Response of FET Amplifiers

Common Gate

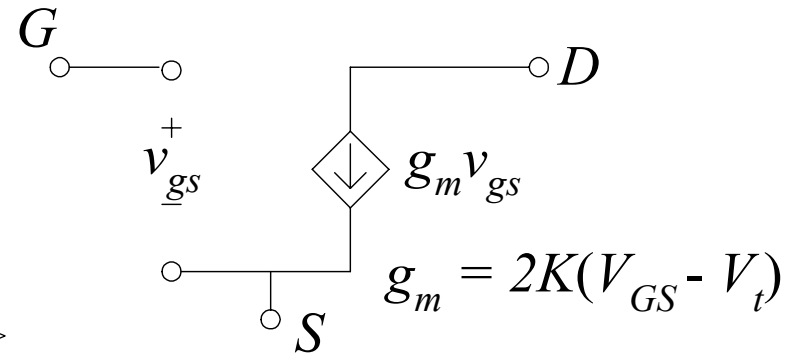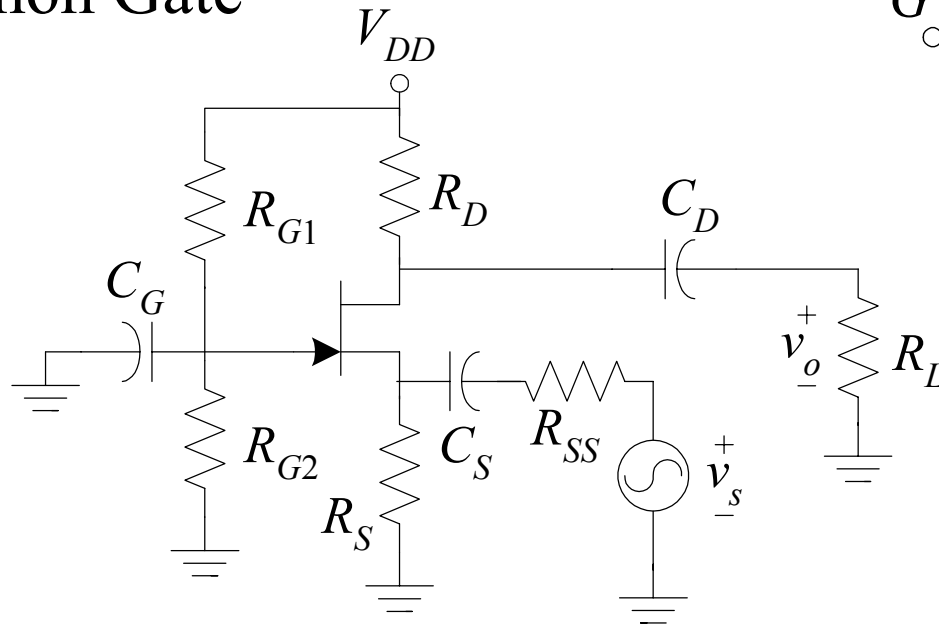

$$g_m = 2K(V_{GS} - V_t)$$

$$R_{C_G} = R_{G1} \parallel R_{G2}$$

$$R_{C_S} = R_{SS} + \left(R_S \parallel \frac{1}{g_m} \right)$$



$$R_{C_D} = R_D + R_L$$

$$\omega_L \approx \frac{1}{R_{C_G} C_G} + \frac{1}{R_{C_S} C_S} + \frac{1}{R_{C_D} C_D}$$

usually $1/(R_{C_S} C_S)$ is the dominant pole

Low-Frequency Response of FET Amplifiers

Common Drain

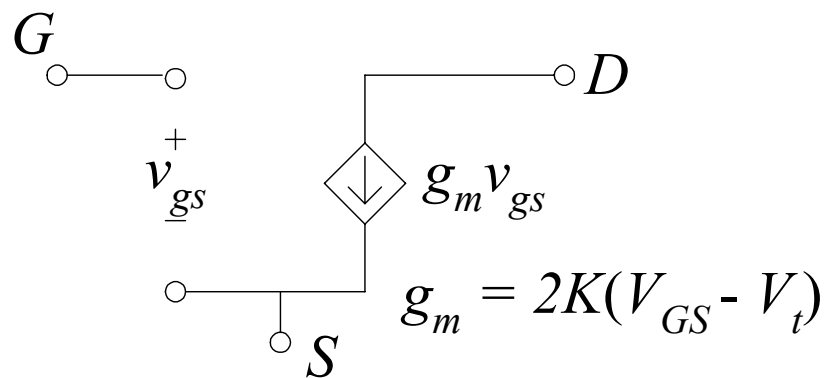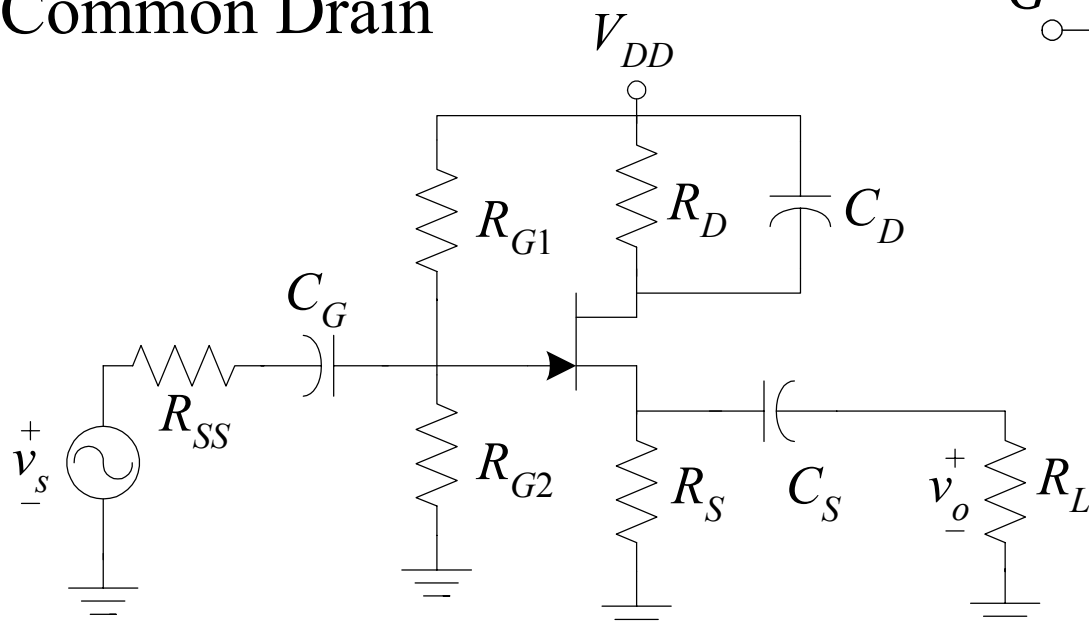

$$\omega_L \approx \frac{1}{R_{C_G} C_G} + \frac{1}{R_{C_S} C_S} + \frac{1}{R_{C_D} C_D}$$

$$R_{C_G} = R_{SS} + R_{G1} \parallel R_{G2}$$



$$R_{C_S} = \left(R_S \parallel \frac{1}{g_m} \right) + R_L$$

$$R_{C_D} = R_D$$

usually $1/(R_{C_S} C_S)$ is the dominant pole

Low-Frequency Response of BJT Amplifiers

Common Emitter

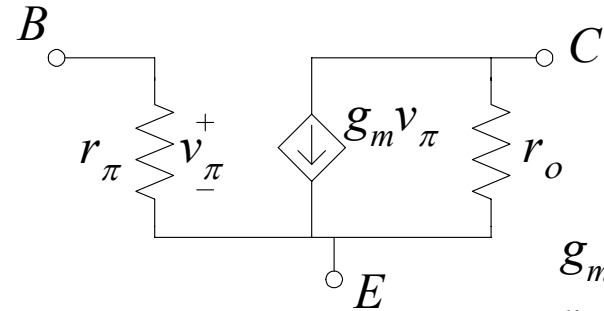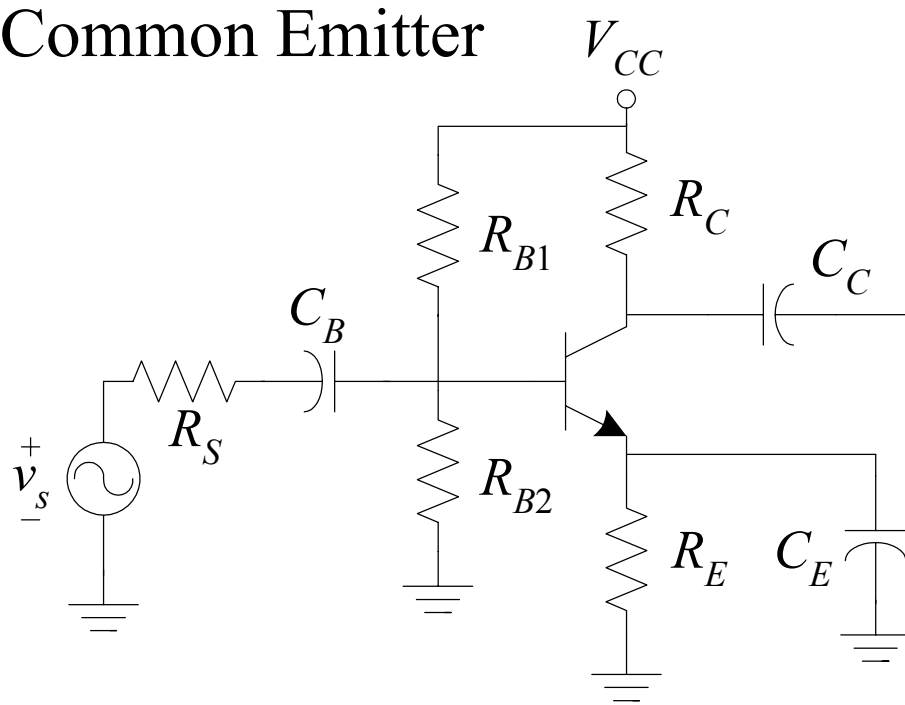

$$g_m = I_C / V_T$$

$$r_\pi = \beta / g_m$$

$$r_o = V_A / I_C$$

$$\omega_L \approx \frac{1}{R_{C_B} C_B} + \frac{1}{R_{C_E} C_E} + \frac{1}{R_{C_C} C_C}$$

usually $1/(R_{C_E} C_E)$ is the dominant pole



$$R_{C_B} = R_S + (R_{B1} \parallel R_{B2} \parallel r_\pi)$$

$$R_{C_E} = R_E \parallel \frac{r_\pi + (R_S \parallel R_{B1} \parallel R_{B2})}{\beta + 1}$$

$$R_{C_C} = R_L + (R_C \parallel r_o)$$

Low-Frequency Response of BJT Amplifiers

Common Base

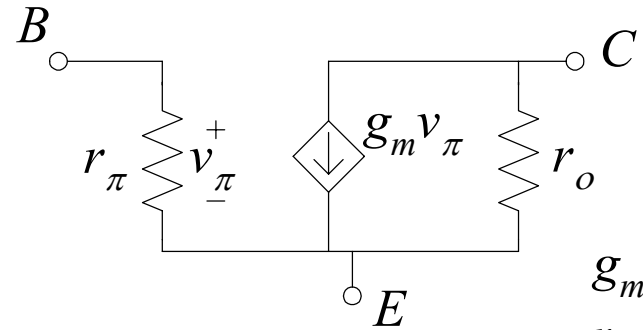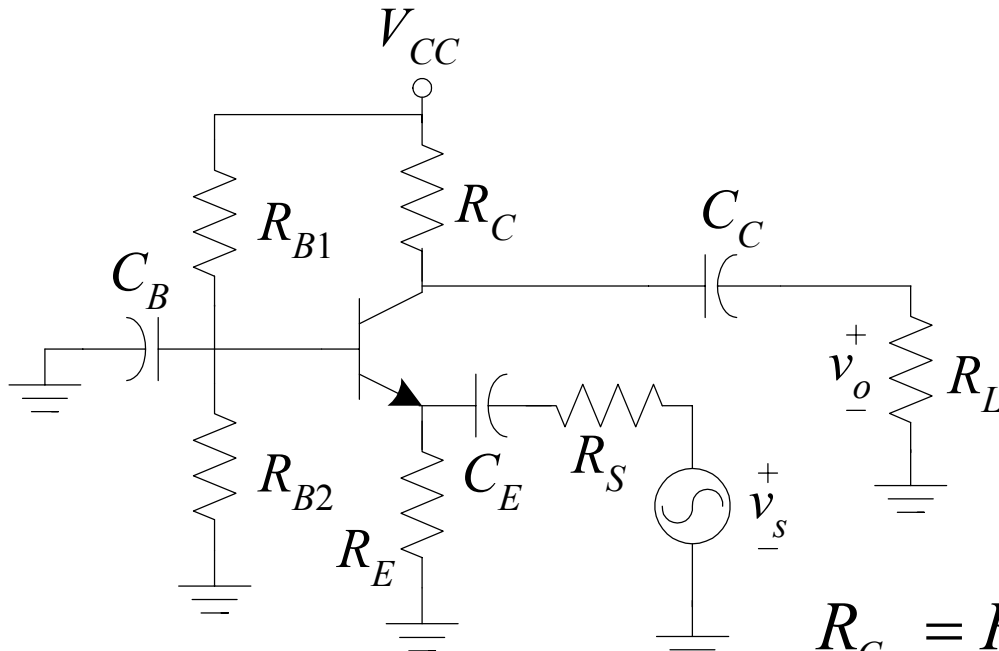

$$g_m = I_C / V_T$$

$$r_\pi = \beta / g_m$$

$$r_o = V_A / I_C$$

$$R_{C_E} = R_S + R_E \parallel r_\pi \parallel 1/g_m$$


$$R_{C_B} = R_{B1} \parallel R_{B2} \parallel [r_\pi + (1 + \beta)(R_E \parallel R_S)]$$

$$\omega_L \approx \frac{1}{R_{C_B} C_B} + \frac{1}{R_{C_E} C_E} + \frac{1}{R_{C_C} C_C}$$

$$R_{C_C} = R_L + (R_C \parallel r_o)$$

usually $1/(R_{C_E} C_E)$ is the dominant pole

Low-Frequency Response of BJT Amplifiers

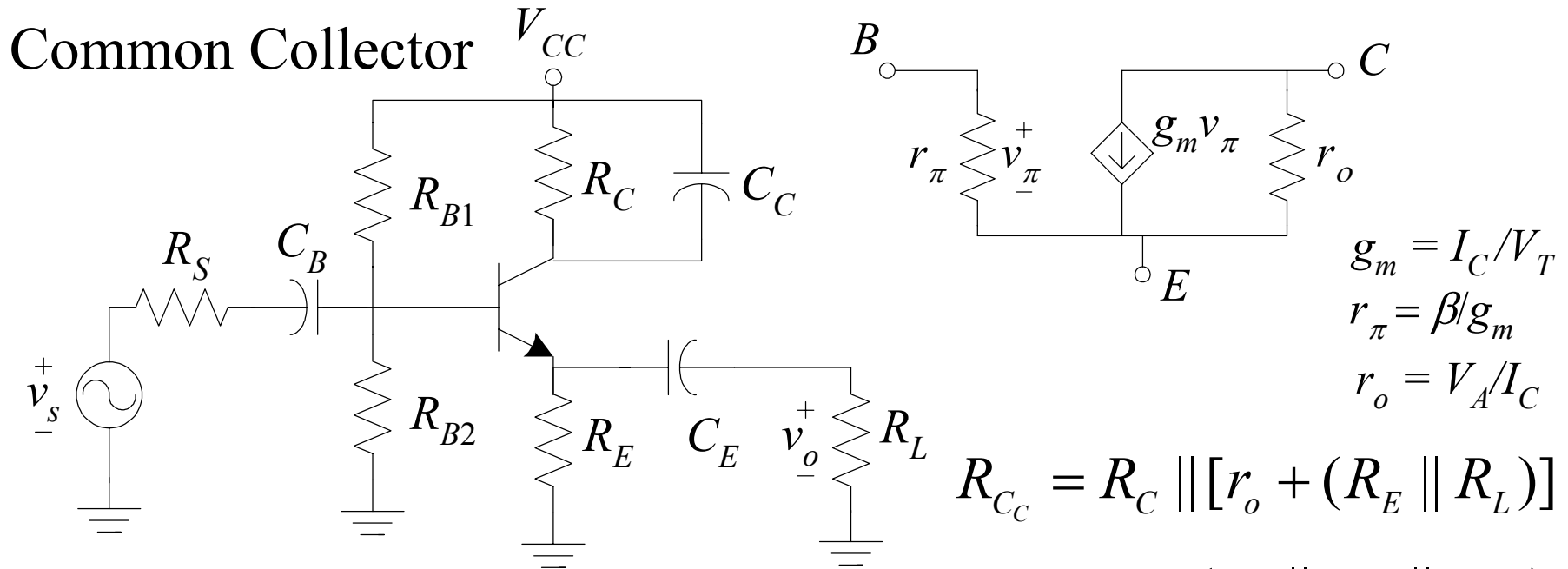

$$\omega_L \approx \frac{1}{R_{C_B} C_B} + \frac{1}{R_{C_E} C_E} + \frac{1}{R_{C_C} C_C}$$

$$R_{C_C} = R_C \parallel [r_o + (R_E \parallel R_L)]$$

$$R_{C_E} = R_L + R_E \parallel \frac{r_\pi + (R_S \parallel R_{B1} \parallel R_{B2})}{\beta + 1}$$

$$R_{C_B} = R_S + R_{B1} \parallel R_{B2} \parallel [r_\pi + (1 + \beta)(R_E \parallel R_L)]$$

usually $1/(R_{C_E} C_E)$ is the dominant pole