




**Simulation Methods for Electronic Circuits**  
**Assignment on Contents 2**


February 2020

Dr. J. E. Rayas Sánchez

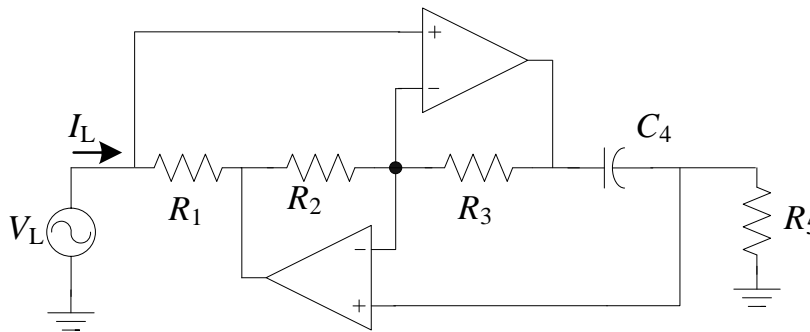
1) Apply the Tableau approach to analyze the generalized impedance converter shown below: (a) draw an oriented graph; (b) obtain the incidence matrix  $A$ ; (c) obtain the matrices  $Y$ ,  $Z$  and  $W$  from the circuit element definitions (assuming ideal Op-Amps); (d) assemble matrix  $T$ ; (e) solve  $Tx = W$  for  $x$  using Matlab or any other similar program; (f) calculate the impedance  $Z_L = V_L/I_L$ . Assume  $R_1 = R_5 = 1 \text{ K}\Omega$ ,  $R_2 = R_3 = 3.3 \text{ K}\Omega$ ,  $C_4 = 1 \text{ }\mu\text{F}$ , and  $V_L = 10 \text{ mV}$  at 1KHz (sinusoidal input). Assume zero initial conditions. From the value found for  $Z_L$  at 1 KHz, what is the equivalent inductance  $L_{eq}$  at that node at 1 KHz?



2) Apply the Nodal formulation to the circuit shown below: (a) draw an oriented graph; (b) obtain the incidence matrix  $A$ ; (c) obtain the matrices  $Y$  and  $J$  from the circuit element definitions; (d) solve  $AYA^T V_n = -AJ$  for  $V_n$  using Matlab at the following frequencies: 10 Hz, 50 MHz, 100 MHz, and 150 MHz. Assume  $G_1 = 100 \text{ }\mu\text{S}$ ,  $R_L = 50 \text{ }\Omega$ ,  $L_1 = L_2 = 60.78 \text{ nH}$ ,  $C_1 = C_3 = 10.16 \text{ pF}$ ,  $C_2 = 36.02 \text{ pF}$ ,  $C_4 = C_5 = 14.87 \text{ pF}$ , and  $|I_i| = 1 \text{ mA}$  at all frequencies. Also assume zero initial conditions. Show  $V_n$  at the four frequencies in magnitude and phase (degrees). Plot  $|A_v| = |V_o/V_i|$  versus frequency, from 10 Hz to 200 MHz (in linear scale).

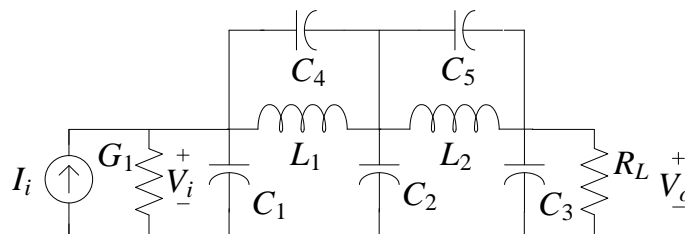


3) Apply the Modified Nodal formulation to the Sallen-Key high-pass 2<sup>nd</sup> order active filter shown below: (a) draw an oriented graph; (b) obtain the incidence matrices  $A_1$  and  $A_2$ ; (c) obtain the matrices  $Y_2$ ,  $Z_2$ ,  $W_2$ ,  $Y_1$  and  $J_1$  from the circuit element definitions (assuming an ideal Op-Amp); (d) solve the MNA equation for  $V_n$  and  $I_2$  using Matlab at 3000 frequency points from 10 Hz to 100 KHz in semi-logarithmic scale. Assume  $R_A = 1.27 \text{ K}\Omega$ ,  $R_B = 2.3 \text{ K}\Omega$ ,  $G_1 = 1/R_A$ ,  $G_2 = 1/R_B$ ,  $C_1 = C_2 = 0.1 \text{ }\mu\text{F}$ , and  $|V_i| = 1 \text{ mV}$  at all frequencies. Plot the magnitude (in dB) and phase (in degrees) of the voltage gain ( $V_{out}/V_{in}$ ) versus frequency in semi-logarithmic scale (from 10 Hz to 100 KHz). Assume zero initial conditions.

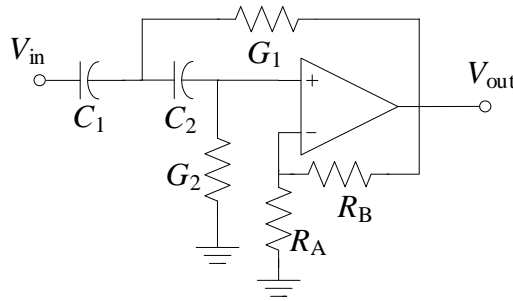

4) For the circuit in problem 1: (a) obtain an MNA formulation using stamps (write down  $\mathbf{H}$  and  $\mathbf{W}$  by inspection); (b) Using Matlab solve  $\mathbf{HX} = \mathbf{W}$  for  $\mathbf{X}$ ; (c) calculate the impedance  $Z_L = V_L/I_L$ ; (d) Compare these results with those obtained in problem 1, and check they are equivalent; (e) Plot the equivalent inductance  $L_{eq}$  versus frequency, from 10 Hz to 100 MHz (in linear scale).

5) For the buffered notch filter illustrated below: a) obtain an MNA formulation using stamps (write down  $\mathbf{H}$  and  $\mathbf{W}$  by inspection); (b) Using Matlab solve  $\mathbf{HX} = \mathbf{W}$  for  $\mathbf{X}$ , from 1Hz to 120Hz, using 301 frequency points linearly distributed; (c) Plot the magnitude of the output voltage versus frequency in linear scale. Assume zero initial conditions and ideal Op-Amps. Take  $R_1 = 19 \text{ K}\Omega$ ,  $R_2 = 57.6 \text{ K}\Omega$ ,  $R_3 = 464 \text{ K}\Omega$ ,  $R_4 = 200 \Omega$ ,  $R_5 = 4.8 \text{ K}\Omega$ ,  $C_1 = C_2 = C_3 = 47 \text{ nF}$ , and  $|V_{in}| = 1 \text{ V}$  at all frequencies.

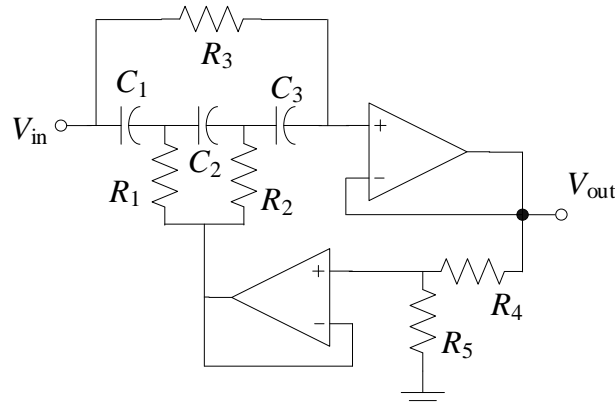

6) For the buffered notch filter of the previous problem: a) express your  $\mathbf{HX} = \mathbf{W}$  formulation into the form  $(\mathbf{H}_1 + s\mathbf{H}_2)\mathbf{X} = \mathbf{W}$ ; (b) using Matlab, obtain the transient response of the circuit from 0 to 500 ms by solving  $\mathbf{H}_2\mathbf{x}' = \mathbf{w} - \mathbf{H}_1\mathbf{x}$  for  $\mathbf{x}$  with a Trapezoidal rule, assuming that the input signal is a pulse with 3 V of amplitude, 200 ms of pulse width, and a rise time and fall time of 5ms; (c) Plot versus time (from 0 to 500 ms) the input and output voltages, as well as the input current.

Submission deadline: March 4, 2020.