



## Simulation Methods for Electronic Circuits Assignment on Contents 4

April 2020



Dr. J. E. Rayas-Sánchez

For the buffered 60-Hz band-reject notch filter illustrated below:

- Simulate the circuit using WinSpice. Plot its AC voltage gain magnitude,  $|A_v|$ , from 20 Hz to 100 Hz, in linear scale. Use  $R_1 = 22 \text{ K}\Omega$ ,  $R_2 = 48.6 \text{ K}\Omega$ ,  $R_3 = 420 \text{ K}\Omega$ ,  $R_4 = 200 \Omega$ ,  $R_5 = 4.8 \text{ K}\Omega$ ,  $C_1 = C_2 = C_3 = 47 \text{ nF}$ , and Op-Amps LM324.
- Develop a Matlab driver to run the SPICE simulations taking as variable parameters all the resistors ( $R_1$  to  $R_5$ ) and all the capacitors ( $C_1$  to  $C_3$ ).
- Using Matlab and WinSpice, perform a Monte Carlo statistical analysis considering the following tolerances: 2.5% for resistors, and 5% for capacitors. Assume Gaussian probability distribution functions (PDF) for all the parameters.
- Using a reasonable number of outcomes (explain how you selected this number), perform a yield estimation for the circuit, considering the following design specifications:

$$|A_v| < 0.2 \text{ for } 59.5 \text{ Hz} \leq f \leq 60.5 \text{ Hz}$$

$$|A_v| > 0.8 \text{ for } f \leq 45 \text{ Hz and } f \geq 75 \text{ Hz}$$

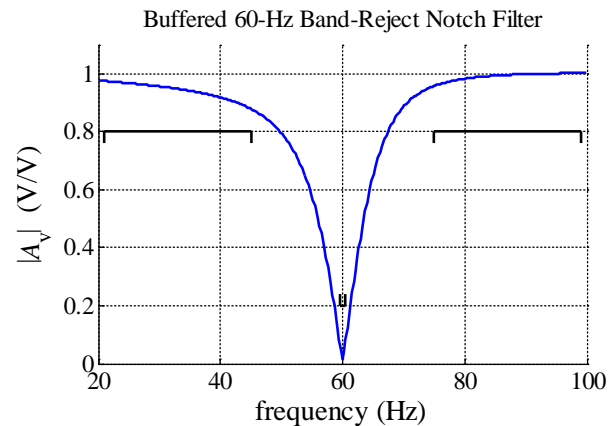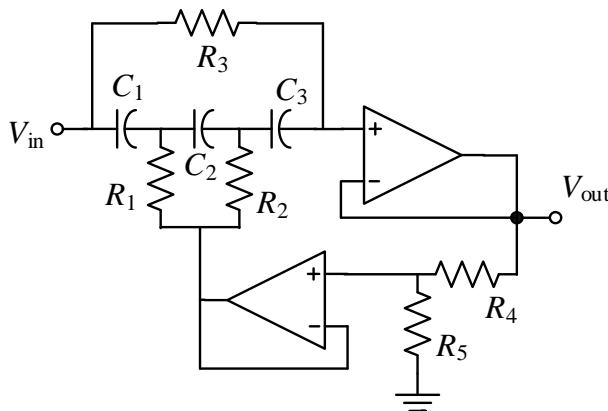

Submission deadline: April 29, 2020.