

Formulation of Circuit Equations

Dr. José Ernesto Rayas-Sánchez

1

Introduction

- A physical circuit is modeled by a number of linear and nonlinear circuit elements connected in a given configuration
- Its behavior is governed by two kinds of equations:
 - Equations for describing the operation of each circuit-element (I-V relationship for each branch)
 - Equations for describing how the circuit-elements are connected (topology)

Circuit Theory – EM Theory

- Voltages and currents cannot be uniquely defined for transmission lines that do not support transverse electromagnetic (TEM) waves
- Classic circuit theory is valid as a quasi-static approximation of general electromagnetic theory
- Kirchhoff's laws are still applicable at high frequencies provided that
 - Distributed-circuit and radiation effects are modeled within circuit elements (they are treated as “black boxes”)
 - Voltages and currents are defined at the terminals of every circuit element

Oriented Graphs


- It is a graphical representation of the nodes and branches of a circuit
- Branches are oriented by means of an arrow
- A graph is connected if there is at least one path made of branches between every pair of nodes
- An oriented graph retains the topological information about a circuit, suppressing the information about the circuit elements

Formulation of Circuit Equations

Dr. José Ernesto Rayas-Sánchez

January 29, 2020


Two-Terminal Elements

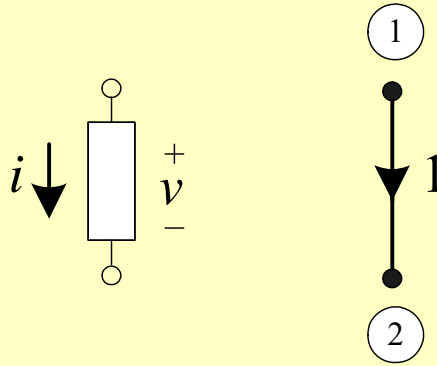

Dr. J. E. Rayas-Sánchez

5


Multi-Terminal Elements

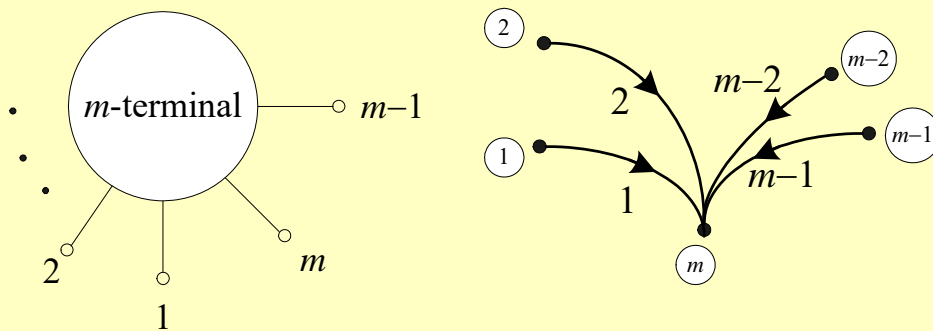

Dr. J. E. Rayas-Sánchez

6

Multi-Port Elements

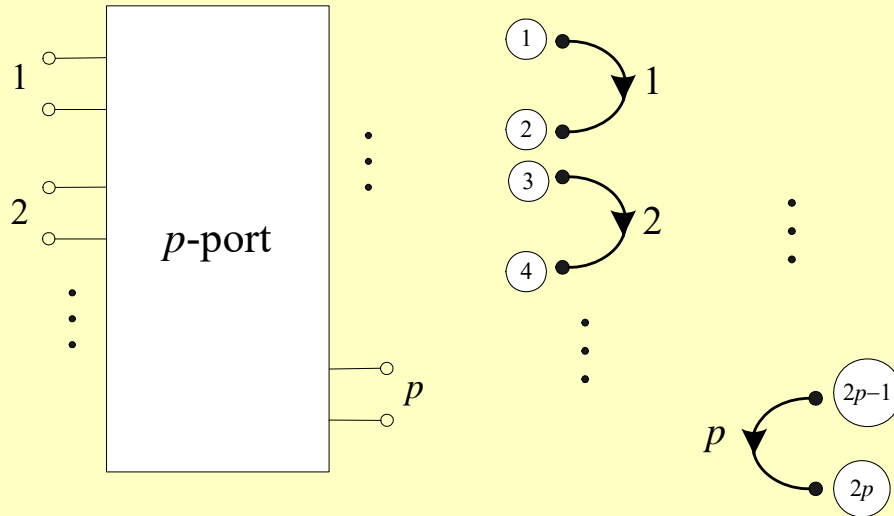

Dr. J. E. Rayas-Sánchez

7

Notation

- Scalars: a, b, c
- Vectors: $\mathbf{a}, \mathbf{b}, \mathbf{c}, \mathbf{V}$
- Matrices: $\mathbf{A}, \mathbf{B}, \mathbf{C}$
- Handwriting...
- Identity matrix: \mathbf{I} or $\mathbf{1}$
- Examples:

$$a \in \mathfrak{R} \quad \mathbf{b} \in \mathfrak{R}^n \quad \mathbf{b} = \begin{bmatrix} b_1 \\ \vdots \\ b_n \end{bmatrix} \quad \mathbf{C} \in \mathfrak{R}^{n \times m} \quad \mathbf{C} = \begin{bmatrix} c_{11} & \dots & c_{1m} \\ \vdots & \ddots & \vdots \\ c_{n1} & \dots & c_{nm} \end{bmatrix}$$

Dr. J. E. Rayas-Sánchez

8

Incidence Matrix A

- It stores the topology information of the circuit
- If the circuit has $n+1$ nodes and b branches,

$$A \in \mathfrak{R}^{n \times b} \quad A = [a_{ij}]$$

$$a_{ij} = \begin{cases} 1 & \text{if branch } j \text{ leaves node } i \\ -1 & \text{if branch } j \text{ enters node } i \\ 0 & \text{if branch } j \text{ does not touch node } i \end{cases}$$

Kirchhoff's Current Law (KCL)

If \mathbf{I} is the vector of branch currents,

$$\mathbf{I} \in \mathfrak{R}^{b \times 1} \quad \mathbf{I} = \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_b \end{bmatrix}$$

$$\mathbf{AI} = \mathbf{0}$$

Kirchhoff's Voltage Law (KVL)

If \mathbf{V}_n is the vector of node voltages, and \mathbf{V}_b is the vector of branch voltages,

$$\mathbf{V}_n \in \mathfrak{R}^{n \times 1} \quad \mathbf{V}_b \in \mathfrak{R}^{b \times 1} \quad \mathbf{V}_n = \begin{bmatrix} V_{n1} \\ V_{n2} \\ \vdots \\ V_{nm} \end{bmatrix} \quad \mathbf{V}_b = \begin{bmatrix} V_{b1} \\ V_{b2} \\ \vdots \\ V_{bb} \end{bmatrix}$$

$$\mathbf{A}^T \mathbf{V}_n - \mathbf{V}_b = \mathbf{0}$$

$$\mathbf{V}_b = \mathbf{A}^T \mathbf{V}_n$$

Tableau Formulation

- \mathbf{I} , \mathbf{V}_b and \mathbf{V}_n are taken as the unknowns
- For a circuit that corresponds to a connected graph with b branches and $n+1$ nodes, the number of unknowns is $2b+n$

- Equations

$$\mathbf{A}\mathbf{I} = \mathbf{0} \quad \mathbf{A}^T \mathbf{V}_n - \mathbf{V}_b = \mathbf{0}$$

provide $n + b$ linearly independent equations

- The rest of the equations (b) must be obtained from the circuit element definitions

Tableau Formulation (cont.)

General representation of a linear circuit element

$$\begin{bmatrix} \mathbf{Y}_1 \\ \mathbf{K}_2 \end{bmatrix} \mathbf{V}_b + \begin{bmatrix} \mathbf{K}_1 \\ \mathbf{Z}_2 \end{bmatrix} \mathbf{I} = \begin{bmatrix} \mathbf{W}_1 \\ \mathbf{W}_2 \end{bmatrix}$$

where

\mathbf{Y}_1 and \mathbf{Z}_2 represent admittances and impedances, respectively;

\mathbf{K}_1 and \mathbf{K}_2 contain dimensionless constants;

and \mathbf{W}_1 and \mathbf{W}_2 include the independent current and voltage sources, as well as the influence of initial conditions on capacitors and inductors

Tableau Formulation (cont.)

Using a more compact notation,

$$\mathbf{YV}_b + \mathbf{ZI} = \mathbf{W}$$

where

$$\mathbf{Y} = [\mathbf{Y}_1 \ \mathbf{K}_2]^T, \mathbf{Z} = [\mathbf{K}_1 \ \mathbf{Z}_2]^T \text{ and } \mathbf{W} = [\mathbf{W}_1 \ \mathbf{W}_2]^T$$

$$\mathbf{Y} \in \mathfrak{R}^{b \times b} \quad \mathbf{Z} \in \mathfrak{R}^{b \times b} \quad \mathbf{W} \in \mathfrak{R}^b$$

Formulation of Circuit Equations

Dr. José Ernesto Rayas-Sánchez

January 29, 2020

Selecting Y , Z and W : Simple Elements

Element	Equation	Y	Z	W
Resistor	$V - RI = 0$	1	$-R$	0
Conductor	$GV - I = 0$	G	-1	0
Capacitor	$sCV - I = CV_0$	sC	-1	CV_0
Inductor	$V - sLI = -LI_0$	1	$-sL$	$-LI_0$
Voltage source	$V = E$	1	0	E
Current source	$I = J$	0	1	J


$$(YV_b + ZI = W)$$

Dr. J. E. Rayas-Sánchez

15


Selecting Y , Z and W : Controlled Sources

VCCS (Voltage-Controlled Current Source)

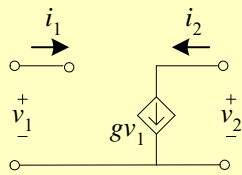

$$\begin{bmatrix} 0 & 0 \\ g & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + \begin{bmatrix} 1 & 0 \\ 0 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

CCVS (Current-Controlled Voltage Source)

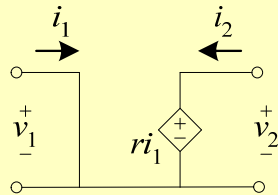

$$\begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ -r & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

Etc.

$$(YV_b + ZI = W)$$

Dr. J. E. Rayas-Sánchez

16

Selecting Y , Z and W : Parameters Z and Y

Any multi-port network modeled by classical impedance or admittance parameters can also be represented by

$$YV_b + ZI = W$$

If the network is modeled by impedance parameters Z :

$$V_b = ZI, Y = -1, W = 0$$

If the network is modeled by admittance parameters Y :


$$I = YV_b, Z = -1, W = 0$$

Selecting Y , Z and W : Parameters ABCD

Any two-port network modeled by classical ABCD parameters can also be represented by

$$YV_b + ZI = W$$

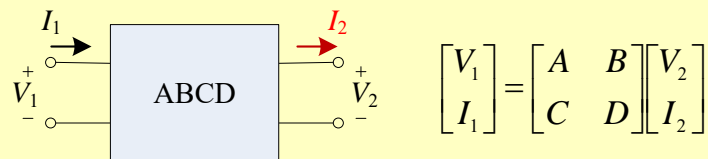If the network is modeled by ABCD parameters:



then

$$\begin{bmatrix} -1 & A \\ 0 & C \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + \begin{bmatrix} 0 & -B \\ -1 & -D \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

Tableau Formulation (cont.)

Combining KVL, KCL and circuit elements,

$$\mathbf{A}^T \mathbf{V}_n - \mathbf{V}_b = \mathbf{0}$$

$$\mathbf{YV}_b + \mathbf{ZI} = \mathbf{W}$$

$$\mathbf{AI} = \mathbf{0}$$

$$\begin{bmatrix} \mathbf{1} & \mathbf{0} & -\mathbf{A}^T \\ \mathbf{Y} & \mathbf{Z} & \mathbf{0} \\ \mathbf{0} & \mathbf{A} & \mathbf{0} \end{bmatrix} \begin{bmatrix} \mathbf{V}_b \\ \mathbf{I} \\ \mathbf{V}_n \end{bmatrix} = \begin{bmatrix} \mathbf{0} \\ \mathbf{W} \\ \mathbf{0} \end{bmatrix}$$

Tableau equation:

$$\mathbf{TX} = \mathbf{W}'$$

$$\mathbf{T} = \begin{bmatrix} \mathbf{1} & \mathbf{0} & -\mathbf{A}^T \\ \mathbf{Y} & \mathbf{Z} & \mathbf{0} \\ \mathbf{0} & \mathbf{A} & \mathbf{0} \end{bmatrix} \quad \mathbf{W}' = \begin{bmatrix} \mathbf{0} \\ \mathbf{W} \\ \mathbf{0} \end{bmatrix}$$

$$\mathbf{T} \in \mathfrak{R}^{(2b+n) \times (2b+n)}$$

$$\mathbf{X} \in \mathfrak{R}^{(2b+n) \times 1}$$

$$\mathbf{W}' \in \mathfrak{R}^{(2b+n) \times 1}$$

Matrix Density D

The density D of a matrix is defined as

$$D = \frac{\text{number of nonzero entries in the matrix}}{\text{total number of all entries in the matrix}}$$

Typically, $D < 10\%$ for \mathbf{T} (very sparse matrix)