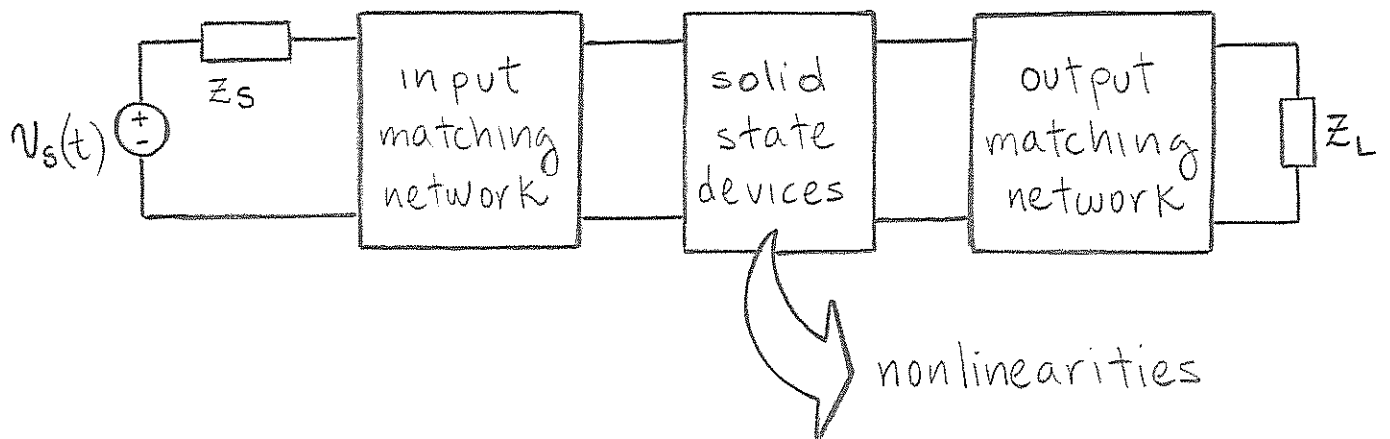


HARMONIC BALANCE


- * Very useful for strongly nonlinear circuits with large signal excitation.
- * Can be used for frequency domain or for steady state time domain analysis

General two-port microwave circuit:




$v_s(t)$ is typically a sinusoidal source with a DC bias component, but could be any waveform

redrawing the microwave circuit:

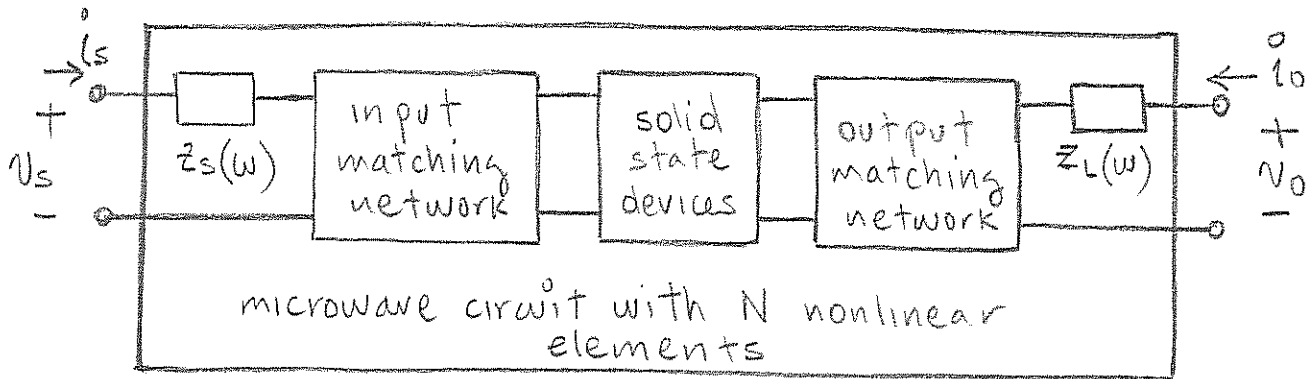

$V_o(t)$ can be zero, or can be used to include any DC bias voltage

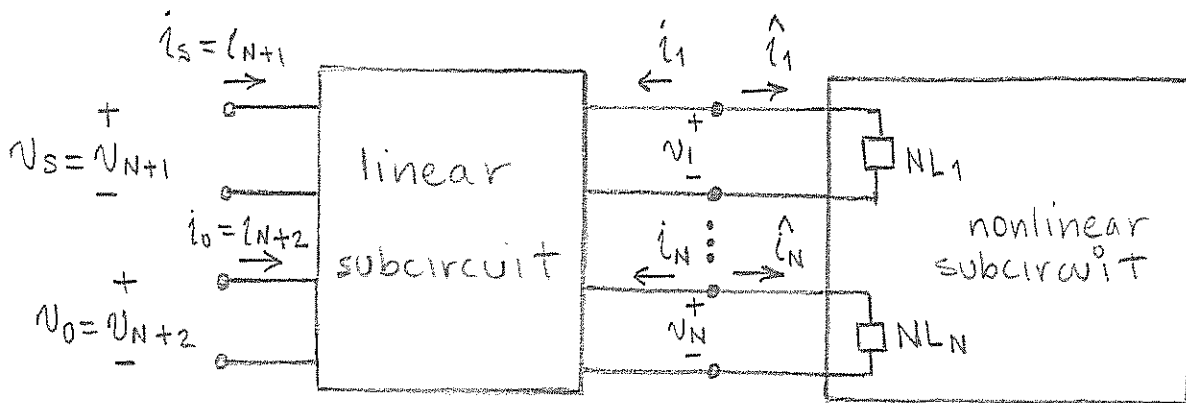separating the linear and nonlinear elements:



NL_n is the n -th nonlinear element

**HARMONIC
BALANCE
(HB)**



find a set of waveforms (or harmonics) V_1, \dots, V_N that give

$$i_n + \hat{i}_n = 0$$

$n = 1, \dots, N$

Assuming that the DC component and the first H harmonics describe all voltages and currents adequately:

$$v_n = v_{n0} + \sum_{k=1}^H |v_{nk}| \cos(k\omega_p t + \vartheta_{nk})$$

$$i_n = i_{n0} + \sum_{k=1}^H |i_{nk}| \cos(k\omega_p t + \phi_{nk})$$

$$v_{N+1} = v_s(t) = v_{s0} + |v_{s1}| \cos(\omega_p t + \vartheta_s)$$


$$v_{N+2} = v_o(t) = v_{o0}$$

let $v_{nk} = |v_{nk}| \frac{\cos \vartheta_{nk}}{\cos \vartheta_{nk}}$, $i_{nk} = |i_{nk}| \frac{\cos \phi_{nk}}{\cos \phi_{nk}}$

$$\tilde{v}_N = \begin{bmatrix} v_{n0} \\ v_{n1} \\ \vdots \\ v_{nH} \end{bmatrix} \quad \tilde{i}_N = \begin{bmatrix} i_{n0} \\ i_{n1} \\ \vdots \\ i_{nH} \end{bmatrix} \quad \tilde{v} = \begin{bmatrix} \tilde{v}_1 \\ \vdots \\ \tilde{v}_N \end{bmatrix} \quad \tilde{i} = \begin{bmatrix} \tilde{i}_1 \\ \vdots \\ \tilde{i}_N \end{bmatrix}$$

HB
equation: $\tilde{i} + \hat{\tilde{i}} = \tilde{0}$

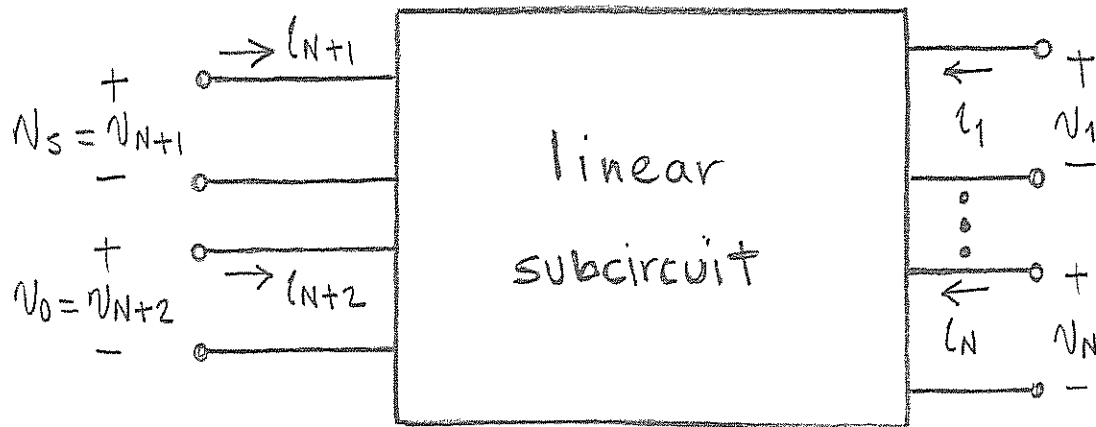ANALYSIS OF THE LINEAR SUBCIRCUIT (Maas, 1997)



at the k -th harmonic:

$$\begin{bmatrix} I_{1k} \\ I_{2k} \\ \vdots \\ I_{N+2,k} \end{bmatrix} = \underline{Y}_k(k\omega_p) \begin{bmatrix} V_{1k} \\ V_{2k} \\ \vdots \\ V_{N+2,k} \end{bmatrix}$$


$\underline{Y}_k(k\omega_p)$ is the admittance matrix at the k -th harmonic

We can show that

$$\underline{I} = \underline{Y} \underline{V} + \underline{I}_p \quad \Rightarrow \quad \text{currents in the linear subcircuit}$$

where \underline{Y} contains all the admittance matrices at the H harmonics

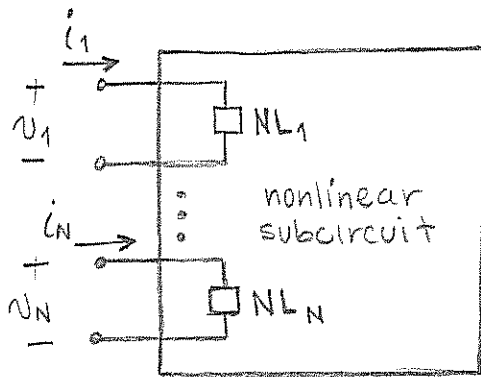ANALYSIS OF THE NONLINEAR SUBCIRCUIT (Maas, 1997)



Since most of the nonlinearities are due to the solid state devices, we will consider nonlinear

- * conductances
- * controlled voltage current sources
- * capacitors

* Nonlinear conductances and controlled sources

$$i_{gn}(t) = g(v_1(t), v_2(t), \dots, v_N(t))$$

each voltage waveform can be obtained by Inverse-Fourier transforming the corresponding vector of harmonics

$$\text{DFT}^{-1} \{ \underline{v}_n \} \rightarrow v_n(t)$$

similarly

$$\text{DFT} \{ i_{gn}(t) \} \rightarrow \underline{\tilde{I}}_{gn} = \begin{bmatrix} I_{gn0} \\ I_{gn1} \\ \vdots \\ I_{gnH} \end{bmatrix}$$

grouping

$$\underline{\tilde{I}}_g = \begin{bmatrix} \underline{\tilde{I}}_{g1} \\ \vdots \\ \underline{\tilde{I}}_{gN} \end{bmatrix}$$

notice that

$$\underline{\tilde{I}}_g = \underline{\tilde{I}}_g(\underline{v})$$

* Nonlinear capacitors

We can show that

$$\underline{\tilde{I}}_c = \int \underline{\tilde{\Omega}} \underline{\tilde{Q}}$$

$\underline{\tilde{\Omega}}$ contains all the harmonic frequencies

$\underline{\tilde{Q}}$ contains the harmonic components of the charge at each nonlinear capacitor

$$\text{HB eq.} \Rightarrow \underline{\underline{I}} + \underline{\underline{I}}^{\wedge} = \underline{\underline{0}}$$

$$\underline{\underline{I}} = \underline{\underline{Y}} \underline{\underline{V}} + \underline{\underline{I}}_P$$

$$\underline{\underline{I}}^{\wedge} = \underline{\underline{I}}_G(\underline{\underline{V}}) + \underline{\underline{I}}_C(\underline{\underline{V}})$$


$$\underline{\underline{I}}_C = j \underline{\underline{\Omega}} \underline{\underline{Q}}(\underline{\underline{V}})$$

HB equation \circ $\underline{\underline{F}}(\underline{\underline{V}}) = \underline{\underline{Y}} \underline{\underline{V}} + \underline{\underline{I}}_P + \underline{\underline{I}}_G(\underline{\underline{V}}) + j \underline{\underline{\Omega}} \underline{\underline{Q}}(\underline{\underline{V}}) = \underline{\underline{0}}$

$\underline{\underline{F}}(\underline{\underline{V}})$ \Rightarrow difference between the currents calculated from the linear and nonlinear subcircuit, at each port, at each harmonic.

solving $\underline{\underline{F}}(\underline{\underline{V}}) = \underline{\underline{0}}$ gives the frequency domain behavior of the nonlinear network

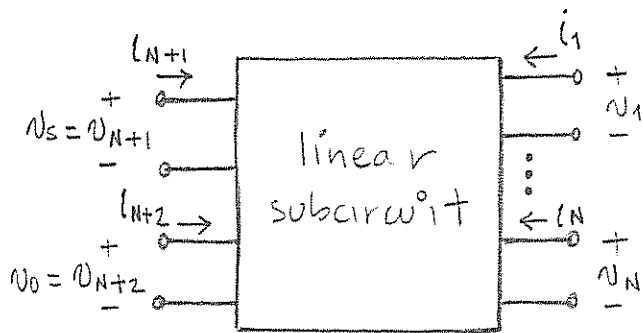ANALYSIS OF THE LINEAR SUBCIRCUIT (more details)



at the k-th harmonic:

$$\begin{bmatrix} I_{1k} \\ I_{2k} \\ \vdots \\ I_{N+2,k} \end{bmatrix} = \tilde{Y}_k(k\omega_p) \begin{bmatrix} V_{1k} \\ V_{2k} \\ \vdots \\ V_{N+2,k} \end{bmatrix}$$

$\tilde{Y}_k(k\omega_p)$: admittance matrix at the k-th harmonic

$$y_{nm}(k\omega_p) = \left. \frac{I_{nk}}{V_{mk}} \right|_{V_{jk} = 0 \quad \substack{j=1, \dots, N+2 \\ j \neq m}}$$

Since

$$I_{nk} = y_{n1}(k\omega_p)V_{1k} + y_{n2}(k\omega_p)V_{2k} + \dots + y_{n,N+2}(k\omega_p)V_{N+2,k}$$

$$\underline{\tilde{I}}_n = \begin{bmatrix} I_{n0} \\ I_{n1} \\ \vdots \\ I_{nH} \end{bmatrix} = \begin{bmatrix} y_{n1}(0)V_{10} + y_{n2}(0)V_{20} + \dots + y_{n,N+2}(0)V_{N+2,0} \\ y_{n1}(\omega_p)V_{11} + y_{n2}(\omega_p)V_{21} + \dots + y_{n,N+2}(\omega_p)V_{N+2,1} \\ \vdots \\ y_{n1}(H\omega_p)V_{1H} + y_{n2}(H\omega_p)V_{2H} + \dots + y_{n,N+2}(H\omega_p)V_{N+2,H} \end{bmatrix}$$

Let $\underline{\tilde{I}}_n = \underline{\tilde{Y}}_{n,1} \underline{\tilde{V}}_1 + \underline{\tilde{Y}}_{n,2} \underline{\tilde{V}}_2 + \dots + \underline{\tilde{Y}}_{n,N+2} \underline{\tilde{V}}_{N+2}$

where $\underline{\tilde{Y}}_{n,m} = \text{diag}(y_{nm}(k\omega_p)) \quad k=0, 1, \dots, H$

$\underline{\tilde{Y}}_{n,m}$ contains elements y_{nm} at all freq. components

Then

$$\begin{bmatrix} \underline{\underline{I}}_1 \\ \underline{\underline{I}}_2 \\ \vdots \\ \underline{\underline{I}}_{N+2} \end{bmatrix} = \begin{bmatrix} \underline{\underline{Y}}_{1,1} & \underline{\underline{Y}}_{1,2} & \dots & \underline{\underline{Y}}_{1,N+2} \\ \underline{\underline{Y}}_{2,1} & \underline{\underline{Y}}_{2,2} & \dots & \underline{\underline{Y}}_{2,N+2} \\ \vdots & \vdots & \ddots & \vdots \\ \underline{\underline{Y}}_{N+2,1} & \dots & \dots & \underline{\underline{Y}}_{N+2,N+2} \end{bmatrix} \begin{bmatrix} \underline{\underline{V}}_1 \\ \underline{\underline{V}}_2 \\ \vdots \\ \underline{\underline{V}}_{N+2} \end{bmatrix}$$

The current in the firsts N ports are

$$\begin{bmatrix} \underline{\underline{I}}_1 \\ \underline{\underline{I}}_2 \\ \vdots \\ \underline{\underline{I}}_N \end{bmatrix} = \begin{bmatrix} \underline{\underline{Y}}_{1,1} & \underline{\underline{Y}}_{1,2} & \dots & \underline{\underline{Y}}_{1,N} \\ \underline{\underline{Y}}_{2,1} & \underline{\underline{Y}}_{2,2} & \dots & \underline{\underline{Y}}_{2,N} \\ \vdots & \vdots & \ddots & \vdots \\ \underline{\underline{Y}}_{N,1} & \underline{\underline{Y}}_{N,2} & \dots & \underline{\underline{Y}}_{N,N} \end{bmatrix} \begin{bmatrix} \underline{\underline{V}}_1 \\ \underline{\underline{V}}_2 \\ \vdots \\ \underline{\underline{V}}_N \end{bmatrix} + \begin{bmatrix} \underline{\underline{Y}}_{1,N+1} & \underline{\underline{Y}}_{1,N+2} \\ \vdots & \vdots \\ \underline{\underline{Y}}_{N,N+1} & \underline{\underline{Y}}_{N,N+2} \end{bmatrix} \begin{bmatrix} \underline{\underline{V}}_{N+1} \\ \underline{\underline{V}}_{N+2} \end{bmatrix}$$

$$\underline{\underline{I}} = \underline{\underline{Y}} \underline{\underline{V}} + \underline{\underline{I}}_p$$

currents in the linear subcircuit

* Nonlinear capacitors (more details)

$$q_n(t) = f_n(v_1(t), v_2(t), \dots, v_N(t))$$

where $v_n(t) \leftarrow \text{DFT}^{-1} \{ \underline{v}_n \}$

taking $\text{DFT} \{ q_n(t) \} \rightarrow \underline{Q}_n = \begin{bmatrix} Q_{n0} \\ Q_{n1} \\ \vdots \\ Q_{nH} \end{bmatrix}$

grouping in a single charge vector

$$\underline{Q} = [\underline{Q}_1^T \quad \underline{Q}_2^T \quad \dots \quad \underline{Q}_N^T]^T \quad (\underline{Q} = \underline{Q}(\underline{V}))$$

The nonlinear capacitor current $i_c(t)$ at the n -th port is

$$i_{cn}(t) = \frac{dq_n(t)}{dt} \quad \text{then}$$

$$\underline{I}_{cn} = \begin{bmatrix} I_{cn0} \\ I_{cn1} \\ \vdots \\ I_{cnH} \end{bmatrix} = \begin{bmatrix} 0 \\ j\omega_p Q_{n1} \\ \vdots \\ jH\omega_p Q_{nH} \end{bmatrix} = j \begin{bmatrix} 0 & & & & \\ & \omega_p & & & \\ & & 2\omega_p & & \\ & & & \ddots & \\ & & & & H\omega_p \end{bmatrix} \underline{Q}_n = j \underline{\omega} \underline{Q}_n$$

grouping in a single capacitor current vector \underline{I}_c

$$\underline{I}_c = \begin{bmatrix} \underline{I}_{c1} \\ \vdots \\ \underline{I}_{cN} \end{bmatrix}, \quad \text{if } \underline{\Omega} = \begin{bmatrix} \omega \\ \omega \\ \vdots \\ \omega \end{bmatrix} \quad \text{then} \quad \underline{I}_c = j \underline{\Omega} \underline{Q}$$