

DRIVING APLAC FROM MATLAB – CB AMPLIFIER EXAMPLE


Dr. J. E. Rayas-Sánchez

APLAC can be driven from Matlab in the following manner:

1. Create the APLAC simulation file (*.i) either with a text editor or using APLAC's schematic editor. Test the APLAC simulation file and make sure it works fine.
2. Redirect the output to text files: substitute "show" commands by "print" commands in the *.i file, so that the results are saved in text files.
3. Write a parameterized Matlab file to drive APLAC simulation: a) generate a new *.i file using Matlab capabilities for manipulating strings; b) use a Matlab statement to run APLAC from the command line with the *.i filename as a parameter; c) read the *.txt files and assign the output data to the corresponding vectors of responses.

Example: Common Base Amplifier


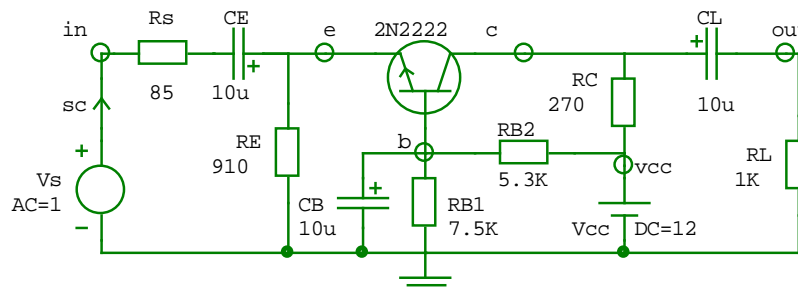
1. Create a conventional APLAC project using APLAC's schematic editor.



```
Sweep
"Common Base Amp - AC Analysis"
LOOP 100 FREQ LOG 10Hz 900MEGHZ
WINDOW=0 grid Y "Av" "dB" -40 20
WINDOW=1 grid Y "Zin" "ohms" 0 1K

Show W=0 Y=MagdB(Vac(out))
Show W=1 Y=Mag(Vac(in)/Iac(sc))
EndSweep
```


Responses

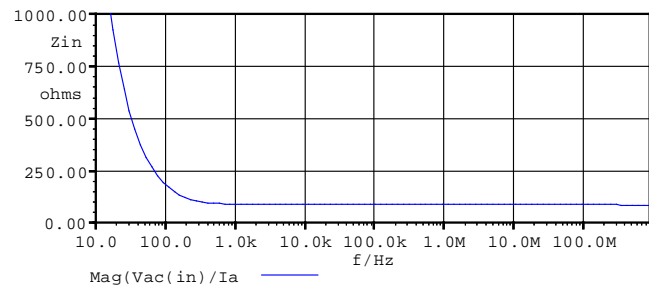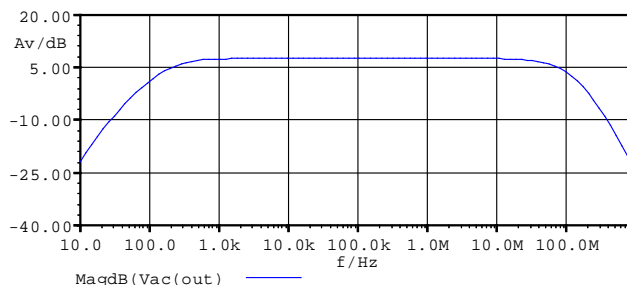

Simulation file (contents of file CB_AMP_student_ver.i)

```
$ -----  
$ File      : C:\... \CB_AMP_student_ver.i  
$ Schema file : C:\... \CB_AMP_student_ver.N  
$ Generated with APLAC Editor version 3.1.2  
$ Wed May 07 11:49:46 2014  
$ -----  
  
Res Rs in node1  
+ 85  
Res RB2 b vcc  
+ 5.3K  
Res RE e GND  
+ 910  
Res RB1 b GND  
+ 7.5K  
Res RC c vcc  
+ 270  
Res RL out GND  
+ 1K  
Bjt 2N2222 c b e  
+ NPN  
+ IS=3.108E-15 XTI=3 EG=1.11 VAF=131.5 BF=217.5  
+ NE=1.541 ISE=190.7E-15 IKF=1.296 XTB=1.5 BR=6.18  
+ NC=2 ISC=0 IKR=0 RC=1 CJC=14.57E-12 VJC=.75  
+ MJC=.3333 FC=.5 CJE=26.08E-12 VJE=.75 MJE=.3333  
+ TR=51.35E-9 TF=451E-12 ITF=.1 VTF=10 XTF=2  
Cap CE e node1  
+ 10u  
Cap CB b GND  
+ 10u  
Volt Vs node2 GND  
+ AC=1  
Volt Vcc vcc GND  
+ DC=12  
Cap CL c out  
+ 10u  
Short sc node2 in  
+ I = sc  
Sweep "Common Base Amp - AC Analysis"  
+ LOOP 100 FREQ LOG 10Hz 900MEGHZ  
+ WINDOW=0 grid Y "Av" "dB" -40 20  
+ WINDOW=1 grid Y "Zin" "ohms" 0 1K  
Show W=0 Y=MagdB(Vac(out))  
Show W=1 Y=Mag(Vac(in)/Iac(sc))  
EndSweep
```

2. Re-directing output to text files

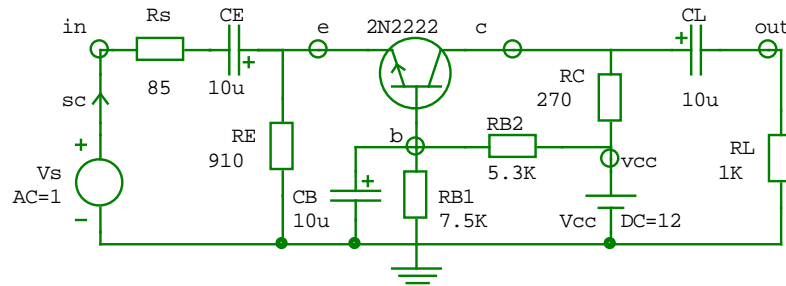

```
Sweep
"Common Base Amp - AC Analysis"
LOOP 100 FREQ LOG 10Hz 900MEGHZ

Print appendfile "ac.txt" real f bl real MagdB(Vac(out)) bl real Mag(Vac(in)/Iac(sc)) lf
EndSweep
```

New simulation file:

```
$ -----
$ File      : C:\...\CB_AMP_txt_out_student_ver.i
$ Schema file : C:\...\CB_AMP_txt_out_student_ver.N
$ Generated with APLAC Editor version 3.1.2
$ Wed May 07 13:10:56 2014
$ -----

Res Rs in node1
+ 85
Res RB2 b vcc
+ 5.3K
Res RE e GND
+ 910
Res RB1 b GND
+ 7.5K
Res RC c vcc
+ 270
Res RL out GND
+ 1K
Bjt 2N2222 c b e
+ NPN
+ IS=3.108E-15 XTI=3 EG=1.11 VAF=131.5 BF=217.5
+ NE=1.541 ISE=190.7E-15 IKF=1.296 XTB=1.5 BR=6.18
+ NC=2 ISC=0 IKR=0 RC=1 CJC=14.57E-12 VJC=.75
+ MJC=.3333 FC=.5 CJE=26.08E-12 VJE=.75 MJE=.3333
+ TR=51.35E-9 TF=451E-12 ITF=.1 VTF=10 XTF=2
Cap CE e node1
+ 10u
Cap CB b GND
+ 10u
Volt Vs node2 GND
+ AC=1
Volt Vcc vcc GND
+ DC=12
Cap CL c out
+ 10u
Short sc node2 in
+ I = sc
Sweep "Common Base Amp - AC Analysis"
+ LOOP 100 FREQ LOG 10Hz 900MEGHZ
```

```
Print appendfile "ac.txt" real f bl real MagdB(Vac(out)) bl real Mag(Vac(in)/Iac(sc)) lf
EndSweep
```

4. Write a parameterized Matlab file to drive APLAC simulation

```
% ~~~~~
%                               Driving CB_Amp_m.i from Matlab
%
% This function drives the Aplac file CB_AMP_m.i from
% Matlab, and returns the simulation results in arrays psi and R.
%
% Usage: [f,mAv,mZin] = CB_Amp_Aplac(x)
%        x = [Rs RB2 RE RB1 RC RL] (ohms).
%        f: Column vector of simulated frequency points (Hz).
%        mAv: Column vector of AC voltage gain magnitude (V/V).
%        mZin: Column vector of AC input impedance magnitude (ohms).

function [f,mAv,mZin] = CB_Amp_Aplac(x)

% Define APLAC Script, as
as{1} = '$ -----';
as{2} = '$ File      : C:\...\CB_AMP_txt_out_student_ver.i';
as{3} = '$ Schema file : C:\...\CB_AMP_txt_out_student_ver.N';
as{4} = '$ Generated with APLAC Editor version 3.1.2';
as{5} = '$ Wed May 07 13:10:56 2014';
as{6} = '$ -----';
as{7} = ['Res Rs in node1 ' mat2str(x(1))];
as{8} = ['Res RB2 b vcc ' mat2str(x(2))];
as{9} = ['Res RE e GND ' mat2str(x(3))];
as{10} = ['Res RB1 b GND ' mat2str(x(4))];
as{11} = ['Res RC c vcc ' mat2str(x(5))];
as{12} = ['Res RL out GND ' mat2str(x(6))];
as{13} = 'Bjt 2N2222 c b e';
as{14} = '+ NPN';
as{15} = '+ IS=3.108E-15 XTI=3 EG=1.11 VAF=131.5 BF=217.5';
as{16} = '+ NE=1.541 ISE=190.7E-15 IKF=1.296 XTB=1.5 BR=6.18';
as{17} = '+ NC=2 ISC=0 IKR=0 RC=1 CJC=14.57E-12 VJC=.75';
as{18} = '+ MJC=.3333 FC=.5 CJE=26.08E-12 VJE=.75 MJE=.3333';
as{19} = '+ TR=51.35E-9 TF=451E-12 ITF=.1 VTF=10 XTF=2';
as{20} = 'Cap CE e node1 10u';
as{21} = 'Cap CB b GND 10u';
as{22} = 'Volt Vs node2 GND AC=1';
as{23} = 'Volt Vcc vcc GND DC=12';
as{24} = 'Cap CL c out 10u';
as{25} = 'Short sc node2 in I = sc';
as{26} = 'Sweep "Common Base Amp - AC Analysis"';
as{27} = '+ LOOP 100 FREQ LOG 10Hz 900MEGHZ';
as{28} = 'Print appendfile "ac.txt" real f bl real MagdB(Vac(out)) bl real
Mag(Vac(in)/Iac(sc)) lf';
as{29} = 'EndSweep';

% Save APLAC Script as a Circuit File in Matlab Working Directory
CircuitFileName = 'CB_Amp_m.i';
ckt_file = str2mat(as);
[rows,columns] = size(ckt_file);
fid = fopen(CircuitFileName,'w+'); % File identifier opened.
for i = 1:rows
    fprintf(fid, '%s', ckt_file(i,:)); % Save each row of ckt_file.
    fprintf(fid, '%s\r\n', '');
end
fclose(fid); % File identifier closed.

% Run APLAC Circuit File
ExecFile = 'C:\command_line_Aplac_Student\aplace -aq ';
system([ExecFile CircuitFileName]);
```

```

% Read APLAC Output Files
load ac.txt
f = ac(:,1);
mAv = ac(:,2);
mZin = ac(:,3);

% Erase APLAC Output Files
delete ac.txt;

```

Testing the APLAC driver

```

% ~~~~~
%   Ploting Responses of a Common Base Amplifier simulated with APLAC

Rs = 85;
RB2 = 5.3e3;
RE = 910;
RB1 = 7.5e3;
RC = 270;
RL = 1e3;

% Calculate Responses
x = [Rs RB2 RE RB1 RC RL];
[f,mAv,mZin] = CB_Amp_Aplac(x);

% Plot Responses
figure
set(axes,'FontName','Times','FontSize',14,'Position',[0.15 0.15 0.75 0.7]);
grid on
hold on
plot(f,mAv,'-k')
set(gca,'XScale','log')
title('Common Base Amplifier')
xlabel('frequency (Hz)')
ylabel('{|v|_v| (dB)');

figure
set(axes,'FontName','Times','FontSize',14,'Position',[0.15 0.15 0.75 0.7]);
grid on
hold on
plot(f,mZin,'-k')
set(gca,'XScale','log')
title('Common Base Amplifier')
xlabel('frequency (Hz)')
ylabel('{|z}_i_n| (ohms)');

```

