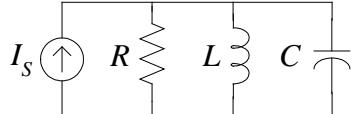


# SIMULATION EXERCISES WITH SPICE – PART 1

Dr. J. E. Rayas-Sánchez

- Simulate the following RLC parallel resonator



```


RLC Tank
* -----
* Dr. J.E. Rayas-Sánchez           February 24, 2016
* -----
*                               RLC Tank
*
Is 0 s DC 0A AC 1mA PULSE(0A 10mA 0s 1ns 1ns 10ns 1.3us)
L s 0 10uH
R s 0 820
C s 0 2.53nF

.control
TRAN 1ns 15us
plot v(s)
.endc


.end

```



After simulation:

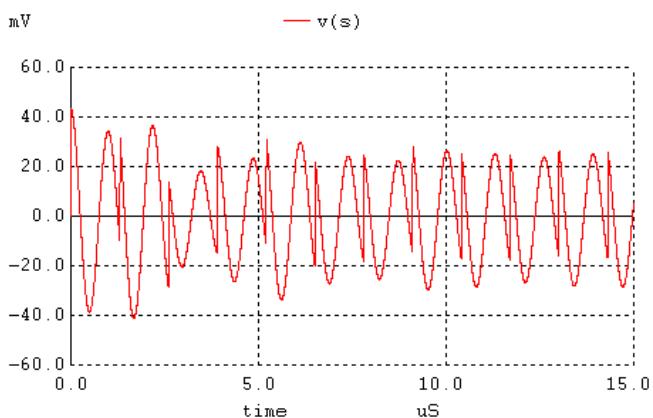

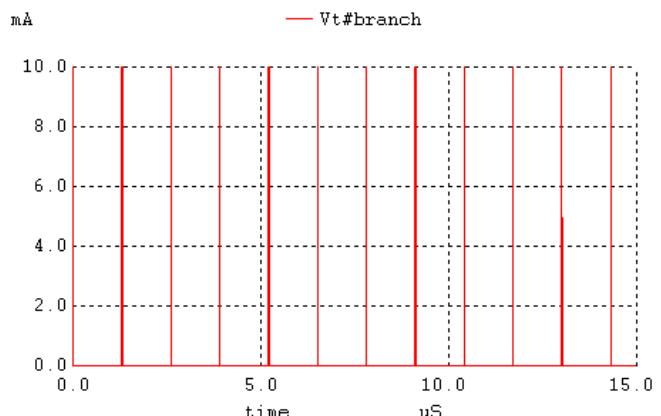
Modifying the netlist to measure the input pulse current:



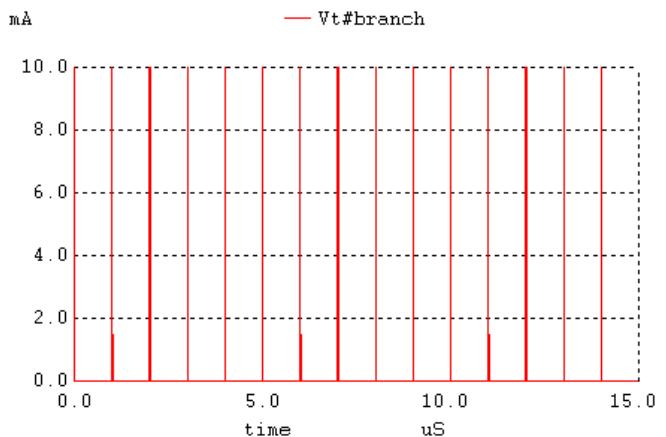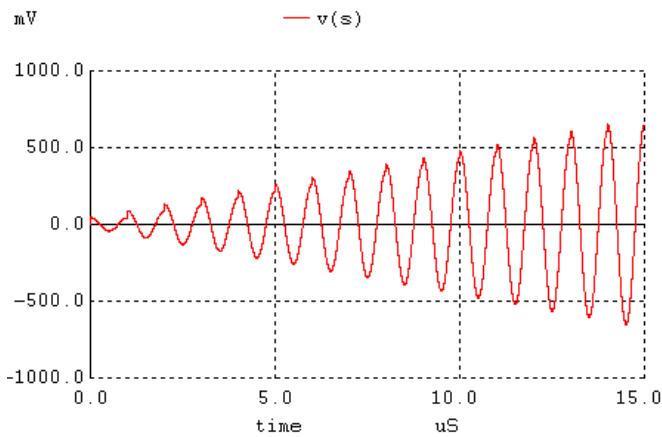
Increasing  $R$  to  $820\text{K}\Omega$ , and synchronizing the pulse period with the resonant frequency:



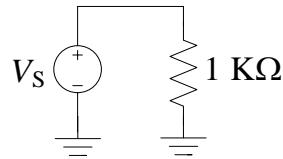
## 2. Apply special transient waveforms to a simple resistor



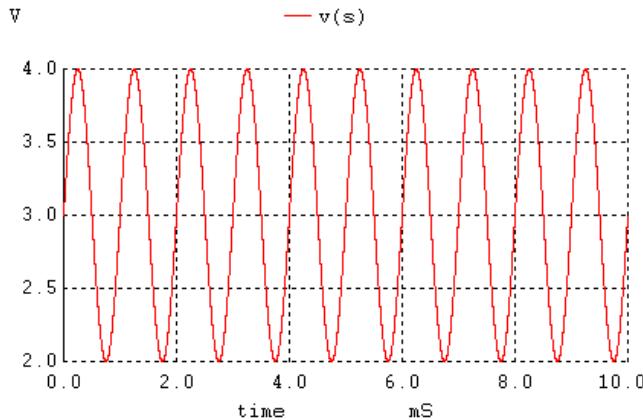
First apply a sinusoidal input signal with 1 V amplitude, 1 KHz frequency and 3 V offset:



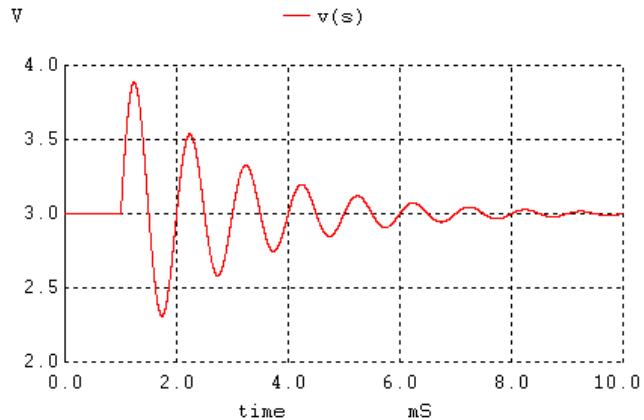
Add a time delay of 1 ms and a damping factor of 500:



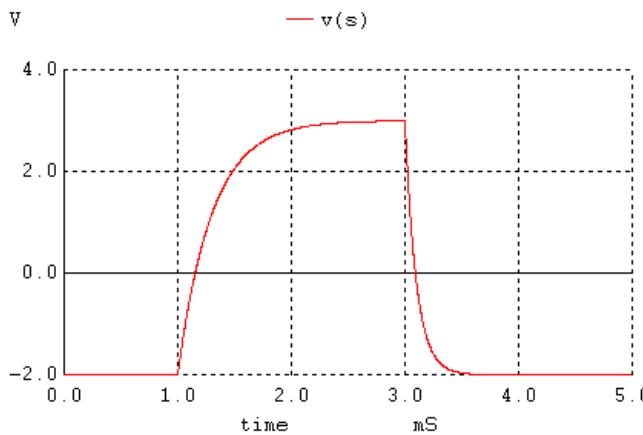
Switch to an exponential pulse input signal, such that you obtain: ( $\tau_1 = 0.3$  ms and  $\tau_2 = 0.1$  ms)



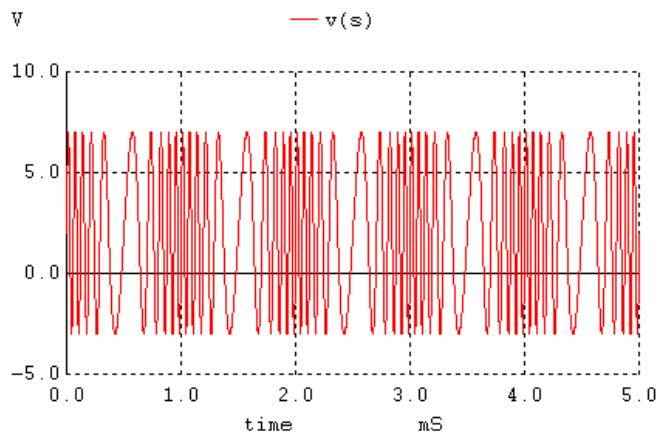
Switch to an FM input signal ( $F_c = 10$  KHz ,  $M = 7$ ,  $F_s = 1$  KHz):



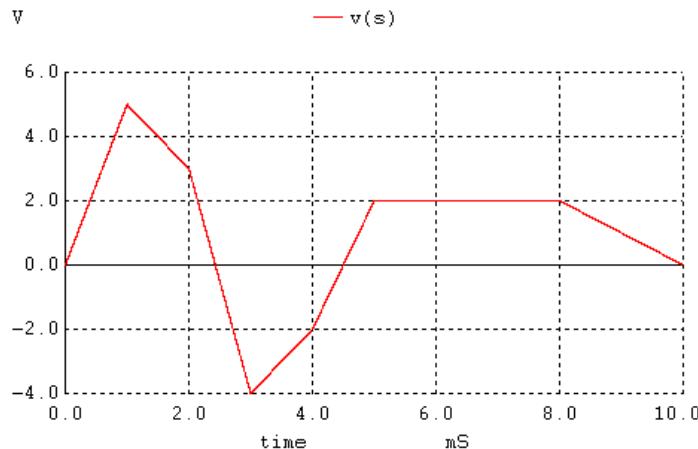Finally, implement the following piece-wise linear transient input signal:



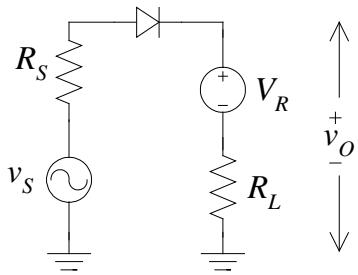3. Perform a transient analysis of the following series clipper



```
Series Clipper
* -----
* Dr. J.E. Rayas-Sánchez February 24, 2016
* -----
* Series Clipper
```


```
Vs    in 0      DC 0V   AC 1V   SIN(0V 4V 1KHz)
Rs    in in2 1
D1    in2 out D1N4004
VR    out out2 DC 2V
RL    out2 0    100
```

```
* 1N4004 - 1A 400V General Purpose Rectifier
* Fairchild (now National Semiconductors)
.MODEL D1N4004 D (IS=3.699E-09 RS=1.756E-02 N=1.774
+ XTI=3.0 EG=1.110 CJO=1.732E-11 M=0.3353
+ VJ=0.3905 FC=0.5 BV=400 IBV=1.0E-03)
```


```
* Quasi Ideal Diode
.model ideal_diode D (Is=1pA n=0.01)
```

```
.TRAN 10E-6 4E-3
.plot tran v(in) v(out)
.end
```



Using quasi-ideal diode:

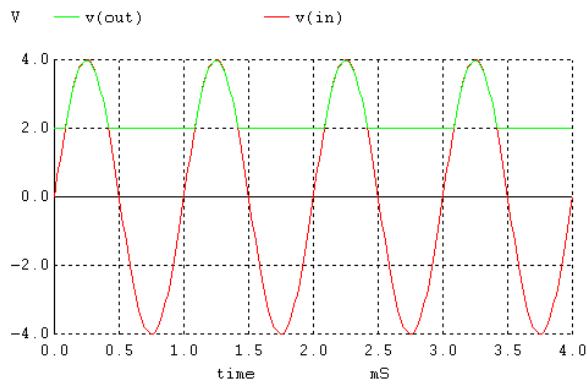


Using 1N4004:

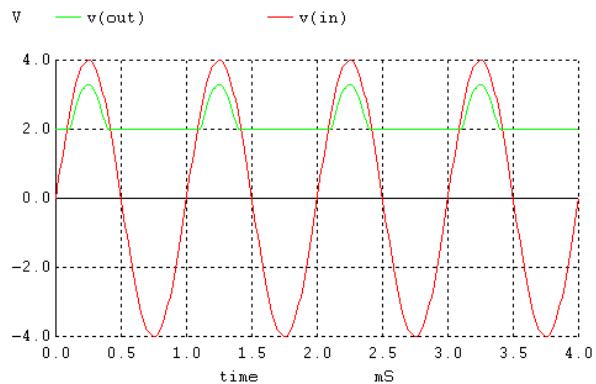

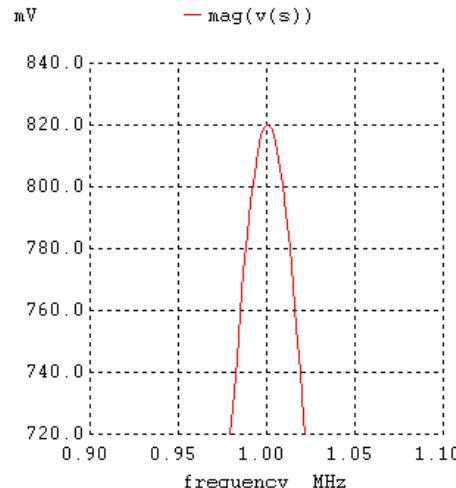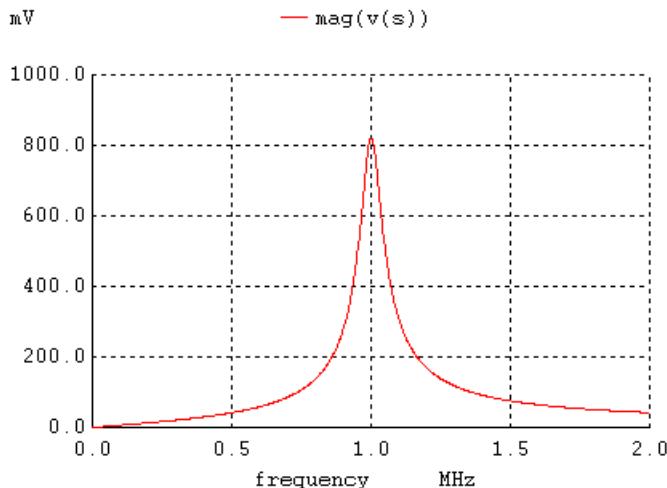4. Perform an AC analysis on the RLC parallel resonator in exercise 1 from 50 Hz to 3 MHz, to obtain the following plot (use  $R = 820 \Omega$  and an AC source with 1 mA amplitude):


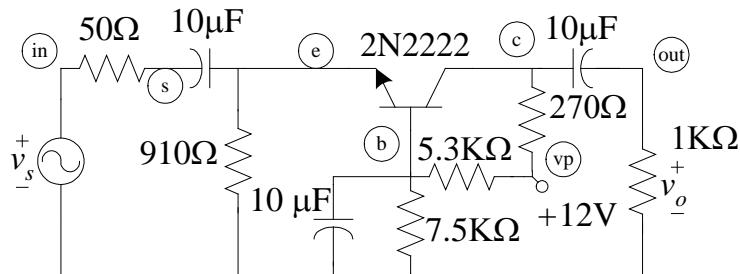
## 5. Simulate the following Common Base Amplifier



Common Base Amplifier

\* -----  
 \* Dr. J.E. Rayas-Sánchez March 25, 2006  
 \* -----  
 \* Common Base Amplifier

```


Vs      in   0     DC  0V     AC  1V
Vcc    vp   0     DC  12V
Q1     c    b   e   Q2N2222
*Q1    c    b   e   npn_ideal
RS     in   s   50
RE     e    0   910
RC     c   vp  270
R1     b   vp  5.3K
R2     b   0   7.5K
RL     out  0   1K
CE     e   s   10uF
CB     b   0   10uF
CL     c   out  10uF

.MODEL Q2N2222 NPN
+(IS=3.108E-15 XTI=3 EG=1.11 VAF=131.5 BF=217.5
+ NE=1.541 ISE=190.7E-15 IKF=1.296 XTB=1.5 BR=6.18
+ NC=2 ISC=0 IKR=0 RC=1 CJC=14.57E-12 VJC=.75
+ MJC=.3333 FC=.5 CJE=26.08E-12 VJE=.75 MJE=.3333
+ TR=51.35E-9 TF=451E-12 ITF=.1 VTF=10 XTF=2)


* Quasi ideal transistors
.model npn_ideal npn (Is=1.8fA Bf=150 VAf=300V)
.model pnp_ideal pnp (Is=1.8fA Bf=150 VAf=300V)

.control
AC DEC 10 10Hz 900MEGHZ
plot vdb(out)
.endc
.end
    
```

Using quasi-ideal transistor:

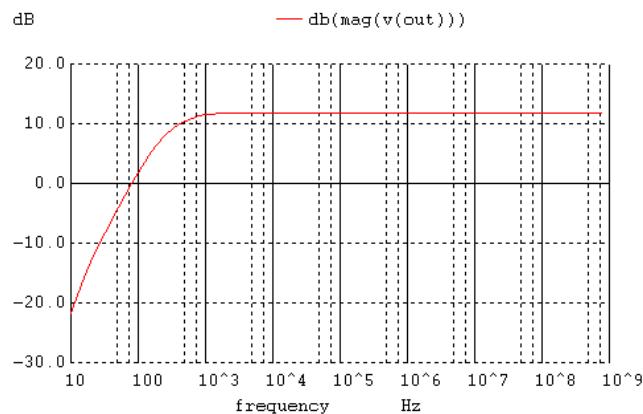


Using 2N2222:

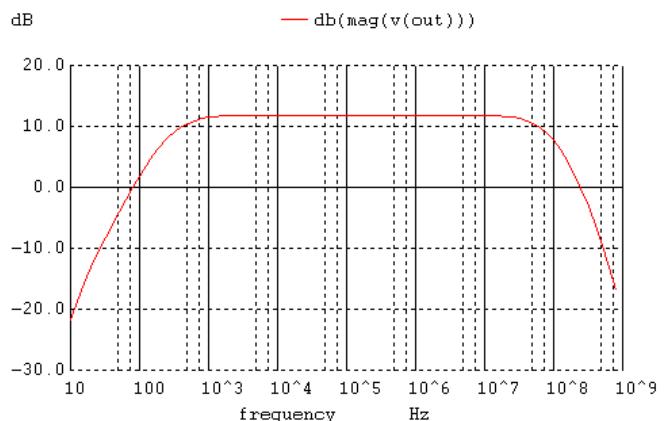


Insert SPICE commands to plot the gain in V/V (not in dB):

Using quasi-ideal transistor:

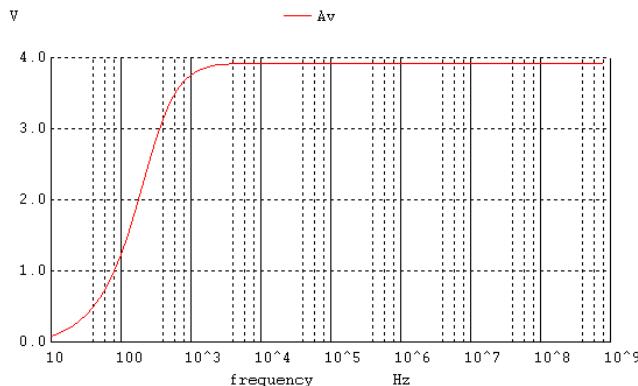


Using 2N2222:

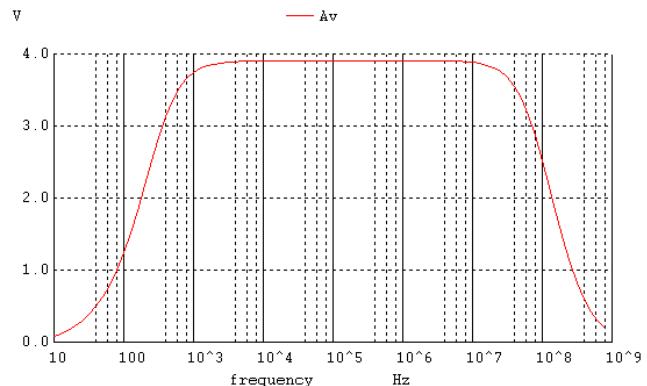


Insert SPICE commands to plot the input impedance:

Using quasi-ideal transistor:

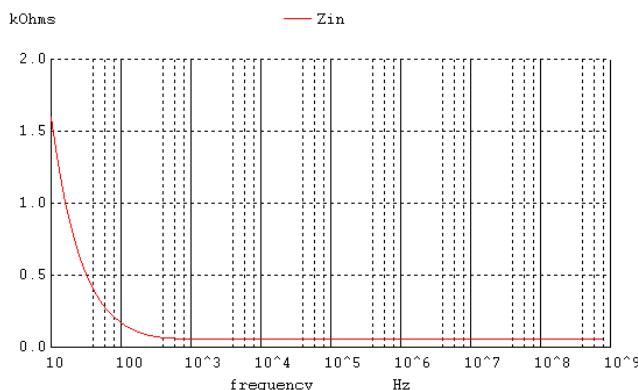


Using 2N2222:

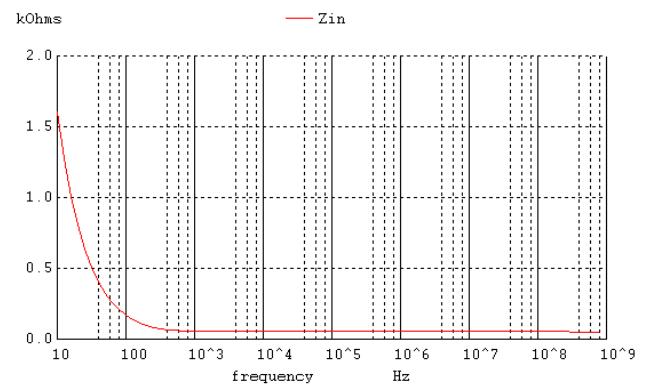


Add SPICE commands to perform a transient analysis using a small amplitude sinusoidal input signal (10mV, 1KHz):

Using quasi-ideal transistor:

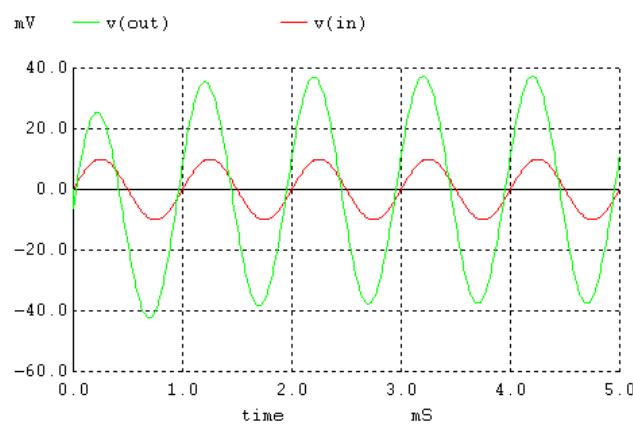


Using 2N2222:

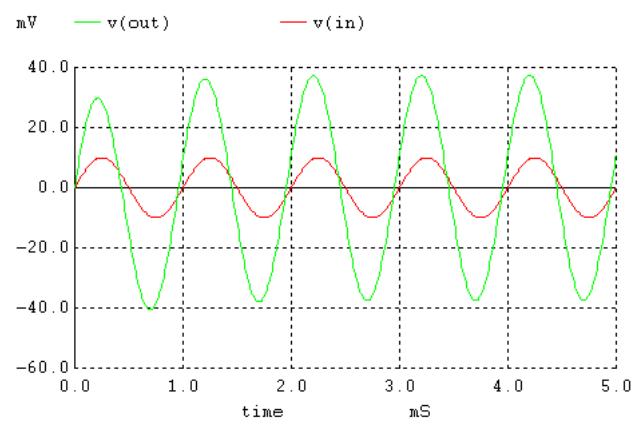


Now make larger the amplitude of the sinusoidal input signal (2V, 1KHz):

Using quasi-ideal transistor:

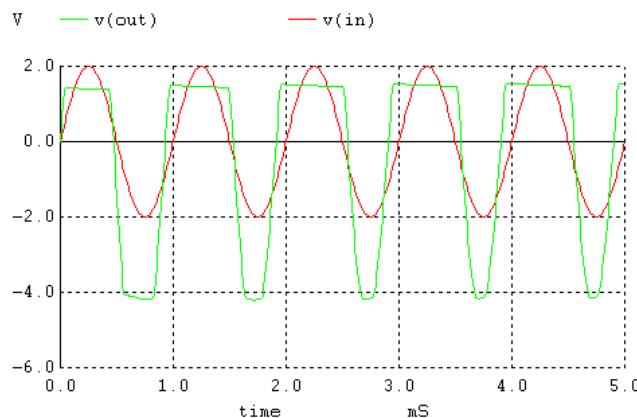

Using 2N2222:

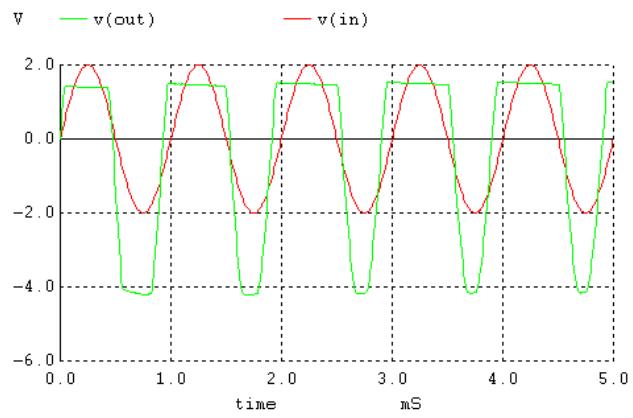

Add to the netlist an operating point SPICE command (.OP) and a transfer function SPICE command (.TF) and check the results: (to show the results in the command windows, you have to add “print all” in the control block)

```
WinSpice v1.04.02
File Edit Settings Help
Circuit: Common Base Amplifier
AC analysis ... 100%
Transient analysis ... 100%
DC Operating Point ... 100%
b = 6.893896e+00
c = 1.018902e+01
e = 6.143936e+00
in = 0.000000e+00
out = 0.000000e+00
s = 0.000000e+00
vcc#branch = -7.67076e-03
vp = 1.200000e+01
vs#branch = 0.000000e+00
Transfer function analysis ...
transfer_function = 0.000000e+00
vs#input_impedance = 1.000000e+20
output_impedance_at_v(out) = 1.000000e+03
WinSpice 82 -> _
```

Why are the transfer function results different to those obtained in the previous AC analyses?