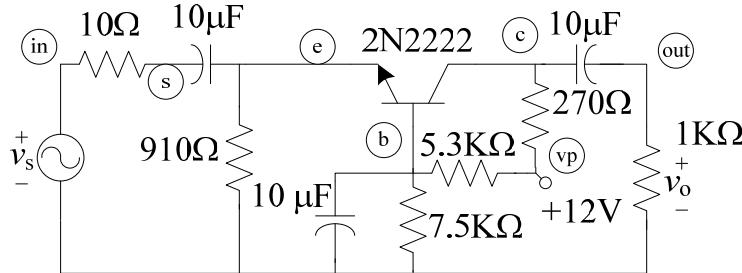


SIMULATION EXERCISES WITH SPICE – PART 3

Dr. J. E. Rayas Sánchez

Use the built-in interactive interpreter available in WinSpice to simulate n times the magnitude of the AC voltage gain $|v_o/v_s|$ and the transient output voltage $v_o(t)$ for the following Common Base amplifier, with $R_S = n10\Omega$, with $n = 1, 2, \dots, 5$. For the transient analysis, assume that v_s is a sinusoidal voltage with 250mV of amplitude and 1KHz of frequency.



Common Base Amplifier

```
* -----
* Dr. J.E. Rayas-Sanchez           February 28, 2016
* -----
* Common Base Amplifier Using the Interactive Interpreter
```

```
Vs      in    0      DC 0V      AC 1V      SIN(0 250mV 1KHz)
Vcc    vp    0      DC 12V
Q1     c     b      e   Q2N2222
RS     in    s      10
RE     e     0      910
RC     c     vp    270
R1     b     vp    5.3K
R2     b     0      7.5K
RL     out   0      1K
CE     e     s      10uF
CB     b     0      10uF
CL     c     out   10uF
.MODEL Q2N2222 NPN
+(IS=3.108E-15 XTI=3 EG=1.11 VAF=131.5 BF=217.5
+ NE=1.541 ISE=190.7E-15 IKF=1.296 XTB=1.5 BR=6.18
+ NC=2 ISC=0 IKR=0 RC=1 CJC=14.57E-12 VJC=.75
+ MJC=.3333 FC=.5 CJE=26.08E-12 VJE=.75 MJE=.3333
+ TR=51.35E-9 TF=451E-12 ITF=.1 VTF=10 XTF=2)

.control
destroy all
let count = 0
while count < 5
    alter RS = 10 + 10*count
    AC DEC 10 10Hz 900MEGHZ
    TRAN 5us 5ms
    let count = count + 1
end
plot db(ac1.v(out)) db(ac2.v(out)) db(ac3.v(out))
+ db(ac4.v(out)) db(ac5.v(out))
plot tran1.v(out) tran2.v(out) tran3.v(out)
+ tran4.v(out) tran5.v(out)
.endc
.end
```

