

Modeling Sensors and other Physical Systems with SPICE

(Part 1)

Dr. José Ernesto Rayas-Sánchez

1

Simulation of Sensors and Transducers

- Sensors, transducers, and other multi-physical components can be simulated in SPICE
- SPICE models for those components are based on:

Analytical functions


Multidimensional vector functions

Nonlinear systems of equations

Systems of nonlinear differential equations

Measurements

Multidimensional Vector Functions

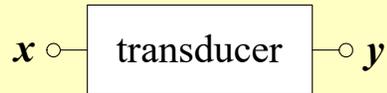

\mathbf{x} Vector of physical variables (temperature, humidity, pressure, volumetric flow, etc.)

\mathbf{y} Vector of electrical outputs (voltage, current, charge, resistance, etc.)

$$\mathbf{y} = \mathbf{f}(\mathbf{x}) \quad \mathbf{f} : \mathbb{R}^n \rightarrow \mathbb{R}^m$$

It is implemented in SPICE by using controlled sources and independent sources (*R. Saleh and A. Yang, 1993*)

Implementing $\mathbf{y} = \mathbf{f}(\mathbf{x})$ with SPICE

- 1) Implement each physical variable, x_1, \dots, x_n with a DC voltage source, isolated from the rest of the circuit
- 2) Implement each constant or any other parameter using also an isolated DC voltage source
- 3) Use a controlled source to implement each function f_1, \dots, f_m , using linear controlled sources, polynomial controlled sources, or nonlinear controlled sources

Linear Controlled Sources

- Types: $i = gv_c$, $v = ev_c$, $i = fi_c$, $v = hi_c$
where $g, e, f, y h$ are real constants, v_c and i_c are the controlling signals
- Syntax

```
GXXXXXXXX N+ N- NC+ NC- VALUE
EXXXXXXXXX N+ N- NC+ NC- VALUE
FXXXXXXXX N+ N- VNAME VALUE
HXXXXXXXX N+ N- VNAME VALUE
```

(VNAME is the name of the voltage source by which the controlling current is flowing)

Examples of Linear Controlled Sources

```
E1 = v5-3 = 3v11
E1 5 3 11 0 3.0
G2 = i1-0 = 0.5 × 10-3 v5
G2 1 0 5 0 0.5MMHO
Hfvcc = v8-15 = 900ivmedir
Hfvcc 8 15 Vmedir 0.9K
F1 = i7-51 = 10ivsens
F1 7 51 VSENS 10
```

Polynomial Controlled Sources

- Types: $i = g(v_c)$, $v = e(v_c)$, $i = f(i_c)$, $v = h(i_c)$
where $g, e, f, y h$ are polynomial functions of one or more variables, and v_c, i_c are the controlling signals

- Syntax

```
GXXXXXXX N+ N- <POLY (ND)> NC1+ NC1- ... p0 <p1 ...> <IC=...>
EXXXXXXX N+ N- <POLY (ND)> NC1+ NC1- ... p0 <p1 ...> <IC=...>
FXXXXXXX N+ N- <POLY (ND)> VN1 <VN2 ...> p0 <p1 ...> <IC=...>
HXXXXXXX N+ N- <POLY (ND)> VN1 <VN2 ...> p0 <p1 ...> <IC=...>
```

(VN1, VN2, ... are the names of the voltage sources through which the controlling currents are flowing, ND is the polynomial dimension, IC are the initial conditions)

Polynomial Controlled Sources (cont.)

Interpretation of polynomial coefficients (p0, p1, ...)

- If ND = 1

$$y = p_0 + (p_1 * a) + (p_2 * a^{**2}) + (p_3 * a^{**3}) + (p_4 * a^{**4}) + (p_5 * a^{**5}) + \dots$$

- If ND = 2

$$y = p_0 + (p_1 * a) + (p_2 * b) + (p_3 * a^{**2}) + (p_4 * a * b) + (p_5 * b^{**2}) + (p_6 * a^{**3}) + (p_7 * a^{**2} * b) + (p_8 * a * b^{**2}) + (p_9 * b^{**3}) + \dots$$

- If ND = 3

$$y = p_0 + (p_1 * a) + (p_2 * b) + (p_3 * c) + (p_4 * a^{**2}) + (p_5 * a * b) + (p_6 * a * c) + (p_7 * b^{**2}) + (p_8 * b * c) + (p_9 * c^{**2}) + (p_{10} * a^{**3}) + (p_{11} * a^{**2} * b) + (p_{12} * a^{**2} * c) + (p_{13} * a * b^{**2}) + (p_{14} * a * b * c) + (p_{15} * a * c^{**2}) + (p_{16} * b^{**3}) + (p_{17} * b^{**2} * c) + (p_{18} * b * c^{**2}) + (p_{19} * c^{**3}) + (p_{20} * a^{**4}) + \dots$$

Examples of Polynomial Controlled Sources

$$GR = i_{17-3} = 10^{-3}(v_{10-3} + 1.5v_{10-3}^2)$$

```
GR 17 3 10 3 0 1M 1.5M
```

$$EX = v_{18} = v_{13} + v_{15} + v_{17}$$

```
EX 18 0 POLY(3) 13 0 15 0 17 0 0 1 1 1
```

$$F1 = i_{12-10} = 1mA - 1.5mAi_{VCC}$$

```
F1 12 10 VCC 1MA -1.5M
```

$$HXY = v_{13-20} = 500i_{VIN1}i_{VIN2}$$

```
HXY 13 20 POLY(2) VIN1 VIN2 0 0 0 0 500
```

Nonlinear Controlled Sources

- Type: $y = b(v_c, i_c)$
where y can be a voltage or a current, b is an arbitrary function of the DC values of the controlling signals v_c and i_c
- Syntax
BXXXXXXXX N+ N- <I=EXPR> <V=EXPR>
- Available functions and operators for the expression:

abs	asinh	cosh	sin			
acos	atan	exp	sinh	+	-	*
acosh	atanh	ln	sqrt	/	^	unary -
asin	cos	log	tan			

Examples of Nonlinear Controlled Sources

$$i_2 = \cos(v_1) + \sin(v_3)$$

$$\text{B1 } 0 \ 2 \ \text{I}=\cos(v(1))+\sin(v(3))$$

$$v_{2-3} = \ln(\cos(\log(v_{1-2}^2))) + v_3 v_1$$

$$\text{B2 } 2 \ 3 \ \text{V}=\ln(\cos(\log(v(1,2)^2)))+v(3)*v(1)$$

$$v_5 = 7e^{\pi i v_d}$$

$$\text{B3 } 5 \ 0 \ \text{V}=7*\exp(\text{pi}*i(Vd))$$

Ejemplo: Sensor de Presión Piezoresistivo

Simular un transductor piezoeléctrico de dos terminales cuya resistencia eléctrica r depende de su estrés mecánico σ (presión) y de su temperatura T , según la ecuación:



$$r = r_0 \left(1 + \alpha T + \frac{2k\sigma}{1 - k\sigma} \right)$$

r_0 es la resistencia del transductor a 0 grados centígrados y 0 KPa de presión ($r_0 = 10\text{K}\Omega$)

α y k son constantes conocidas ($\alpha = 5 \times 10^{-3}$ y $k = 0.006$)

Sensor de Presión Piezoresistivo
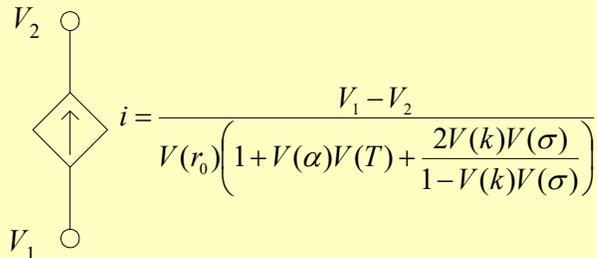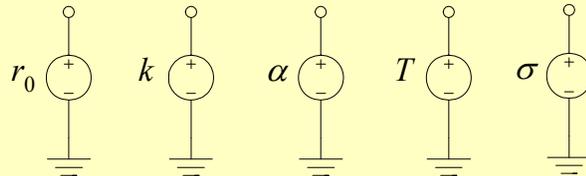
$$r = r_0 \left(1 + \alpha T + \frac{2k\sigma}{1 - k\sigma} \right)$$



Dr. J. E. Rayas-Sánchez

13

Sensor de Presión Piezoresistivo (cont)

$$r = r_0 \left(1 + \alpha T + \frac{2k\sigma}{1 - k\sigma} \right) \quad (r_0 = 10\text{K}\Omega, \alpha = 5 \times 10^{-3}, k = 0.006)$$

probando la ecuación...


```
Strain Transducer Equation
*
vk k 0 DC 0.006
vT T 0 DC 0
valfa alpha 0 DC 5e-3
vsigma sigma 0 DC 0
vr0 r0 0 DC 10K
bp 0 r i=v(r0)*(1+v(alpha)*v(T)+2*v(k)*v(sigma)/(1-v(k)*v(sigma)))
RL r 0 1
.control
DC vsigma 0 100 0.1
plot v(r)
DC vT -40 120 0.1
plot v(r)
DC vsigma 0 100 1 vT -40 120 20
plot v(r)
.endc
.end
```

Dr. J. E. Rayas-Sánchez

14

Sensor de Presión Piezoresistivo (cont)
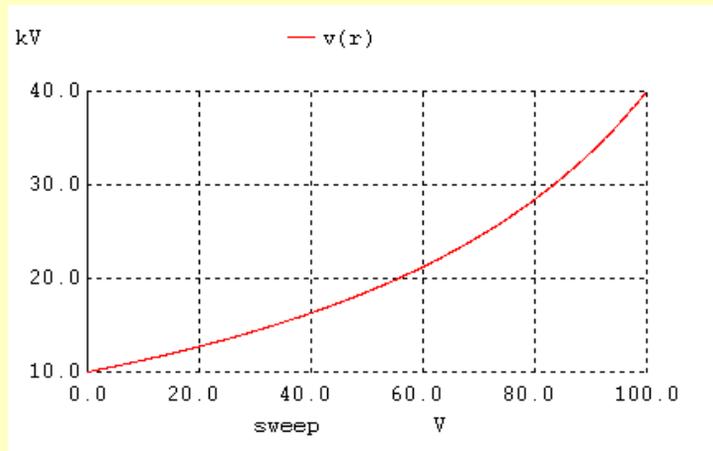
$$r = r_0 \left(1 + \alpha T + \frac{2k\sigma}{1 - k\sigma} \right) \quad r \text{ vs. } \sigma \text{ con } T = 0 \text{ }^\circ\text{C}$$




Dr. J. E. Rayas-Sánchez

15

Sensor de Presión Piezoresistivo (cont)
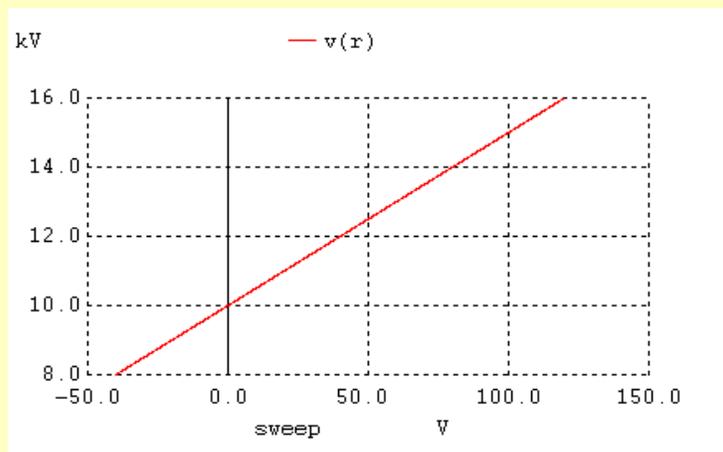
$$r = r_0 \left(1 + \alpha T + \frac{2k\sigma}{1 - k\sigma} \right) \quad r \text{ vs. } T \text{ con } \sigma = 0 \text{ KPa}$$




Dr. J. E. Rayas-Sánchez

16

Sensor de Presión Piezoresistivo (cont)
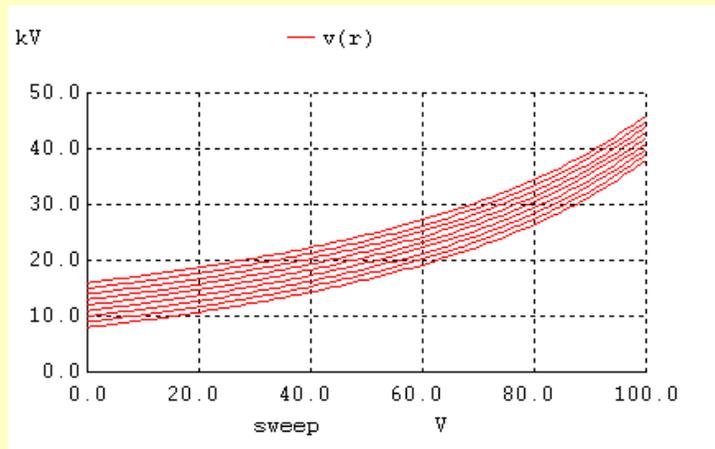
$$r = r_0 \left(1 + \alpha T + \frac{2k\sigma}{1 - k\sigma} \right) \quad r \text{ vs. } \sigma \text{ con } T: -40 \text{ a } 120 \text{ } ^\circ\text{C}$$



Dr. J. E. Rayas-Sánchez

17

Sensor de Presión Piezoresistivo (cont)

Plotting in WinSpice with suitable text labels:

```
.control
destroy all
DC vsigma 0 100 0.1
r = v(r)
plot r xunits KPa yunits Ohms xlabel sigma
DC vT -40 120 0.1
r = v(r)
plot r xunits Celsius yunits Ohms xlabel T
DC vsigma 0 100 1 vT -40 120 20
r = v(r)
plot r xunits KPa yunits Ohms xlabel sigma
.endc
```


(only for WinSpice version 2004 or newer)

Dr. J. E. Rayas-Sánchez

18

Sensor de Presión Piezoresistivo (cont)
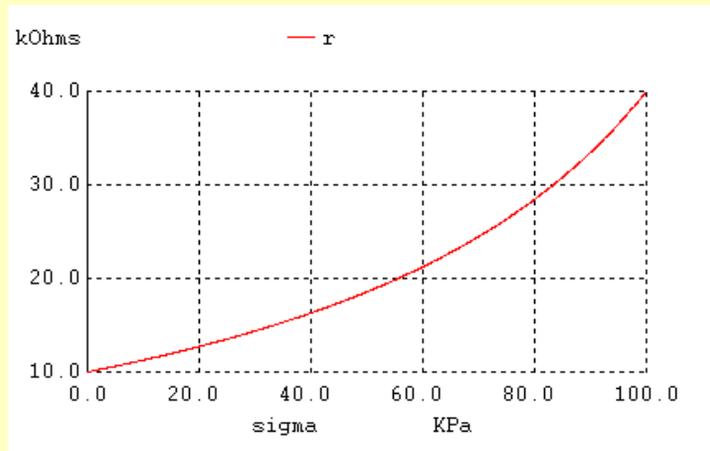
$$r = r_0 \left(1 + \alpha T + \frac{2k\sigma}{1 - k\sigma} \right) \quad r \text{ vs. } \sigma \text{ con } T = 0 \text{ }^\circ\text{C}$$




Dr. J. E. Rayas-Sánchez

19

Sensor de Presión Piezoresistivo (cont)
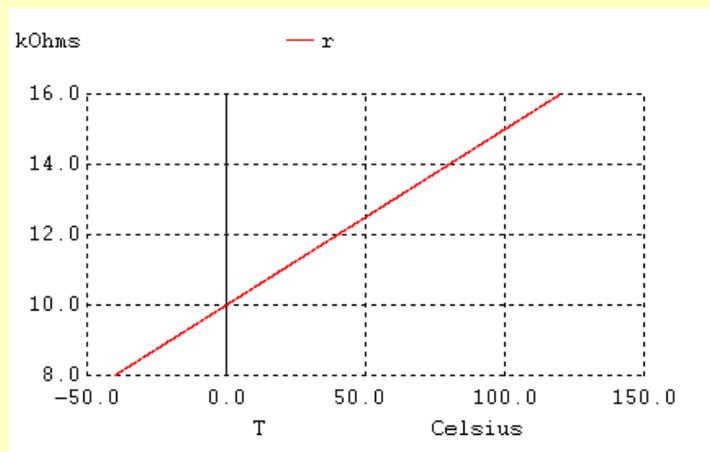
$$r = r_0 \left(1 + \alpha T + \frac{2k\sigma}{1 - k\sigma} \right) \quad r \text{ vs. } T \text{ con } \sigma = 0 \text{ KPa}$$




Dr. J. E. Rayas-Sánchez

20

Sensor de Presión Piezoresistivo (cont)
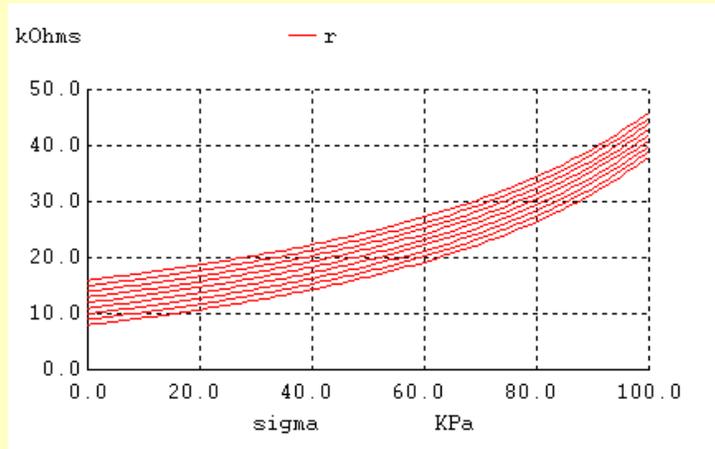
$$r = r_0 \left(1 + \alpha T + \frac{2k\sigma}{1 - k\sigma} \right) \quad r \text{ vs. } \sigma \text{ con } T: -40 \text{ a } 120 \text{ } ^\circ\text{C}$$




Dr. J. E. Rayas-Sánchez

21

Usando el Sensor de Presión Piezoresistivo
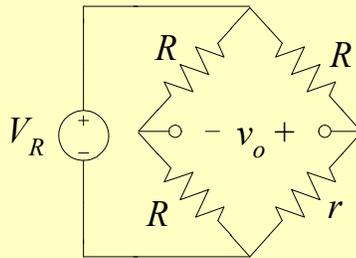
$$r = r_0 \left(1 + \alpha T + \frac{2k\sigma}{1 - k\sigma} \right)$$



$$V_R = 5V$$

$$R = 10K\Omega$$


Strain Transducer in Wheatstone Bridge

```
*
VR vcc 0 5V
R1 vcc outn 10K
R2 vcc outp 10K
R3 outn 0 10K
vk k 0 DC 0.006
vT T 0 DC 0
valfa alpha 0 DC 5e-3
vsigma sigma 0 DC 0
vr0 r0 0 DC 10K
bp outp 0 i=v(outp)/(v(r0)*(1+v(alpha)*v(T)
+ +2*v(k)*v(sigma)/(1-v(k)*v(sigma))))
.control
DC vsigma 0 100 0.1
plot v(outp,outn)
DC vT -40 120 0.1
plot v(outp,outn)
DC vsigma 0 100 1 vT -40 120 20
plot v(outp,outn)
.endc
.end
```

Dr. J. E. Rayas-Sánchez


22

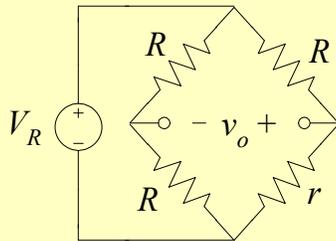Usando el Sensor de Presión Piezoresistivo (cont)




$$r = r_0 \left(1 + \alpha T + \frac{2k\sigma}{1 - k\sigma} \right)$$

v_o vs. σ con $T = 0$ °C

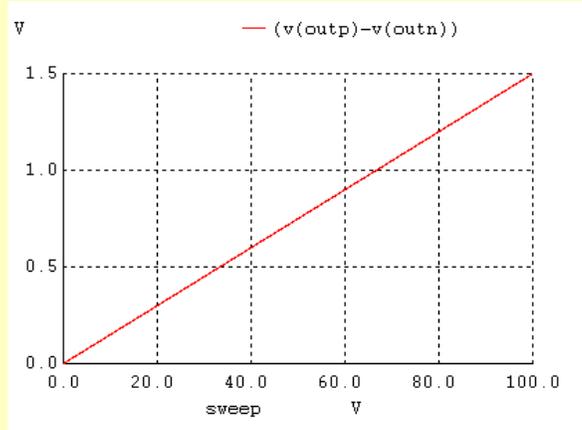


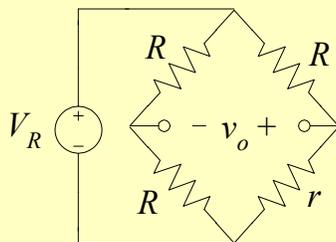Usando el Sensor de Presión Piezoresistivo (cont)




$$r = r_0 \left(1 + \alpha T + \frac{2k\sigma}{1 - k\sigma} \right)$$

v_o vs. T con $\sigma = 0$ kPa

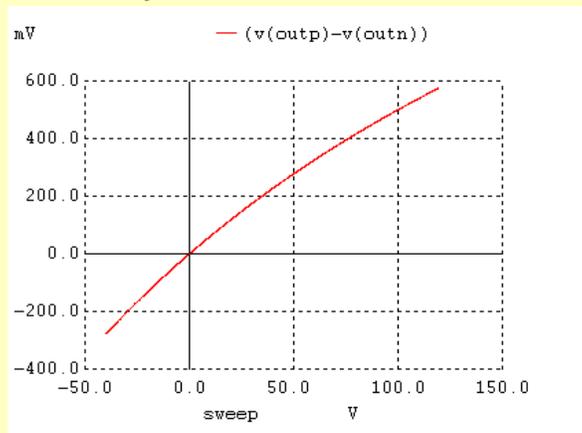


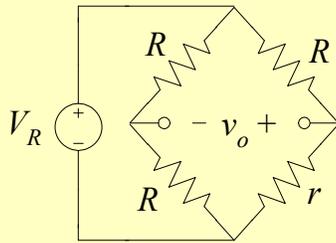Usando el Sensor de Presión Piezoresistivo (cont)



$$r = r_0 \left(1 + \alpha T + \frac{2k\sigma}{1 - k\sigma} \right)$$


v_o vs. σ con $T: -40$ a 120 °C

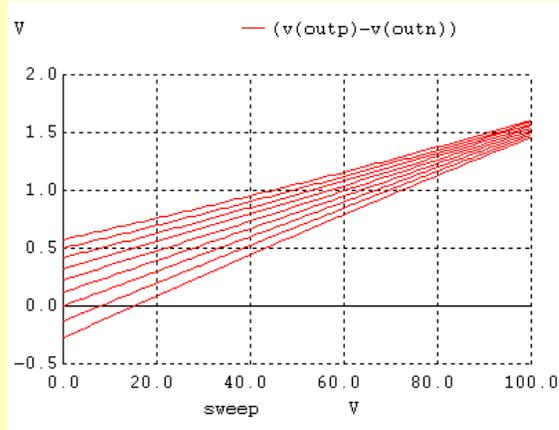

Dr. J. E. Rayas-Sánchez


25

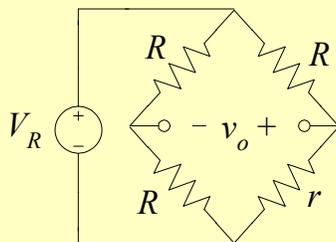Usando el Sensor de Presión Piezoresistivo (cont)



$$r = r_0 \left(1 + \alpha T + \frac{2k\sigma}{1 - k\sigma} \right)$$

v_o vs. σ con $T = 0$ °C

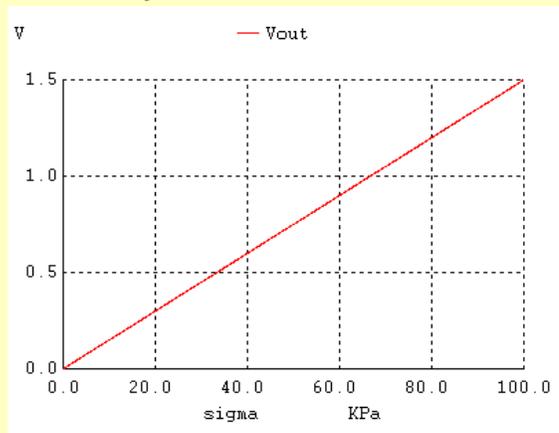


Dr. J. E. Rayas-Sánchez

(controlling labels and units)


26

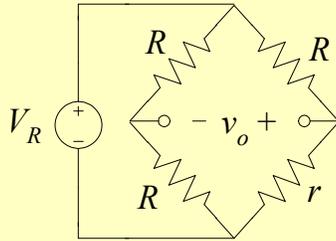Usando el Sensor de Presión Piezoresistivo (cont)



$$r = r_0 \left(1 + \alpha T + \frac{2k\sigma}{1 - k\sigma} \right)$$


v_o vs. T con $\sigma = 0$ kPa

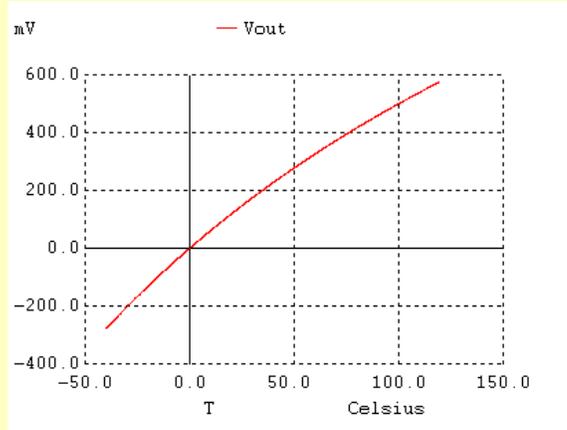

Dr. J. E. Rayas-Sánchez


(controlling labels and units) 27

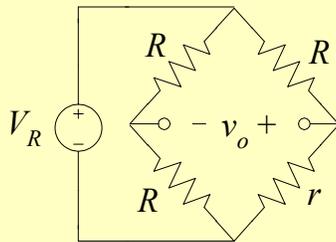Usando el Sensor de Presión Piezoresistivo (cont)



$$r = r_0 \left(1 + \alpha T + \frac{2k\sigma}{1 - k\sigma} \right)$$

v_o vs. σ con $T : -40$ a 120 °C

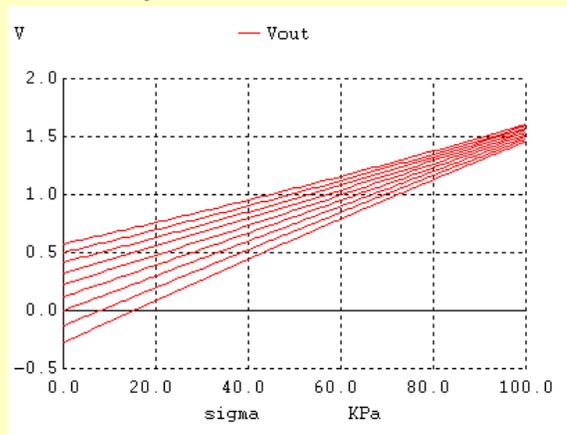

Dr. J. E. Rayas-Sánchez

(controlling labels and units) 28