

Modeling Sensors and other Physical Systems with SPICE

(Part 2)


Dr. José Ernesto Rayas-Sánchez

1

Characterization of Sensors and Transducers

- Analytical functions
 - Multidimensional vector functions ✓
 - Nonlinear systems of equations
 - Systems of nonlinear differential equations
- Measurements

System of Nonlinear Equations

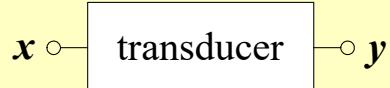

x Vector of physical variables (temperature, humidity, pressure, volumetric flow, etc.)

y Vector of electrical outputs (voltage, current, charge, resistance, etc.)


$$\mathbf{f}(x, y) = \mathbf{0}$$

$$x \in \mathbb{R}^n \quad f, y \in \mathbb{R}^m \quad f : \mathbb{R}^{n+m} \rightarrow \mathbb{R}^m$$

Implementing $\mathbf{f}(x, y) = \mathbf{0}$ with SPICE

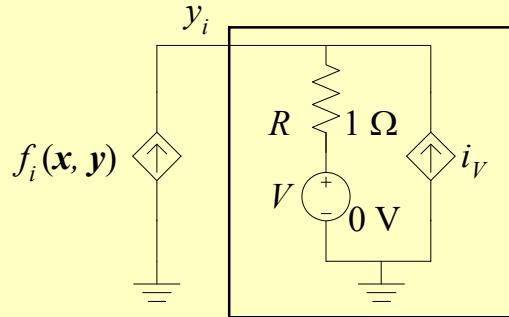
- 1) Implement each physical variable, x_i, \dots, x_n with a DC voltage source, isolated from the rest of the circuit
- 2) Implement each constant or any other parameter using also an isolated DC voltage source
- 3) Use a linear or nonlinear voltage controlled current source to implement each function f_1, \dots, f_m , and connect them to the following infinite input impedance subcircuit named Variable

Implementing $f(x, y) = 0$ with SPICE (cont.)



SPICE finds the voltage y_i such that the current $f_i = 0$, for $i = 1 \dots m$

Subcircuit Variable

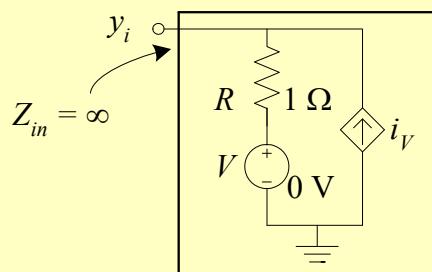

```
.SUBCKT Variable Yi
RR Yi internal 1
VV internal 0 0V
FIV 0 Yi VV 1
.ENDS
```

Example of Simulating $f(x, y) = \mathbf{0}$

$$f(x, y) = \begin{bmatrix} 10y_1 - x_1 \\ y_1 + x_2 y_2 \end{bmatrix} = \mathbf{0}$$

$$x_1 = [0, 10]$$

$$x_2 = 0.5$$

System of Equations, Example 1

```

Vx1 x1 0 DC 1
Vx2 x2 0 DC 0.5
b1 0 y1 i = 10*v(y1) - v(x1)
XY1 y1 Variable
b2 0 y2 i = v(y1) + v(x2)*v(y2)
XY2 y2 Variable
.NODESET V(y1)=0 V(y2)=0

.SUBCKT Variable Yi
RR Yi internal 1
VV internal 0 OV
FIV 0 Yi VV 1
.ENDS

.control
DC Vx1 0 10 1
plot v(y1) v(y2)
.endc
.end

```

Dr. J. E. Rayas-Sánchez


7

Example of Simulating $f(x, y) = \mathbf{0}$ (cont.)

$$f(x, y) = \begin{bmatrix} 10y_1 - x_1 \\ y_1 + x_2 y_2 \end{bmatrix} = \mathbf{0}$$

$$x_1 = [0, 10]$$

$$x_2 = 0.5$$

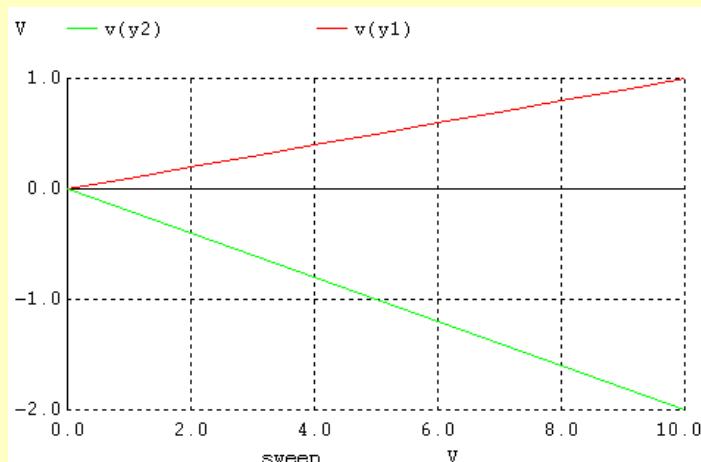


Dr. J. E. Rayas-Sánchez

8

Characterization of Sensors and Transducers

- Analytical functions
 - Multidimensional vector functions ✓
 - Nonlinear systems of equations ✓
 - Systems of nonlinear differential equations
- Measurements

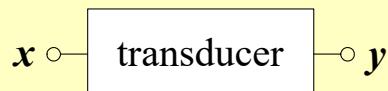System of Nonlinear Differential Equations



x Vector of physical variables (temperature, humidity, pressure, volumetric flow, etc.)

y Vector of electrical outputs (voltage, current, charge, resistance, etc.)

$$\mathbf{f}(\mathbf{x}, \mathbf{y}, \mathbf{y}', t) = \mathbf{0}$$


$$\mathbf{x} \in \mathbb{R}^n \quad \mathbf{f}, \mathbf{y} \in \mathbb{R}^m \quad \mathbf{y}' \in \mathbb{R}^{m'} \quad t \in \mathbb{R} \quad \mathbf{f} : \mathbb{R}^{n+m+m'+1} \rightarrow \mathbb{R}^m$$

\mathbf{y}' contains the first order derivatives w.r.t time t of some of the elements of \mathbf{y}

Implementing $f(x, y, y', t) = 0$ with SPICE

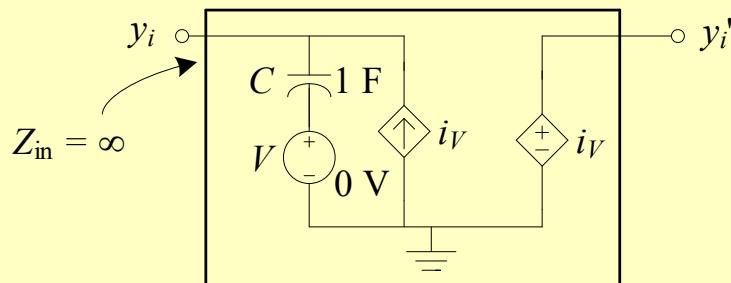- 1) Implement each physical variable, x_i, \dots, x_n with a DC voltage source, isolated from the rest of the circuit
- 2) Implement each constant or any other parameter using also an isolated DC voltage source
- 3) Use a voltage controlled current source to implement each function f_1, \dots, f_m ,
- 4) If function f_i does not contain a derivative, connect f_i to the subcircuit named Variable
- 5) If function f_i contains a derivative, connect f_i to the following infinite input impedance subcircuit named Derivative


Implementing $f(x, y, y', t) = 0$ with SPICE (cont.)



SPICE finds the voltage y_i such that the current $f_i = 0$

$$i_V = C \frac{dy_i}{dt} = y'_i$$

Subcircuit Derivative

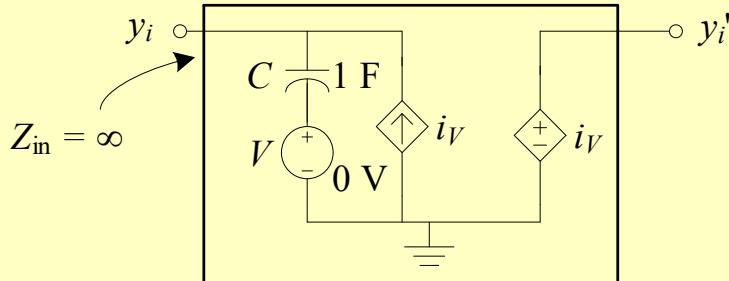

```
.SUBCKT Derivative Yi Yi_prime
CC Yi internal 1
VV internal 0 0V
FIV 0 Yi VV 1
HIV Yi_prime 0 VV 1
.ENDS
```

Ejemplo de Derivación con SPICE


$$x = \sin(2\pi t)$$

$$\frac{dx}{dt} = ?$$

```
Derivative, Example 1
Vx in 0 DC 0 SIN(0 1 1)
Xx_dxdt in out Derivative
.SUBCKT Derivative Yi Yi_prime
CC Yi internal 1
VV internal 0 0V
FIV 0 Yi VV 1
HIV Yi_prime 0 VV 1
.ENDS
.control
destroy all
TRAN 1ms 3s
plot v(in) v(out)
.endc
.end
```

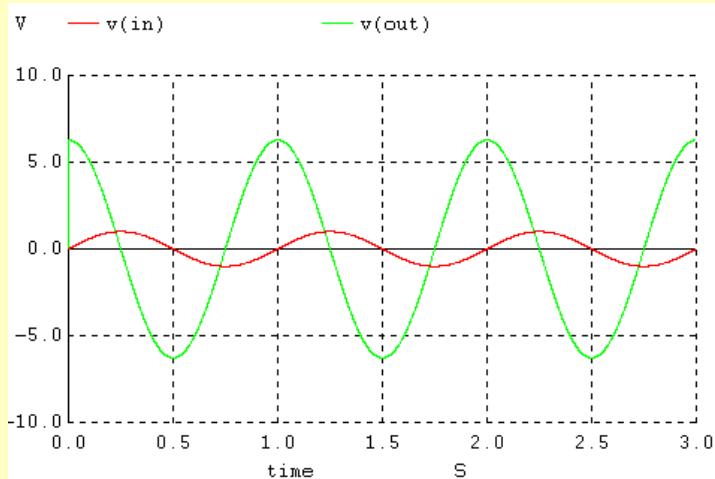Ejemplo de Derivación con SPICE (cont.)

$$x = \sin(2\pi t) \quad \frac{dx}{dt} = ?$$




Dr. J. E. Rayas-Sánchez

15

Ejemplo de Solución de $f(y, y', t) = 0$

$$\frac{dy}{dt} = 1 - y^2 \quad \rightarrow \quad f(y, t) = \frac{dy}{dt} - 1 + y^2 = 0$$

$$y(0) = 0$$

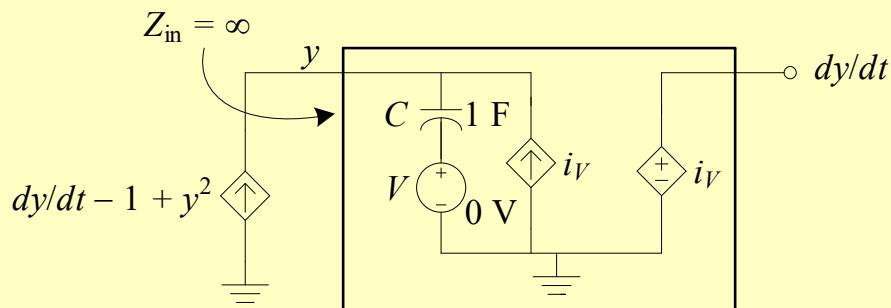

Dr. J. E. Rayas-Sánchez

16

Ejemplo de Solución de $f(y, y', t) = \mathbf{0}$ (cont.)

$$f(y, t) = \frac{dy}{dt} - 1 + y^2 = 0$$


$$y(0) = 0$$

```
Solving SNL_Diff_Eq, Example 1
b1 0 in i = v(out) - 1 + v(in)*v(in)
Xy_dydt in out Derivative
.IC v(in) = 0
.SUBCKT Derivative Yi Yi_prime
CC Yi internal 1
VV internal 0 0V
FIv 0 Yi VV 1
HIv Yi_prime 0 VV 1
.ENDS
.control
TRAN 1ms 3s
plot v(in) v(out)
.endc
.end
```

Ejemplo de Solución de $f(y, y', t) = \mathbf{0}$ (cont.)

$$f(y, t) = \frac{dy}{dt} - 1 + y^2 = 0$$

$$y(0) = 0$$

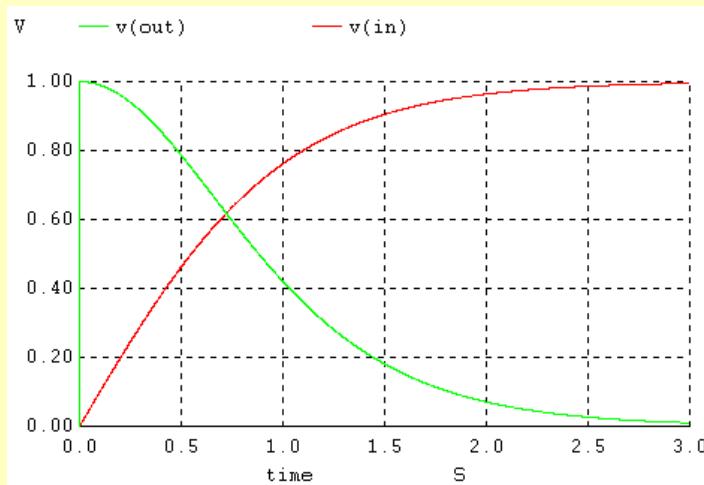

Ejemplo de Solución de $f(y, y', t) = \mathbf{0}$ (cont.)

$$f(y, t) = \frac{dy}{dt} - 1 + y^2 = 0 \quad \text{Otra forma equivalente:}$$

$$y(0) = 0$$

```
Solving SNL_Diff_Eq, Example 1
GG 0 in poly(2) out 0 in 0 -1 1 0 0 0 1
Xy_dydt in out Derivative
.IC v(in) = 0
.SUBCKT Derivative Yi Yi_prime
CC Yi internal 1
VV internal 0 0V
FIv 0 Yi VV 1
HIv Yi_prime 0 VV 1
.ENDS
.control
TRAN 1ms 3s
plot v(in) v(out)
.endc
.end
```