

Modeling Sensors and other Physical Systems with SPICE

(Part 3)


Dr. José Ernesto Rayas-Sánchez

1

Characterization of Sensors and Transducers

- Analytical functions ✓
 - Multidimensional vector functions ✓
 - Nonlinear systems of equations ✓
 - Systems of nonlinear differential equations ✓
- Measurements


Sensors Characterized by Measurements

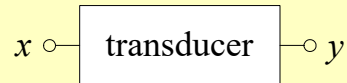

x Physical variable (temperature, humidity, pressure, volumetric flow, etc.)

y Output voltage, a piece-wise linear function of x

Piece-Wise Linear Functions

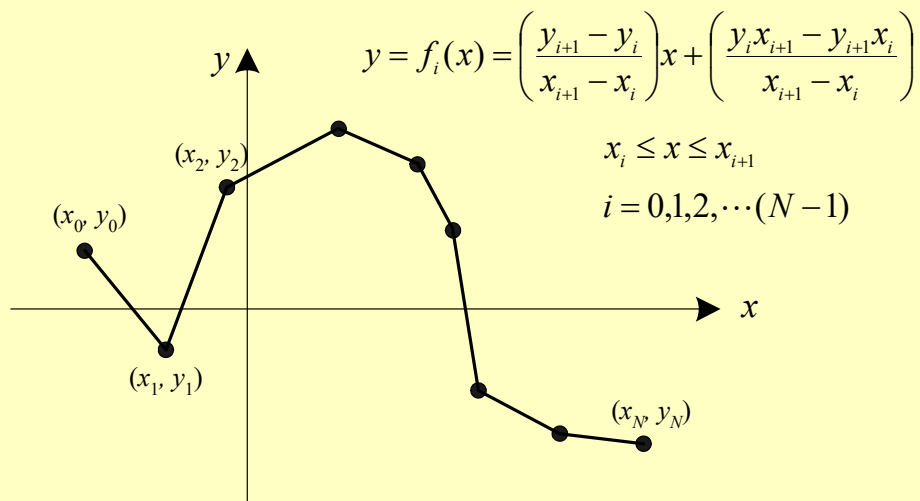


Implementing Piece-Wise Linear Functions

- 1) Implement each point (x_i, y_i) with a couple of DC voltage sources, for $i = 0 \dots N-1$
- 2) For each interval $x_i \leq x \leq x_{i+1}$, with $i = 0 \dots N-1$, call a subcircuit `LineSegment` with an arbitrary but unique name. The six nodes of the subcircuit should be used for x, y, x_i, y_i, x_{i+1} , and y_{i+1}

Dr. J. E. Rayas-Sánchez

5

Subcircuit LineSegment

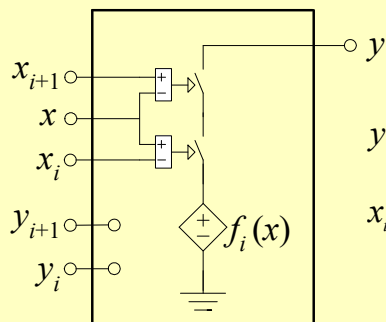

$$y = f_i(x) = \left(\frac{y_{i+1} - y_i}{x_{i+1} - x_i} \right) x + \left(\frac{y_i x_{i+1} - y_{i+1} x_i}{x_{i+1} - x_i} \right)$$

$$x_i \leq x \leq x_{i+1}$$

```
.SUBCKT LineSegment x y Xi Yi Xin Yin
bfi in1 0 V = ((v(Yin)-v(Yi))/(v(Xin)-v(Xi)))*v(x) +
+ (v(Yi)*v(Xin)-v(Yin)*v(Xi))/(v(Xin)-v(Xi))
s1 in2 in1 x Xi SwitchModel off
s2 y in2 Xin x SwitchModel off
.model SwitchModel sw
.ENDS
```

Dr. J. E. Rayas-Sánchez

6

Example

Piece-wise Linear function, Example 1

```

Vx0 x0 0 DC 0
Vy0 y0 0 DC 0
Vx1 x1 0 DC 0.5
Vy1 y1 0 DC 1
Vx2 x2 0 DC 1
Vy2 y2 0 DC 3
Vx3 x3 0 DC 1.5
Vy3 y3 0 DC -1
Vx4 x4 0 DC 2
Vy4 y4 0 DC -2
Vx5 x5 0 DC 2.5
Vy5 y5 0 DC 4
Vx x 0 DC 0
xlins1 x y x0 y0 x1 y1 LineSegment
xlins2 x y x1 y1 x2 y2 LineSegment
xlins3 x y x2 y2 x3 y3 LineSegment
xlins4 x y x3 y3 x4 y4 LineSegment
xlins5 x y x4 y4 x5 y5 LineSegment


.SUBCKT LineSegment x y Xi Yi Xin Yin
bfi in1 0 v = ((v(Yin)-v(Yi))/(v(Xin)-v(Xi)))*v(x) +
+ (v(Yi)*v(Xin)-v(Yin)*v(Xi))/(v(Xin)-v(Xi))
s1 in2 in1 x Xi SwitchModel off
s2 y in2 Xin x SwitchModel off
.model SwitchModel sw
.ENDS

.control
DC Vx 0.01 2.5 0.01
plot v(y)
.endc
.end
    
```

Dr. J. E. Rayas-Sánchez

7

Example (cont.)

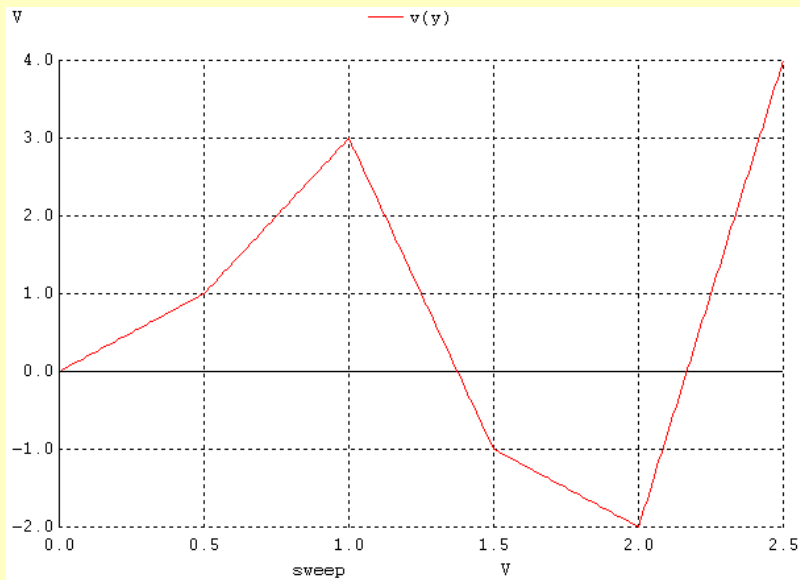

Dr. J. E. Rayas-Sánchez

8

References

- R. Saleh and A. Yang, “Modeling Mixed Systems with SPICE3,” *IEEE Circuits and Devices Magazine*, vol. 9, pp. 7-11, Sept. 1993.
- C. D. Johnson, *Process Control Instrumentation Technology*. Toronto, ON: Wiley, 1988.
- J. Fraden, *AIP Handbook of Modern Sensors: Physics, Designs and Applications*. New York, NY: American Institute of Physics, 1993.
- <https://www.omega.com/en-us/technical-reference>
- S. Franco, *Design with Operational Amplifiers and Analog Integrated Circuits*. New York, NY: McGraw Hill, 1988.