

BJT Biasing Circuits

Dr. José Ernesto Rayas Sánchez

Some figures of this presentation were taken from the instructional resources of the following textbooks:
A. S. Sedra and K. C. Smith, *Microelectronic Circuits*. New York, NY: Oxford University Press, 2003.

1

Outline

- Biasing a BJT
- Examples of biasing circuits
- Stability of the bias point
- Examples of stabilizing bias points


Biasing a Bipolar Transistor

- A BJT can be biased in any of its operational regions


		Collector-Base Junction (CB)	
		Forward-biased	Reversed-biased
Base-Emitter Junction (BE)	Forward-biased	Saturation Region (switch on)	Active Region (good amplifier)
	Reversed-biased	Inverted Active Region (poor amplifier)	Cutoff Region (switch off)

- For most applications, BJTs are biased in the active region
- The bias point is also called the operation point, and is defined by the transistor DC voltages and currents

BJT Biasing Circuits – Example 1

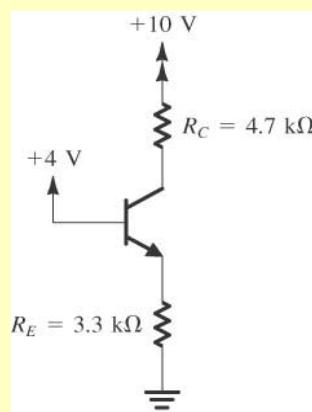


BJT Biasing Circuits – Example 2

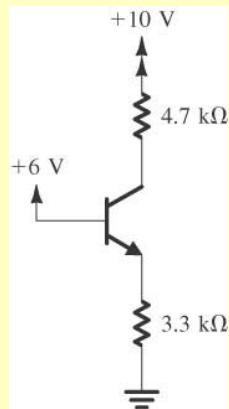

Dr. J. E. Rayas Sánchez

5


BJT Biasing Circuits – Example 3

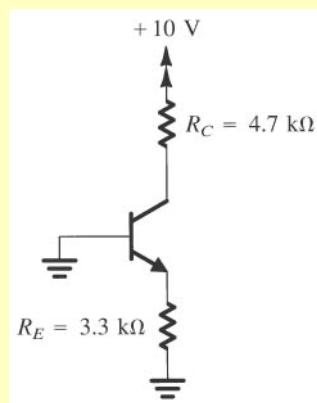

Dr. J. E. Rayas Sánchez

6


BJT Biasing Circuits – Example 4

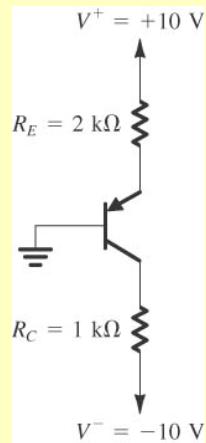

Dr. J. E. Rayas Sánchez

7


BJT Biasing Circuits – Example 5

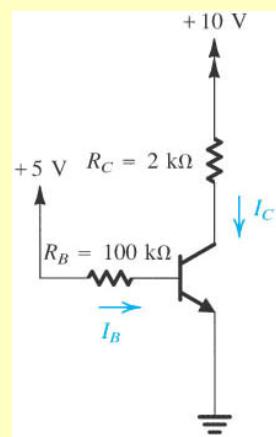

Dr. J. E. Rayas Sánchez

8


BJT Biasing Circuits – Example 6

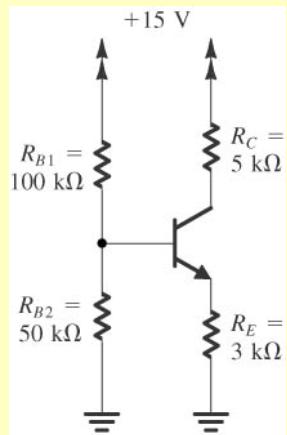

Dr. J. E. Rayas Sánchez

9


BJT Biasing Circuits – Example 7

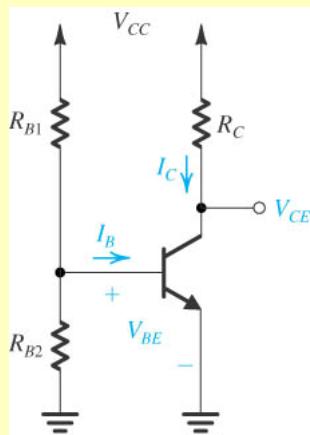

Dr. J. E. Rayas Sánchez

10


BJT Biasing Circuits – Example 8

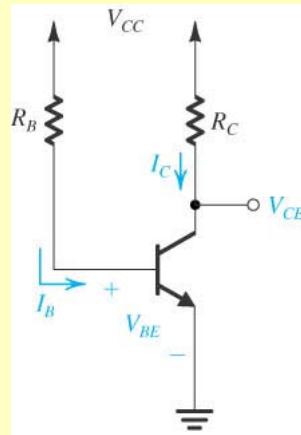

Dr. J. E. Rayas Sánchez

11


BJT Biasing Circuits – Example 9

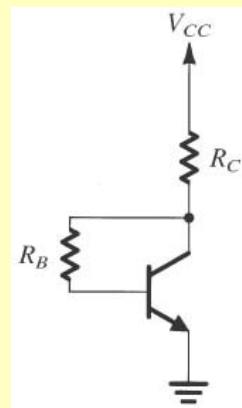


Dr. J. E. Rayas Sánchez

12


BJT Biasing Circuits – Example 10

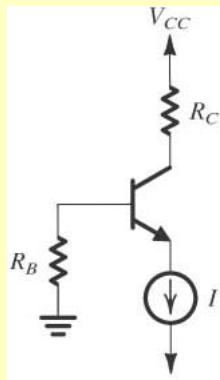


Current source I can be implemented by:

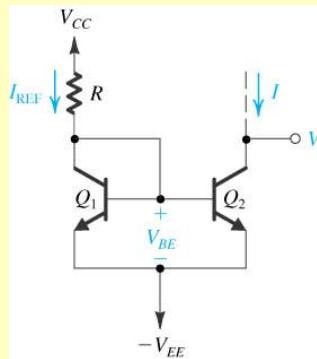

BJT Biasing Circuits – Example 11

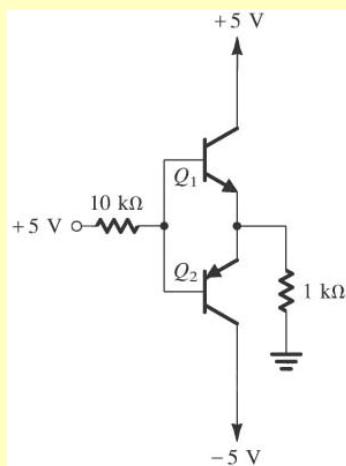

BJT Biasing Circuits – Example 12

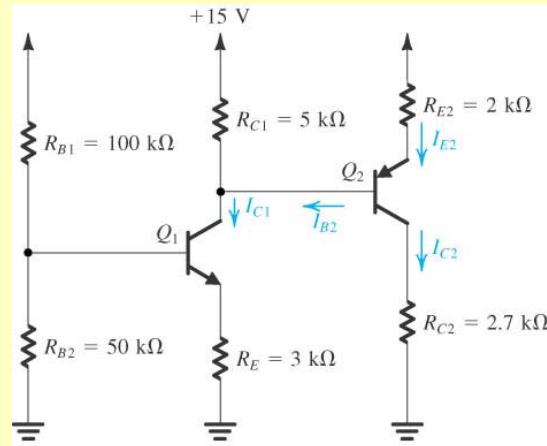

Dr. J. E. Rayas Sánchez

15


Bias Stability

- A bias point is stable if it is little sensitive to variations of BJT internal parameters, mainly β and V_{BE}
- The bias point stability depends on the biasing circuit topology and element values
- Some biasing circuits can be made more stable than others

Dr. J. E. Rayas Sánchez

16

Making a Bias Point Stable – Example 1

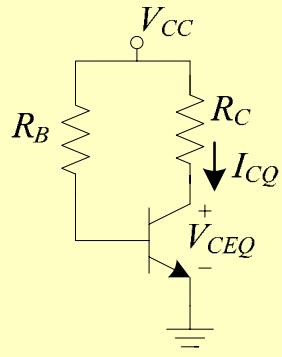

$$V_{CEQ} = V_{CC} - I_{CQ}R_C$$


$$I_{CQ} = \beta \frac{V_{CC} - V_{BE}}{R_B}$$

Making $V_{CC} \gg V_{BE}$

$$I_{CQ} \approx \beta \frac{V_{CC}}{R_B}$$

This biasing circuit can make the bias point stable against variations in V_{BE} only

Making a Bias Point Stable – Example 2

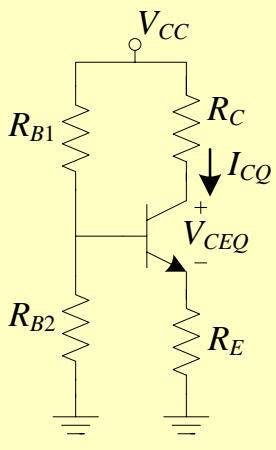

$$V_{TH} = \frac{R_{B2}V_{CC}}{R_{B1} + R_{B2}} \quad R_{TH} = R_{B1} \parallel R_{B2}$$

$$V_{CEQ} = V_{CC} - I_{CQ}(R_E + R_C)$$

$$I_{CQ} = \frac{V_{TH} - V_{BE}}{\frac{R_{TH}}{\beta} + R_E}$$

Making $R_E \gg R_{TH}/\beta$ and $V_{TH} \gg V_{BE}$

$$I_{CQ} \approx \frac{V_{TH}}{R_E}$$

This biasing circuit can make the bias point stable against variations in V_{BE} and β