

# **BJT Small-Signal Models**

**Dr. José Ernesto Rayas Sánchez**

Some figures of this presentation were taken from the instructional resources of the following textbook:  
A. S. Sedra and K. C. Smith, *Microelectronic Circuits*. New York, NY: Oxford University Press, 2003.


1

## **Outline**

---

- DC Bias + small-signal excitation
- Load lines
- Amplification process in BJTs
- Small-signal models
- DC and small-signal analysis: example
- N-port networks
- Z, Y and H-parameters
- Manufacturing data sheets


## DC Bias + Small-Signal Excitation

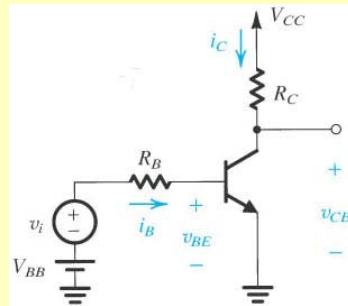

If  $v_i = 0$  (bias only):


$$V_{BB} - i_B R_B - v_{BE} = 0$$
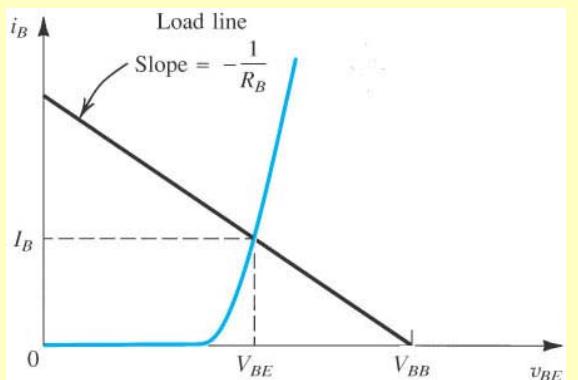
$$i_B = \frac{V_{BB} - v_{BE}}{R_B} \quad \rightarrow \text{Input Load Line}$$



Dr. J. E. Rayas Sánchez

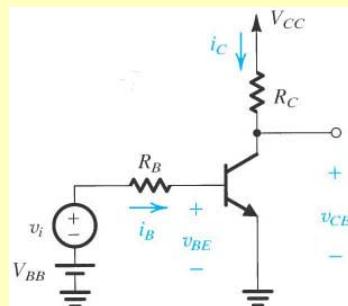
## DC Bias + Small-Signal Excitation (cont)



If  $v_i = 0$  (bias only):


$$V_{CC} - i_C R_C - v_{CE} = 0$$
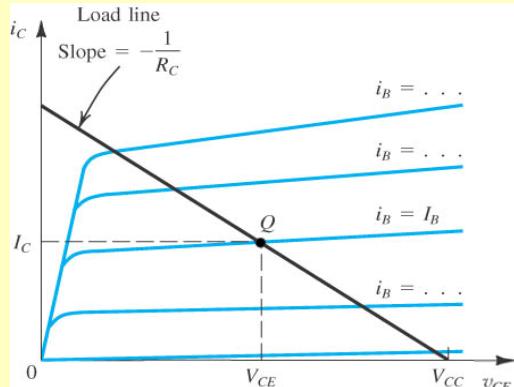
$$i_C = \frac{V_{CC} - v_{CE}}{R_C} \quad \rightarrow \text{Load Line}$$



Dr. J. E. Rayas Sánchez

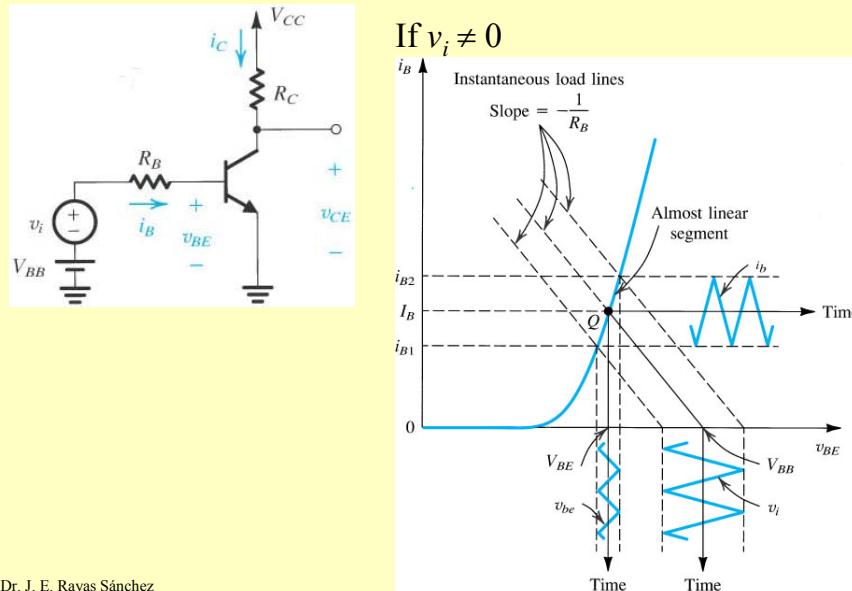
## DC Bias + Small-Signal Excitation (cont)



Dr. J. E. Rayas Sánchez

5
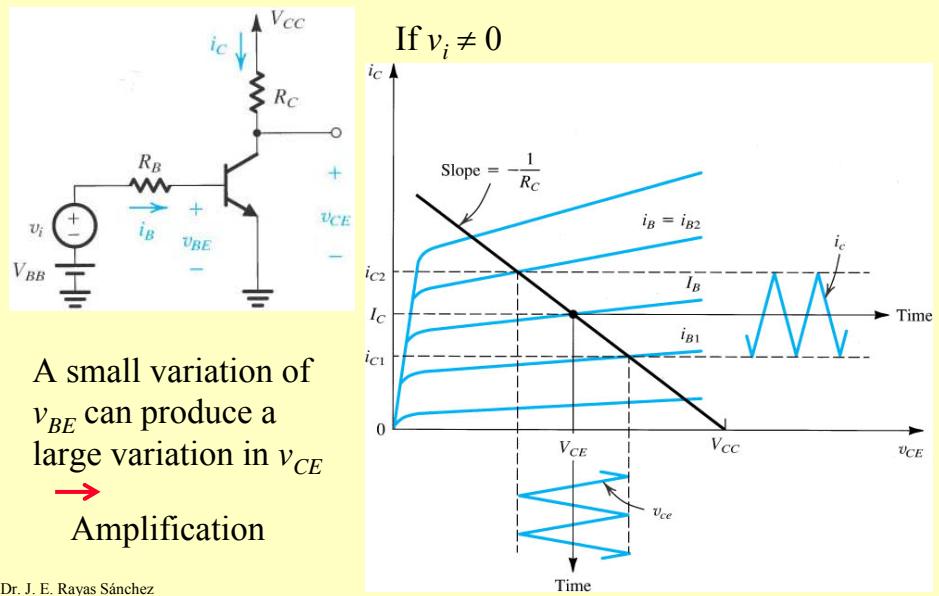
## DC Bias + Small-Signal Excitation (cont)





Dr. J. E. Rayas Sánchez



6

## BJT Small-Signal Models: T Model using $\beta$

- Neglecting output resistance,  $r_o$

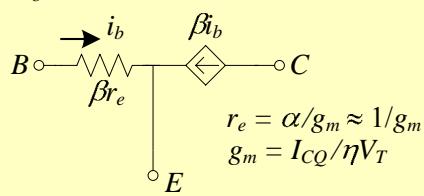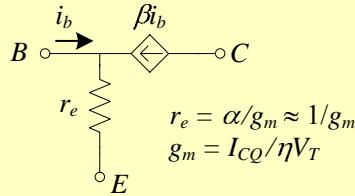

- Considering  $r_o$

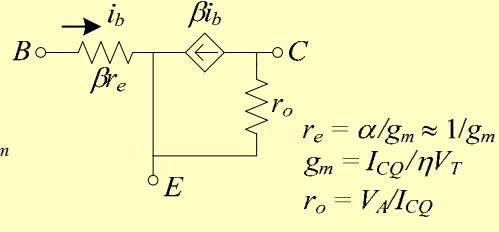
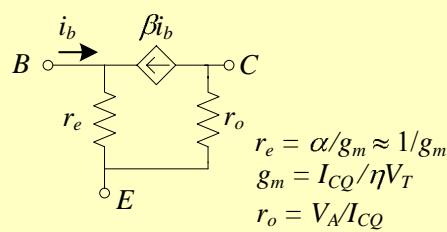


Dr. J. E. Rayas Sánchez



7

## BJT Small-Signal Models: T Model using $\alpha$

- Neglecting output resistance,  $r_o$

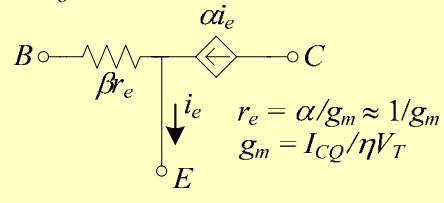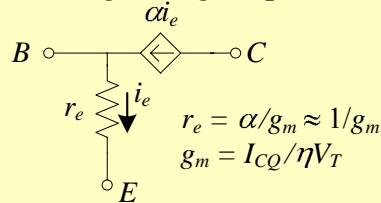

- Considering  $r_o$

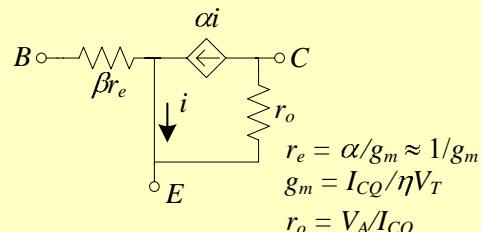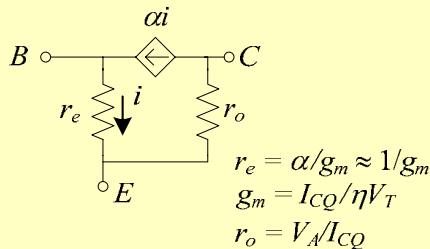


Dr. J. E. Rayas Sánchez


8

## BJT Small-Signal Models: Hybrid $\pi$ Model

- Neglecting output resistance,  $r_o$

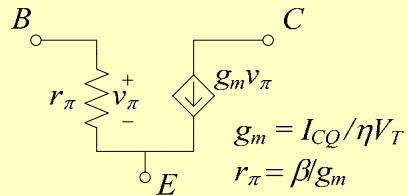


- Considering  $r_o$

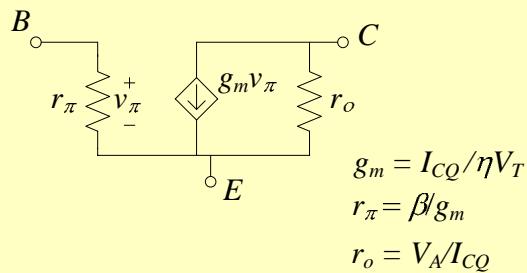

Dr. J. E. Rayas Sánchez

9
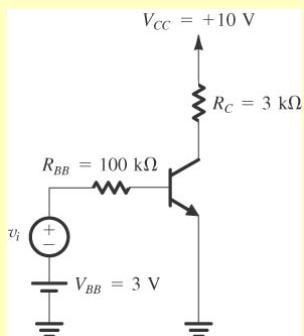
## DC and Small-Signal Analysis – Example



$$\beta = 100$$

$$\eta = 1$$

$$g_m = \frac{I_{CQ}}{\eta V_T} = \frac{0.23\text{ mA}}{25\text{ mV}} = 92\text{ m}\Omega^{-1}$$


$$r_\pi = \frac{\beta}{g_m} = \frac{100}{92\text{ m}\Omega^{-1}} = 1.087\text{ k}\Omega$$

Bias point calculation (DC analysis)

$$I_B = \frac{3\text{ V} - 0.7\text{ V}}{100\text{ k}\Omega} = 0.023\text{ mA}$$

$$I_C = 100I_B = 2.3\text{ mA}$$

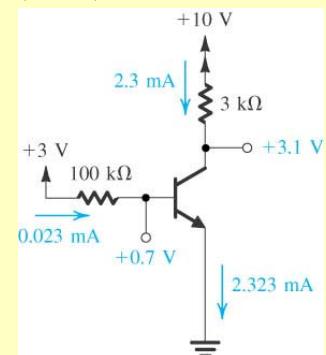
$$V_{CE} = 10\text{ V} - 2.3\text{ mA}(3\text{ k}\Omega) = 3.1\text{ V}$$



Dr. J. E. Rayas Sánchez



10
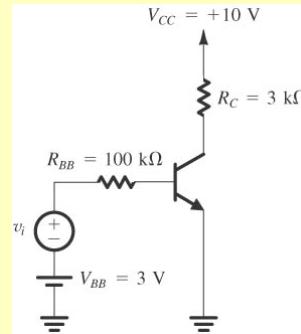
## DC and Small-Signal Analysis – Example (cont)



$$\begin{aligned}\beta &= 100 \\ \eta &= 1 \\ g_m &= 92 \text{ mΩ}^{-1} \\ r_\pi &= 1.087 \text{ kΩ}\end{aligned}$$

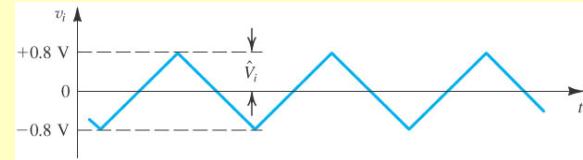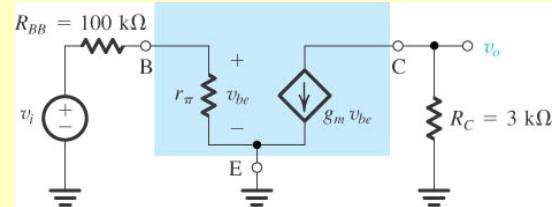
Small-signal equivalent circuit (neglecting  $r_o$ ):





Dr. J. E. Rayas Sánchez

11

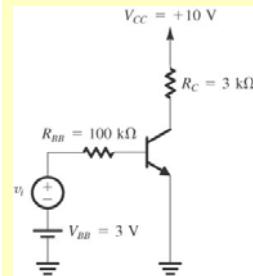
## DC and Small-Signal Analysis – Example (cont)



Small-signal analysis

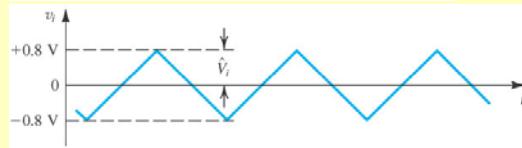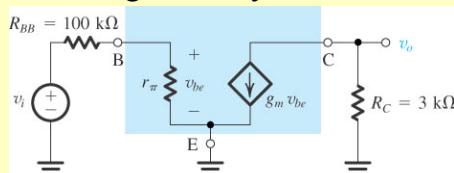
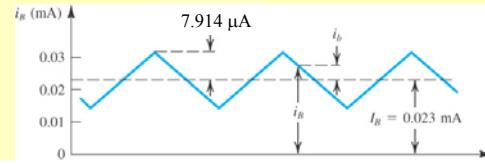
$$i_b = \frac{v_i}{R_{BB} + r_\pi} = \frac{0.8 \text{ V}}{100 \text{ kΩ} + 1.087 \text{ kΩ}} = 7.914 \text{ μA}$$



Dr. J. E. Rayas Sánchez


12

## BJT Small-Signal Models


Dr. José Ernesto Rayas Sánchez

February 19, 2007

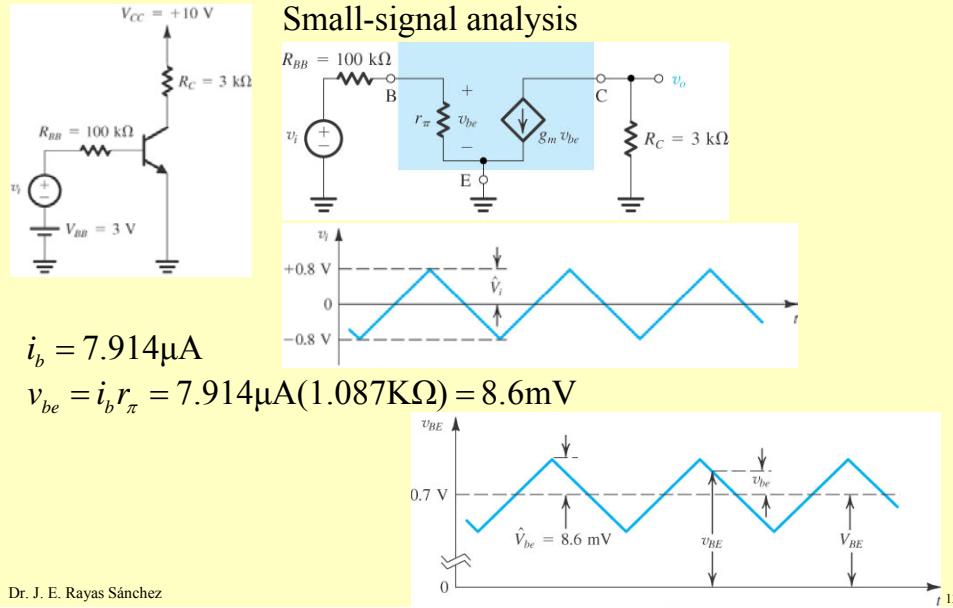
### DC and Small-Signal Analysis – Example (cont)


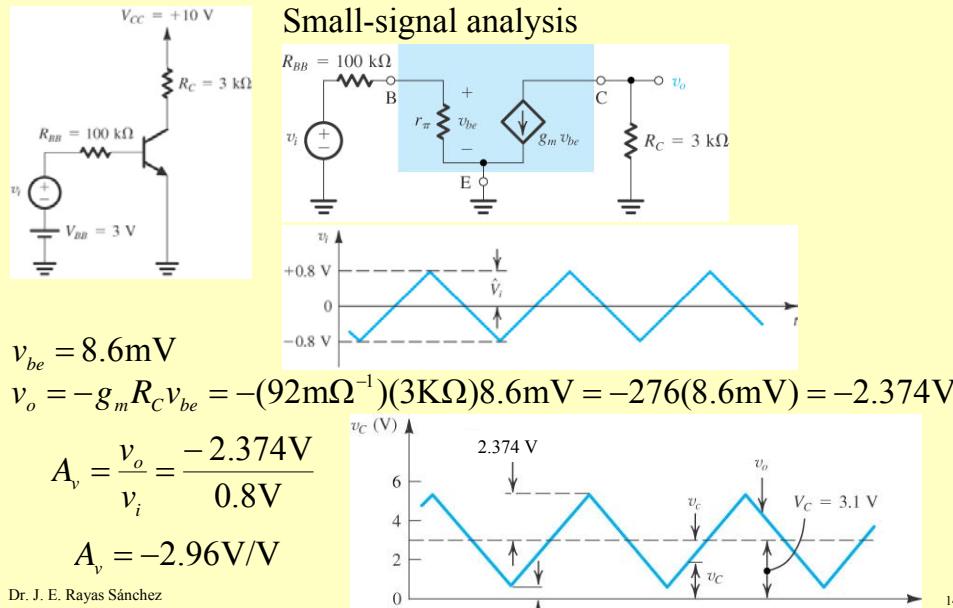
### DC and Small-Signal Analysis – Example (cont)



## N-Ports Networks (Linear Circuits)

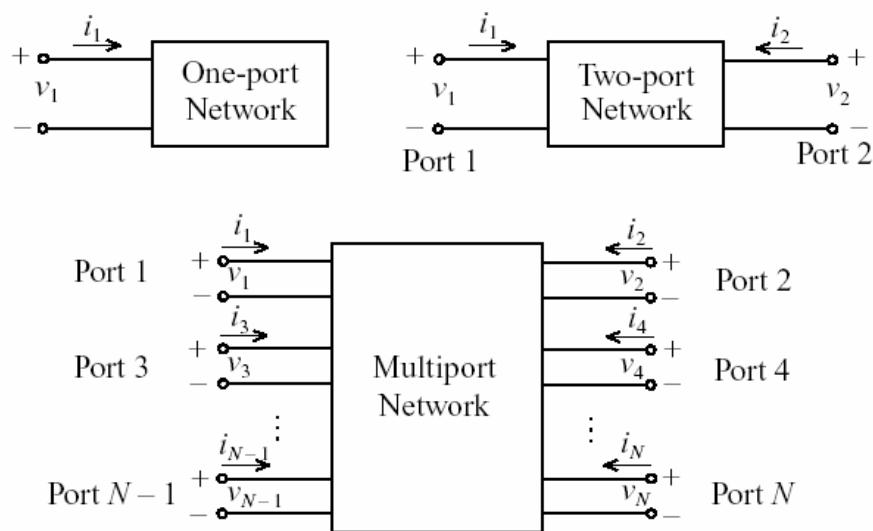

Dr. J. E. Rayas Sánchez

(R. Ludwig and P. Bretschko, RF Circuit Design, Prentice Hall, 2000) 15

## Impedance Matrix Representation ( $\mathbf{Z}$ )

$$\mathbf{V} = \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix} \quad \mathbf{I} = \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix} \quad \mathbf{V} = \mathbf{Z}\mathbf{I}$$

$$\mathbf{Z} = \begin{bmatrix} Z_{11} & Z_{12} & \dots & Z_{1N} \\ Z_{21} & Z_{22} & \dots & Z_{2N} \\ \vdots & & & \\ Z_{N1} & Z_{N2} & \dots & Z_{NN} \end{bmatrix}$$

Each element of matrix  $\mathbf{Z}$  is given by

$$Z_{ij} = \frac{V_i}{I_j} \Big|_{I_k=0 \text{ for } k \neq j}$$

Dr. J. E. Rayas Sánchez

16


## Admittance Matrix Representation ( $\mathbf{Y}$ )

$$\mathbf{V} = \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix} \quad \mathbf{I} = \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix} \quad \mathbf{Y} = \begin{bmatrix} Y_{11} & Y_{12} & \dots & Y_{1N} \\ Y_{21} & Y_{22} & \dots & Y_{2N} \\ \vdots & & & \\ Y_{N1} & Y_{N2} & \dots & Y_{NN} \end{bmatrix} \quad \mathbf{I} = \mathbf{Y}\mathbf{V}$$

Each element of matrix  $\mathbf{Y}$  is given by

$$Y_{ij} = \left. \frac{I_i}{V_j} \right|_{V_k=0 \text{ for } k \neq j}$$

## Z-Parameters for 2-Port Networks

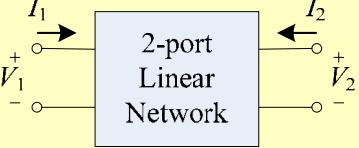


$$\mathbf{V} = \mathbf{Z}\mathbf{I}$$


$$\mathbf{V} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \mathbf{I} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\mathbf{Z} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$

Equivalent circuit:

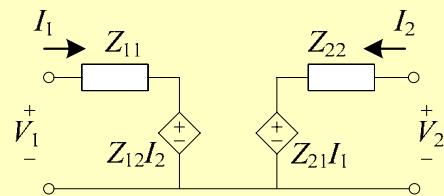

## Y-Parameters for 2-Port Networks

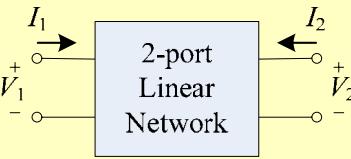


$$\mathbf{I} = \mathbf{Y}\mathbf{V}$$


$$\mathbf{V} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \mathbf{I} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\mathbf{Y} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$$

Equivalent circuit:

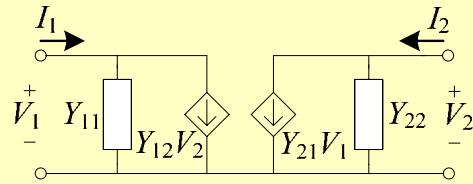

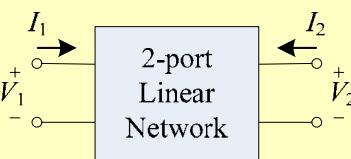
## H-Parameters (Hybrid) for 2-Port Networks




$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \mathbf{H} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$\mathbf{H} = \begin{bmatrix} H_{11} & H_{12} \\ H_{21} & H_{22} \end{bmatrix}$$

Equivalent circuit:

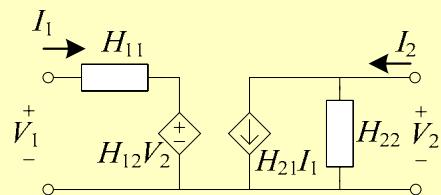


## H-Parameters for a BJT

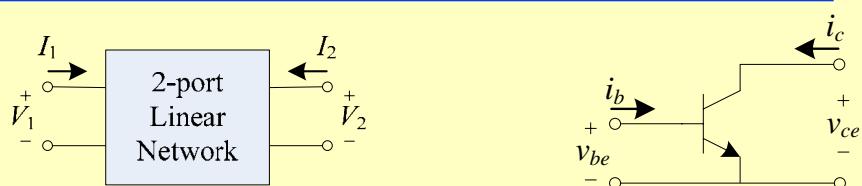


$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} H_{11} & H_{12} \\ H_{21} & H_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} v_{eb} \\ i_c \end{bmatrix} = \begin{bmatrix} h_{ie} & h_{re} \\ h_{fe} & h_{oe} \end{bmatrix} \begin{bmatrix} i_b \\ v_{ce} \end{bmatrix}$$

Equivalent circuit:

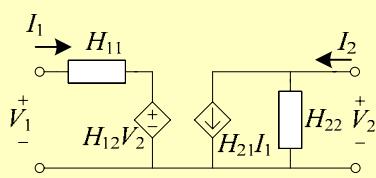

Equivalent circuit at low freq.:

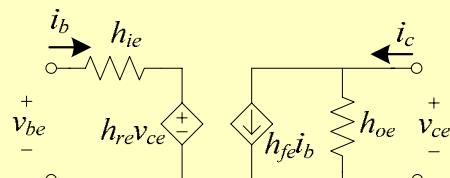


Dr. J. E. Rayas Sánchez

21


## BJT Manufacturing Data Sheets

**2N3904**

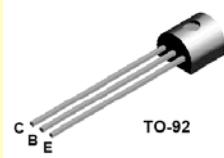


TO-92

**MMBT3904**

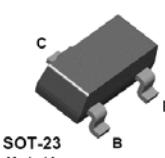

SOT-23  
Mark: 1A

**PZT3904**

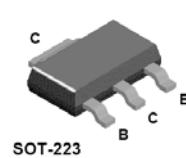

### NPN General Purpose Amplifier

This device is designed as a general purpose amplifier and switch. The useful dynamic range extends to 100 mA as a switch and to 100 MHz as an amplifier.

#### Absolute Maximum Ratings\*

$T_A = 25^\circ\text{C}$  unless otherwise noted

Symbol	Parameter	Value	Units
$V_{CEO}$	Collector-Emitter Voltage	40	V
$V_{CBO}$	Collector-Base Voltage	60	V
$V_{EBO}$	Emitter-Base Voltage	6.0	V
$I_C$	Collector Current - Continuous	200	mA
$T_J, T_{Stg}$	Operating and Storage Junction Temperature Range	-55 to +150	°C

Dr. J. E. Rayas Sánchez

22

## BJT Manufacturing Data Sheets (cont)

<b>Electrical Characteristics</b>		<small><math>T_A = 25^\circ\text{C}</math> unless otherwise noted</small>			
Symbol	Parameter	Test Conditions	Min	Max	Units
<b>OFF CHARACTERISTICS</b>					
$V_{(\text{BR})\text{CEO}}$	Collector-Emitter Breakdown Voltage	$I_C = 1.0 \text{ mA}, I_B = 0$	40		V
$V_{(\text{BR})\text{CBO}}$	Collector-Base Breakdown Voltage	$I_C = 10 \mu\text{A}, I_E = 0$	60		V
$V_{(\text{BR})\text{EBO}}$	Emitter-Base Breakdown Voltage	$I_E = 10 \mu\text{A}, I_C = 0$	6.0		V
$I_{BL}$	Base Cutoff Current	$V_{CE} = 30 \text{ V}, V_{EB} = 3\text{V}$		50	nA
$I_{CEX}$	Collector Cutoff Current	$V_{CE} = 30 \text{ V}, V_{EB} = 3\text{V}$		50	nA
<b>ON CHARACTERISTICS*</b>					
$h_{FE}$	DC Current Gain	$I_C = 0.1 \text{ mA}, V_{CE} = 1.0 \text{ V}$	40		
		$I_C = 1.0 \text{ mA}, V_{CE} = 1.0 \text{ V}$	70		
		$I_C = 10 \text{ mA}, V_{CE} = 1.0 \text{ V}$	100		
		$I_C = 50 \text{ mA}, V_{CE} = 1.0 \text{ V}$	60		
		$I_C = 100 \text{ mA}, V_{CE} = 1.0 \text{ V}$	30		
$V_{CE(\text{sat})}$	Collector-Emitter Saturation Voltage	$I_C = 10 \text{ mA}, I_B = 1.0 \text{ mA}$ $I_C = 50 \text{ mA}, I_B = 5.0 \text{ mA}$		0.2 0.3	V
$V_{BE(\text{sat})}$	Base-Emitter Saturation Voltage	$I_C = 10 \text{ mA}, I_B = 1.0 \text{ mA}$ $I_C = 50 \text{ mA}, I_B = 5.0 \text{ mA}$	0.65	0.85 0.95	V

Dr. J. E. Rayas Sánchez

23

## BJT Manufacturing Data Sheets (cont)

<b>SMALL SIGNAL CHARACTERISTICS</b>					
$f_T$	Current Gain - Bandwidth Product	$I_C = 10 \text{ mA}, V_{CE} = 20 \text{ V}, f = 100 \text{ MHz}$	300		MHz
$C_{\text{obo}}$	Output Capacitance	$V_{CB} = 5.0 \text{ V}, I_E = 0, f = 1.0 \text{ MHz}$		4.0	pF
$C_{\text{ibo}}$	Input Capacitance	$V_{EB} = 0.5 \text{ V}, I_C = 0, f = 1.0 \text{ MHz}$		8.0	pF
NF	Noise Figure	$I_C = 100 \mu\text{A}, V_{CE} = 5.0 \text{ V}, R_S = 1.0 \text{k}\Omega, f = 10 \text{ Hz to } 15.7 \text{ kHz}$		5.0	dB

### SWITCHING CHARACTERISTICS

$t_d$	Delay Time	$V_{CC} = 3.0 \text{ V}, V_{BE} = 0.5 \text{ V},$		35	ns
$t_r$	Rise Time	$I_C = 10 \text{ mA}, I_{B1} = 1.0 \text{ mA}$		35	ns
$t_s$	Storage Time	$V_{CC} = 3.0 \text{ V}, I_C = 10 \text{ mA}$		200	ns
$t_f$	Fall Time	$I_{B1} = I_{B2} = 1.0 \text{ mA}$		50	ns


### Spice Model

NPN ( $I_S = 6.734f$   $X_{Ti} = 3$   $E_g = 1.11$   $V_{af} = 74.03$   $B_f = 416.4$   $N_e = 1.259$   $I_{se} = 6.734$   $I_{kf} = 66.78m$   $X_{tb} = 1.5$   $B_r = .7371$   $N_c = 2$   $I_{sc} = 0$   $I_{kr} = 0$   $R_c = 1$   $C_{jc} = 3.638p$   $M_{je} = .3085$   $V_{jc} = .75$   $F_c = .5$   $C_{je} = 4.493p$   $M_{je} = .2593$   $V_{je} = .75$   $T_r = 239.5n$   $T_f = 301.2p$   $I_{tf} = .4$   $V_{tf} = 4$   $X_{tf} = 2$   $R_b = 10$ )

Dr. J. E. Rayas Sánchez

24


## BJT Manufacturing Data Sheets (cont)

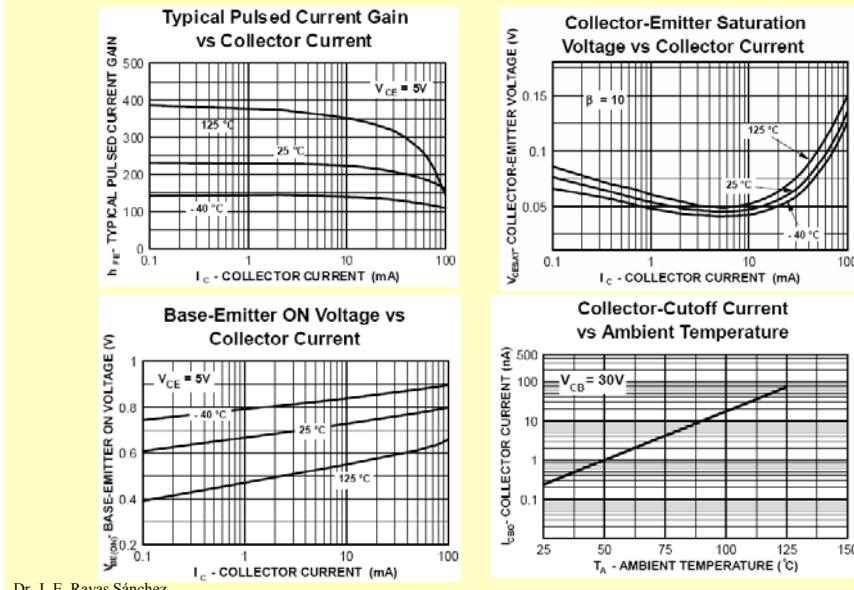

Dr. J. E. Rayas Sánchez

25


## BJT Manufacturing Data Sheets (cont)

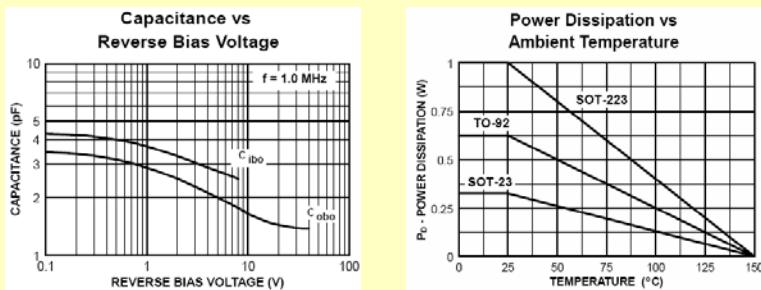

Dr. J. E. Rayas Sánchez


26

## BJT Manufacturing Data Sheets (cont)

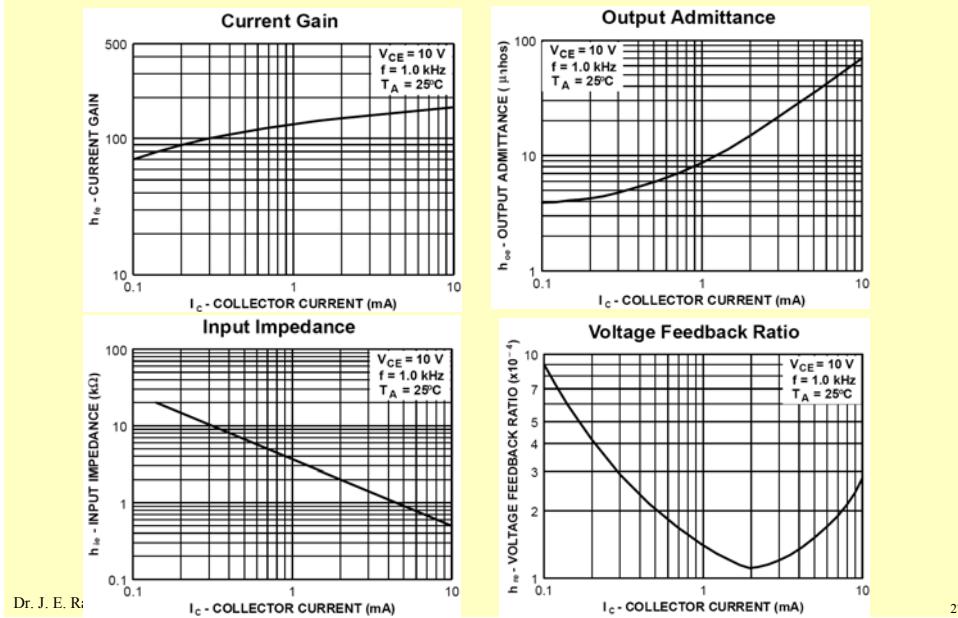


## Getting $\pi$ Parameters from H-Parameters

Hybrid  $\pi$  Model:

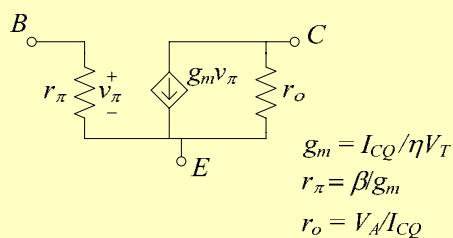

Hybrid-Parameters Model:

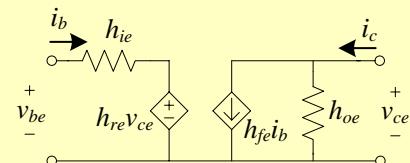

$$r_\pi \approx h_{ie}$$

$$g_m \approx h_{fe} / h_{ie}$$

$$r_o = 1 / h_{oe}$$

$$V_A = I_{CQ} / h_{oe}$$