

# **Introduction to CMOS Logic Design**

**Dr. José Ernesto Rayas Sánchez**

Most figures of this presentation were taken from the instructional resources of the following textbook:

A. S. Sedra and K. C. Smith, *Microelectronic Circuits*. New York, NY: Oxford University Press, 2003.


1

## **Outline**


---

- Technologies and logic families
- Transfer characteristics
- Transition and propagation times
- Modeling CMOS Inverters
- Matched CMOS Inverters
- Dynamic operation of CMOS inverters
- General structure of CMOS logic circuits
- Examples of CMOS logic gates
- Dimensioning transistors in CMOS logic circuits

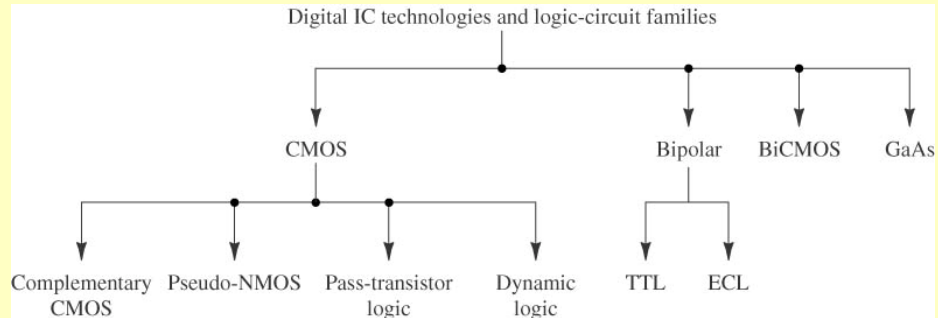
## Digital IC Technologies and Logic Families


 
## Typical Inverter Voltage Transfer Characteristic


 
## Transition Times and Propagation Delays



Dr. J. E. Rayas Sánchez

5


## Ohmic Region (review)

If  $v_{GS} \geq V_{TH}$  and  $v_{DS}$  is small ( $v_{DS} \ll v_{GS} - V_{TH}$ ),

→ ohmic region or deep triode region

$$r_{DS} = \frac{v_{DS}}{i_{DS}} \approx \frac{1}{\mu_n C_{OX} \frac{W}{L} (v_{GS} - V_{TH})} = \frac{1}{2K(v_{GS} - V_{TH})}$$


for  $v_{DS}$  small

 

Dr. J. E. Rayas Sánchez

6

## A CMOS Inverter

 


$$r_{DSN} \approx \frac{1}{\mu_n C_{OX} \frac{W_n}{L_n} (v_{GS} - V_{THn})}$$

$$r_{DSP} \approx \frac{1}{\mu_p C_{OX} \frac{W_p}{L_p} (v_{SG} - |V_{THp}|)}$$

Dr. J. E. Rayas Sánchez

7



 
## Transfer Characteristic of a Matched Inverter



Dr. J. E. Rayas Sánchez

8

## A CMOS Inverter when $v_I = V_{DD}$

 
 
 


$$r_{DSN} \approx \frac{1}{\mu_n C_{OX} \frac{W_n}{L_n} (V_{DD} - V_{THn})}$$

Dr. J. E. Rayas Sánchez

9

## A CMOS Inverter when $v_I = 0V$

  
 


$$r_{DSP} \approx \frac{1}{\mu_p C_{OX} \frac{W_p}{L_p} (v_{DD} - |V_{THp}|)}$$

Dr. J. E. Rayas Sánchez

10


## Inverter Current vs Input Voltage

  




Dr. J. E. Rayas Sánchez

11
 
## Dynamic Operation with a Capacitive Load



 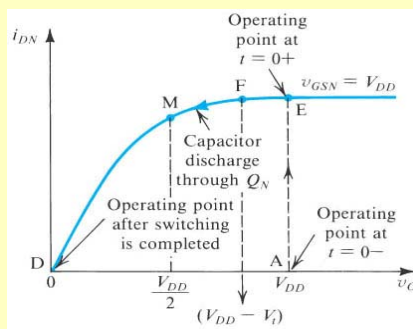 
When  $v_I$  switches from 0 to  $V_{DD}$ :



Dr. J. E. Rayas Sánchez

12
 
## Power Consumption with a Capacitive Load



The energy stored in  $C$  is:

$$W_C = \frac{1}{2} C (v_O(t))^2$$


when  $t = 0^-$  ( $C$  is fully charged)

$$W_C(t = 0^-) = \frac{1}{2} C V_{DD}^2$$

which is the energy that must be dissipated by  $Q_N$  when  $C$  is discharged, and by  $Q_P$  when  $C$  is charged. Hence, the total energy per cycle is:

$$W_{total} = C V_{DD}^2 = \int_0^T P_D dt = P_D T$$


$$P_D = f C V_{DD}^2$$

 

Dr. J. E. Rayas Sánchez

13



 
## General Structure of CMOS Logic Circuits



Dr. J. E. Rayas Sánchez

14




## Pull-Down Networks - Examples

   

Dr. J. E. Rayas Sánchez

15

## Pull-Up Networks - Examples

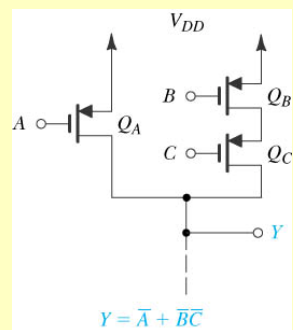  

Dr. J. E. Rayas Sánchez

16



## Examples...

---

## Dimensioning...

---