

Zener Diodes and Applications

Dr. José Ernesto Rayas Sánchez

Some figures of this presentation were taken from the instructional resources of the following textbooks:
A. S. Sedra and K. C. Smith, *Microelectronic Circuits*. New York, NY: Oxford University Press, 2003.

1

Outline


- I-V characteristics of a Zener diode
- Models for a Zener diode
- Manufacturer's data sheets
- Obtaining model parameters from data sheets
- Voltage regulators
- Other applications of Zener diodes

Zener Diodes and Applications


Dr. José Ernesto Rayas Sánchez

January 29, 2007

I-V Characteristics of a Zener Diode

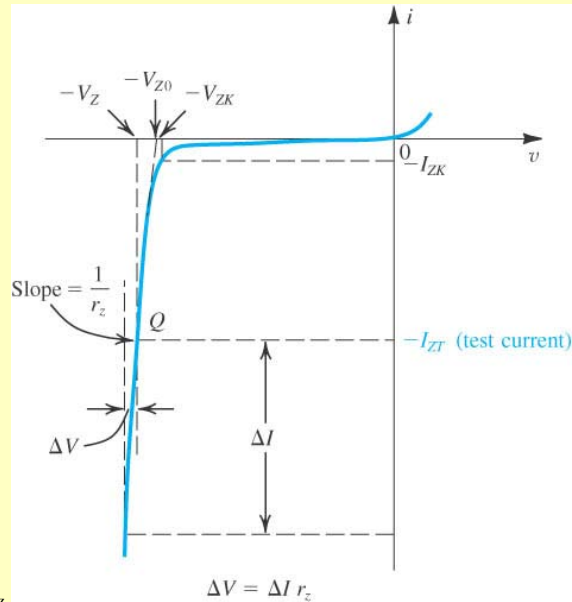



Symbol:

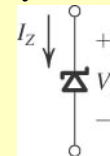

Dr. J. E. Rayas Sánchez

3

Modeling a Zener Diode in Regulation

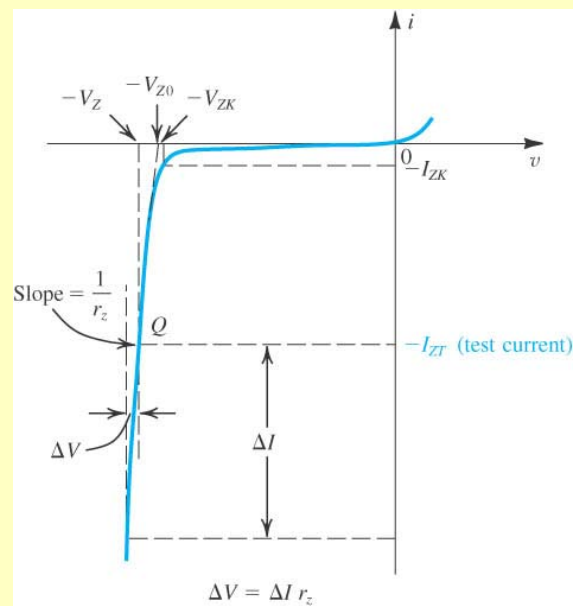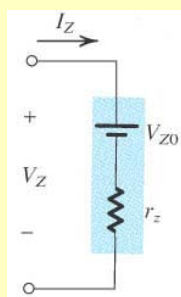

Dr. J. E. Rayas Sánchez


4

Zener Diodes and Applications


Dr. José Ernesto Rayas Sánchez

January 29, 2007

A Zener Diode Model for all Regions

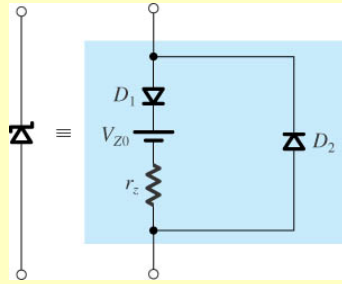

(D_1 is an ideal diode)

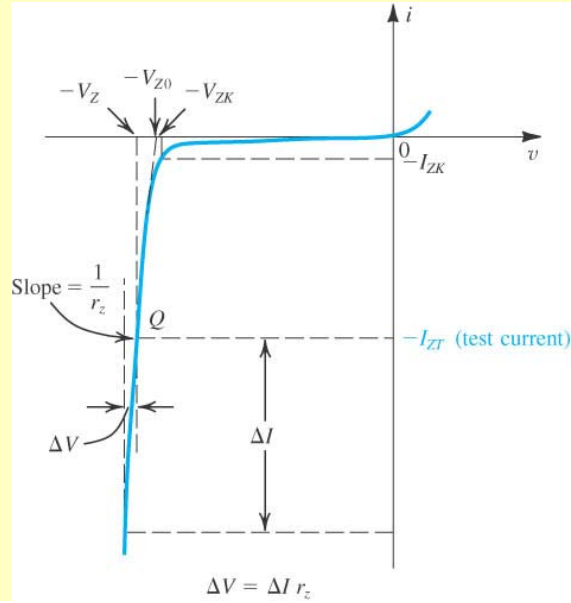

Dr. J. E. Rayas Sánchez

5

Manufacturers Data Sheets for Zener Diodes

ON
ON Semiconductor
http://onsemi.com

1N957B Series
500 mW DO-35 Hermetically Sealed Glass Zener Voltage Regulators



MAXIMUM RATINGS (Note 1.)

Rating	Symbol	Value	Unit
Max. Steady State Power Dissipation @ $T_1 \leq 75^\circ\text{C}$, Lead Length = 3/8" Derate above 75°C	P_D	500	mW
		4.0	mW/°C
Operating and Storage Temperature Range	T_J, T_{stg}	-65 to +200	°C

ELECTRICAL CHARACTERISTICS ($T_A = 25^\circ\text{C}$ unless otherwise noted, $V_F = 1.5\text{ V Max}$ @ $I_F = 200\text{ mA}$ for all types)

Device (Note 2.)	Device Marking	Zener Voltage (Note 3.)			Zener Impedance (Note 4.)			Leakage Current		I_{ZM} (Note 5.)	
		V_Z (Volts)			@ I_{ZT}	Z_{ZT} @ I_{ZT}	Z_{ZK} @ I_{ZK}	I_R @ V_R			
		Min	Nom	Max	mA	Ω	Ω	mA	μA		Volts
1N957B	1N957B	6.46	6.8	7.14	18.5	4.5	700	1.0	150	5.2	47
1N958B	1N958B	7.125	7.5	7.875	16.5	5.5	700	0.5	75	5.7	42
1N959B	1N959B	7.79	8.2	8.61	15	6.5	700	0.5	50	6.2	38
1N960B	1N960B	8.645	9.1	9.555	14	7.5	700	0.5	25	6.9	35
1N961B	1N961B	9.5	10	10.5	12.5	8.5	700	0.25	10	7.6	32
1N962B	1N962B	10.45	11	11.55	11.5	9.5	700	0.25	5	8.4	28

Dr. J. E. Rayas Sánchez

6

Getting Zener Model Parameters



From the manufacturer's data sheet we get:

- V_{ZT} and Z_{ZT} @ I_{ZT}
- I_{ZM}

then

$$r_z = Z_{ZT}$$

$$V_{Z0} = V_{ZT} - I_{ZT} r_z$$

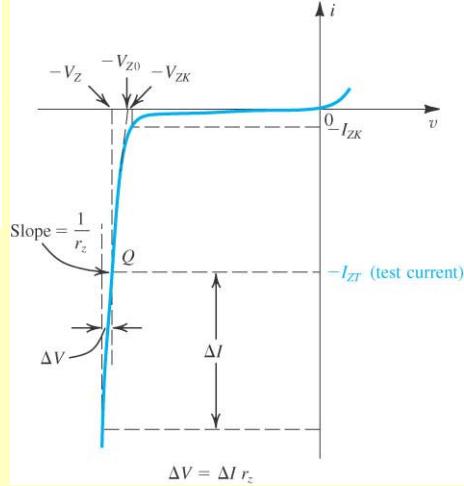
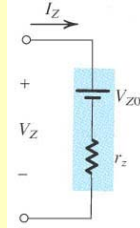


A practical current range for voltage regulation is $0.3I_{ZT} \leq I_Z \leq I_{ZM}$

Dr. J. E. Rayas Sánchez

7



Typical Linear DC Voltage Source

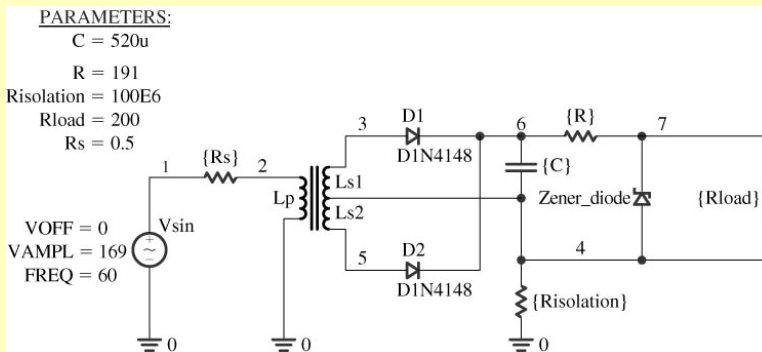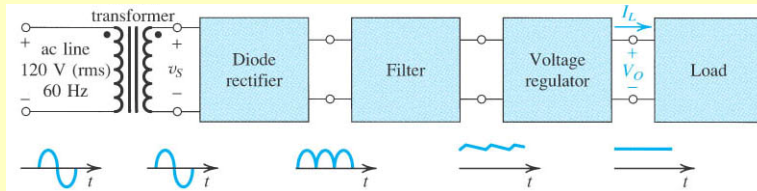



Dr. J. E. Rayas Sánchez

8


Typical Linear DC Voltage Source (cont)

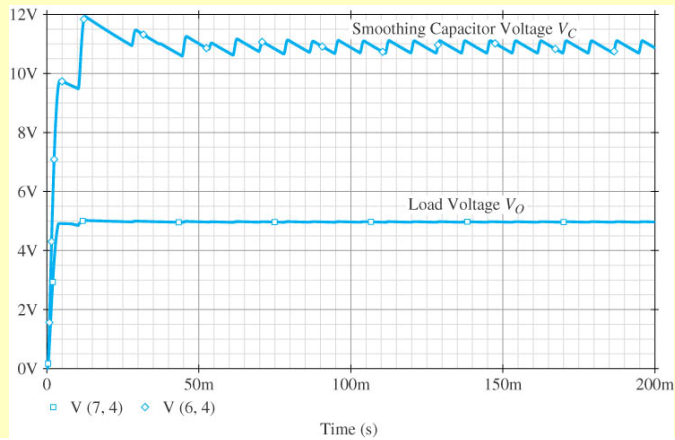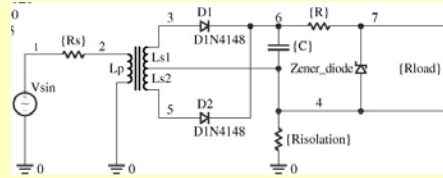

Typical Linear DC Voltage Source (cont)

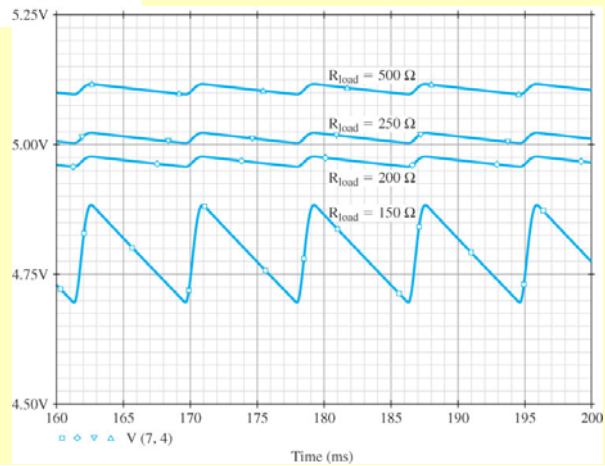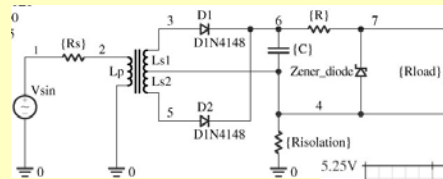

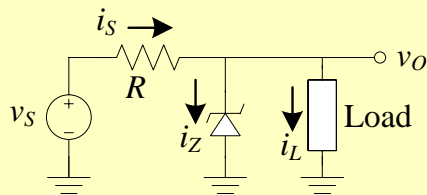Designing a Zener-Based Voltage Regulator



$$\text{If } V_{S\min} \leq v_S \leq V_{S\max}$$

$$I_{L\min} \leq i_L \leq I_{L\max}$$

Find a feasible range of R such that

$$0.3I_{ZT} \leq i_Z \leq I_{ZM}$$

$$v_O = \frac{R}{R + r_z} V_{Z0} + \frac{r_z}{R + r_z} v_S - (R \parallel r_z) i_L$$

$$\frac{\partial v_O}{\partial v_S} = \frac{r_z}{R + r_z}$$

$$\frac{\partial v_O}{\partial i_L} = -(R \parallel r_z)$$

Other Applications of Zener Diodes (Clippers)

