

# Multi-Stage Amplifiers

**Dr. José Ernesto Rayas Sánchez**

Some figures of this presentation were taken from the instructional resources of the following textbook:  
A. S. Sedra and K. C. Smith, *Microelectronic Circuits*. New York, NY: Oxford University Press, 2003.

1

## Outline


---

- Introduction
- Basic properties of a general amplifier with  $N$  stages
- Type of coupling between stages
- Capacitive coupling
- Inductive coupling
- Direct coupling

## Introduction

- Most of the practical amplifiers consists of several amplification stages
- Input stages provide high input impedance and high noise immunity (CMRR)
- Intermediate stage provide most of the amplification gain
- Output stages provide low output impedance (for a voltage output), and adjust the DC levels

## A General Amplifier with $N$ Stages

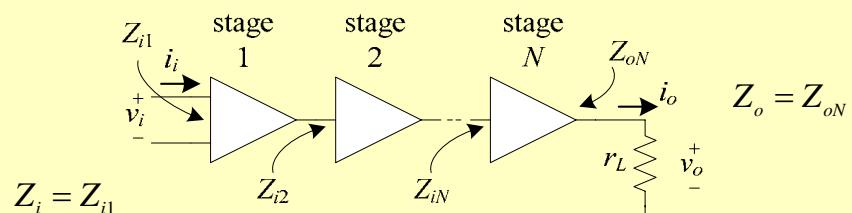


$$A_v = \frac{v_o}{v_i} = (A_{v1})(A_{v2}) \dots (A_{vN})$$

If the gain is expressed in dB:

$$A_{v_{dB}} = 20 \log \left| \frac{v_o}{v_i} \right| = 20 \log [(| A_{v1} |)(| A_{v2} |) \dots (| A_{vN} |)]$$

$$A_{v_{dB}} = 20 \log \left| \frac{v_o}{v_i} \right| = A_{v1dB} + A_{v2dB} + \dots + A_{vN dB}$$
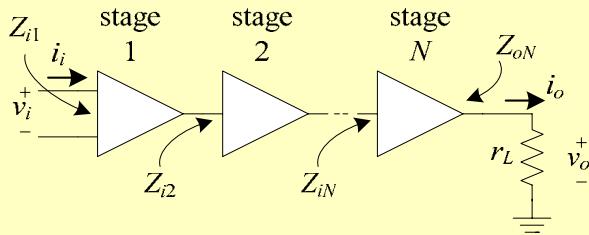
## A General Amplifier with $N$ Stages (cont)




Similarly:

$$A_i = \frac{i_o}{i_i} = (A_{i1})(A_{i2}) \dots (A_{iN})$$

Total power gain:

$$A_v A_i = \left( \frac{i_o r_L}{i_i Z_i} \right) \left( \frac{i_o}{i_i} \right) = \frac{1}{2} \frac{i_o^2 r_L}{i_i^2 Z_i} = \frac{p_o}{p_i} = A_p$$
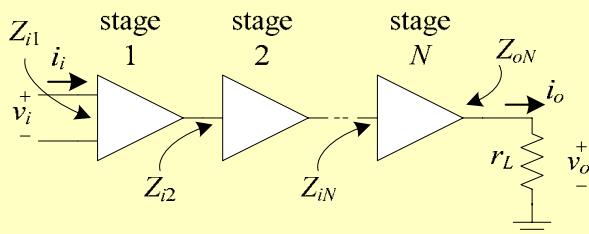
## A General Amplifier with $N$ Stages (cont)



Distortion Limits:  $DL^+$ ,  $DL^-$

Usually,

$$DL^+ = DL_{N-1}^+, \text{ and } DL^- = DL_N^-$$

However, an intermediate stage can be saturated before the output stage

## Types of Coupling between Amp. Stages

- Capacitive coupling
- Inductive coupling
- Direct coupling
- Optical coupling

## Capacitive Coupling


### Advantages

- ☺ Makes independent the biasing point of each stage
- ☺ Can be ignored at mid and high frequencies
- ☺ It is suitable for discrete configurations

### Disadvantages

- ☹ Affects the amplification at low frequencies
- ☹ Makes difficult impedance matching
- ☹ Large capacitors (electrolytic) are noisy
- ☹ Unsuitable for integrated circuits


## Capacitive Coupling – Example 1

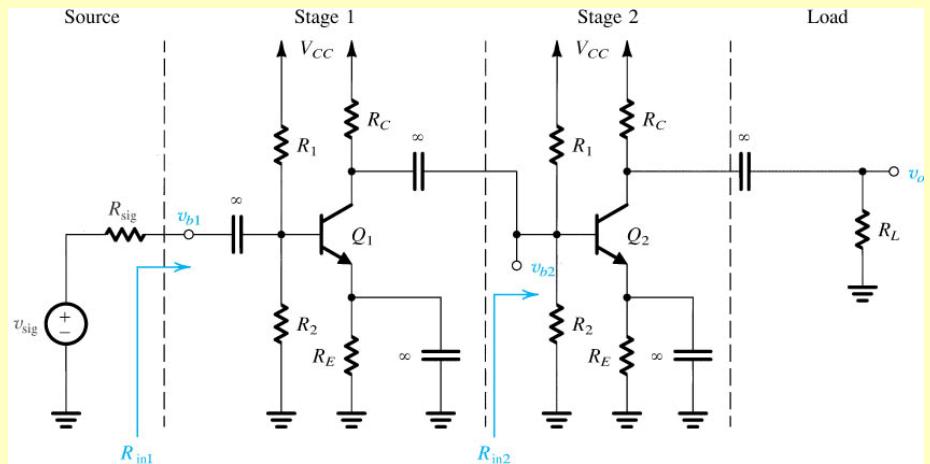

Dr. J. E. Rayas Sánchez

9


## Capacitive Coupling – Example 2

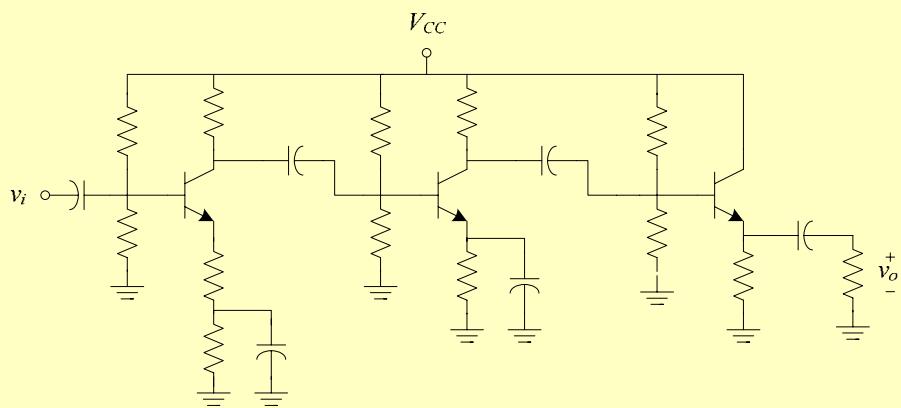

Dr. J. E. Rayas Sánchez

10

## Capacitive Coupling – Example 3

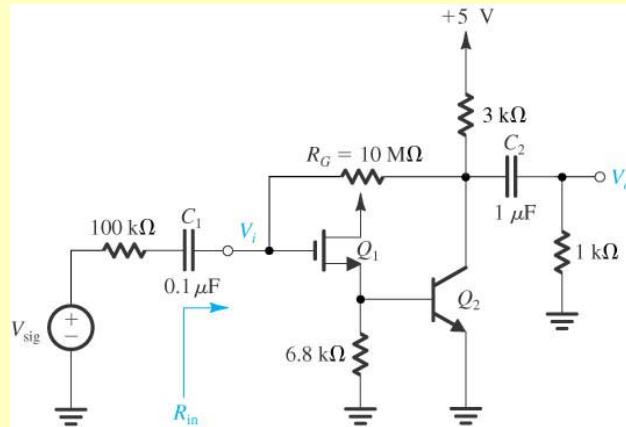

Dr. J. E. Rayas Sánchez

11

## Inductive Coupling

### Advantages

- ☺ Makes independent the biasing point of each stage
- ☺ Produce electrical isolation (magnetic coupling)
- ☺ Facilitate impedance matching
- ☺ Allows a tuned coupling


### Disadvantages

- ☹ Transformers are bulky, heavy and expensive
- ☹ Introduce non-linear effects
- ☹ Unsuitable for integrated circuits
- ☹ Affects amplification at low and high frequencies

Dr. J. E. Rayas Sánchez

12

## Inductive Coupling – Example

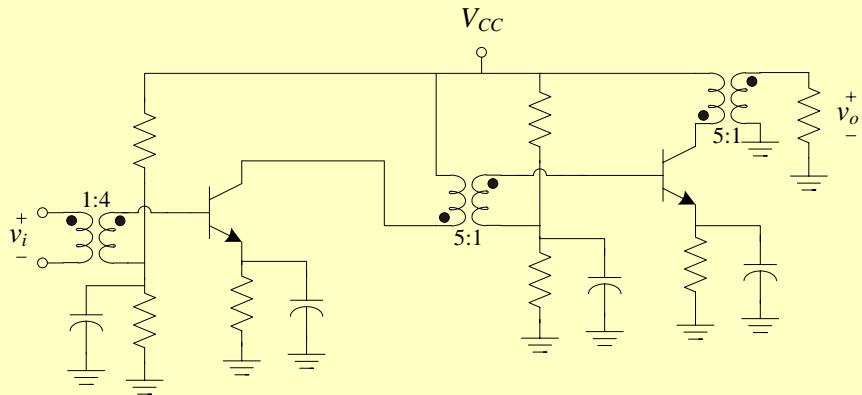

Dr. J. E. Rayas Sánchez

13

## Direct Coupling

### Advantages

- ☺ Allow amplification of DC signals
- ☺ Low cost
- ☺ Ideal for integrated circuits


### Disadvantages

- ☹ The bias point of each stage depends on the remaining stages
- ☹ Their design can be complicated
- ☹ Unsuitable for integrated circuits

Dr. J. E. Rayas Sánchez

14


## Direct Coupling – Example 1

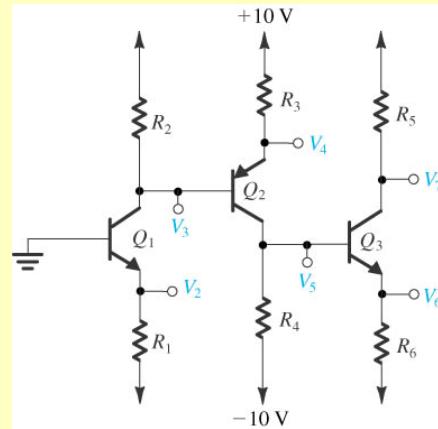

Dr. J. E. Rayas Sánchez

15


## Direct Coupling – Example 2

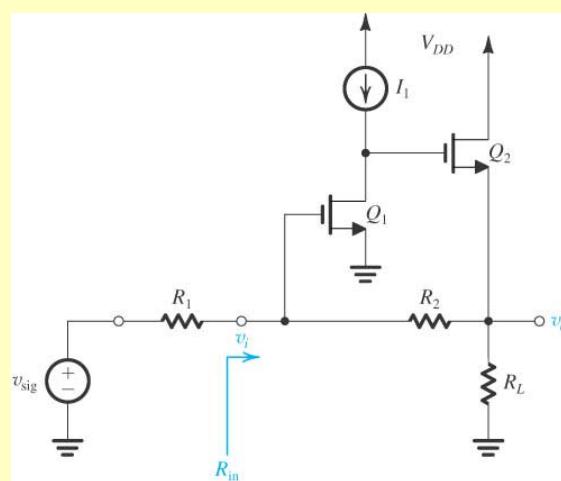

Dr. J. E. Rayas Sánchez

16


### Direct Coupling – Example 3

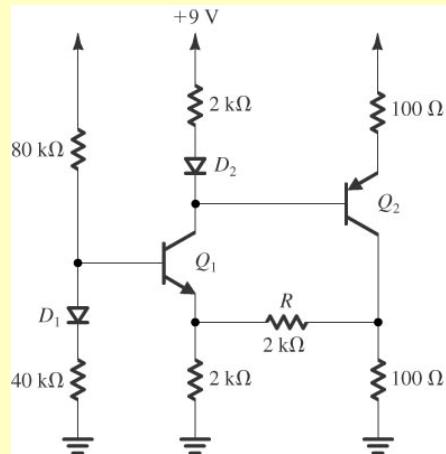

Dr. J. E. Rayas Sánchez

17


### Direct Coupling – Example 4

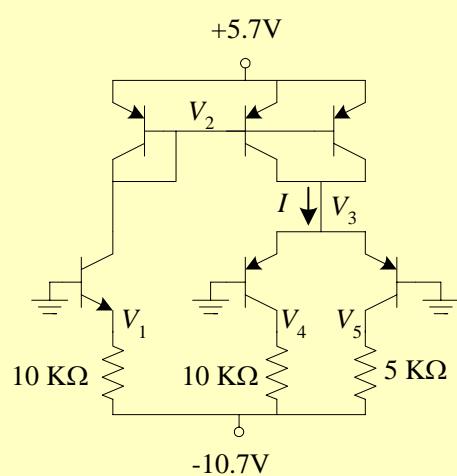

Dr. J. E. Rayas Sánchez

18


## Direct Coupling – Example 5

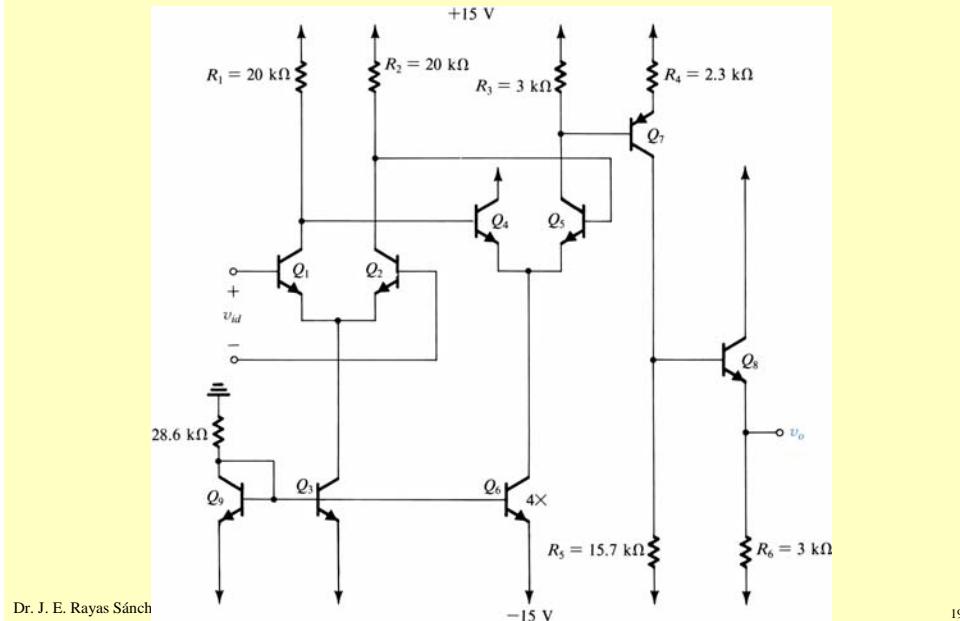

Dr. J. E. Rayas Sánchez

19

## Direct Coupling – Example 6

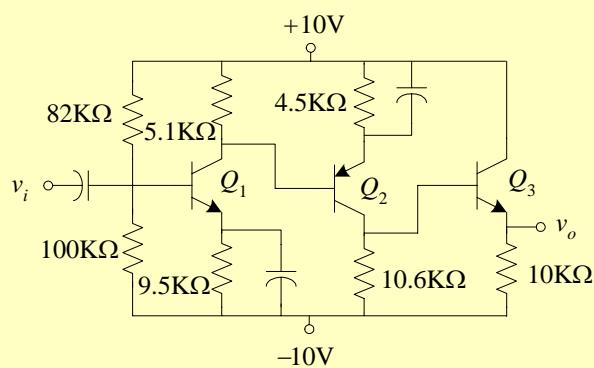

Dr. J. E. Rayas Sánchez

20

## Direct Coupling – Example 7

