

Frequency Response

(Part 2)

Dr. José Ernesto Rayas Sánchez

The Time Constant Method

- It is an approximate method to calculate ω_L and ω_H
- Works well for most amplifiers
- Assumes that all the poles are real, that there is a dominant pole and no dominant zero
- No poles and zeros calculations required
- Very suitable for deriving design formulas



The Short-Circuit Time Constant Method (LF)

- 1) Replace the amplifier by its low frequency model
- 2) Calculate the resistance R_i in parallel with the capacitor C_i , considering all the remaining capacitors as short circuits
- 3) Repeat step 2) for each capacitor ($i = 1, 2, \dots, n_L$)
- 4) Calculate ω_L using

$$\omega_L \approx \sum_{i=1}^{n_L} \frac{1}{R_i C_i}$$

Low-Frequency Response of FET Amplifiers

Common Source

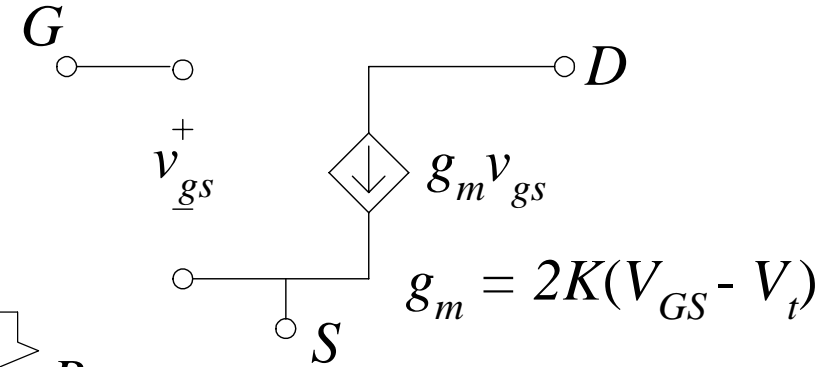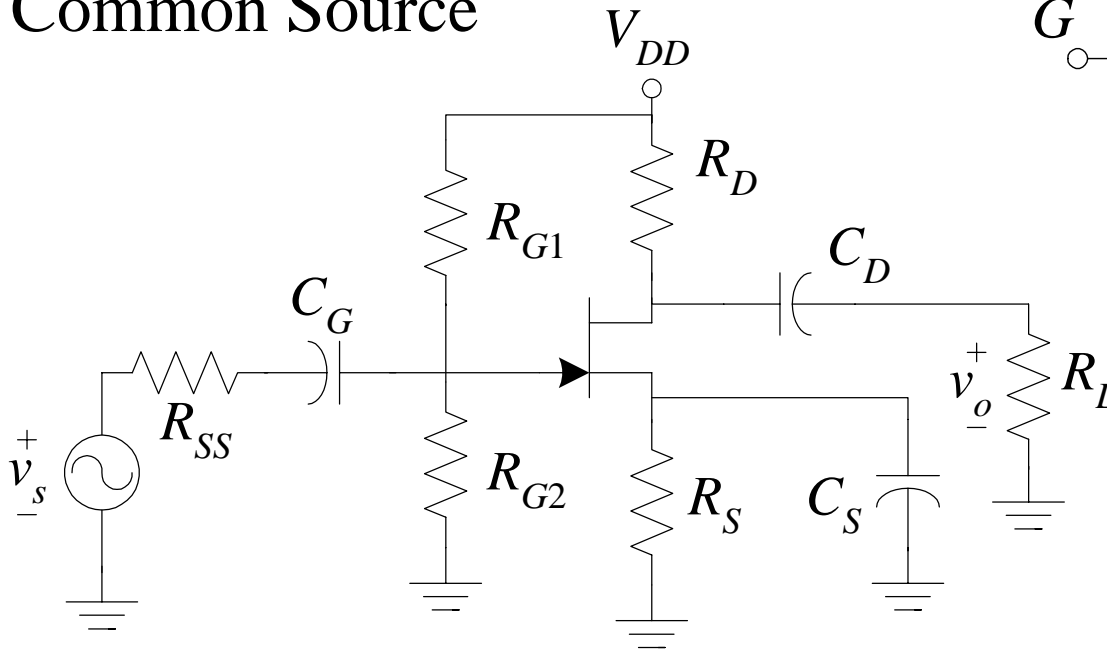

$$R_{C_G} = R_{SS} + R_{G1} \parallel R_{G2}$$

$$R_{C_S} = R_S \parallel \frac{1}{g_m}$$



$$R_{C_D} = R_L + R_D$$

$$\omega_L \approx \frac{1}{R_{C_G} C_G} + \frac{1}{R_{C_S} C_S} + \frac{1}{R_{C_D} C_D}$$

usually $1/(R_{C_S} C_S)$ is the dominant pole

Low-Frequency Response of FET Amplifiers

Common Gate

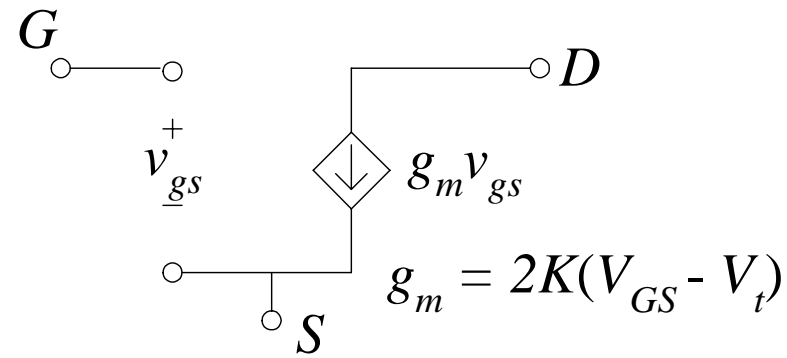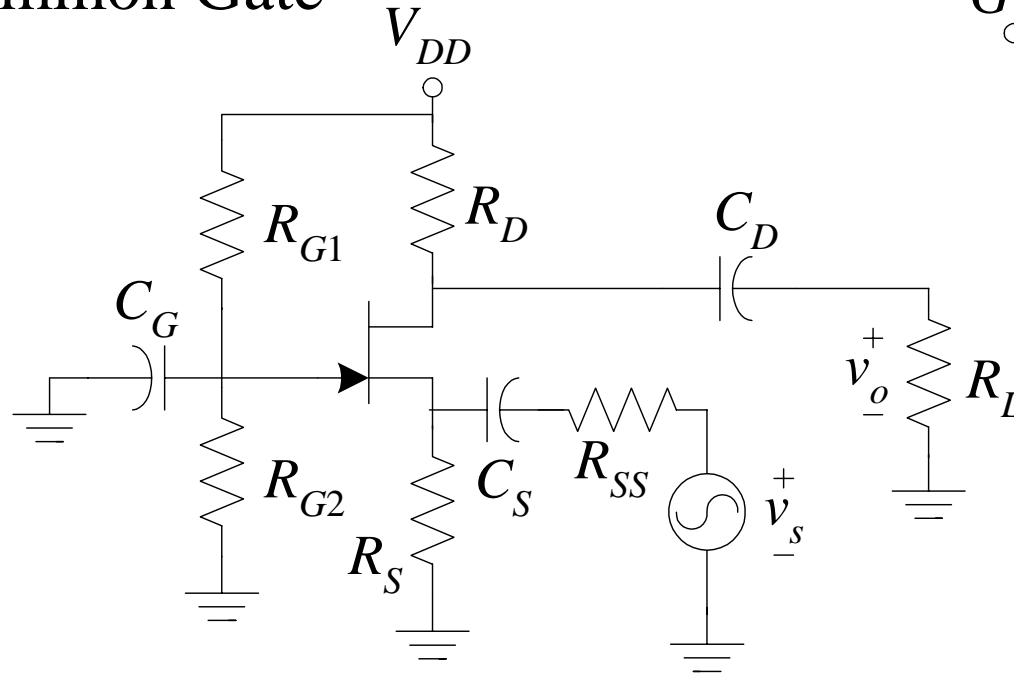

$$R_{C_G} = R_{G1} \parallel R_{G2}$$

$$R_{C_S} = R_{SS} + \left(R_S \parallel \frac{1}{g_m} \right)$$



$$R_{C_D} = R_D + R_L$$

$$\omega_L \approx \frac{1}{R_{C_G} C_G} + \frac{1}{R_{C_S} C_S} + \frac{1}{R_{C_D} C_D}$$

usually $1/(R_{C_S} C_S)$ is the dominant pole

Low-Frequency Response of FET Amplifiers

Common Drain

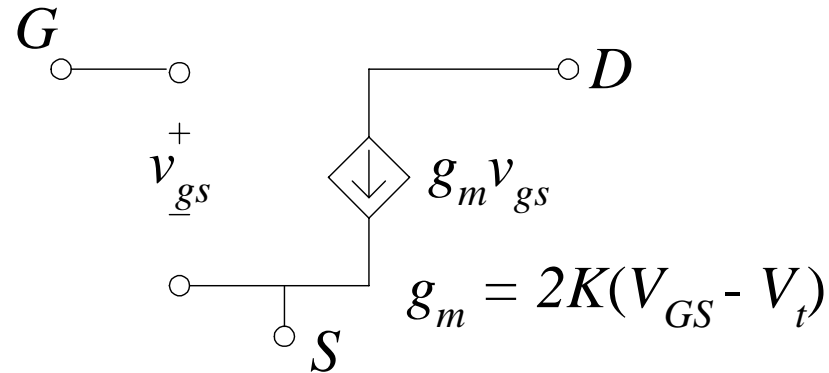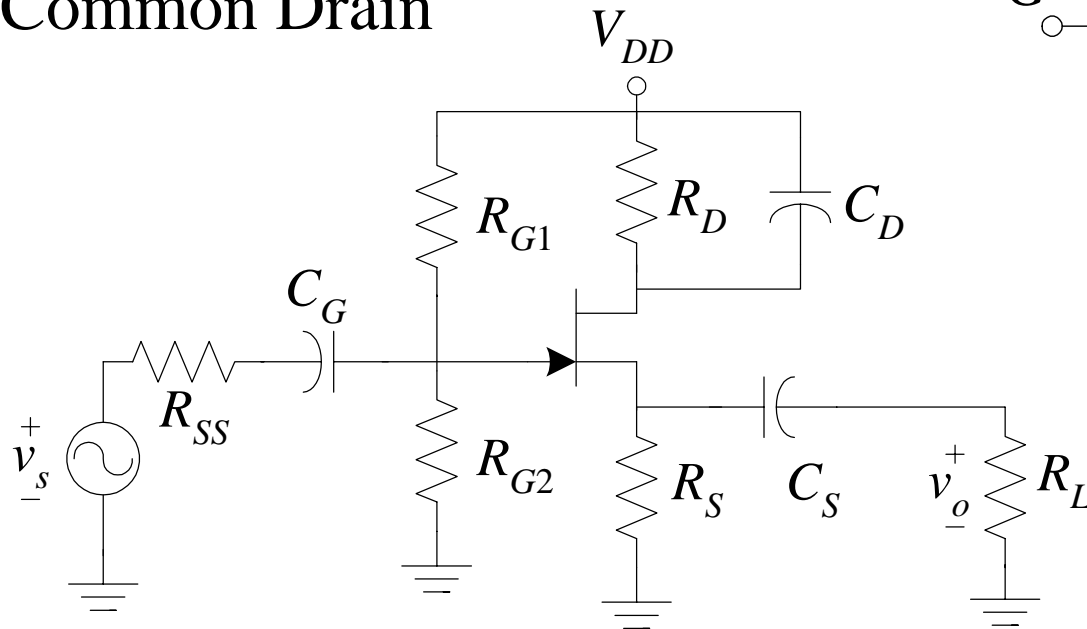

$$\omega_L \approx \frac{1}{R_{C_G} C_G} + \frac{1}{R_{C_S} C_S} + \frac{1}{R_{C_D} C_D}$$

$$R_{C_G} = R_{SS} + R_{G1} \parallel R_{G2}$$


$$R_{C_S} = \left(R_S \parallel \frac{1}{g_m} \right) + R_L$$

$$R_{C_D} = R_D$$

usually $1/(R_{C_S} C_S)$ is the dominant pole

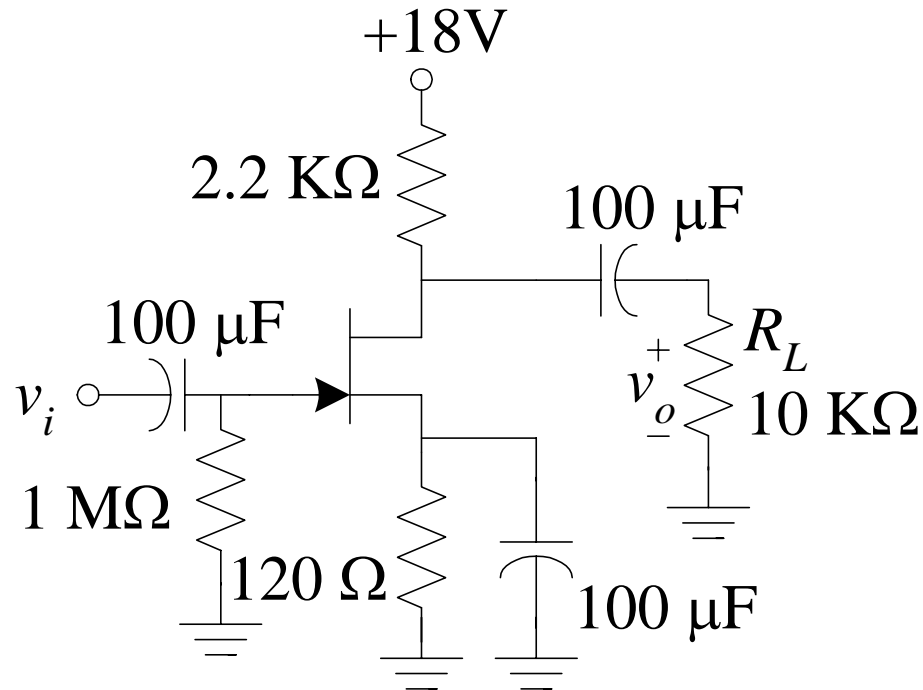
Example

Calculate the cutoff low-frequency for the following JFET amplifier (assume $V_P = -3\text{ V}$, $I_{DSS} = 7\text{ mA}$)



Low-Frequency Response of BJT Amplifiers

Common Emitter

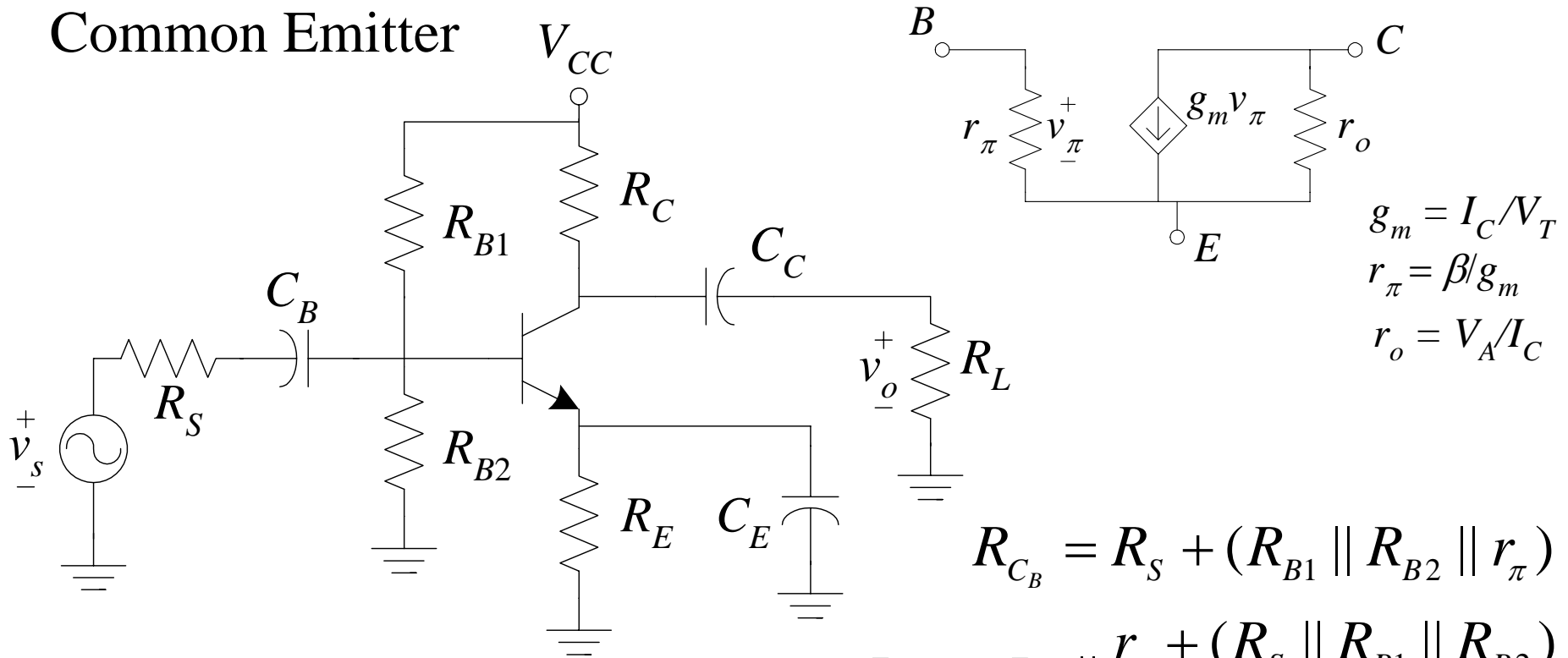

$$g_m = I_C / V_T$$

$$r_\pi = \beta / g_m$$

$$r_o = V_A / I_C$$

$$R_{C_B} = R_S + (R_{B1} \parallel R_{B2} \parallel r_\pi)$$

$$R_{C_E} = R_E \parallel \frac{r_\pi + (R_S \parallel R_{B1} \parallel R_{B2})}{\beta + 1}$$



$$R_{C_C} = R_L + (R_C \parallel r_o)$$

$$\omega_L \approx \frac{1}{R_{C_B} C_B} + \frac{1}{R_{C_E} C_E} + \frac{1}{R_{C_C} C_C}$$

usually $1/(R_{C_E} C_E)$ is the dominant pole

Low-Frequency Response of BJT Amplifiers

Common Base

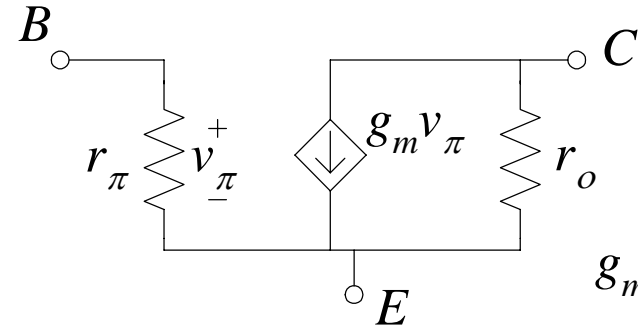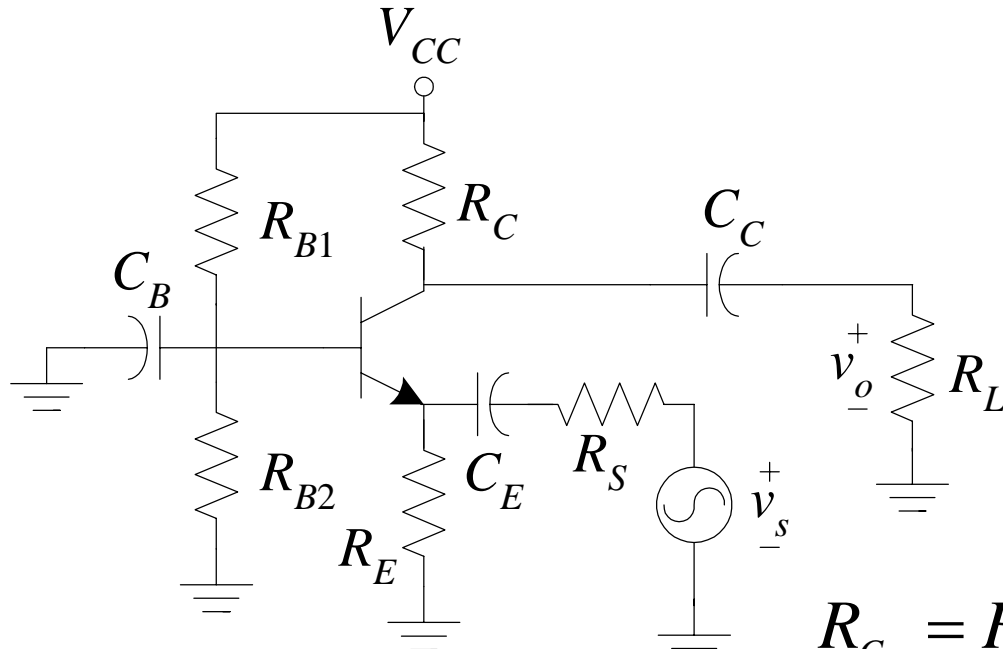

$$g_m = I_C / V_T$$

$$r_\pi = \beta / g_m$$

$$r_o = V_A / I_C$$

$$R_{C_E} = R_S + R_E \parallel r_\pi \parallel 1 / g_m$$

$$R_{C_B} = R_{B1} \parallel R_{B2} \parallel [r_\pi + (1 + \beta)(R_E \parallel R_S)]$$



$$R_{C_C} = R_L + (R_C \parallel r_o)$$

$$\omega_L \approx \frac{1}{R_{C_B} C_B} + \frac{1}{R_{C_E} C_E} + \frac{1}{R_{C_C} C_C}$$

usually $1/(R_{C_E} C_E)$ is the dominant pole

Low-Frequency Response of BJT Amplifiers

Common Collector

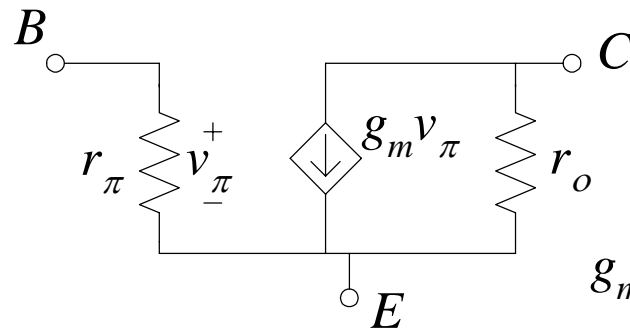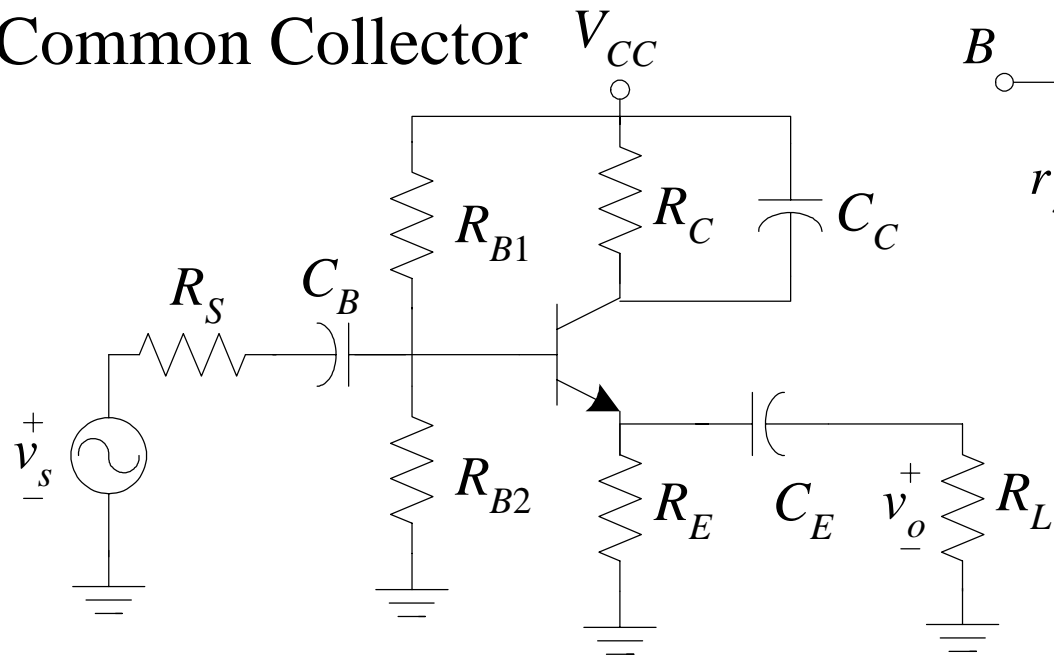

$$g_m = I_C / V_T$$

$$r_\pi = \beta / g_m$$

$$r_o = V_A / I_C$$

$$R_{C_C} = R_C \parallel [r_o + (R_E \parallel R_L)]$$

$$R_{C_E} = R_L + R_E \parallel \frac{r_\pi + (R_S \parallel R_{B1} \parallel R_{B2})}{\beta + 1}$$


$$R_{C_B} = R_S + R_{B1} \parallel R_{B2} \parallel [r_\pi + (1 + \beta)(R_E \parallel R_L)]$$

$$\omega_L \approx \frac{1}{R_{C_B} C_B} + \frac{1}{R_{C_E} C_E} + \frac{1}{R_{C_C} C_C}$$



usually $1/(R_{C_E} C_E)$ is the dominant pole

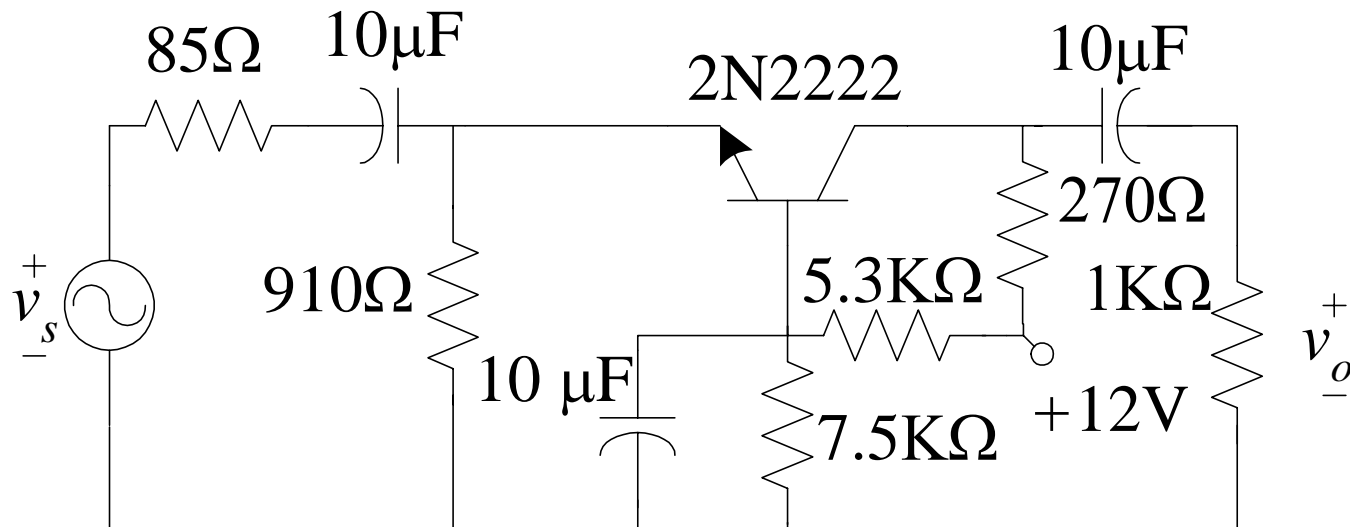Example

Calculate the cutoff low-frequency for the following BJT amplifier



Base Común (repass)

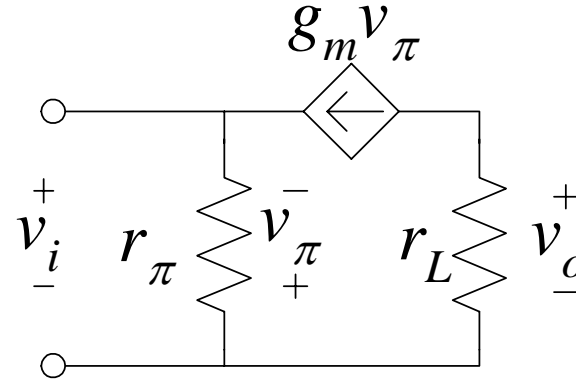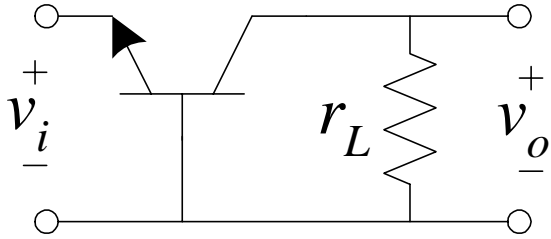


$$v_o = -g_m v_\pi r_L$$

$$v_i = -v_\pi$$

$$A_V = \frac{v_o}{v_i} = g_m r_L$$
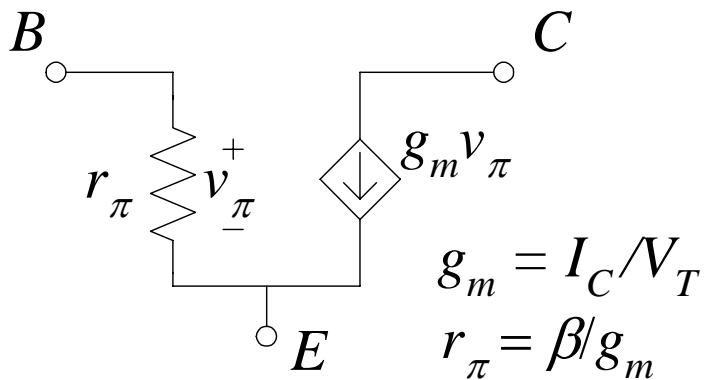
$$Z_{in} = r_\pi \parallel \frac{v_\pi}{g_m v_\pi} = r_\pi \parallel \frac{1}{g_m} \approx \frac{1}{g_m}$$



Assignment

Solve problems 7.29 and 7.31 from the textbook