
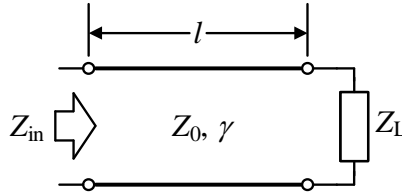


**PROBLEMS**


1. A lossy transmission line has the following per-unit length parameters:  $L = 289.05$  nH/m,  $C = 115.62$  pF/m,  $R = 6.3$   $\Omega$ /m, and  $G = 5$  mS/m. For simplicity, it is assumed that these four parameters are frequency-independent. a) Calculate the characteristic impedance of the line,  $Z_0$ , at 10 MHz and 100 MHz; b) Make 3 plots versus frequency, from 10 MHz to 10 GHz, of  $|Z_0|$ ,  $\alpha$  (attenuation constant) and  $\beta$  (propagation constant).
2. The transmission line illustrated below uses the same per-unit length parameters as in the previous problem. The load impedance  $Z_L$  consists of an 80- $\Omega$  resistor in series with a 10-nH inductor. Calculate the input impedance of the transmission line  $Z_{in}$  at 100 MHz, at the following distances from the load: a)  $l = 1$  cm, b)  $l = 10$  cm, and c)  $l = 1$  m.

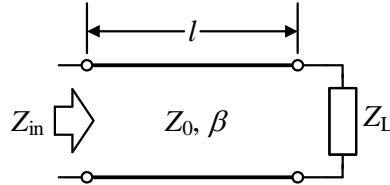

3. Solve previous problem but now neglecting losses.




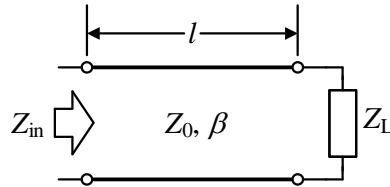4. For the following lossless transmission line circuit, calculate the reflection coefficient at the load,  $\Gamma$ , the SWR on the line, and the input impedance,  $Z_{in}$ , at a distance  $l$  from the load. Assume  $Z_0 = 50$   $\Omega$ ,  $Z_L = 40 + j20$   $\Omega$ , and  $l =$ : a)  $\lambda/4$ ; b)  $0.35\lambda$ .




5. A lossless transmission line is connected to a  $R_L = 75$   $\Omega$ . a) If the measured SWR at the load is 2.2, find the two possible values for  $Z_0$ . b) What is the value of the SWR when measured at a distance  $l = 0.3\lambda$  away from the load?
6. A coaxial line has a characteristic impedance  $Z_0 = 75$   $\Omega$ , a physical length  $l = 2.5$  m, and is filled with a dielectric whose  $\epsilon_r = 2.56$ . If it is operating at 5 GHz and is connected to a load impedance  $Z_L = 37.5 + j75$   $\Omega$ , calculate the reflection coefficient at the load,  $\Gamma$ , the reflection coefficient at the input,  $\Gamma_{l=2.5m}$ , the SWR on the line, and the impedance at the input of the coaxial line,  $Z_{in}$ . Use  $c = 0.3$  Gm/s.

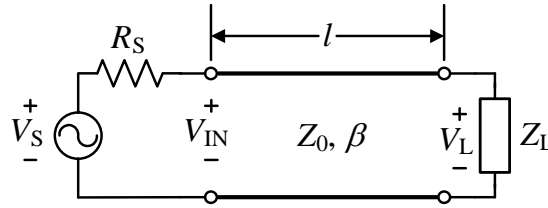7. The following transmission line circuit has  $V_S = 15 \text{ Vrms}$ ,  $R_S = 75 \Omega$ ,  $Z_0 = 75 \Omega$ ,  $Z_L = 55 - j30 \Omega$  at the operating frequency. Calculate the average power delivered to the load if: a)  $l = \lambda/4$ ; and b)  $l = 0.3\lambda$ .



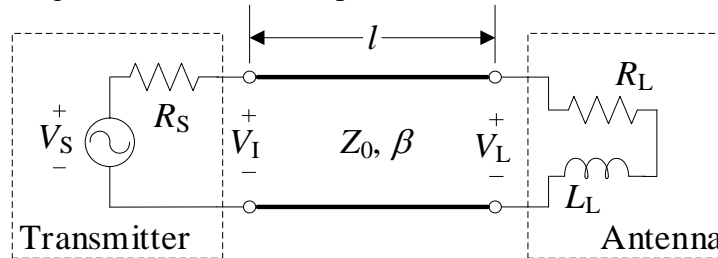8. A  $50\text{-}\Omega$  radio transmitter is connected to an antenna through a  $50\text{-}\Omega$  coaxial line. The antenna can be represented by a resistor  $R_L = 70 \Omega$  in series with an inductor  $L_L = 5 \text{ nH}$  when operating at  $3 \text{ GHz}$ . If the transmitter can deliver  $25 \text{ W}$  when connected to a matched load, a) What is the value of the equivalent source voltage,  $V_S$ ? b) how much power is delivered to the antenna at  $3 \text{ GHz}$ ?






9. A lossless transmission line (TL) has a characteristic impedance  $Z_0 = 50 \Omega$  and uses an effective permittivity  $\epsilon_e = 3.8$ . If a load impedance  $Z_L = 500 \Omega$  is connected to the transmission line, calculate the magnitude of the reflection coefficient at the load,  $|\Gamma|$ , at the following frequencies: a)  $3 \text{ GHz}$ , b)  $3 \text{ GHz} + 150 \text{ MHz}$ , and c)  $3 \text{ GHz} - 150 \text{ MHz}$ . If a quarter-wave transformer (QWT) is inserted between the TL and  $Z_L$  to achieve a perfect match at  $3 \text{ GHz}$ , calculate: d) its characteristic impedance  $Z_T$ , and e) its physical length  $l_T$ . Finally, calculate the magnitude of the reflection coefficient at the end of the TL (or the QWT input),  $|\Gamma|$ , at the following frequencies: f)  $3 \text{ GHz}$ , g)  $3 \text{ GHz} + 150 \text{ MHz}$ , and h)  $3 \text{ GHz} - 150 \text{ MHz}$ .

## SOLUTIONS

1. a)  $Z_0 = 46.69 \Omega \angle 7.7^\circ$  at 10 MHz;  
 $Z_0 = 49.96 \Omega \angle 0.97^\circ$  at 100 MHz;

b)

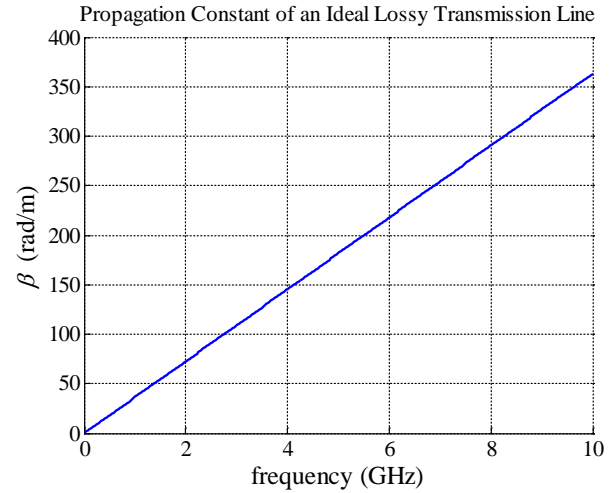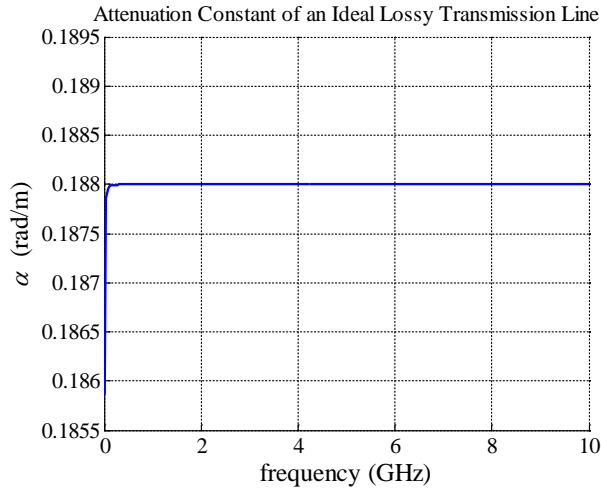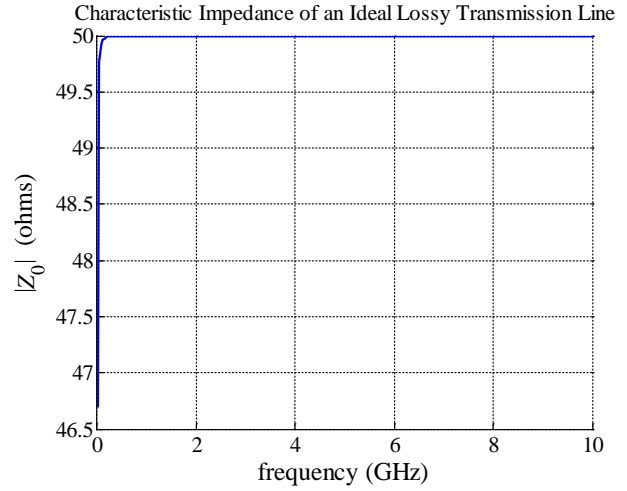

2. a)  $Z_{in} = 80.38 \Omega \angle 2.43^\circ$ ; b)  $Z_{in} = 72.35 \Omega \angle -14.13^\circ$ ; c)  $Z_{in} = 61.52 \Omega \angle -13.08^\circ$ .  
 Notice that  $Z_L = 80.25 \Omega \angle 4.49^\circ$  (when the transmission line is electrically very short,  $Z_{in} \approx Z_L$ ).
3. a)  $Z_{in} = 80.64 \Omega \angle 2.44^\circ$ ; b)  $Z_{in} = 74.26 \Omega \angle -15.02^\circ$ ; c)  $Z_{in} = 68.39 \Omega \angle -20.09^\circ$ .
4.  $\Gamma = 0.2425 \angle 104.04^\circ$  and  $SWR = 1.64$  in both cases. a)  $Z_{in} = 55.90 \Omega \angle -26.56^\circ$ ; b)  $Z_{in} = 33.19 \Omega \angle -15.29^\circ$ .
5. a)  $Z_{01} = 165 \Omega$ ,  $Z_{02} = 34.09 \Omega$ . b) Same value ( $SWR = 2.2$ ) because the transmission line is lossless.
6.  $\Gamma = 0.62 \angle 82.87^\circ$ ,  $\Gamma_l = 0.62 \angle -37.12^\circ$ ,  $SWR = 4.2656$ , and  $Z_{in} = 183.70 \Omega \angle -50.58^\circ$ .
7. a)  $P_{avg} = 695.22$  mW; b)  $P_{avg} = 695.22$  mW (same value because the transmission line is lossless and  $R_S = Z_0$ ).
8. a)  $V_S = 100$  V; b)  $P_{avg} = 15.03$  W.
9. a), b), c)  $|\Gamma| = 0.8182$  at all frequencies; d)  $Z_T = 158.114 \Omega$ ; e)  $l_T = 12.825$  mm; f)  $|\Gamma| = 0$  at  $f = 3$  GHz; g)  $|\Gamma| = 0.11096$  at  $f = 3$  GHz + 150 MHz; and h)  $|\Gamma| = 0.11096$  at  $f = 3$  GHz - 150 MHz.