## IMPEDANCE MATCHING CIRCUITS

Dr. J. E. Rayas-Sánchez May 4, 2020

## PROBLEMS

- 1. Using an L-section, find the two possible solutions to match a 75- $\Omega$  transmission line to a load impedance  $Z_L = (10 + j30) \Omega$ .
- 2. Using an L-section, find the two possible solutions to match a 50- $\Omega$  line at 100 MHz to a load impedance  $Z_L$  consisting of a 100- $\Omega$  resistor in parallel with a 10-pF capacitor.
- 3. Using an L-section, find the two possible solutions to match a 50- $\Omega$  line at 380 MHz to a load impedance  $Z_L$  consisting of a 35- $\Omega$  resistor in series with a 6-nH inductor. Implement in Keysight ADS both solutions and confirm the correct performance of the matching circuits by plotting  $|S_{11}|$  from 10 MHz to 800 MHz
- 4. The transmitter illustrated below is operating at 1 GHz on a 75- $\Omega$  system and has an output impedance  $Z_{\rm S} = (90 + j30) \Omega$ . The transmitter must be directly connected to an antenna whose input impedance is equivalent to the series combination of a resistor  $R_{\rm L} = 75 \Omega$  and an inductor  $L_{\rm L} = 3$ nH. Using the L-Section matching network indicated below, find the values of  $L_X$  and  $C_B$  such that maximum power is delivered to the antenna.



5. A load impedance  $Z_L$  consisting of a 100- $\Omega$  resistor in parallel with a 1-pF capacitor is to be match at 5 GHz to a transmission line whose characteristic impedance is  $Z_0 = 50 \Omega$ . Using a single-stub series tuning network as illustrated below: a) find the first two distances  $d_1$  and  $d_2$  from the load where the stub could be connected; b) connecting the stub at the minimum distance from the load, find the length  $l_{oc}$  for an open-circuited stub, and the length  $l_{sc}$  for a short-circuited stub; c) assuming transmission lines on air (or free-space), implement in Keysight ADS the solution for d minimum and  $l_{oc}$ .



6. Repeat problem 5 using a single-stub shunt tuning network.

7. A load impedance at 5 GHz is  $Z_L = (30 + j90) \Omega$ . A single-stub shunt tuning network, as illustrated below, is used to match  $Z_L$  to  $Z_0 = 50 \Omega$ . a) Find the first two distances  $d_1$  and  $d_2$  from the load where the stub could be connected; b) Connecting the stub at the minimum distance from the load, find the length  $l_{oc}$  for an open-circuited stub, and the length  $l_{sc}$  for a short-circuited stub.



- 8. Design a 3-section binomial impedance transformer to match at 1 GHz a load impedance  $Z_L = 100 \Omega$  to a transmission line with characteristic impedance  $Z_0 = 50 \Omega$ . Calculate the theoretical bandwidth  $\Delta f$  at  $\Gamma_m = -20$  dB. Calculate the corresponding lengths of the three sections assuming ideal transmission lines on air. Implement your design in Keysight ADS and confirm the theoretical results.
- 9. Design a 5-section Butterworth impedance transformer to match a load impedance  $Z_L = 200 \Omega$  to a transmission line whose characteristic impedance is  $Z_0 = 50 \Omega$ . Calculate the theoretical fractional bandwidth for a maximum reflection of -60 dB. Calculate the corresponding lengths of the five sections to achieve a perfect match at 15 GHz, assuming ideal transmission lines with effective relative dielectric constant  $\varepsilon_e = 3.2$ .
- 10. Implement in microstrip technology the impedance transformer of Problem 8. Assume that the substrate height is H = 2 mm, with a relative dielectric constant  $\varepsilon_r = 4$ . For the dielectric losses, use a loss tangent tan( $\delta$ ) = 0.01. For the metallic losses, assume that all metal traces (including the ground plane) are made of copper with conductivity  $\sigma = 5.8 \times 10^7$  S/m and thickness t = 0.6 mil = 15.24 µm (half-once copper). Simulate the corresponding circuit in Keysight ADS.

**SOLUTIONS** 



Dr. J. E. Rayas-Sánchez

Impedance Matching Circuits



Impedance Matching Circuits

4

- 4.  $L_X = 3.89 \text{ nH}; C_B = 1.45 \text{ pF}.$
- 5.  $d_1 = 0.279\lambda$ ,  $d_2 = 0.392\lambda$ . Using  $d = 0.279\lambda$ , then  $l_{oc} = 0.0645\lambda$  and  $l_{sc} = 0.3145\lambda$ . Since  $\varepsilon_e = 1$  (air or free-space) and f = 5 GHz,  $\lambda = 60$  mm. Hence d = 16.74 mm and  $l_{oc} = 3.87$  mm. ADS simulation:



6.  $d_1 = 0.0288\lambda$ ,  $d_2 = 0.1416\lambda$ . Using  $d = 0.0288\lambda$ , then  $l_{oc} = 0.3145\lambda$  and  $l_{sc} = 0.0645\lambda$ . Since  $\varepsilon_e = 1$  and f = 5 GHz,  $\lambda = 60$  mm. Hence d = 1.728 mm and  $l_{oc} = 18.87$  mm. ADS simulation:



- 7.  $d_1 = 0.2696\lambda$ ,  $d_2 = 0.3808\lambda$ . Using  $d = 0.2696\lambda$ , then  $l_{oc} = 0.3133\lambda$  and  $l_{sc} = 0.0633\lambda$ .
- 8.  $Z_1 = 54.535 \Omega$ ,  $Z_2 = 70.71 \Omega$ ,  $Z_3 = 91.685 \Omega$ ,  $l_1 = l_2 = l_3 = 75$  mm. The theoretical bandwidth is  $\Delta f = 919.13$  MHz. Implementation in Keysight ADS with ideal transmission lines:





It is confirmed a Butterworth response centered at 1 GHz, with  $|\Gamma| = 0.333 = -9.54$  dB at low frequencies.

Zooming-in to measure the bandwidth at  $\Gamma_m = 0.1 = -20$  dB, and simulating up to 6 GHz:



It is seen that  $\Delta f = (1,456 - 542)$  MHz = 914 MHz at  $\Gamma_m = 0.1$ , which is very close to the theoretical prediction (919.13 MHz). It is also confirmed a periodic impedance matching at 1 GHz, 3 GHz, 5 GHz, etc.

9.  $Z_1 = 52.26 \ \Omega$ ,  $Z_2 = 64.975 \ \Omega$ ,  $Z_3 = 100 \ \Omega$ ,  $Z_4 = 153.905 \ \Omega$ ,  $Z_5 = 191.35 \ \Omega$ . The expected relative bandwidth for maximum reflection  $\Gamma_m = 0.001 = -60 \ \text{dB}$  is 34.85%. Centering the impedance transformer at  $f_0 = 15 \ \text{GHz}$ , the expected theoretical bandwidth is  $\Delta f = 5.227 \ \text{GHz}$ . The five TL lengths are  $l_1 = \ldots = l_5 = 2.7951 \ \text{mm}$ . Implementation in Keysight ADS with ideal transmission lines:





It is confirmed a Butterworth response centered at 15 GHz, with  $|\Gamma| = 0.6 = -4.44$  dB at low frequencies.





It is seen that the actual bandwidth  $\Delta f$  is equal to (17.56 – 12.42) GHz = 5.14 GHz at  $\Gamma_m$ , which is close to the theoretical expected bandwidth (5.227 GHz).

10. Using Gupta's formulas:

 $W_1/H = 1.767$  for  $Z_0 = 54.535 \ \Omega$  and  $\varepsilon_r = 4$  $W_2/H = 1.0829$  for  $Z_0 = 70.71 \ \Omega$  and  $\varepsilon_r = 4$  $W_3/H = 0.61071$  for  $Z_0 = 91.685 \ \Omega$  and  $\varepsilon_r = 4$ 

Since H = 2mm, then  $W_1 = 3.534$ mm,  $W_2 = 2.1659$ mm,  $W_3 = 1.2214$ mm.

The effective dielectric constant for each segment of microstrip line is:

 $\varepsilon_{e1} = 3.0813$  for  $W_1/H = 1.767$  and  $\varepsilon_{r} = 4$  $\varepsilon_{e2} = 2.9689$  for  $W_2/H = 1.0829$  and  $\varepsilon_{r} = 4$  $\varepsilon_{e3} = 2.8599$  for  $W_3/H = 0.61071$  and  $\varepsilon_{r} = 4$ 

The corresponding physical lengths are ( $f_0 = 1$ GHz):

 $l_1 = \lambda_1/4 = 42.7264 \text{ mm}, l_2 = \lambda_2/4 = 43.5276 \text{ mm}, l_3 = \lambda_3/4 = 44.3495 \text{ mm}$ 

Implementing the circuit in Keysight ADS:



It is seen that the impedance matching is centered at 1 GHz, with  $|\Gamma| = 0.333 = -9.54$  dB at low frequencies, as expected. However, the response is strictly no longer a Butterworth response (maximally flat).

Zooming-in to measure the bandwidth at  $\Gamma_m = 0.1 = -20$  dB, and simulating up to 6 GHz:



It is seen that  $\Delta f = (1,470 - 535.1)$  MHz = 934.9 MHz at  $\Gamma_m = 0.1$ , which is still close to the theoretical prediction (919.13 MHz). It is also seen that the periodic impedance matching at 1 GHz, 3 GHz, 5 GHz, etc. is affected by the microstrip losses.