HIGH-FREQUENCY FILTER DESIGN

Dr. J. E. Rayas-Sánchez May 14, 2020

PROBLEMS

- 1. Using the Insertion-Loss method, design a low-pass filter, in current source configuration, with the following specifications: a) Cut-off frequency at 1 GHz; b) Reference impedance of 50 Ω ; c) Minimum attenuation of 40 dB at 5 GHz; d) Chebyshev filtering profile with a 3-dB ripple level. Verify your design using Keysight ADS.
- Using the Insertion-Loss method, design a low-pass filter prototype, in voltage source configuration, with the following specifications: a) Cut-off frequency at 5 GHz; b) Reference impedance of 50 Ω;
 c) Minimum attenuation of 40 dB at 10 GHz; d) Chebyshev filtering profile with a 3-dB ripple level. Verify your design using Keysight ADS.
- 3. Using the Insertion-Loss method, design a high-pass filter prototype with the following specifications: a) Cut-off frequency at 4 GHz; b) Reference impedance of 50 Ω ; c) Minimum insertion loss of 70 dB at 1 GHz; d) Chebyshev response with a 3-dB ripple level. Verify your design using Keysight ADS.
- 4. Using the Insertion-Loss method, design a fourth-order band-pass filter prototype with the following specifications: a) Center frequency at 3 GHz; b) Relative bandwidth of 25%; c) Reference impedance of 50 Ω ; d) Butterworth filtering profile. Check your design using Keysight ADS.
- 5. Using the Insertion-Loss method, design a sixth-order stop-band filter prototype with the following specifications: a) Center frequency at 10 GHz; b) Fractional bandwidth of 34%; c) Reference impedance of 50 Ω ; d) Chebyshev filtering profile with a 0.5-dB ripple level. Check your design using Keysight ADS.
- 6. Implement the filter in the above problem 1 using ideal transmission lines on air ($\varepsilon_r = 1$). Do not use series stubs, only parallel stubs are allowed. Verify your design using Keysight ADS.
- 7. Implement the filter in the above problem 6 using microstrip lines on a dielectric substrate with relative dielectric constant $\varepsilon_r = 4$ and substrate height H = 16 mil. Check the final structure responses using Keysight ADS.

1

SOLUTIONS







 $V_{\rm s}$

freq, GHz



High-Frequency Filter Design



6.





Notice the periodicity of the filter responses.

Zooming-in to measure the ripple amplitude:



7.

Using Gupta's formulas:

 $W_0/H = 2.0438$ for $Z_0 = 50 \Omega$ and $\varepsilon_r = 4$ (input/output microstrip lines) $W_1/H = 1.2858$ for $Z_0 = 64.931 \Omega$ and $\varepsilon_r = 4$ $W_2/H = 1.0976$ for $Z_0 = 70.255 \Omega$ and $\varepsilon_r = 4$ $W_3/H = 0.0239$ for $Z_0 = 217.435 \Omega$ and $\varepsilon_r = 4$

Dr. J. E. Rayas-Sánchez

High-Frequency Filter Design

Since H = 16 mil, thenThe effective relative permittivity for each segment of microstrip line is: $W_0 = 32.70$ mil $\varepsilon_{e0} = 3.1179$ for $W_0/H = 2.0438$ and $\varepsilon_r = 4$ $W_1 = 20.57$ mil $\varepsilon_{e1} = 3.0063$ for $W_1/H = 1.2858$ and $\varepsilon_r = 4$ $W_2 = 17.56$ mil $\varepsilon_{e2} = 2.9717$ for $W_2/H = 1.0976$ and $\varepsilon_r = 4$ $W_3 = 0.3824$ mil $\varepsilon_{e3} = 2.5732$ for $W_3/H = 0.0239$ and $\varepsilon_r = 4$

Calculating the corresponding physical lengths:

 $l_0 = 100$ mil (arbitrarily selected) $l_1 = \lambda_1/8 = 851.49$ mil $l_2 = \lambda_2/8 = 856.44$ mil $l_3 = \lambda_3/8 = 920.37$ mil

Implementing the microstrip circuit in ADS:







Zooming-in to measure the ripple amplitude:



Notice that the response of this microstrip filter is almost identical (up to 2.5 GHz) to that one using ideal transmission lines (see problem 6).