

# **High-Frequency Filters**

(Part 1)

**Dr. José Ernesto Rayas-Sánchez**

1

## Outline

---

- Filter design at high frequencies
- General characteristics of filters
- Methods for filter design at high-frequencies
- The insertion loss method
- Example of a low-pass prototype filter design


## Filter Design at High-Frequencies

- Lumped inductors and capacitors are unsuitable for frequencies above 500 MHz
- At high-frequencies, we use distributed elements
- An impedance-normalized low-pass filter is the basic building block
- We also use a normalized frequency  $\Omega$
- Transformations are used to convert lumped elements to distributed elements (e.g. Richards transformation, Kuroda identities, etc.)
- Transfer function is usually attenuation or insertion loss (instead of voltage gain)

Dr. J. E. Rayas-Sánchez

3

## Types of Filters

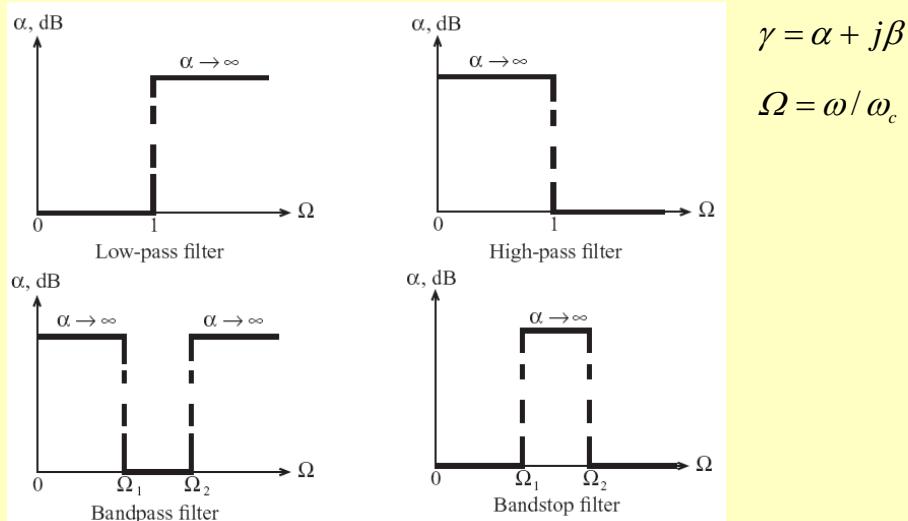

Dr. J. E. Rayas-Sánchez


(R. Ludwig and P. Bretschko, RF Circuit Design, Prentice Hall, 2000) 4

## High-Frequency Filters (Part 1)

Dr. José Ernesto Rayas-Sánchez

May 12, 2020


### Types of Filtering Profiles

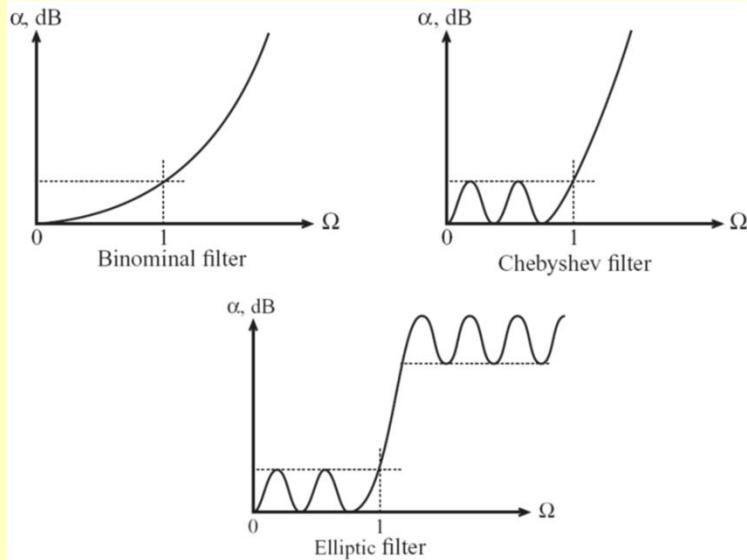

Dr. J. E. Rayas-Sánchez

(R. Ludwig and P. Brettko, RF Circuit Design, Prentice Hall, 2000) <sub>5</sub>

### Filter Response Parameters

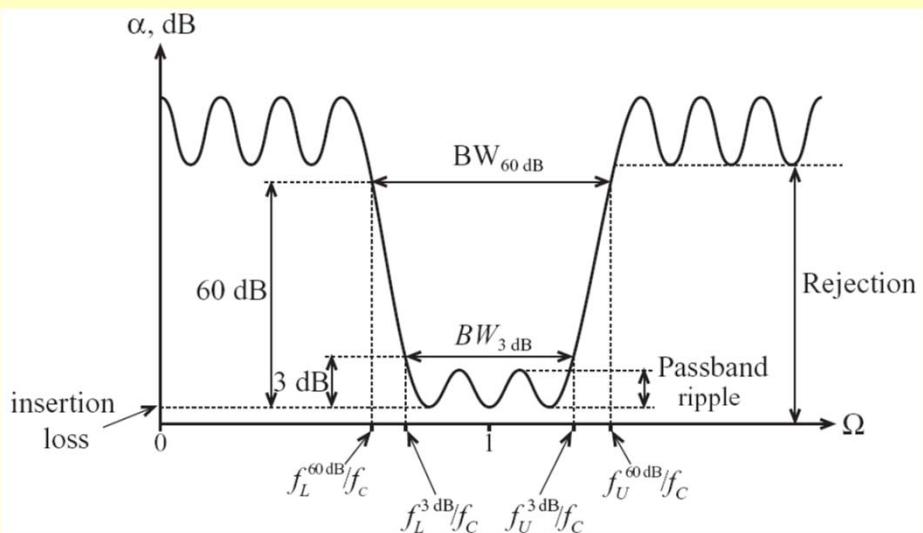

Dr. J. E. Rayas-Sánchez


(R. Ludwig and P. Brettko, RF Circuit Design, Prentice Hall, 2000) <sub>6</sub>

## High-Frequency Filters (Part 1)

Dr. José Ernesto Rayas-Sánchez

May 12, 2020


### Filter Response Parameters (cont.)

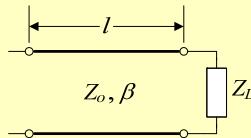

$$P_{av} = \frac{1}{2} \frac{|V_o^+|^2}{Z_o} (1 - |\Gamma|^2)$$

$$P_{LR} = \frac{P_{inc}}{P_L} \text{ (power loss ratio)}$$

$$IL = 10 \log \frac{P_{inc}}{P_L} = -10 \log (1 - |\Gamma|^2)$$

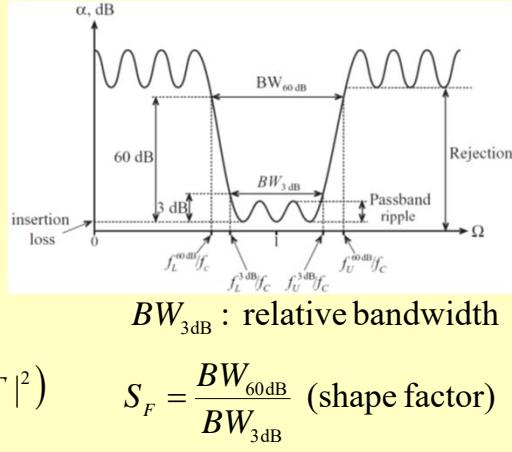

$$BW_{3dB} : \text{relative bandwidth}$$

$$S_F = \frac{BW_{60dB}}{BW_{3dB}} \text{ (shape factor)}$$

$$Q_{LD} = \frac{1}{BW_{3dB}} = \frac{f_c}{f_U^{3dB} - f_L^{3dB}} \text{ (loaded Q)}$$

Dr. J. E. Rayas-Sánchez

(R. Ludwig and P. Bretschko, RF Circuit Design, Prentice Hall, 2000) ,

### General Methods for Filter Design


- The Image Parameter method
- The Insertion Loss method
- CAD techniques

Dr. J. E. Rayas-Sánchez

8
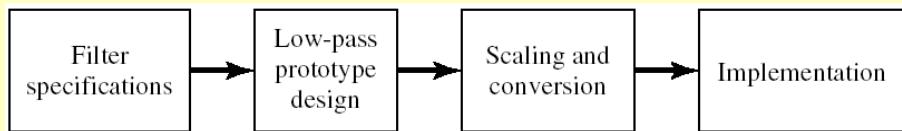
## The Insertion Loss Method

- It uses network synthesis techniques from a completely specified frequency response
- The characterizing response is the power-loss ratio (or the insertion loss)
- General procedure:



Dr. J. E. Rayas-Sánchez

(D. M. Pozar, *Microwave Engineering*, Wiley, 2005) ,

## Power-Loss Ratio Characterization

$$P_{LR} = \frac{P_{inc}}{P_L} = \frac{\text{power from the source}}{\text{power delivered to the load}} = \frac{P_{inc}}{P_{inc} - P_{ref}} = (1 - |\Gamma|^2)^{-1}$$

$$IL = 10 \log P_{LR} = -10 \log(1 - |\Gamma(\omega)|^2)$$

$$P_{LR} = \frac{1}{1 - |\Gamma(\omega)|^2}$$

It can be shown that  $\Gamma(\omega)$  is an even function of  $\omega$  ( $\Gamma(\omega)$  can be represented by even series of the form  $k_0 + k_2\omega^2 + k_4\omega^4 + \dots$ )

Since  $|\Gamma(\omega)| \leq 1$ , it can be expressed as

$$|\Gamma(\omega)|^2 = \frac{M(\omega^2)}{M(\omega^2) + N(\omega^2)} \quad \text{then} \quad P_{LR} = 1 + \frac{M(\omega^2)}{N(\omega^2)}$$

Dr. J. E. Rayas-Sánchez

10

## Power-Loss Ratio Filtering Profiles

- Maximally Flat profile (or Binomial or Butterworth)


$$P_{LR} = 1 + k^2 \left( \frac{\omega}{\omega_c} \right)^{2N}$$

$N$ : filter order

- Chebyshev profile

$$P_{LR} = 1 + k^2 T_N^2 \left( \frac{\omega}{\omega_c} \right)$$

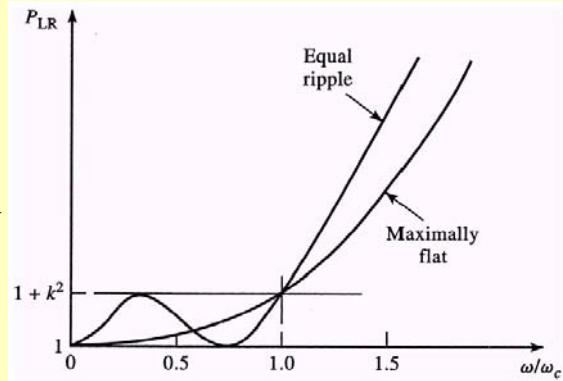$T_N(x)$  is the Chebyshev polynomial of order  $N$




Dr. J. E. Rayas-Sánchez


(D. M. Pozar, *Microwave Engineering*, Wiley, 2005) 11

## Normalized Low-Pass Prototypes

- Series source

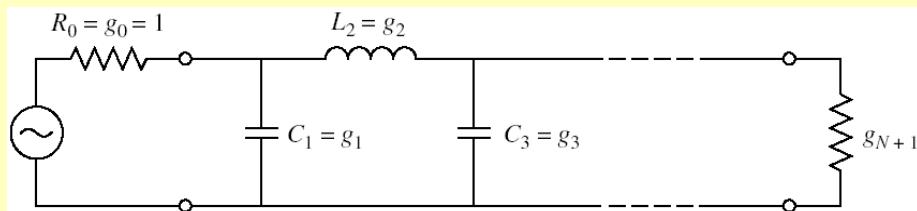

- Shunt source

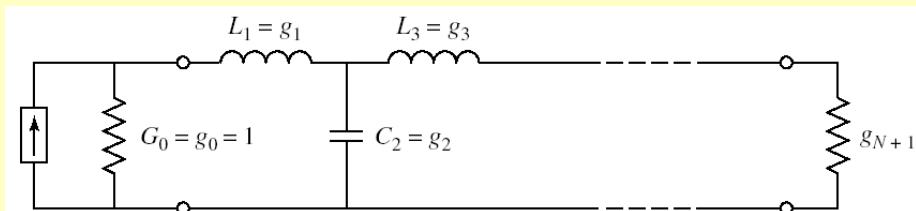


Dr. J. E. Rayas-Sánchez


(D. M. Pozar, *Microwave Engineering*, Wiley, 2005) 12

### Normalized Low-Pass Prototypes (cont.)

- Series source

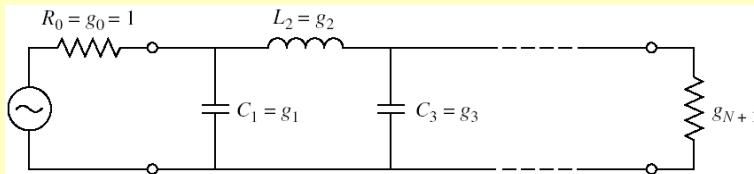

- Shunt source

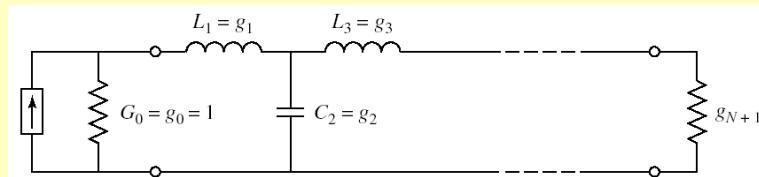


$$g_{N+1} = \begin{cases} \text{Scaled load resistance if } g_N \text{ is a shunt capacitor} \\ \text{Scaled load conductance if } g_N \text{ is a series inductor} \end{cases}$$

Dr. J. E. Rayas-Sánchez

(D. M. Pozar, *Microwave Engineering*, Wiley, 2005) 13
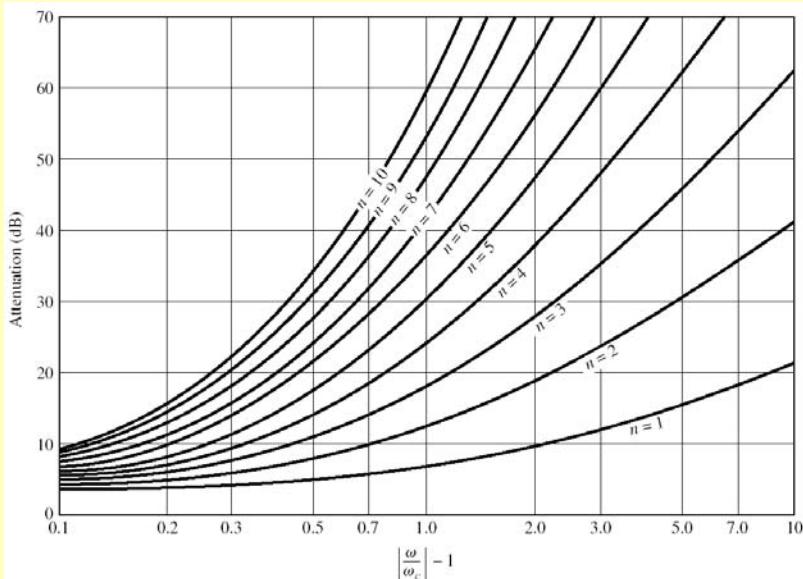
### Attenuation for L-P Prototypes (Butterworth)



Dr. J. E. Rayas-Sánchez

(D. M. Pozar, *Microwave Engineering*, Wiley, 2005) 14

## High-Frequency Filters (Part 1)

Dr. José Ernesto Rayas-Sánchez

May 12, 2020

### Element Values L-P Prototypes (Butterworth)

(Assuming  $g_0 = 1$  and  $\omega_c = 1$ )


$N$	$g_1$	$g_2$	$g_3$	$g_4$	$g_5$	$g_6$	$g_7$	$g_8$	$g_9$	$g_{10}$	$g_{11}$
1	2.0000	1.0000									
2	1.4142	1.4142	1.0000								
3	1.0000	2.0000	1.0000	1.0000							
4	0.7654	1.8478	1.8478	0.7654	1.0000						
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000					
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0000				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000			
8	0.3902	1.1111	1.6629	1.9615	1.9615	1.6629	1.1111	0.3902	1.0000		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0000	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129	1.0000

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures* (Dedham, Mass.: Artech House, 1980) with permission.

Dr. J. E. Rayas-Sánchez

(D. M. Pozar, *Microwave Engineering*, Wiley, 2005) 15
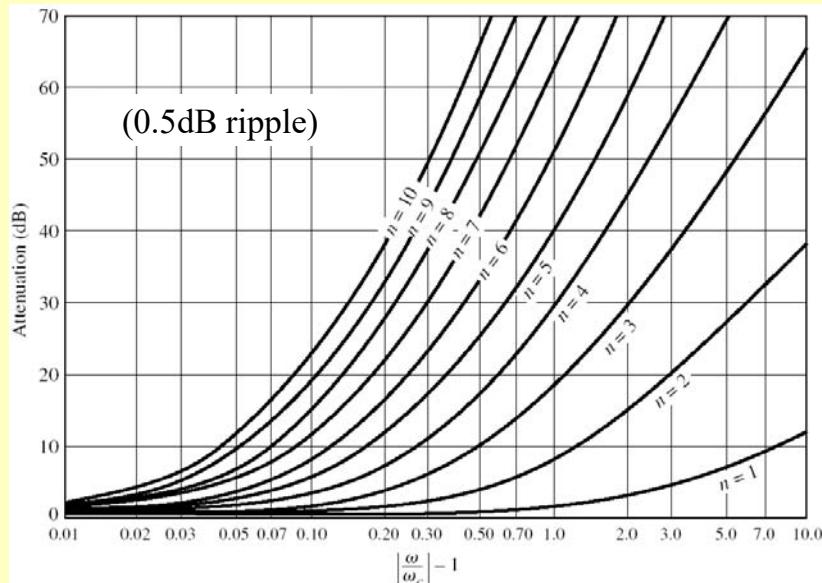
### Attenuation for L-P Prototypes (Chebyshev)



Dr. J. E. Rayas-Sánchez


(D. M. Pozar, *Microwave Engineering*, Wiley, 2005) 16

## High-Frequency Filters (Part 1)

Dr. José Ernesto Rayas-Sánchez

May 12, 2020
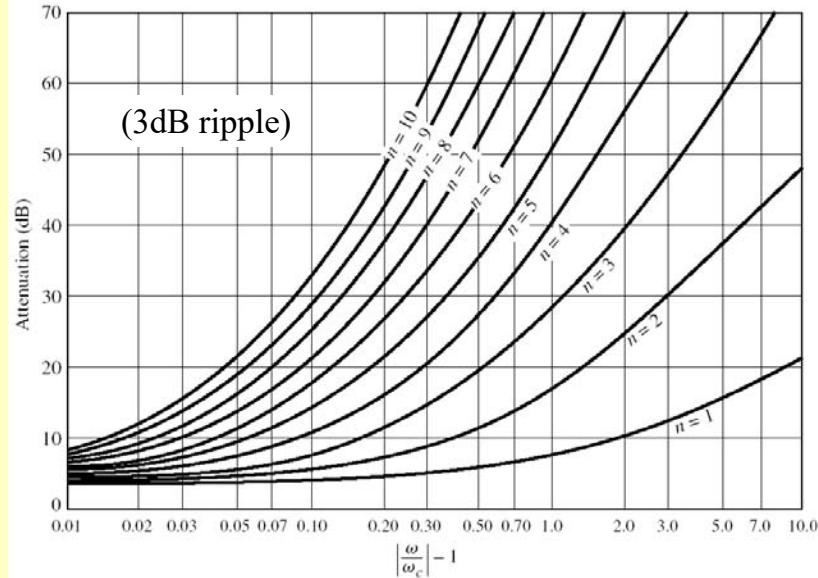
### Attenuation for L-P Prototypes (Chebyshev)



Dr. J. E. Rayas-Sánchez

(D. M. Pozar, *Microwave Engineering*, Wiley, 2005) 17

### Element Values L-P Prototypes (Chebyshev)

(Assuming  $g_0 = 1$  and  $\omega_c = 1$ )

N	0.5 dB Ripple										
	$g_1$	$g_2$	$g_3$	$g_4$	$g_5$	$g_6$	$g_7$	$g_8$	$g_9$	$g_{10}$	$g_{11}$
1	0.6986	1.0000									
2	1.4029	0.7071	1.9841								
3	1.5963	1.0967	1.5963	1.0000							
4	1.6703	1.1926	2.3661	0.8419	1.9841						
5	1.7058	1.2296	2.5408	1.2296	1.7058	1.0000					
6	1.7254	1.2479	2.6064	1.3137	2.4758	0.8696	1.9841				
7	1.7372	1.2583	2.6381	1.3444	2.6381	1.2583	1.7372	1.0000			
8	1.7451	1.2647	2.6564	1.3590	2.6964	1.3389	2.5093	0.8796	1.9841		
9	1.7504	1.2690	2.6678	1.3673	2.7239	1.3673	2.6678	1.2690	1.7504	1.0000	
10	1.7543	1.2721	2.6754	1.3725	2.7392	1.3806	2.7231	1.3485	2.5239	0.8842	1.9841

(In this case,  $\omega_c$  is at  $-0.5$  dB)

Dr. J. E. Rayas-Sánchez

(D. M. Pozar, *Microwave Engineering*, Wiley, 2005) 18

## High-Frequency Filters (Part 1)

Dr. José Ernesto Rayas-Sánchez

May 12, 2020

### Element Values L-P Prototypes (Chebyshev)

(Assuming  $g_0 = 1$  and  $\omega_c = 1$ )

<i>N</i>	$g_1$	$g_2$	$g_3$	$g_4$	$g_5$	$g_6$	$g_7$	$g_8$	$g_9$	$g_{10}$	$g_{11}$
1	1.9953	1.0000									
2	3.1013	0.5339	5.8095								
3	3.3487	0.7117	3.3487	1.0000							
4	3.4389	0.7483	4.3471	0.5920	5.8095						
5	3.4817	0.7618	4.5381	0.7618	3.4817	1.0000					
6	3.5045	0.7685	4.6061	0.7929	4.4641	0.6033	5.8095				
7	3.5182	0.7723	4.6386	0.8039	4.6386	0.7723	3.5182	1.0000			
8	3.5277	0.7745	4.6575	0.8089	4.6990	0.8018	4.4990	0.6073	5.8095		
9	3.5340	0.7760	4.6692	0.8118	4.7272	0.8118	4.6692	0.7760	3.5340	1.0000	
10	3.5384	0.7771	4.6768	0.8136	4.7425	0.8164	4.7260	0.8051	4.5142	0.6091	5.8095

Source: Reprinted from G. L. Matthaei, L. Young, and E. M. T. Jones, *Microwave Filters, Impedance-Matching Networks, and Coupling Structures* (Dedham, Mass.: Artech House, 1980) with permission.

Dr. J. E. Rayas-Sánchez

(D. M. Pozar, *Microwave Engineering*, Wiley, 2005) 19

### De-Normalized Element Values L-P Prototypes

The final element values for a low-pass prototype are obtained from:

$$L_k = \frac{R_0 g_k}{\omega_c} \quad \leftarrow g_k = (\omega_c L_k)/R_0$$

$$C_k = \frac{g_k}{R_0 \omega_c} \quad \leftarrow g_k = (\omega_c C_k) R_0$$

$$R_L = \begin{cases} R_0 / g_{N+1} & \text{if } g_{N+1} \text{ corresponds to a load conductance} \\ R_0 g_{N+1} & \text{if } g_{N+1} \text{ corresponds to a load resistance} \end{cases}$$

$R_0$  is the actual source resistance = reference impedance  $Z_0$

Dr. J. E. Rayas-Sánchez

20


## Example: Low-Pass Filter Prototype

Design a low-pass filter with the following specifications:

- Cut-off frequency at 3 GHz
- For a  $75\text{-}\Omega$  system
- Minimum attenuation of 20 dB at 5 GHz
- Butterworth filtering profile
- Use a series voltage source topology

## Example: Low-Pass Filter Prototype (cont.)

ADS simulation:

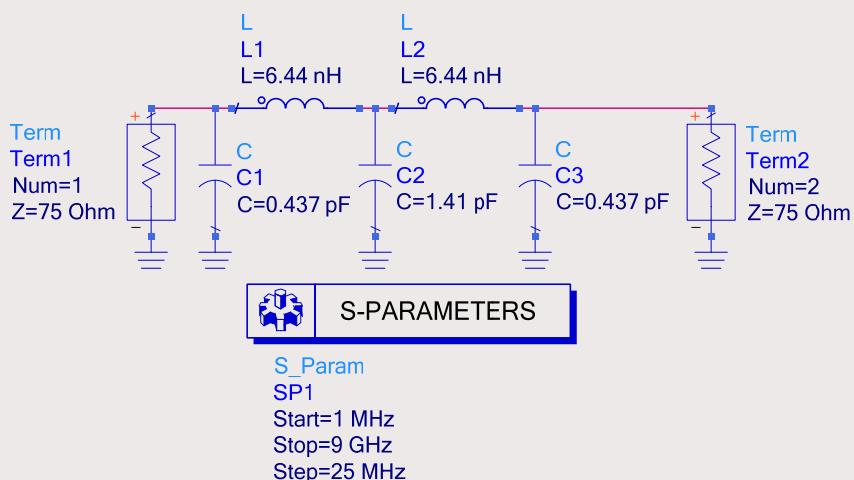


## High-Frequency Filters (Part 1)

Dr. José Ernesto Rayas-Sánchez

May 12, 2020

### Example: Low-Pass Filter Prototype (cont.)

ADS simulation results:

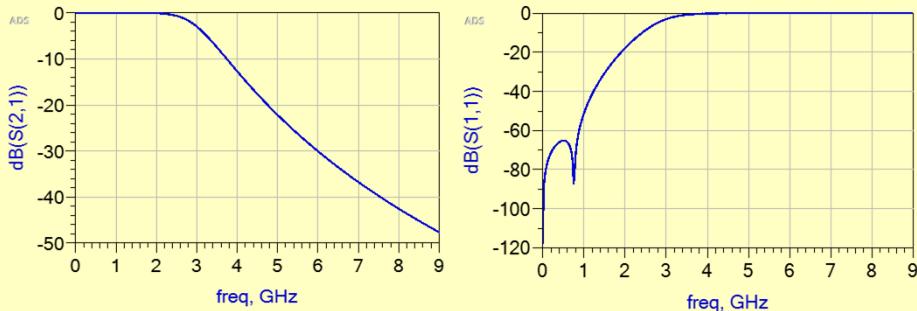


Dr. J. E. Rayas-Sánchez

23

### Example: Low-Pass Filter Prototype (cont.)

ADS simulation results (cont.):

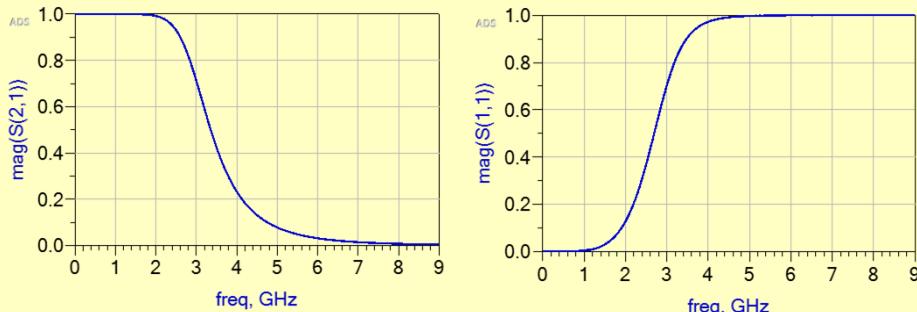


Dr. J. E. Rayas-Sánchez

24

## Example: Low-Pass Filter Prototype (cont.)

ADS simulation results (cont.):

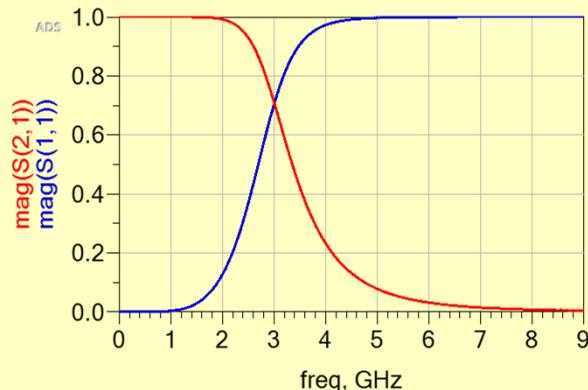

$$|S_{11}|^2 + |S_{21}|^2 = 1$$