

Impedance Matching Circuits (Part 1)

Dr. José Ernesto Rayas-Sánchez

April 25, 2020

Impedance Matching Circuits

(Part 1)

Dr. José Ernesto Rayas-Sánchez

1

Outline


- Benefits of impedance matching
- Properties of an impedance matching network
- Techniques for impedance matching
- Matching with L-sections
- Example of matching with L-sections

Impedance Matching Benefits

- Maximum power delivered to the load (assuming the source is also matched)
- Power loss in the feeding line is minimized
- Reflections are eliminated on the feeding line
- Impedance matching sensitive loads (such as antennas, low-noise amplifiers, etc.) improve the signal-to-noise ratio of the system

Properties of an Impedance Matching Network

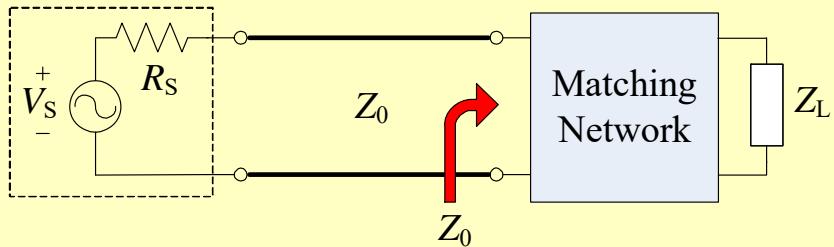- Physical complexity
- Bandwidth
- Adjustability (to match a variable load impedance)




Techniques for Impedance Matching

- Matching with L-Sections (lumped elements)
- Single-stub tuning
- Double-stub tuning
- Multi-section impedance transformers
- Tapered lines

Matching with L-Sections

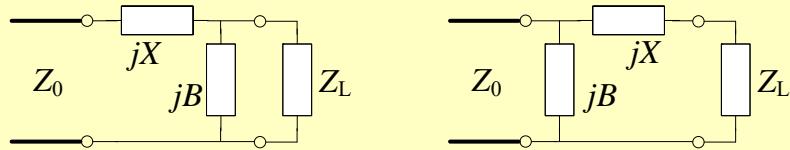- Since it uses lumped elements, it is applicable only if the frequency is low enough or the circuit size is small enough
- Two possible L-Sections:




X : Reactance, B : Susceptance

If $X > 0$, X is an inductor; if $X < 0$, X is a capacitor


If $B > 0$, B is a capacitor; if $B < 0$, B is an inductor

Finding X and B in L-Sections

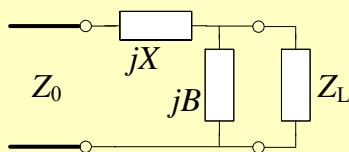- Analytical solutions
- Smith-Chart solutions
- If $R_L > Z_0$ use:



- If $R_L < Z_0$ use:

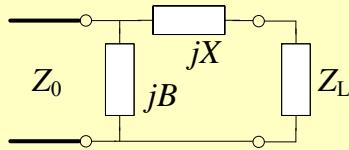


$$Z_L = R_L + jX_L \quad 7$$

Dr. J. E. Rayas-Sánchez

Analytical Solutions for L-Sections


- If $R_L > Z_0$ use:

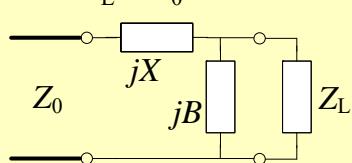

$$B = \frac{X_L \pm \sqrt{R_L/Z_0} \sqrt{X_L^2 - R_L Z_0 + R_L^2}}{X_L^2 + R_L^2}$$

$$X = (Z_0/R_L)[B(R_L^2 + X_L^2) - X_L]$$

- If $R_L < Z_0$ use:

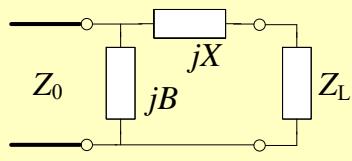

$$X = \pm \sqrt{R_L(Z_0 - R_L)} - X_L$$

$$B = \frac{X + X_L}{(X + X_L)^2 + R_L^2}$$

Each case yields 2 valid solutions

Dr. J. E. Rayas-Sánchez


8

Impedance Matching Circuits (Part 1)

Dr. José Ernesto Rayas-Sánchez

April 25, 2020


Smith Chart

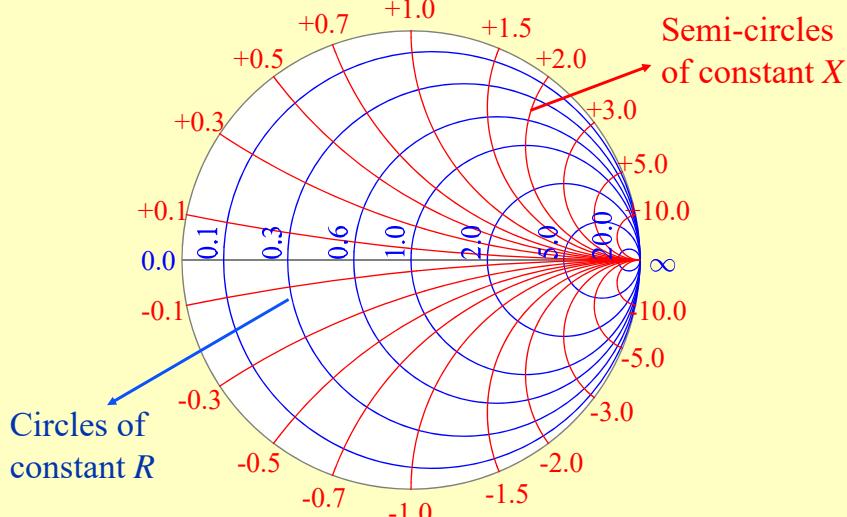

Dr. J. E. Rayas-Sánchez

9

Smith Chart: Z in Series with jX – Example 1

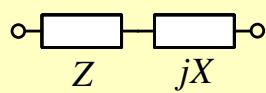


Example 1:

$$Z = (15 + j25) \Omega$$

$$X = 75 \Omega$$


$$Z_{eq} = (15 + j100) \Omega$$

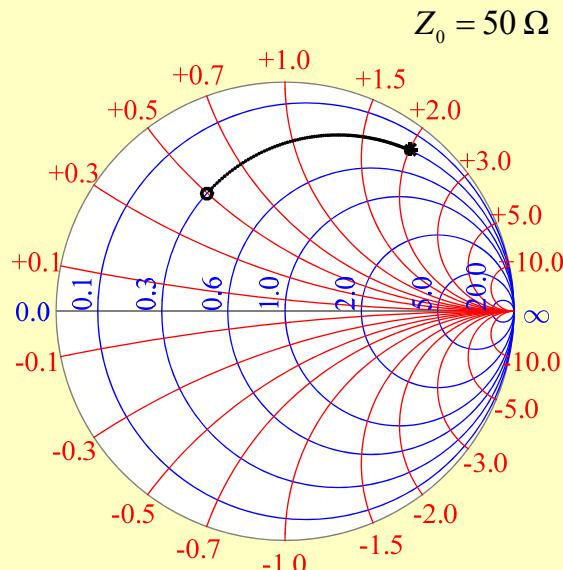

Dr. J. E. Rayas-Sánchez

10

Smith Chart: Z in Series with jX – Example 2

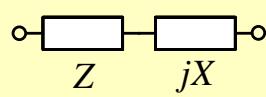


Example 2:

$$Z = (100 - j150) \Omega$$

$$X = 135 \Omega$$


$$Z_{\text{eq}} = (100 - j15) \Omega$$

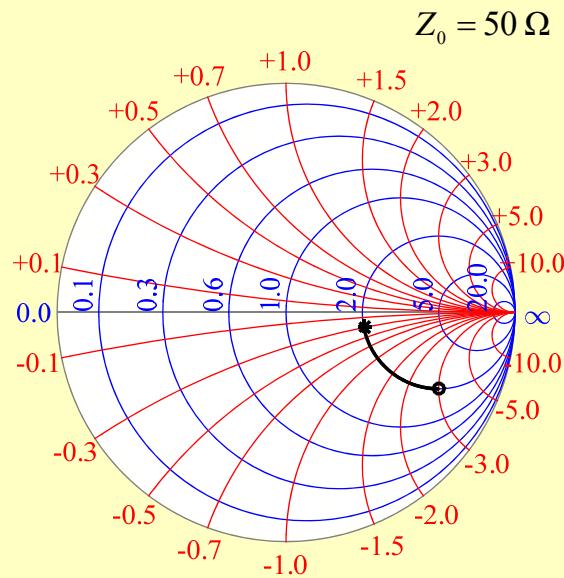

Dr. J. E. Rayas-Sánchez

11

Smith Chart: Z in Series with jX – Example 3

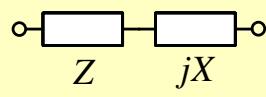


Example 3:

$$Z = (50 + j250) \Omega$$

$$X = -250 \Omega$$

$$Z_{\text{eq}} = 50 \Omega$$

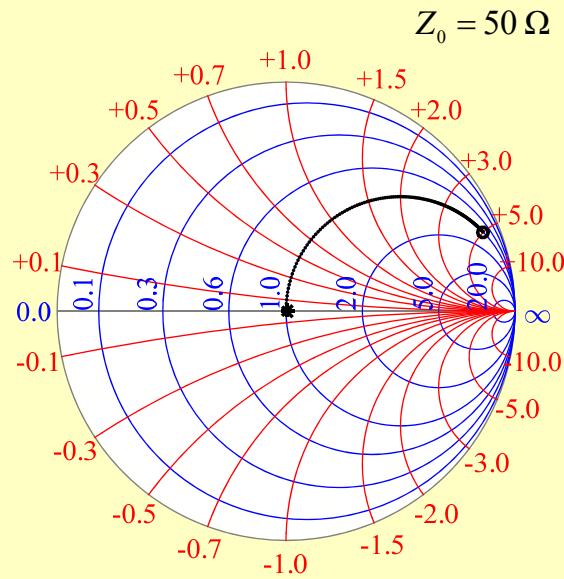

Dr. J. E. Rayas-Sánchez


12

Impedance Matching Circuits (Part 1)

Dr. José Ernesto Rayas-Sánchez

April 25, 2020

Smith Chart: Z in Parallel with jB – Example 1

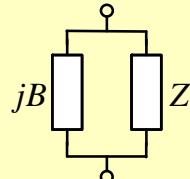


Example 1:

$$Z = (50 - j100) \Omega$$

$$B = -0.01 \text{ S}$$

$$Y = Z^{-1} = (0.004 + j0.008) \text{ S}$$

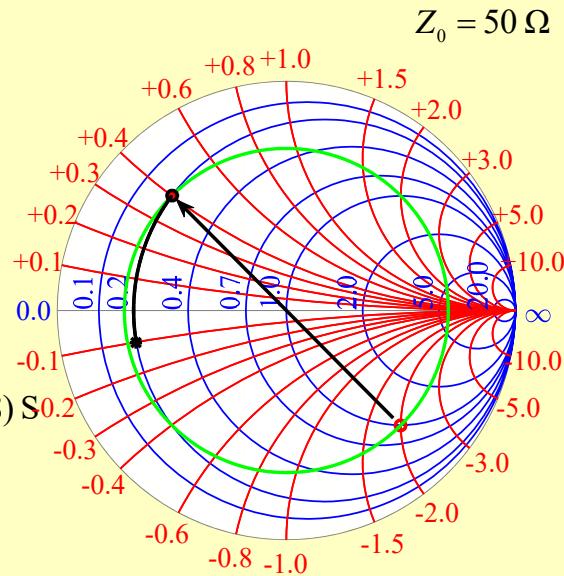
$$Y_{\text{eq}} = (0.004 - j0.002) \text{ S}$$



Dr. J. E. Rayas-Sánchez

13

Smith Chart: Z in Parallel with jB – Example 2

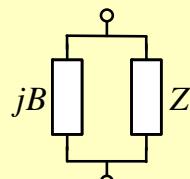


Example 2:

$$Z = (100 + j100) \Omega$$

$$B = 0.015 \text{ S}$$

$$Y = Z^{-1} = (0.005 - j0.005) \text{ S}$$
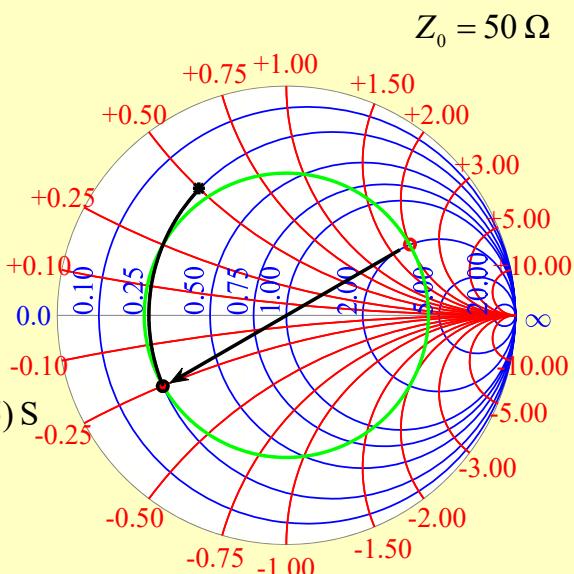
$$Y_{\text{eq}} = (0.005 + j0.01) \text{ S}$$



Dr. J. E. Rayas-Sánchez


14

Impedance Matching Circuits (Part 1)

Dr. José Ernesto Rayas-Sánchez

April 25, 2020

Smith Chart: Z in Parallel with jB – Example 3

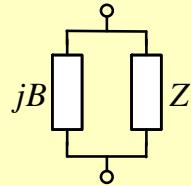


Example 3:

$$Z = (40 - j20) \Omega$$

$$B = -0.01 \text{ S}$$

$$Y = Z^{-1} = (0.02 + j0.01) \text{ S}$$

$$Y_{\text{eq}} = 0.02 \text{ S}$$

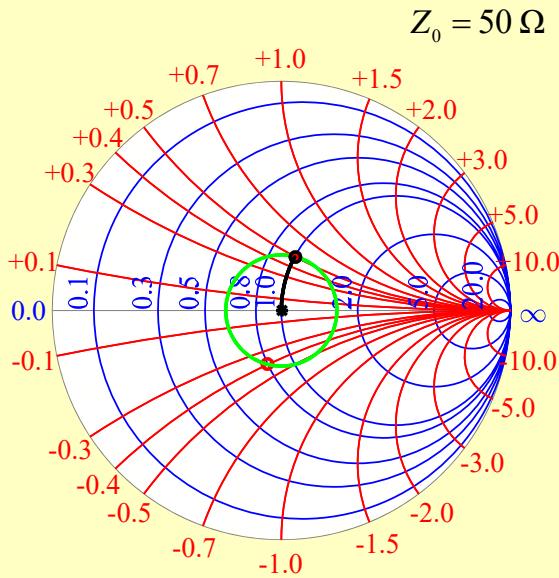

Dr. J. E. Rayas-Sánchez

15

Matching with L-Sections – Example 1

Find a matching network for a $100\text{-}\Omega$ system at 500 MHz to match a load consisting of a $200\text{-}\Omega$ resistor in series with a 3.18-pF capacitor.

$$Z_L = R_L + \frac{1}{j2\pi f C_L} = (200 - j100) \Omega$$

$$Z_0 = 100 \Omega$$

$$z_L = \frac{Z_L}{Z_0} = 2 - j$$

Dr. J. E. Rayas-Sánchez

(D. M. Pozar, *Microwave Engineering*, Wiley, 2005) 16

Impedance Matching Circuits (Part 1)



Dr. José Ernesto Rayas-Sánchez

April 25, 2020

Matching with L-Sections – Example 1 (cont.)

$$z_L = \frac{Z_L}{Z_0} = 2 - j$$

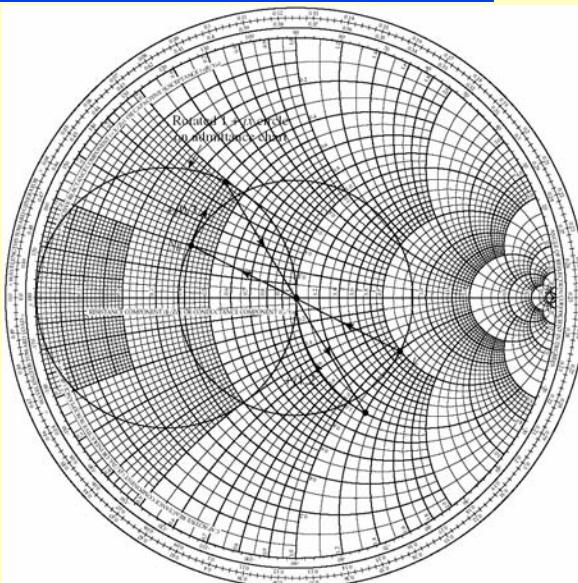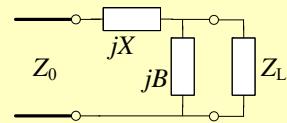z_L is inside the circle $1+jx$, then we use:




Dr. J. E. Rayas-Sánchez

(D. M. Pozar, Microwave Engineering, Wiley, 2005) 17

Matching with L-Sections – Example 1 (cont.)

$$z_L = \frac{Z_L}{Z_0} = 2 - j$$

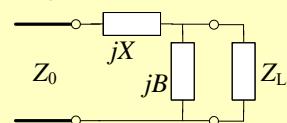z_L is inside the circle $1+jx$, then we use:




$$jb = +j0.29$$

$$jx = +j1.22$$

$$B = b / Z_0 = 0.0029 \text{ S}$$

$$X = (1.22)Z_0 = 122 \Omega$$

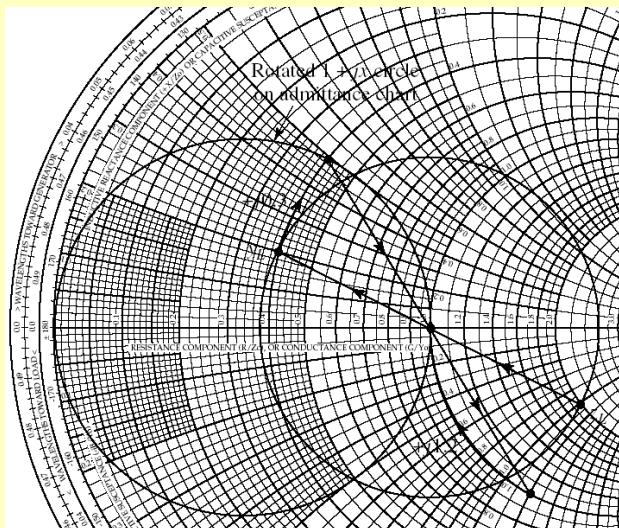

Dr. J. E. Rayas-Sánchez


(D. M. Pozar, Microwave Engineering, Wiley, 2005) 18

Impedance Matching Circuits (Part 1)

Dr. José Ernesto Rayas-Sánchez

April 25, 2020

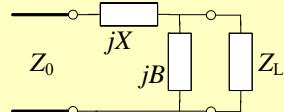Matching with L-Sections – Example 1 (cont.)




$$B = 0.0029 \text{ S}$$

$$X = 122 \Omega$$

$$C_B = \frac{B}{2\pi f} = 0.92 \text{ pF}$$

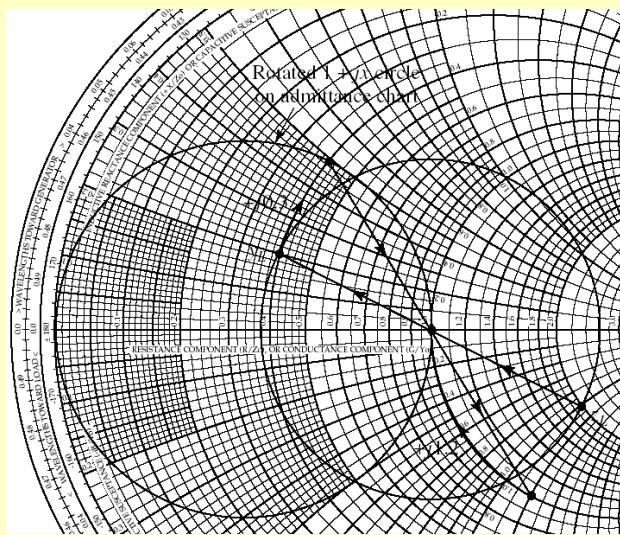
$$L_x = \frac{X}{2\pi f} = 38.8 \text{ nH}$$



Dr. J. E. Rayas-Sánchez

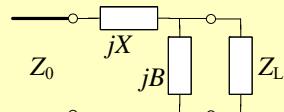(D. M. Pozar, Microwave Engineering, Wiley, 2005) 19

Matching with L-Sections – Example 1 (cont.)




Second solution:

$$jb = -j0.69$$

$$jx = -j1.22$$

$$L_B = \frac{-1}{2\pi f B} = 46.1 \text{ nH}$$
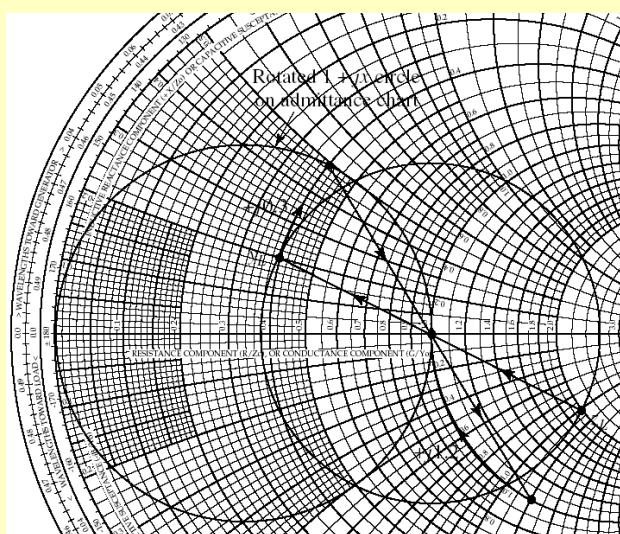
$$C_x = \frac{-1}{2\pi f X} = 2.61 \text{ pF}$$



Dr. J. E. Rayas-Sánchez

(D. M. Pozar, Microwave Engineering, Wiley, 2005) 20



Impedance Matching Circuits (Part 1)

Dr. José Ernesto Rayas-Sánchez

April 25, 2020

Matching with L-Sections – Example 1 (cont.)

Two solutions:

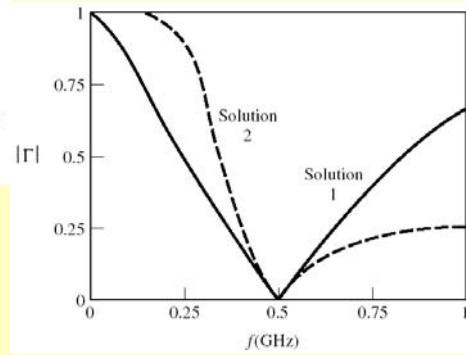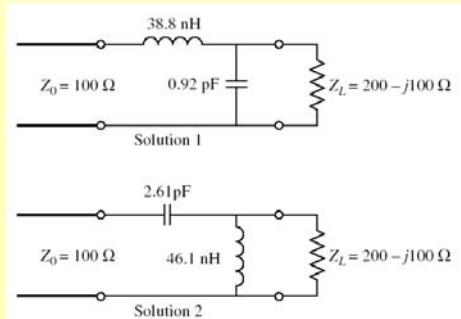


Dr. J. E. Rayas-Sánchez

(D. M. Pozar; *Microwave Engineering*, Wiley, 2005) 21

Matching with L-Sections – Example 1 (cont.)


$$z_L = \frac{Z_L}{Z_0} = 2 - j$$

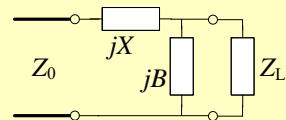z_L is inside the circle
 $1+jx$, then we use:



First solution:
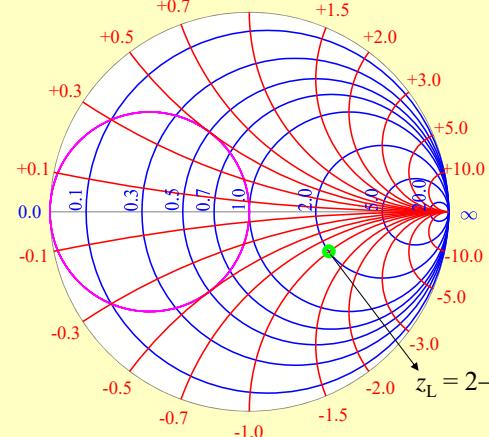
$$\begin{aligned} jb &= +j0.29 \\ jx &= +j1.22 \end{aligned}$$



Dr. J. E. Rayas-Sánchez

22

Impedance Matching Circuits (Part 1)


Dr. José Ernesto Rayas-Sánchez

April 25, 2020

Matching with L-Sections – Example 1 (cont.)


$$z_L = \frac{Z_L}{Z_0} = 2 - j$$

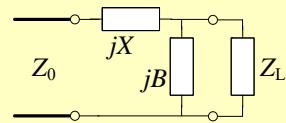z_L is inside the circle
 $1+jx$, then we use:



First solution:

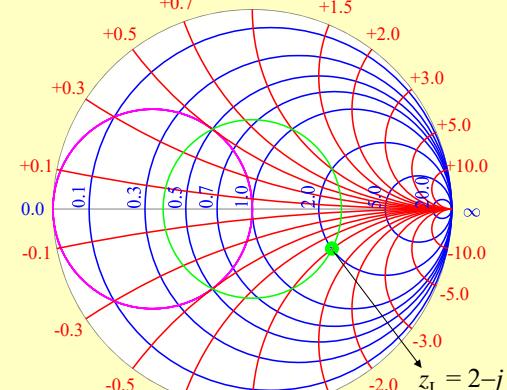
$$\begin{aligned} jb &= +j0.29 \\ jx &= +j1.22 \end{aligned}$$



Matching with L-Sections – Example 1 (cont.)


$$z_L = \frac{Z_L}{Z_0} = 2 - j$$

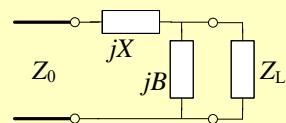z_L is inside the circle
 $1+jx$, then we use:



First solution:
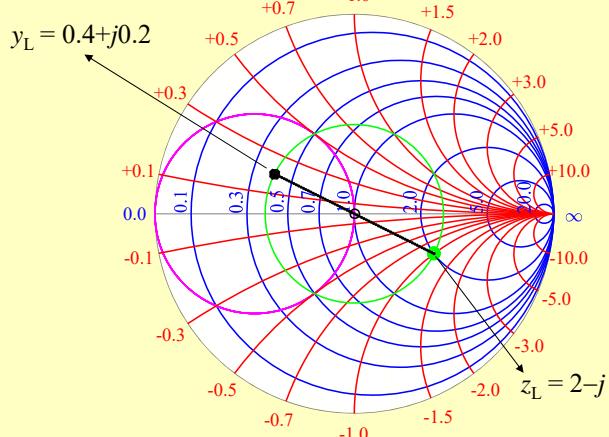
$$\begin{aligned} jb &= +j0.29 \\ jx &= +j1.22 \end{aligned}$$



Impedance Matching Circuits (Part 1)


Dr. José Ernesto Rayas-Sánchez

April 25, 2020

Matching with L-Sections – Example 1 (cont.)


$$z_L = \frac{Z_L}{Z_0} = 2 - j$$

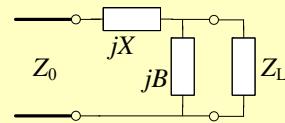z_L is inside the circle $1+jx$, then we use:



First solution:

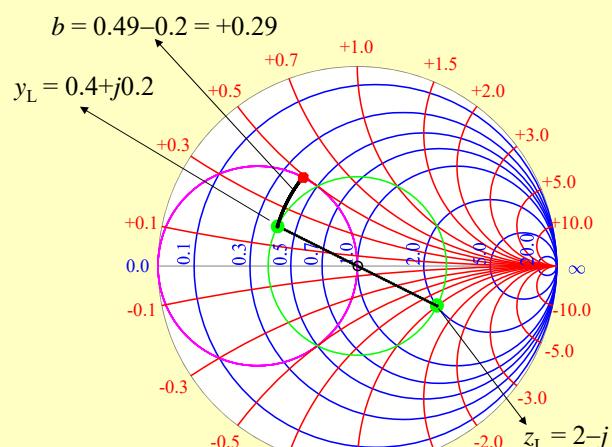
$$\begin{aligned} jb &= +j0.29 \\ jx &= +j1.22 \end{aligned}$$



Matching with L-Sections – Example 1 (cont.)


$$z_L = \frac{Z_L}{Z_0} = 2 - j$$

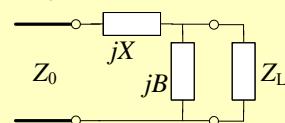z_L is inside the circle $1+jx$, then we use:



First solution:
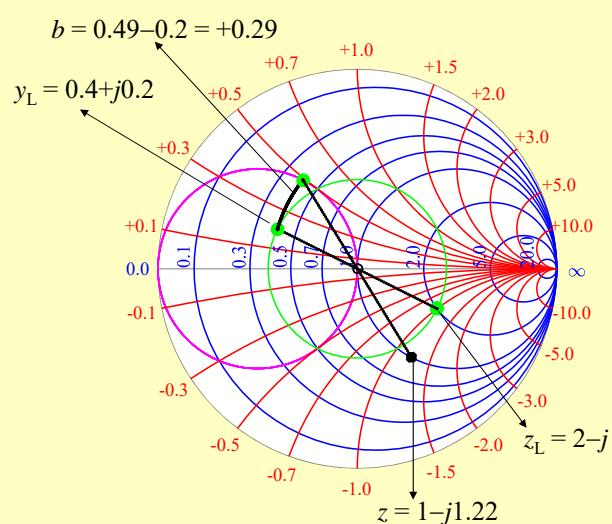
$$\begin{aligned} jb &= +j0.29 \\ jx &= +j1.22 \end{aligned}$$



Impedance Matching Circuits (Part 1)


Dr. José Ernesto Rayas-Sánchez

April 25, 2020

Matching with L-Sections – Example 1 (cont.)


$$z_L = \frac{Z_L}{Z_0} = 2 - j$$

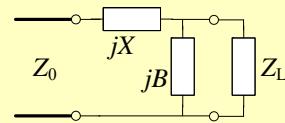z_L is inside the circle $1+jx$, then we use:



First solution:
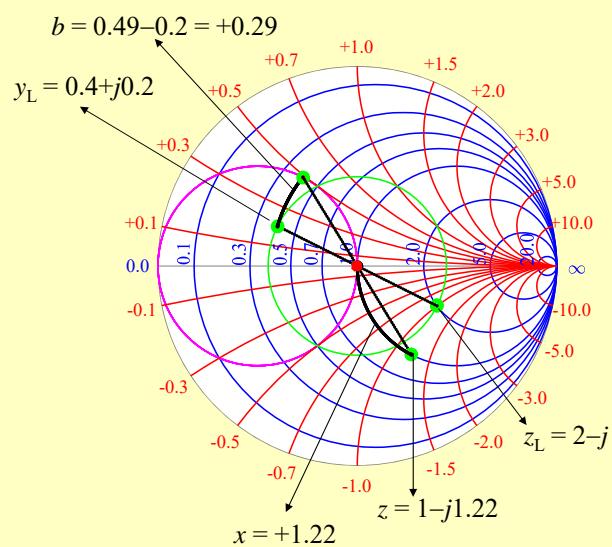
$$\begin{aligned} jb &= +j0.29 \\ jx &= +j1.22 \end{aligned}$$




Dr. J. E. Rayas-Sánchez

27

Matching with L-Sections – Example 1 (cont.)


$$z_L = \frac{Z_L}{Z_0} = 2 - j$$

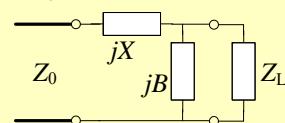z_L is inside the circle $1+jx$, then we use:



Second solution:
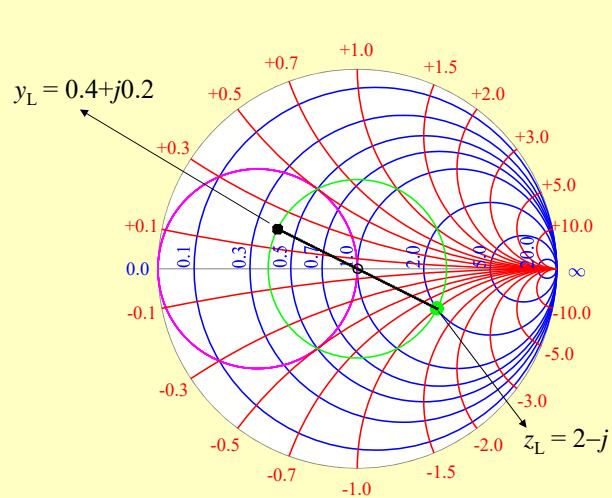
$$\begin{aligned} jb &= -j0.69 \\ jx &= -j1.22 \end{aligned}$$




Dr. J. E. Rayas-Sánchez

28

Matching with L-Sections – Example 1 (cont.)

$$z_L = \frac{Z_L}{Z_0} = 2 - j$$

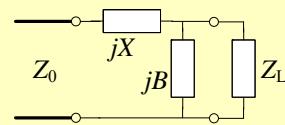
z_L is inside the circle $1+jx$, then we use:



Second solution:

$$jb = -j0.69$$


$$jx = -j1.22$$

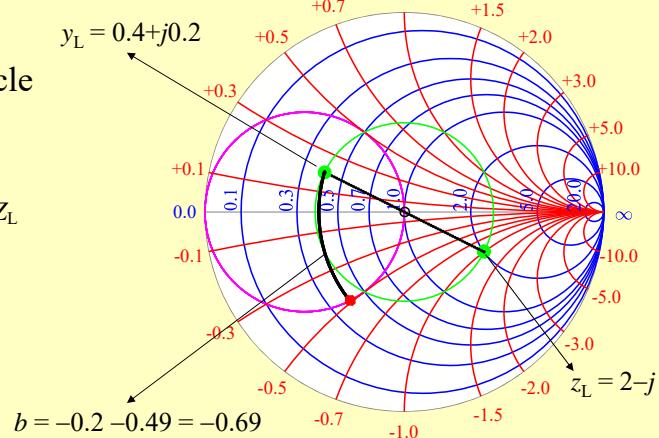

Matching with L-Sections – Example 1 (cont.)

$$z_L = \frac{Z_L}{Z_0} = 2 - j$$

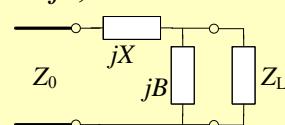
z_L is inside the circle $1+jx$, then we use:



Second solution:

$$jb = -j0.69$$

$$jx = -j1.22$$

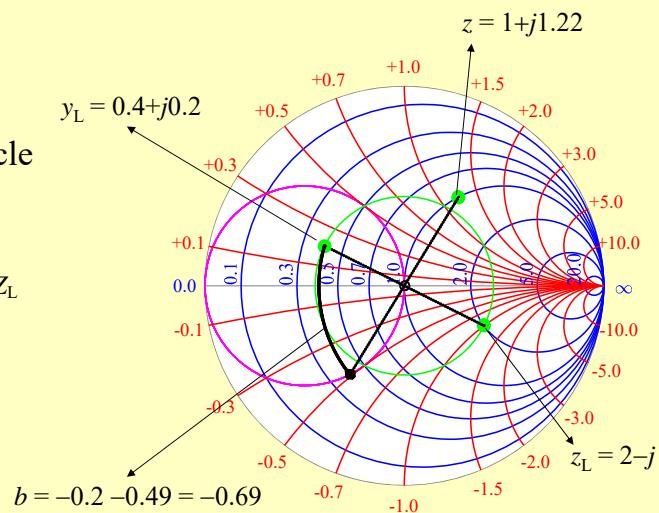

Impedance Matching Circuits (Part 1)


Dr. José Ernesto Rayas-Sánchez

April 25, 2020

Matching with L-Sections – Example 1 (cont.)

$$z_L = \frac{Z_L}{Z_0} = 2 - j$$

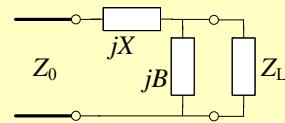z_L is inside the circle $1+jx$, then we use:



Second solution:

$$\begin{aligned} jb &= -j0.69 \\ jx &= -j1.22 \end{aligned}$$

