

Impedance Matching Circuits (Part 4)

Dr. José Ernesto Rayas-Sánchez

April 30, 2020

Impedance Matching Circuits

(Part 4)

Dr. José Ernesto Rayas-Sánchez


1

Outline

- Quarter-wave transformer
- Bandwidth of a quarter-wave transformer
- Multi-sectional transformers

Quarter-Wave Transformer

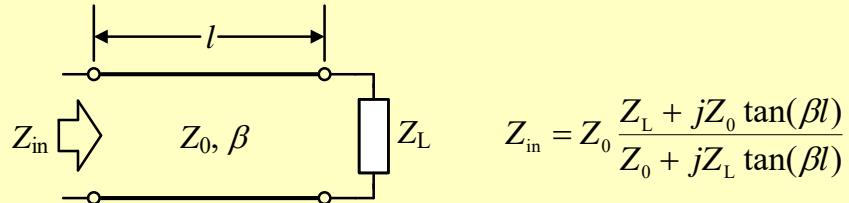- Simple technique for impedance matching
- It can achieve perfect match at a single frequency




$$\text{If } l = \frac{\lambda}{4} \Rightarrow Z_{in} = \frac{Z_0^2}{Z_L}$$

Dr. J. E. Rayas-Sánchez

3

Quarter-Wave Transformer (cont.)

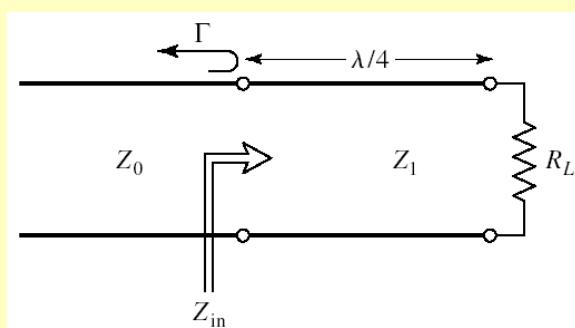

To make $\Gamma = 0$,

$$Z_1 = \sqrt{R_L Z_0}$$

Z_1 must be the geometric mean of Z_0 and R_L

Dr. J. E. Rayas-Sánchez


4

Impedance Matching Circuits (Part 4)

Dr. José Ernesto Rayas-Sánchez

April 30, 2020

Quarter-Wave Transformer - Example

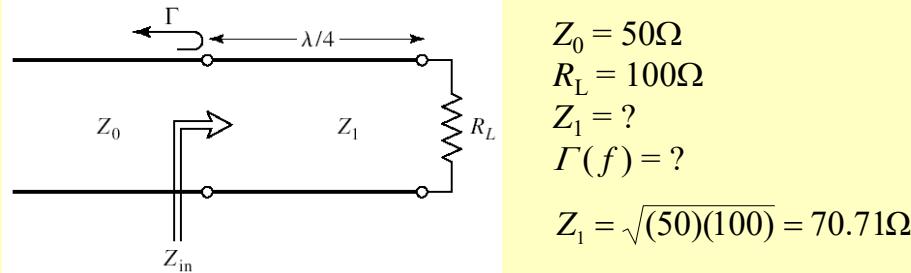

$\Gamma = 0$ only at the frequencies at which the electrical length of the matching section is 90° , 270° , ...


$$\text{Since } \Gamma_l = \frac{Z_{in}(l) - Z_0}{Z_{in}(l) + Z_0} \text{ and } Z_{in}(l) = Z_0 \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)}$$

$$\beta l = \left(\frac{2\pi}{\lambda} \right) \left(\frac{\lambda_0}{4} \right) = \left(\frac{2\pi f}{v_p} \right) \left(\frac{v_p}{4f_0} \right) = \frac{\pi}{2} \frac{f}{f_0}$$


Dr. J. E. Rayas-Sánchez

5

Quarter-Wave Transformer - Example

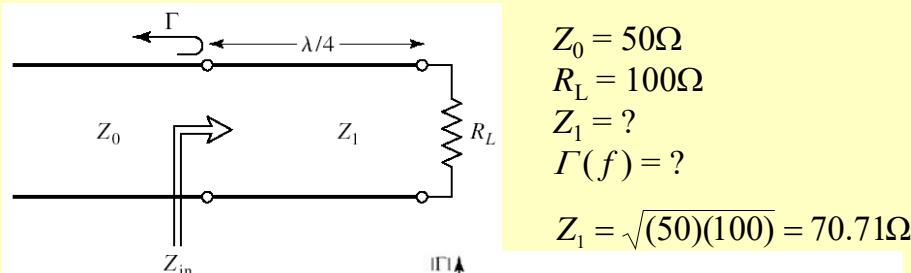
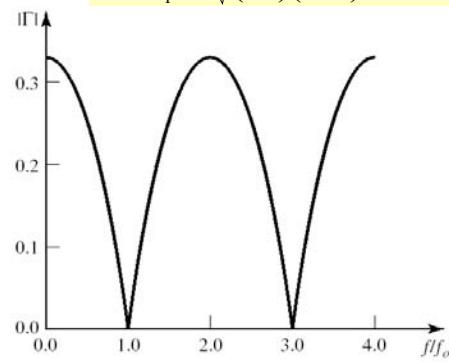
$$\beta l = \frac{\pi}{2} \frac{f}{f_0}$$



Dr. J. E. Rayas-Sánchez



6

Impedance Matching Circuits (Part 4)

Dr. José Ernesto Rayas-Sánchez

April 30, 2020


Quarter-Wave Transformer - Bandwidth

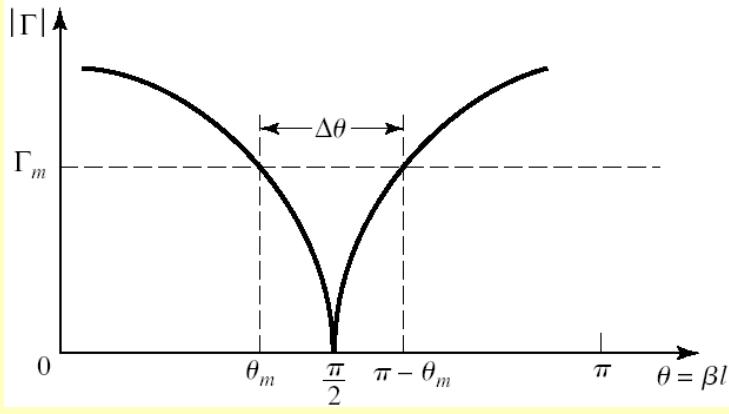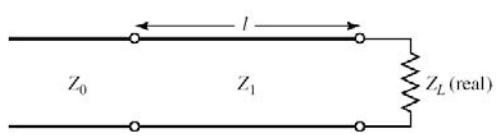

Dr. J. E. Rayas-Sánchez

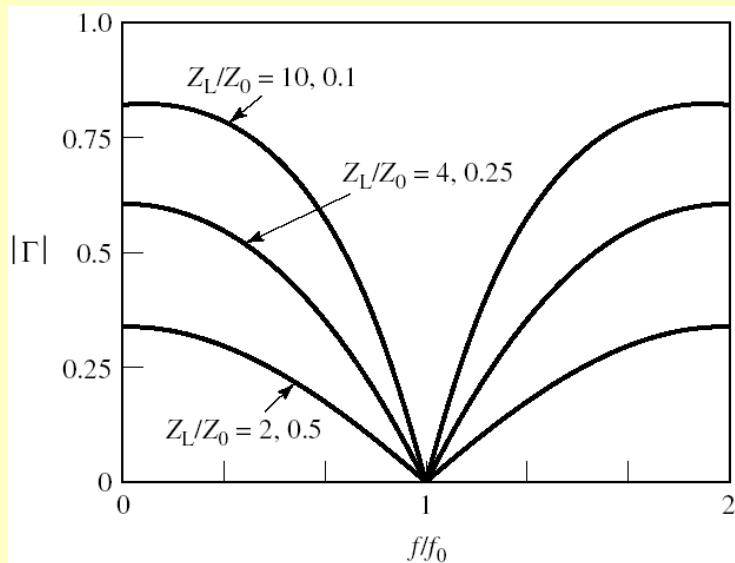(D. M. Pozar, *Microwave Engineering*, Wiley, 2005) 7

Quarter-Wave Transformer - Bandwidth (cont.)



Dr. J. E. Rayas-Sánchez


(D. M. Pozar, *Microwave Engineering*, Wiley, 2005) 8

Impedance Matching Circuits (Part 4)

Dr. José Ernesto Rayas-Sánchez

April 30, 2020

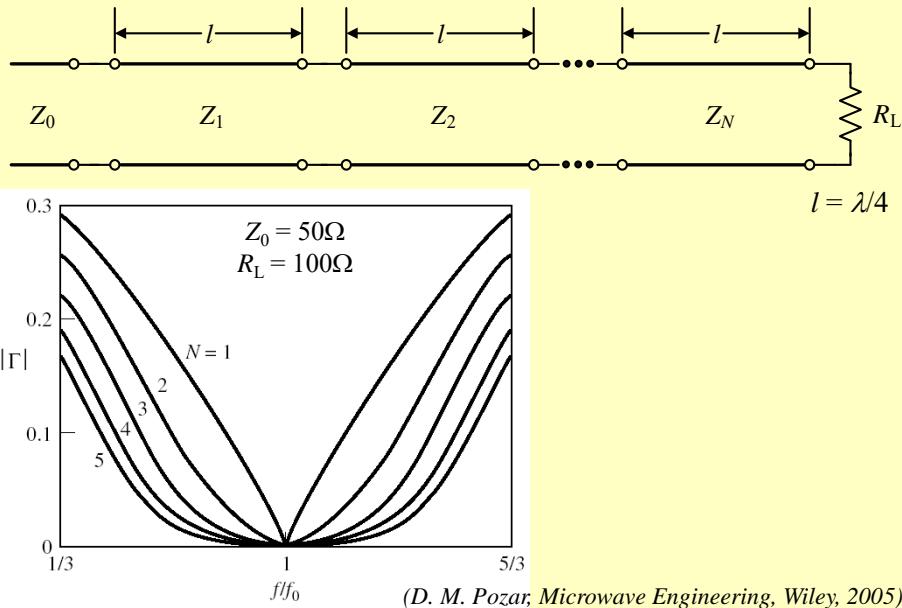Multi-Section Binomial Transformer Matching



Dr

(D. M. Pozar, Microwave Engineering, Wiley, 2005)

Multi-Section Transformer - Binomial Coeff.

Z_L/Z_0	$N = 2$		$N = 3$			$N = 4$					
	Z_1/Z_0	Z_2/Z_0	Z_1/Z_0	Z_2/Z_0	Z_3/Z_0	Z_1/Z_0	Z_2/Z_0	Z_3/Z_0	Z_4/Z_0		
1.0	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000		
1.5	1.1067	1.3554	1.0520	1.2247	1.4259	1.0257	1.1351	1.3215	1.4624		
2.0	1.1892	1.6818	1.0907	1.4142	1.8337	1.0444	1.2421	1.6102	1.9150		
3.0	1.3161	2.2795	1.1479	1.7321	2.6135	1.0718	1.4105	2.1269	2.7990		
4.0	1.4142	2.8285	1.1907	2.0000	3.3594	1.0919	1.5442	2.5903	3.6633		
6.0	1.5651	3.8336	1.2544	2.4495	4.7832	1.1215	1.7553	3.4182	5.3500		
8.0	1.6818	4.7568	1.3022	2.8284	6.1434	1.1436	1.9232	4.1597	6.9955		
10.0	1.7783	5.6233	1.3409	3.1623	7.4577	1.1613	2.0651	4.8424	8.6110		
Z_L/Z_0	$N = 5$					$N = 6$					
	Z_1/Z_0	Z_2/Z_0	Z_3/Z_0	Z_4/Z_0	Z_5/Z_0	Z_1/Z_0	Z_2/Z_0	Z_3/Z_0	Z_4/Z_0	Z_5/Z_0	Z_6/Z_0
1.0	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000
1.5	1.0128	1.0790	1.2247	1.3902	1.4810	1.0064	1.0454	1.1496	1.3048	1.4349	1.4905
2.0	1.0220	1.1391	1.4142	1.7558	1.9569	1.0110	1.0790	1.2693	1.5757	1.8536	1.9782
3.0	1.0354	1.2300	1.7321	2.4390	2.8974	1.0176	1.1288	1.4599	2.0549	2.6577	2.9481
4.0	1.0452	1.2995	2.0000	3.0781	3.8270	1.0225	1.1661	1.6129	2.4800	3.4302	3.9120
6.0	1.0596	1.4055	2.4495	4.2689	5.6625	1.0296	1.2219	1.8573	3.2305	4.9104	5.8275
8.0	1.0703	1.4870	2.8284	5.3800	7.4745	1.0349	1.2640	2.0539	3.8950	6.3291	7.7302
10.0	1.0789	1.5541	3.1623	6.4346	9.2687	1.0392	1.2982	2.2215	4.5015	7.7030	9.6228

Dr. J. E. Rayas-Sánchez

(D. M. Pozar, Microwave Engineering, Wiley, 2005)

Muti-Section Transformer - Binomial (cont.)

- Previous tables provide line impedances to achieve a binomial (Butterworth) response for the following cases:



$$N = 2, 3, \dots, 6$$

$$T = Z_L/Z_0 = 1, 1.5, 2, 3, 4, 6, 8, \text{ and } 10$$

- If $Z_L < Z_0$, the same tables can be used by using the row that corresponds to $T = Z_0/Z_L$, and making the coefficient of section k equal to Z_0/Z_k
- The fractional bandwidth at Γ_m is given by

$$\frac{\Delta f}{f_0} = 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{1}{2} \left(\frac{\Gamma_m}{A} \right)^{1/N} \right] \quad A = 2^{-(N+1)} |\ln(T)|$$

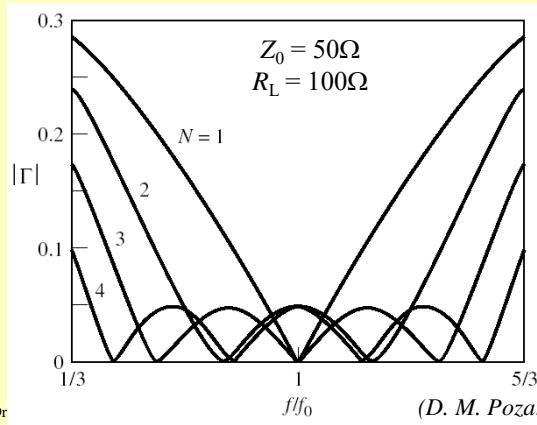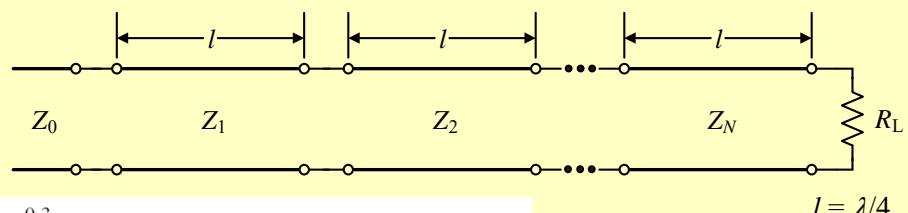Muti-Section Chebyshev Transformer Matching



Impedance Matching Circuits (Part 4)

Dr. José Ernesto Rayas-Sánchez

April 30, 2020

Muti-Section Transformer - Chebyshev Coeff.

Z_L/Z_0	$N = 2$				$N = 3$			
	$\Gamma_m = 0.05$		$\Gamma_m = 0.20$		$\Gamma_m = 0.05$		$\Gamma_m = 0.20$	
	Z_1/Z_0	Z_2/Z_0	Z_1/Z_0	Z_2/Z_0	Z_1/Z_0	Z_2/Z_0	Z_3/Z_0	Z_1/Z_0
1.0	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000
1.5	1.1347	1.3219	1.2247	1.2247	1.1029	1.2247	1.3601	1.2247
2.0	1.2193	1.6402	1.3161	1.5197	1.1475	1.4142	1.7429	1.2855
3.0	1.3494	2.2232	1.4565	2.0598	1.2171	1.7321	2.4649	1.3743
4.0	1.4500	2.7585	1.5651	2.5558	1.2662	2.0000	3.1591	1.4333
6.0	1.6047	3.7389	1.7321	3.4641	1.3383	2.4495	4.4833	1.5193
8.0	1.7244	4.6393	1.8612	4.2983	1.3944	2.8284	5.7372	1.5766
10.0	1.8233	5.4845	1.9680	5.0813	1.4385	3.1623	6.9517	1.6415
$N = 4$								
Z_L/Z_0	$\Gamma_m = 0.05$				$\Gamma_m = 0.20$			
	Z_1/Z_0	Z_2/Z_0	Z_3/Z_0	Z_4/Z_0	Z_1/Z_0	Z_2/Z_0	Z_3/Z_0	Z_4/Z_0
1.0	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000
1.5	1.0892	1.1742	1.2775	1.3772	1.2247	1.2247	1.2247	1.2247
2.0	1.1201	1.2979	1.5409	1.7855	1.2727	1.3634	1.4669	1.5715
3.0	1.1586	1.4876	2.0167	2.5893	1.4879	1.5819	1.8965	2.0163
4.0	1.1906	1.6414	2.4369	3.3597	1.3692	1.7490	2.2870	2.9214
6.0	1.2290	1.8773	3.1961	4.8820	1.4415	2.0231	2.9657	4.1623
8.0	1.2583	2.0657	3.8728	6.3578	1.4914	2.2428	3.5670	5.3641
10.0	1.2832	2.2268	4.4907	7.7930	1.5163	2.4210	4.1305	6.5950

Dr. J. E. Rayas-Sánchez

(D. M. Pozar, Microwave Engineering, Wiley, 2005) 13

Muti-Section Transformer - Binomial Example

- Design a four-section Butterworth impedance transformer to match at 5 GHz a load impedance $Z_L = 150 \Omega$ to a transmission line with characteristic impedance $Z_0 = 50 \Omega$
- Calculate the theoretical fractional bandwidth for a maximum reflection of -40 dB
- Calculate the corresponding lengths of the four sections of the impedance transformer, assuming an effective dielectric constant $\epsilon_e = 3.38$

Dr. J. E. Rayas-Sánchez

14