

# The Smith Chart

(Part 1)

**Dr. José Ernesto Rayas-Sánchez**

1

## Outline

---

- Origins of the Smith Chart
- Mathematical basis of the Smith Chart
- Smith Chart interpretation
- Basic Smith Chart applications
  - Calculating  $\Gamma$ ,  $RL$ ,  $SWR$
  - Calculating  $\Gamma_l$  and  $Z_{in}$
  - Circles of  $SWR$ ,  $V_{max}$  and  $V_{min}$


## The Smith Chart

- Developed in 1939 by P. H. Smith at Bell Labs
- Very useful for visualizing transmission line phenomena and impedance matching problems
- It is part of most current CAD tools and modern measurement equipments
- It is essentially a plot of  $\Gamma$  in polar coordinates
- Any impedance can be mapped in the  $\Gamma$  plane

Dr. J. E. Rayas-Sánchez

3

## The Smith Chart (cont.)

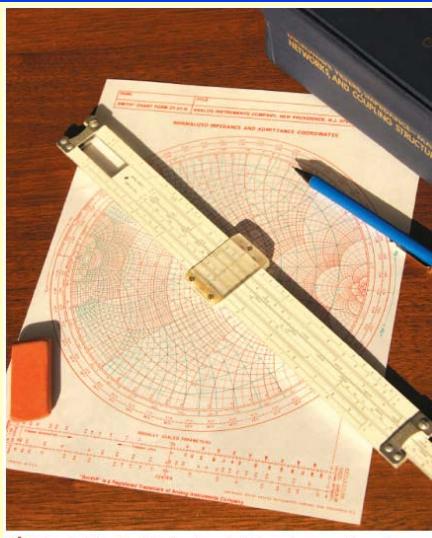


**Figure 1.** The Smith chart and slide rule were the primary microwave design tools in the 1970s and before.

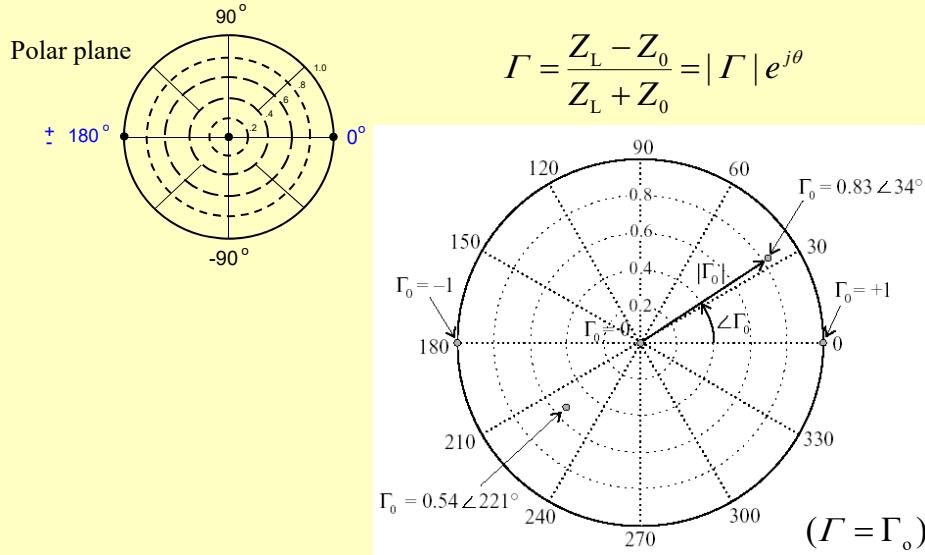Dr. J. E. Rayas-Sánchez

(J. Rautio, IEEE Microwave Magazine, 2007) 4

## The Smith Chart (cont.)



Dr. J. E. Rayas-Sánchez

(R. Ludwig and P. Bretschko, RF Circuit Design, Prentice Hall, 2000) 5

## The Smith Chart (cont.)

$$\Gamma = \frac{Z - Z_0}{Z + Z_0} = |\Gamma| e^{j\theta}$$

Normalizing  $Z$  w.r.t  $Z_o$

$$\frac{z-1}{z+1} = |\Gamma| e^{j\theta} \quad \text{where} \quad z = \frac{Z}{Z_o}$$

$$z = \frac{1 + |\Gamma| e^{j\theta}}{1 - |\Gamma| e^{j\theta}}$$

$$r + jx = \frac{(1 + \Gamma_r) + j\Gamma_i}{(1 - \Gamma_r) - j\Gamma_i}$$

Solving for  $r$  and  $x$

$$r = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

$$x = \frac{2\Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

Rearranging

$$\left( \Gamma_r - \frac{r}{1+r} \right)^2 + \Gamma_i^2 = \left( \frac{1}{1+r} \right)^2$$


$$(\Gamma_r - 1)^2 + \left( \Gamma_i - \frac{1}{x} \right)^2 = \left( \frac{1}{x} \right)^2$$

Dr. J. E. Rayas-Sánchez

6
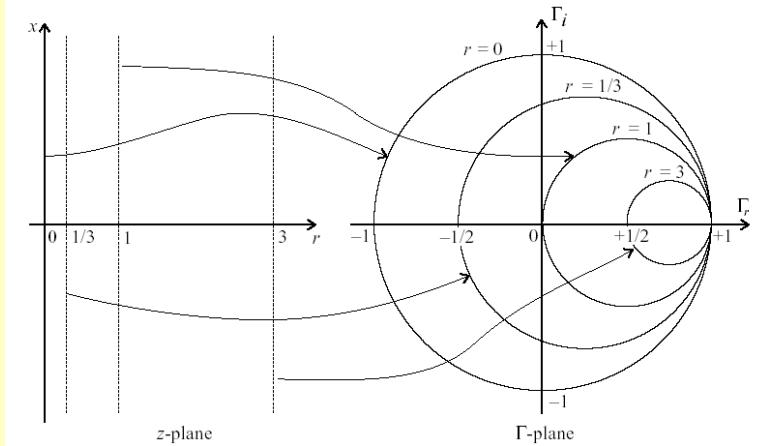
## The Smith Chart – Circles of Constant $r$

$$\left( \Gamma_r - \frac{r}{1+r} \right)^2 + \Gamma_i^2 = \left( \frac{1}{1+r} \right)^2$$




Dr. J. E. Rayas-Sánchez

(R. Ludwig and P. Bretschko, RF Circuit Design, Prentice Hall, 2000) 7
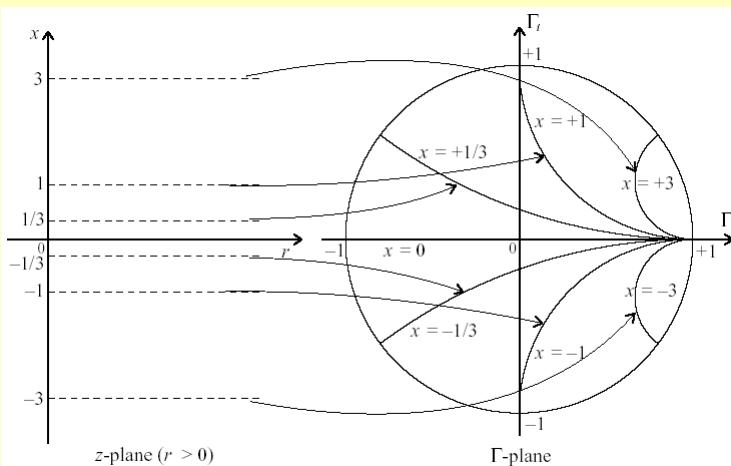
## The Smith Chart – Circles of Constant $x$


$$(\Gamma_r - 1)^2 + \left( \Gamma_i - \frac{1}{x} \right)^2 = \left( \frac{1}{x} \right)^2$$



Dr. J. E. Rayas-Sánchez

(R. Ludwig and P. Bretschko, RF Circuit Design, Prentice Hall, 2000) 8

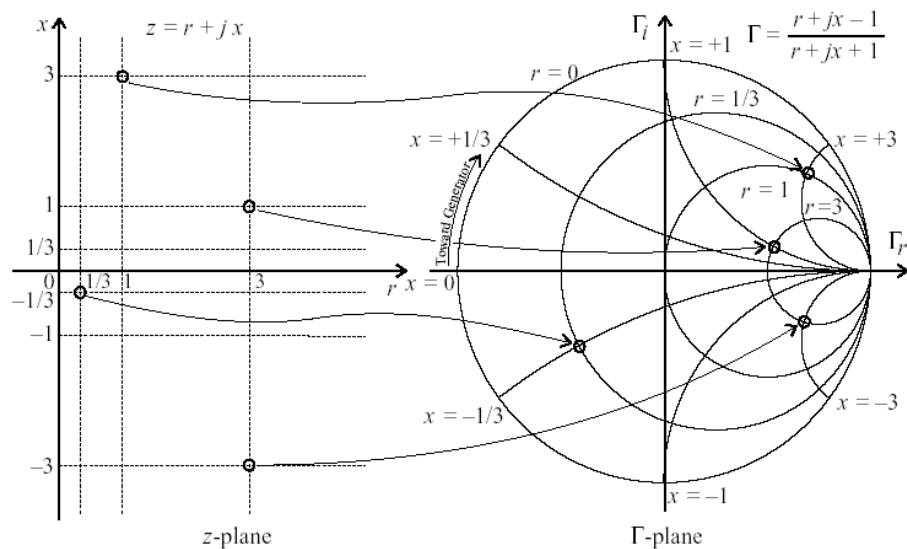
## The Smith Chart – Combining both Circles



Dr. J. E. Rayas-Sánchez

(R. Ludwig and P. Bretschko, RF Circuit Design, Prentice Hall, 2000) ,


## The Smith Chart – Interpretation

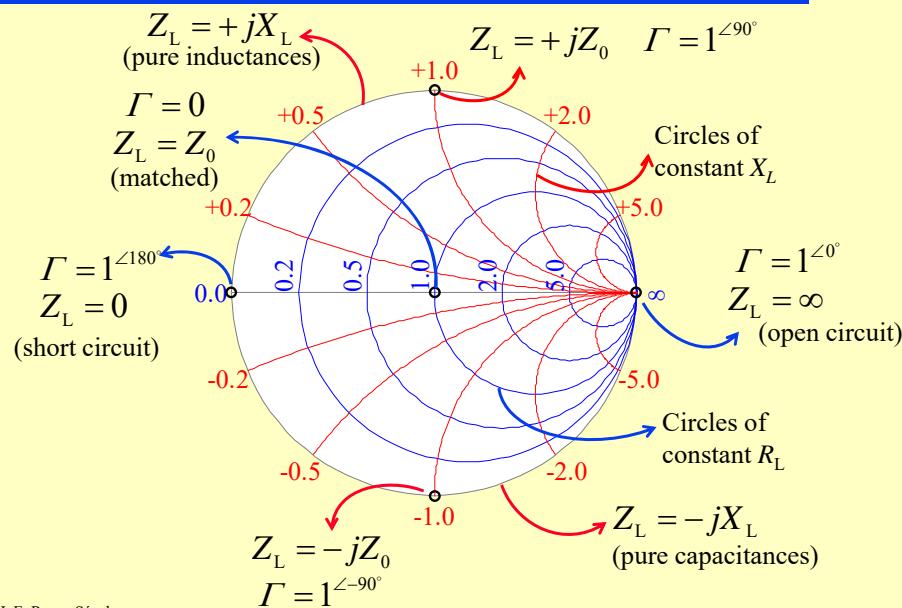

Dr. J. E. Rayas-Sánchez

10


## Practical Smith Chart

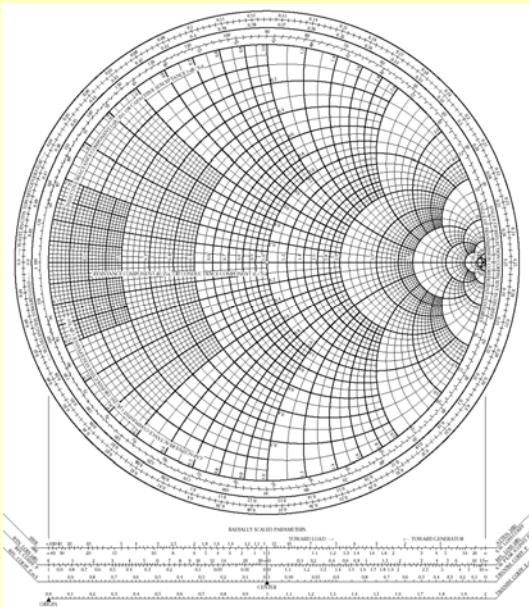

Dr. J. E. Rayas-Sánchez

11

## Practical Smith Chart (cont.)

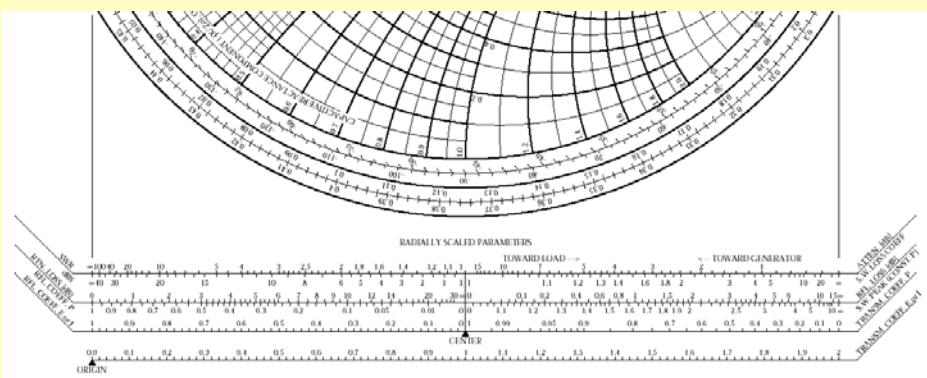

Dr. J. E. Rayas-Sánchez

12

## Smith Chart – Calculating $\Gamma$ , $RL$ , $SWR$

Example:

$$Z_0 = 50 \Omega$$


$$Z_L = 25 + j75 \Omega$$

$$\Gamma = ?$$

$$RL = ?$$

$$SWR = ?$$

$$z_L = 0.5 + j1.5$$

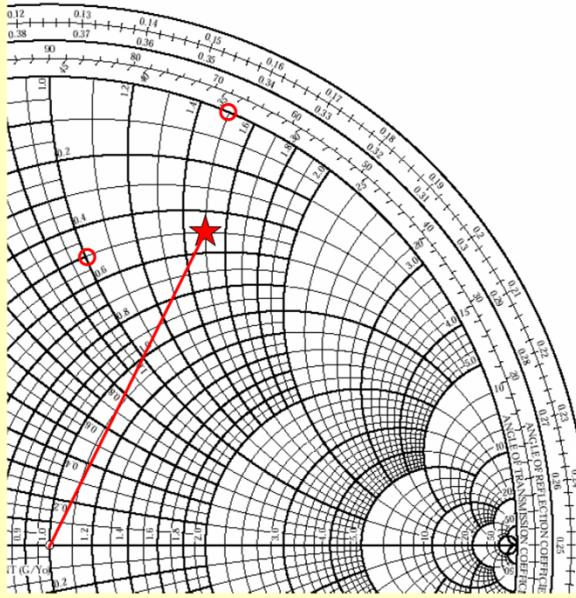

Dr. J. E. Rayas-Sánchez

13

## Smith Chart – Calculating $\Gamma$ , $RL$ , $SWR$ (cont.)


Example:

$$Z_0 = 50 \Omega$$

$$Z_L = 25 + j75 \Omega$$

$$z_L = 0.5 + j1.5$$

$$\Gamma = |\Gamma| e^{j\theta} = |\Gamma| e^{j63.4^\circ}$$

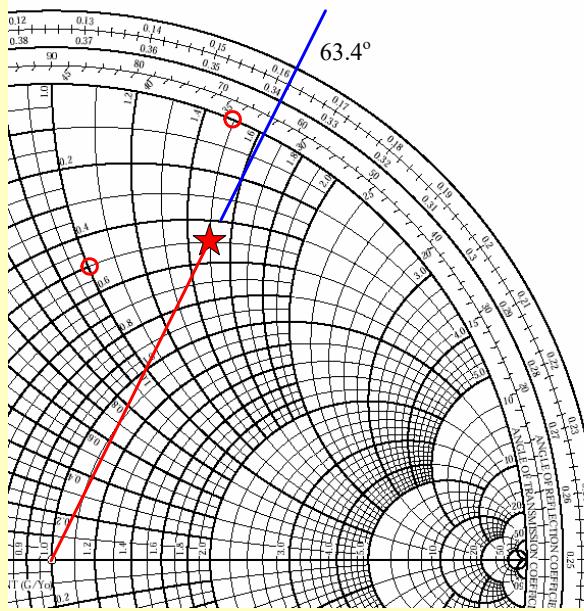

Dr. J. E. Rayas-Sánchez

14

## Smith Chart – Calculating $\Gamma$ , $RL$ , $SWR$ (cont.)


Example:

$$Z_0 = 50 \Omega$$

$$Z_L = 25 + j75 \Omega$$

$$z_L = 0.5 + j1.5$$

$$\Gamma = |\Gamma| e^{j\theta} = |z_L - Z_0| / (z_L + Z_0)$$

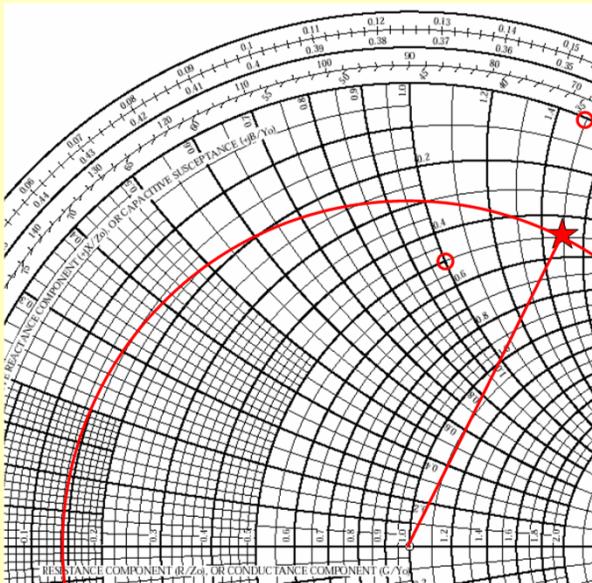

Dr. J. E. Rayas-Sánchez

15

## Smith Chart – Calculating $\Gamma$ , $RL$ , $SWR$ (cont.)

Example:

$$Z_0 = 50 \Omega$$



$$Z_L = 25 + j75 \Omega$$

$$z_L = 0.5 + j1.5$$

$$SWR \approx 7$$

$$RL \approx 2.5 \text{ dB}$$

$$\Gamma \approx 0.75 e^{j63.4^\circ}$$

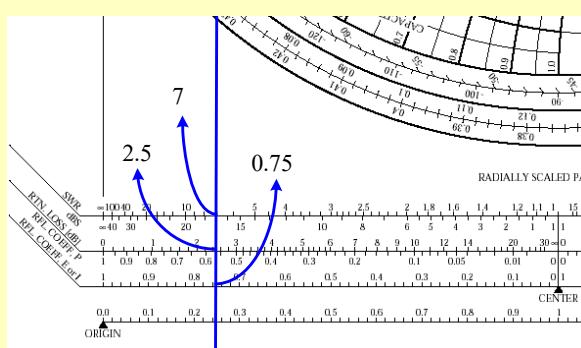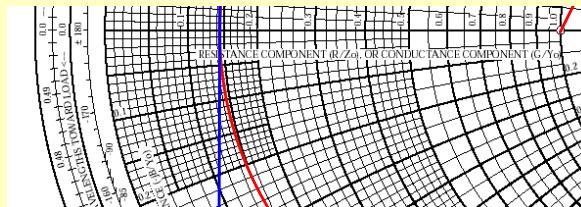

Dr. J. E. Rayas-Sánchez

16

## Smith Chart – Circles of SWR

Example:

$$Z_0 = 50 \Omega$$


$$Z_L = 25 + j75 \Omega$$

$$z_L = 0.5 + j1.5$$

$$SWR \approx 7$$

$$RL \approx 2.5 \text{ dB}$$

$$\Gamma \approx 0.75 e^{j63.4^\circ}$$

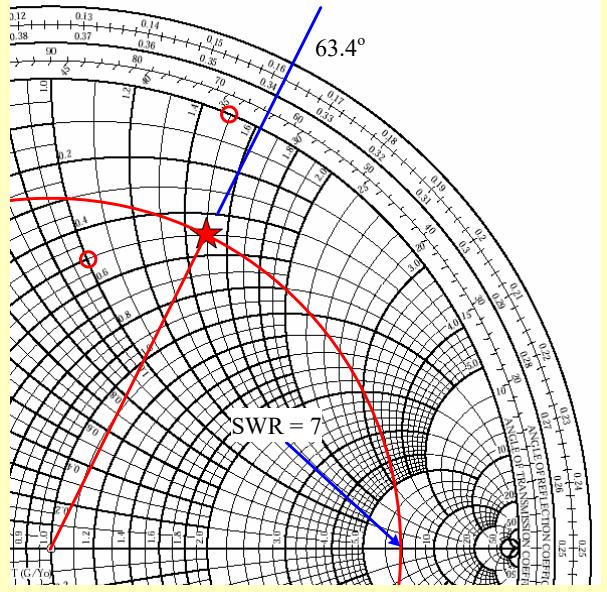

Dr. J. E. Rayas-Sánchez

17

## Smith Chart – Circles of SWR (cont.)

Examples:


$$Z_0 = 50 \Omega$$

$$\text{a) } Z_L = 50 \Omega$$

$$\text{b) } Z_L = 48.5 \Omega$$

$$\text{c) } Z_L = 75 + j25 \Omega$$



$$\text{d) } Z_L = 10 - j5 \Omega$$

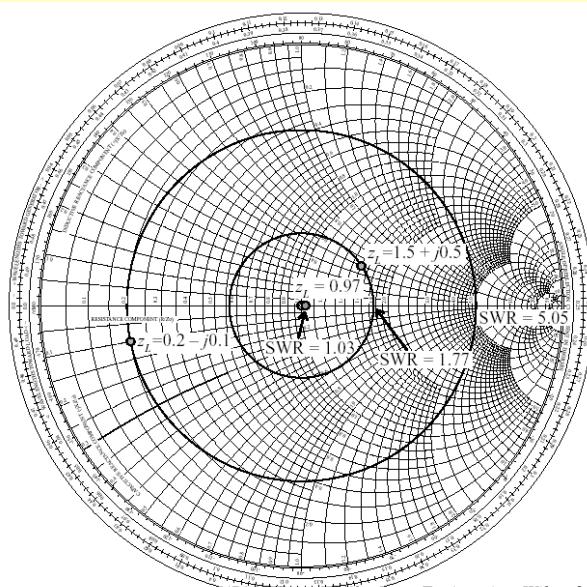

(D. M. Pozar, Microwave Engineering, Wiley, 2005) 18

Dr. J. E. Rayas-Sánchez

## Smith Chart – Calculating $\Gamma_l$

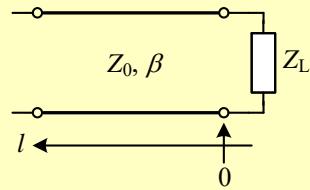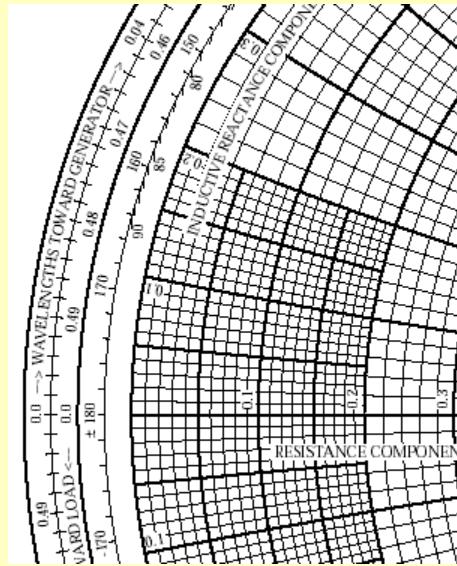

$$\Gamma_l(l) = \frac{V_0^- e^{-j\beta l}}{V_0^+ e^{j\beta l}} = \frac{V_0^-}{V_0^+} e^{-2j\beta l} = \Gamma e^{-2j\beta l}$$

$$\text{Since } \beta = \frac{2\pi}{\lambda}$$



$$\Gamma_l(l) = \Gamma e^{-2j\frac{2\pi}{\lambda}l} \quad (\text{Period} = \lambda/2)$$

$\frac{l}{\lambda}$  is the length in wavelengths

Dr. J. E. Rayas-Sánchez

19

## Smith Chart – Calculating $Z_{in}$

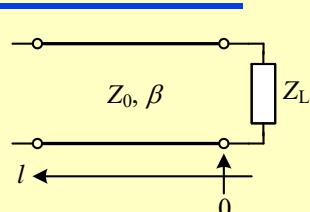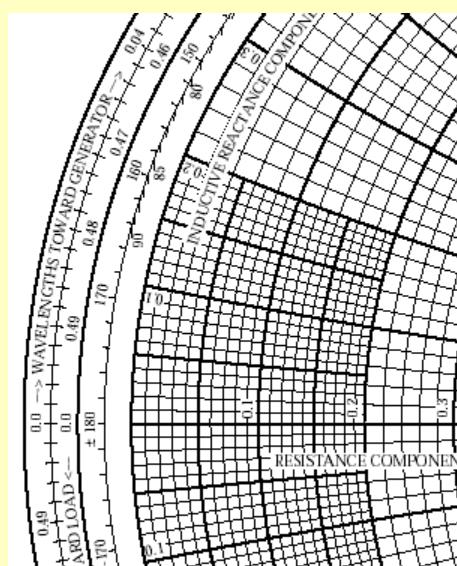

$$\Gamma_l(l) = \Gamma e^{-2j\frac{2\pi}{\lambda}l}$$

$\frac{l}{\lambda}$  is the length in wavelengths

$$\Gamma_l = \frac{Z_{in}(l) - Z_0}{Z_{in}(l) + Z_0}$$

Dr. J. E. Rayas-Sánchez

20

## Smith Chart – Calculating $\Gamma_l$ and $Z_{in}$

Example:

$$Z_0 = 50 \Omega$$

$$Z_L = 25 + j75 \Omega$$

$$l = 1 \text{ cm}$$

$$f = 1 \text{ GHz}$$

$$\epsilon_e = 4$$


$$\Gamma_l = ?$$

$$Z_{in} = ?$$

$$z_L = 0.5 + j1.5$$

$$\Gamma \approx 0.75 e^{j63.4^\circ}$$

Dr. J. E. Rayas-Sánchez

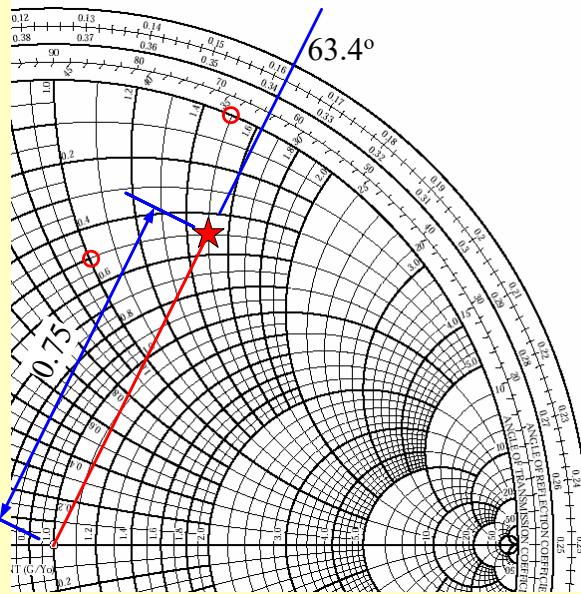

21

## Smith Chart – Calculating $\Gamma_l$ and $Z_{in}$ (cont.)

Example:

$$Z_0 = 50 \Omega$$

$$Z_L = 25 + j75 \Omega$$

$$l = 1 \text{ cm}$$

$$f = 1 \text{ GHz}$$

$$\epsilon_e = 4$$


$$\Gamma_l = ?$$

$$Z_{in} = ?$$

$$\lambda = \frac{v_p}{f} = \frac{c}{f\sqrt{\epsilon_e}}$$

$$\lambda = \frac{0.3 \text{ Gm/s}}{1 \text{ GHz} \sqrt{4}} = 15 \text{ cm}$$

Dr. J. E. Rayas-Sánchez

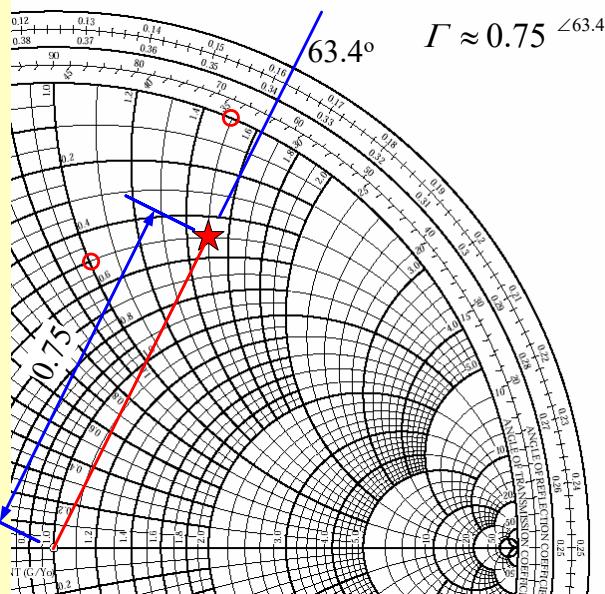

22

## Smith Chart – Calculating $\Gamma_l$ and $Z_{in}$ (cont.)

Example:

$$Z_0 = 50 \Omega$$

$$Z_L = 25 + j75 \Omega$$

$$l = 1 \text{ cm}$$

$$f = 1 \text{ GHz}$$


$$\varepsilon_e = 4$$

$$\Gamma_l = ?$$

$$Z_{in} = ?$$

$$\frac{l}{\lambda} = \frac{1 \text{ cm}}{15 \text{ cm}} = 0.067$$

$$0.162 + 0.067 = 0.229$$

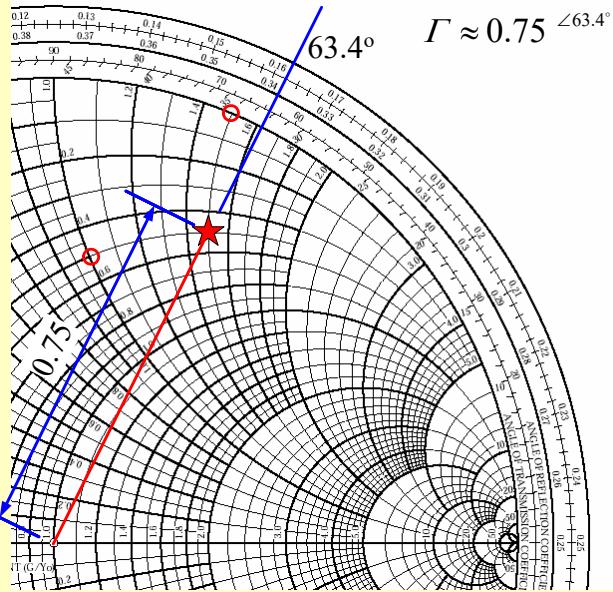

Dr. J. E. Rayas-Sánchez

23

## Smith Chart – Calculating $\Gamma_l$ and $Z_{in}$ (cont.)

Example:

$$Z_0 = 50 \Omega$$

$$Z_L = 25 + j75 \Omega$$

$$l = 1 \text{ cm}$$

$$f = 1 \text{ GHz}$$


$$\varepsilon_e = 4$$

$$\Gamma_l = ?$$

$$Z_{in} = ?$$

$$\frac{l}{\lambda} = \frac{1 \text{ cm}}{15 \text{ cm}} = 0.067$$

$$0.162 + 0.067 = 0.229$$

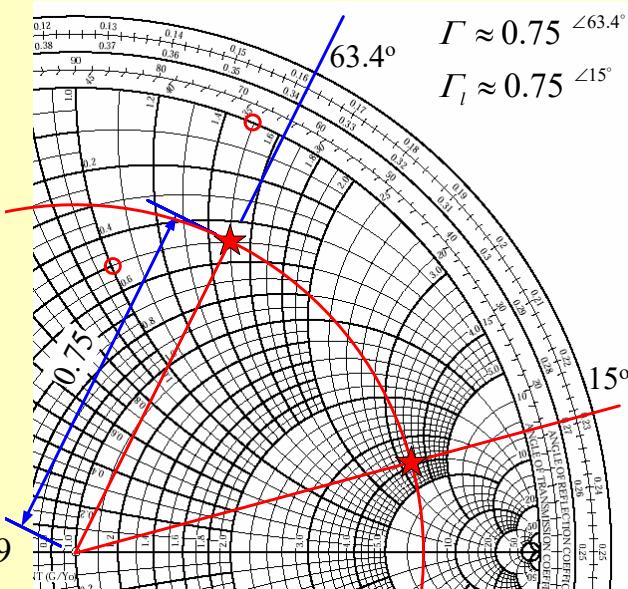

Dr. J. E. Rayas-Sánchez

24

## Smith Chart – Calculating $\Gamma_l$ and $Z_{in}$ (cont.)

Example:

$$Z_0 = 50 \Omega$$

$$Z_L = 25 + j75 \Omega$$

$$l = 1 \text{ cm}$$

$$f = 1 \text{ GHz}$$

$$\epsilon_e = 4$$

$$\Gamma_l = ?$$


$$Z_{in} = ?$$

$$z_{in} = 3.8 + j3.4$$

$$Z_{in} = 50(3.8 + j3.4) \Omega$$

$$Z_{in} \approx 190 + j170 \Omega$$

Dr. J. E. Rayas-Sánchez

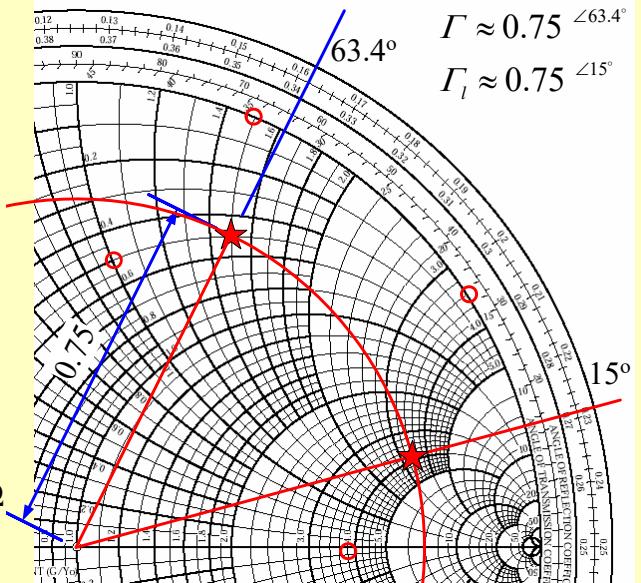

25

## Smith Chart – Circles of SWR, $V_{max}$ and $V_{min}$

Since  $|V(l)| = |V_0^+| |1 + |\Gamma| e^{+j(\theta - 2\beta l)}|$

where  $\Gamma = |\Gamma| e^{j\theta}$

We can locate the positions of  $V_{max}$  and  $V_{min}$  along the line

Example:

$$Z_0 = 50 \Omega$$


$$Z_L = 60 + j40 \Omega$$

$$z_L = 1.2 + j0.8 \Omega$$

$$SWR \approx 2.1$$

$$WL_{max} = 0.25\lambda - 0.172\lambda$$

$$WL_{max} = 0.078\lambda$$

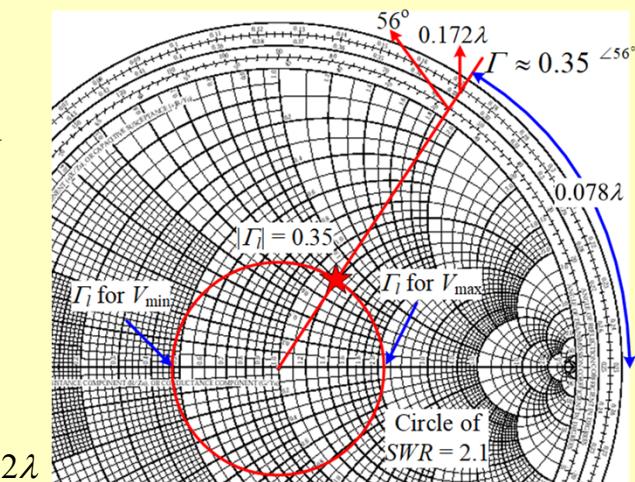

26