

Frequency-Domain Analysis of Transmission Line Circuits

(Part 1)


Dr. José Ernesto Rayas-Sánchez

1

Outline

- N -port networks
- Impedance matrix representation (Z-parameters)
- Admittance matrix representation (Y-parameters)
- Hybrid matrix representation (H-parameters)
- Scattering matrix representation (S-parameters)
- Meaning of the S-parameters
- Conversion between Y-Z-S parameters
- Properties of the S matrix


An N -port High-Speed Network

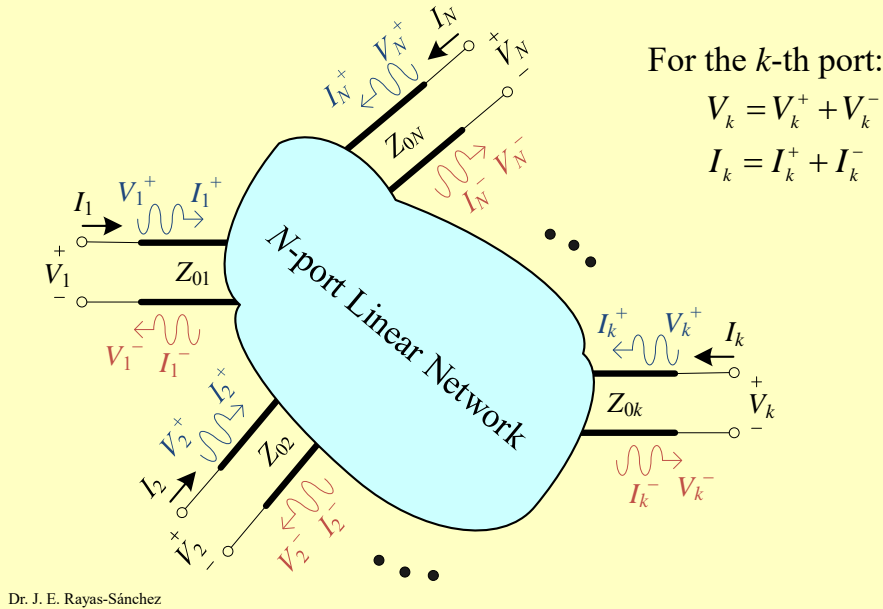

Dr. J. E. Rayas-Sánchez

3

Examples of N -port Networks

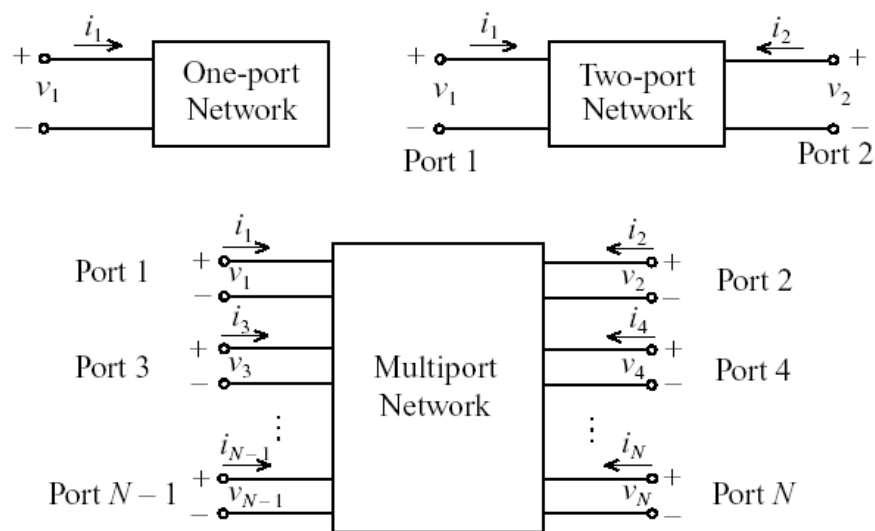

Dr. J. E. Rayas-Sánchez

(R. Ludwig and P. Bretchko, *RF Circuit Design*, Prentice Hall, 2000)

4

Impedance Matrix Representation (\mathbf{Z})


$$\mathbf{V} = \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix} \quad \mathbf{I} = \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix} \quad \mathbf{V} = \mathbf{Z}\mathbf{I}$$

$$\mathbf{Z} = \begin{bmatrix} Z_{11} & Z_{12} & \cdots & Z_{1N} \\ Z_{21} & Z_{22} & \cdots & Z_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ Z_{N1} & Z_{N2} & \cdots & Z_{NN} \end{bmatrix}$$

Each element of matrix \mathbf{Z} is given by

$$Z_{ij} = \left. \frac{V_i}{I_j} \right|_{I_k=0 \text{ for } k \neq j}$$

Z-Parameters for 2-Port Networks

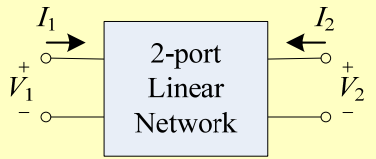


$$\mathbf{V} = \mathbf{Z}\mathbf{I}$$

$$\mathbf{V} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \mathbf{I} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\mathbf{Z} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$

Equivalent circuit:

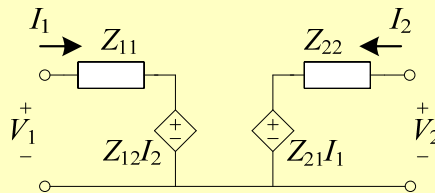

Admittance Matrix Representation (\mathbf{Y})


$$\mathbf{V} = \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix} \quad \mathbf{I} = \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix} \quad \mathbf{I} = \mathbf{Y}\mathbf{V}$$

$$\mathbf{Y} = \begin{bmatrix} Y_{11} & Y_{12} & \cdots & Y_{1N} \\ Y_{21} & Y_{22} & \cdots & Y_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ Y_{N1} & Y_{N2} & \cdots & Y_{NN} \end{bmatrix}$$

Each element of matrix \mathbf{Y} is given by

$$Y_{ij} = \left. \frac{I_i}{V_j} \right|_{V_k=0 \text{ for } k \neq j}$$

Y-Parameters for 2-Port Networks

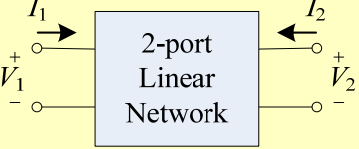


$$\mathbf{I} = \mathbf{Y}\mathbf{V}$$


$$\mathbf{V} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \mathbf{I} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\mathbf{Y} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$$


Equivalent circuit:

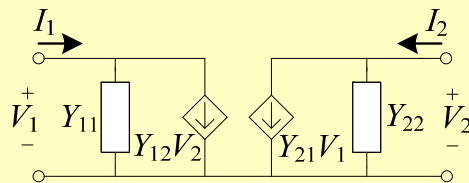

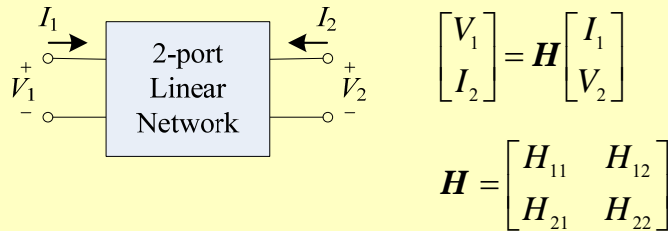H-Parameters (Hybrid) for 2-Port Networks



Equivalent circuit:

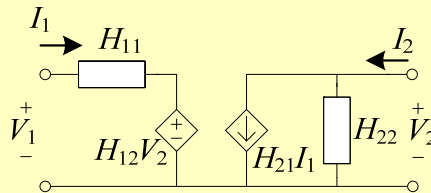

Dr. J. E. Rayas-Sánchez

9

Some Properties of the \mathbf{Z} and \mathbf{Y} Matrices

- If the network is reciprocal (passive and not containing any nonreciprocal media such as ferrites or plasmas), then \mathbf{Z} and \mathbf{Y} are symmetric,

$$Z_{ij} = Z_{ji} \quad Y_{ij} = Y_{ji}$$


- If the network is lossless, all the elements in \mathbf{Z} and \mathbf{Y} are purely imaginary
- In most practical cases, high-speed interconnects can be considered as reciprocal networks, and in some cases, lossless networks

Dr. J. E. Rayas-Sánchez


10

The Scattering Matrix Representation (S)

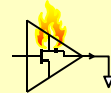- They can be more easily obtained at high frequencies:
 - Incident and reflected waves can be measured using a Vector Network Analyzer (VNA)
 - They do not require “shorts” or “opens” (active devices might oscillate or self-destruct)
- They are more directly related to high-frequency effects (Γ , T , IL , RL , SWR , etc.)
- We can convert back and forth between S , Y and Z parameters



The Scattering Matrix (S)

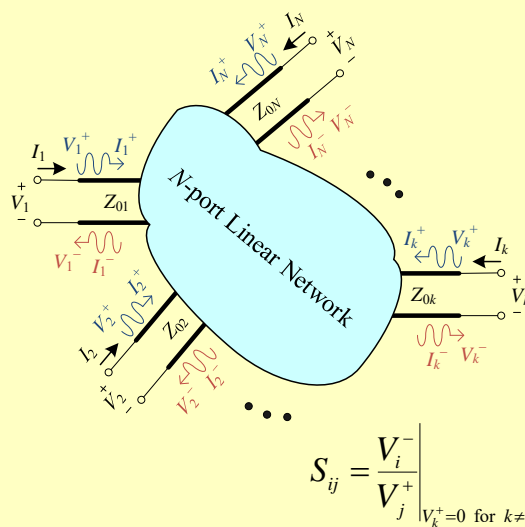

$$\mathbf{V}^+ = \begin{bmatrix} V_1^+ \\ V_2^+ \\ \vdots \\ V_N^+ \end{bmatrix} \quad \mathbf{V}^- = \begin{bmatrix} V_1^- \\ V_2^- \\ \vdots \\ V_N^- \end{bmatrix}$$

$$\mathbf{V}^- = \mathbf{S} \mathbf{V}^+$$

$$\mathbf{S} = \begin{bmatrix} S_{11} & S_{12} & \dots & S_{1N} \\ S_{21} & S_{22} & \dots & S_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ S_{N1} & S_{N2} & \dots & S_{NN} \end{bmatrix}$$

$V_k^+ = 0$ if we terminate port k with a matched load ($Z_{Lk} = Z_{0k}$)

Meaning of the S-parameters

- S_{ii} represents the reflection coefficient at port i when all the remaining ports are terminated with matched loads
- S_{ij} represents the transmission coefficient from port j to port i when all the other ports are terminated with matched loads

Meaning of the S-parameters (cont.)

S_{11} : forward reflection coefficient (input match)

S_{22} : reverse reflection coefficient (output match)

S_{21} : forward transmission coefficient (gain or loss)

S_{12} : reverse transmission coefficient (isolation)

$$S_{ii} \neq \Gamma_i \quad S_{ii} = \left. \frac{V_i^-}{V_i^+} \right|_{V_k^+ = 0 \text{ for } k \neq i} = \Gamma_i \Big|_{V_k^+ = 0 \text{ for } k \neq i}$$

$$S_{ij} \neq T_{ji} \quad S_{ij} = \left. \frac{V_i^-}{V_j^+} \right|_{V_k^+ = 0 \text{ for } k \neq j} = T_{ji} \Big|_{V_k^+ = 0 \text{ for } k \neq j}$$

Conversion between S and Y and Z Matrices

$$\left. \begin{aligned} S &= (Z + I)^{-1}(Z - I) \\ Z &= (I + S)(I - S)^{-1} \end{aligned} \right\} \begin{array}{l} \text{(normalized } Z, \\ \text{assuming all ports} \\ \text{have the same } Z_0) \end{array}$$

where I is the identity matrix (N by N)

$$Z = Y^{-1}$$

$$Y = Z^{-1}$$

Conversion between S and Y and Z (cont.)

$$S = (ZY_0 + I)^{-1}(ZY_0 - I)$$

$$Z = Y_0^{-1}(I + S)(I - S)^{-1}$$

where I is the identity matrix (N by N) and

$$Y_0 = \text{diag}(1/Z_{01} \quad 1/Z_{02} \quad \dots \quad 1/Z_{0N})$$

$$Z = Y^{-1}$$

$$Y = Z^{-1}$$

Some Properties of the S Matrix

- If the network is reciprocal (passive and not containing any nonreciprocal media such as ferrites or plasmas), then S is symmetric,

$$S_{ij} = S_{ji}$$

- If the network is lossless, matrix S is unitary (orthonormal complex)

$$\sum_{k=1}^N S_{ki} S_{ki}^* = 1 \quad \sum_{k=1}^N S_{ki} S_{kj}^* = 0$$

- In most practical cases, high-speed interconnects can be considered as reciprocal networks, and in some cases, lossless networks