

# **Frequency-Domain Analysis of Transmission Line Circuits**

(Part 3)

**Dr. José Ernesto Rayas-Sánchez**

1

## **Outline**

---

- Differential transmission lines
- Common mode signaling
- Differential mode signaling
- Mode conversion
- Even and odd modes
- 2-coupled lossless transmission line theory
- Termination techniques
- Differential or Mixed-Mode S-parameters

## Differential Transmission Lines

For high data rates, differential signaling is more used due to:


- Radiation is reduced (cancellation of fields)
- Receiver rejects signals that are common to both lines (high CMRR at the receiver)
- Signal voltage amplitudes can be smaller



Dr. J. E. Rayas-Sánchez

(M. Resso, 2005) 3
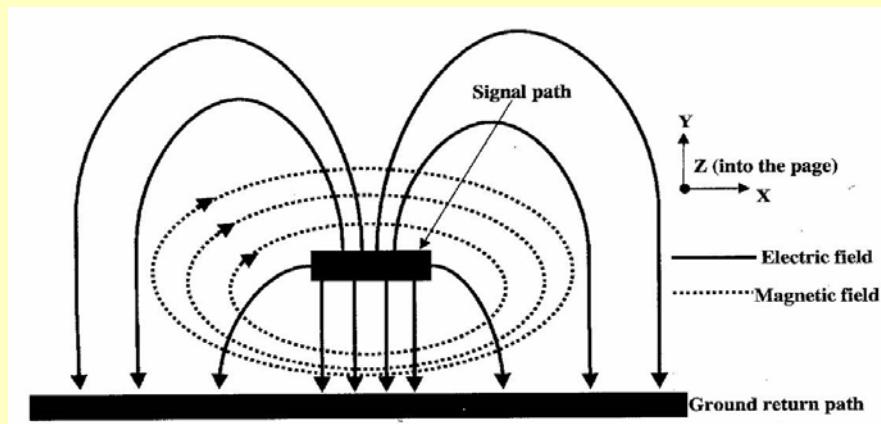
## Electromagnetic Fields in a Microstrip Line



Dr. J. E. Rayas-Sánchez

4

## Frequency-Domain Analysis of Transmission Line Circuits (Part 3)



Dr. José Ernesto Rayas-Sánchez

March 6, 2020
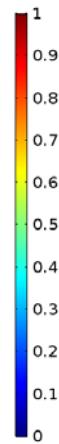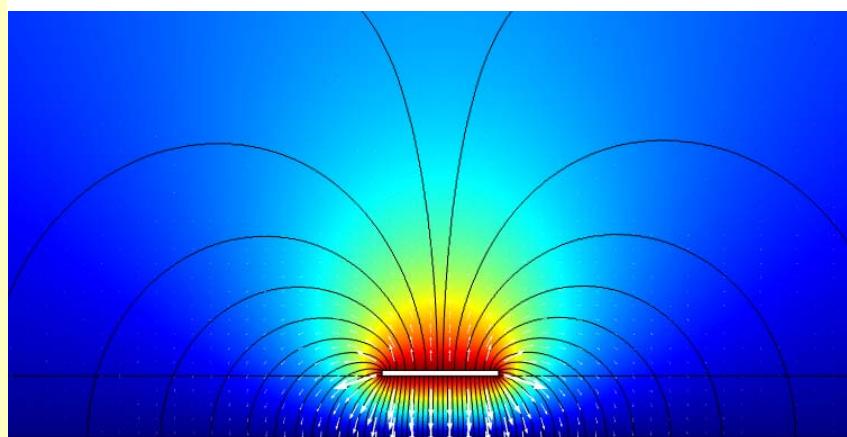
### Electric Field Distribution

Substrate: Air ( $\epsilon_r = 1$ )

Surface: Electric potential (V) Streamline: Electric field Arrow Surface: Electric field



Dr. J. E. Rayas-Sánchez



COMSOL

5
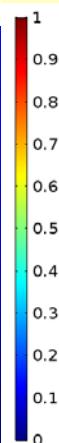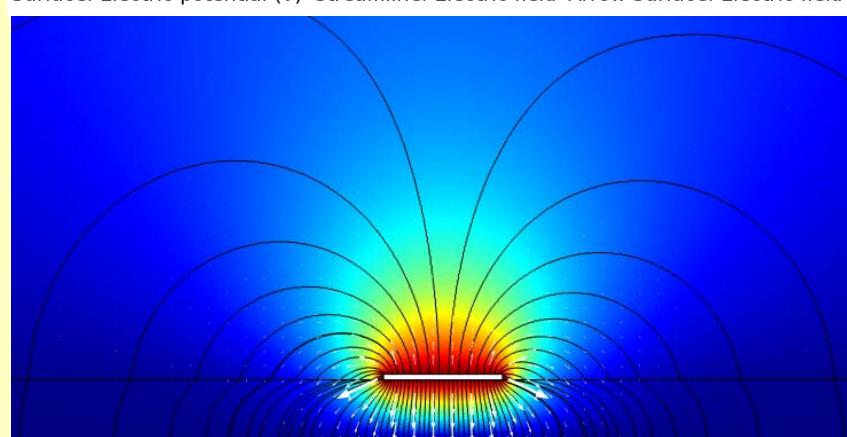
### Electric Field Distribution (cont.)

Substrate: FR4 ( $\epsilon_r = 4.5$ )

Surface: Electric potential (V) Streamline: Electric field Arrow Surface: Electric field



Dr. J. E. Rayas-Sánchez


COMSOL

6
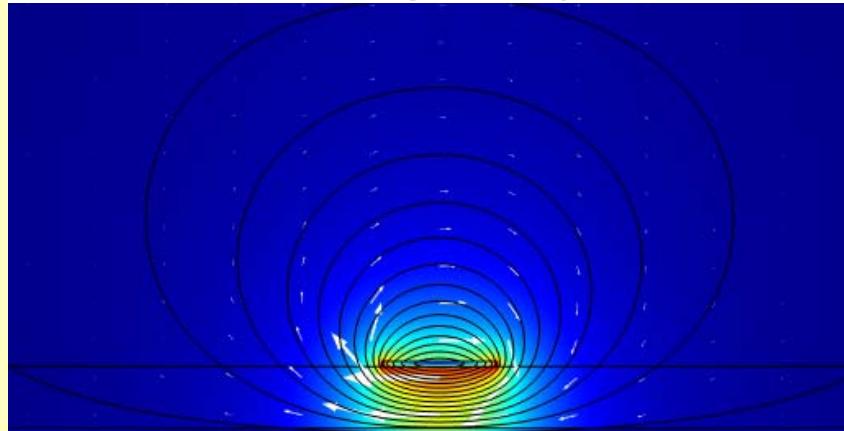
## Magnetic Field Distribution

Substrate: Air or FR4

Surface: Magnetic flux density norm (T) Arrow Surface: Magnetic flux density  
Streamline: Magnetic flux density



Dr. J. E. Rayas-Sánchez

COMSOL

## Differential Signaling for High-Speed Links

- Differential signaling can operate at much higher data rates
- High speed links operating in excess of ~1 Gb/s use differential signaling (e.g. Infiniband, PCI-Express).
- Differential signals are already used for high speed clocks




Dr. J. E. Rayas-Sánchez

(H. Heck 2002)
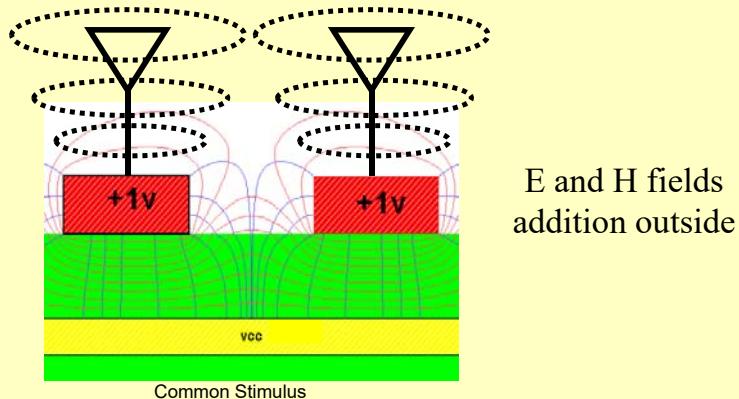
## Common Mode Signaling

As data rates go up, frequencies increase, lines become antennas (both send and receive) and corrupt the communication (BER, crosstalk, etc)




Dr. J. E. Rayas-Sánchez

(M. Resso, 2005)<sub>9</sub>
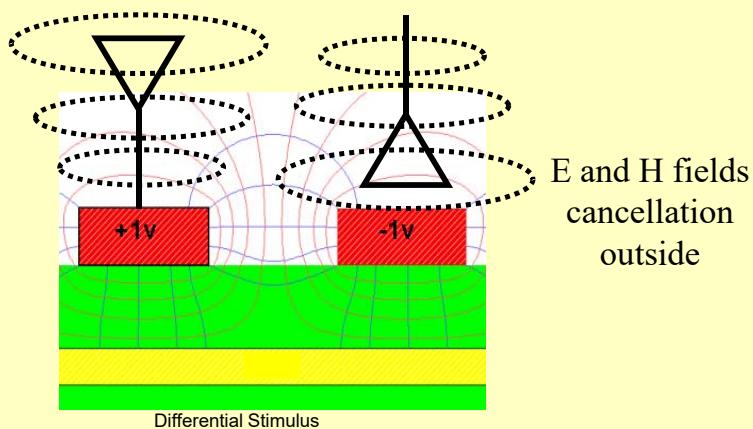
## Differential Mode Signaling

Using differential excitations (differential transmission lines), most of the outside electromagnetic field cancels




Dr. J. E. Rayas-Sánchez

(M. Resso, 2005)<sub>10</sub>
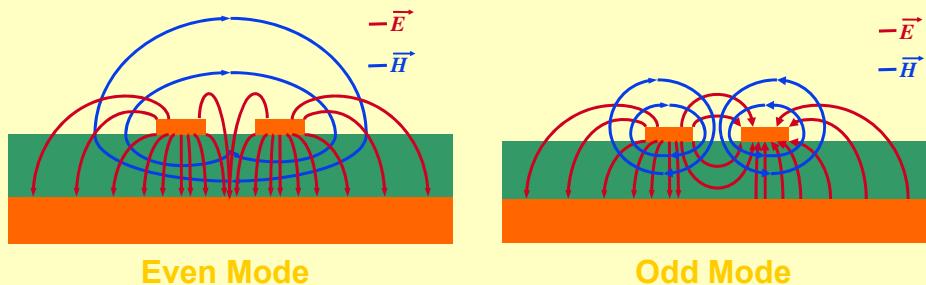
## Even Mode and Odd Mode

- Practical differential pairs operate at even and odd modes simultaneously
- Even mode – excited in phase with equal amplitudes
- Odd mode – driven 180° out of phase with equal amplitudes




Dr. J. E. Rayas-Sánchez


(H. Heck 2002)<sub>11</sub>

## Even Mode and Odd Mode (cont.)


### Differential Mode

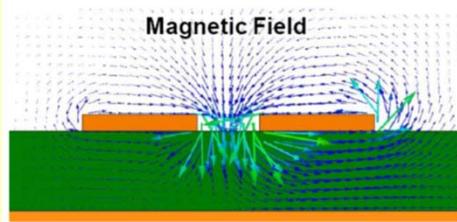


### Common Mode

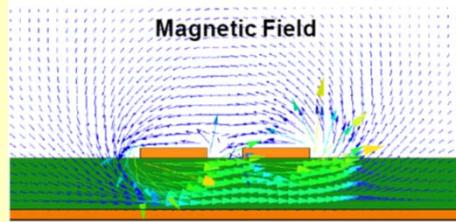

### Electric Field

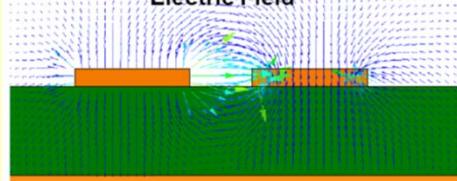

### Electric Field

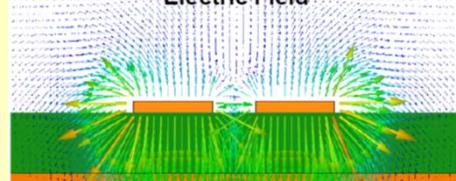


Dr. J. E. Rayas-Sánchez

(P. Huray and S. Pytel, 2009)<sub>12</sub>
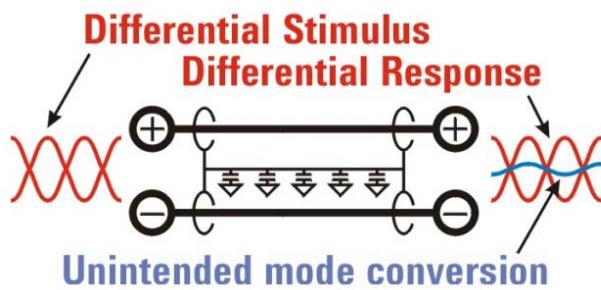
## Mode Conversion


- Is produced by asymmetries in the differential pairs
- Can cause a differential signal to be converted to a common mode signal (radiation, crosstalk, etc.)



Dr. J. E. Rayas-Sánchez

(M. Resso, 2005)<sub>13</sub>

## Lossless Transmission Lines

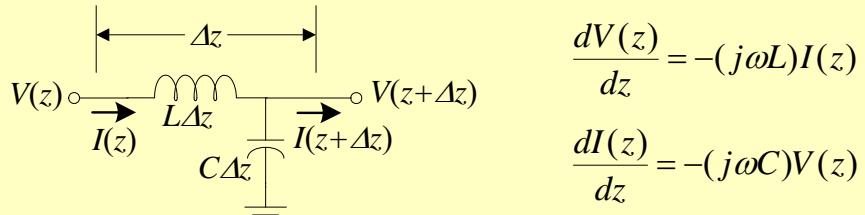

$$\frac{dV(z)}{dz} = -(j\omega L)I(z)$$

$$\frac{dI(z)}{dz} = -(j\omega C)V(z)$$

$$\frac{dV}{dz} = -j\omega LI$$

$$\frac{dI}{dz} = -j\omega CV$$

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$I(z) = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z}$$

$$\beta = \omega \sqrt{LC}$$

$$Z_0 = \sqrt{\frac{L}{C}} \quad v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$


$$-\frac{d}{dz} \begin{bmatrix} V \\ I \end{bmatrix} = \begin{bmatrix} 0 & Z_L \\ Y_C & 0 \end{bmatrix} \begin{bmatrix} V \\ I \end{bmatrix}$$

$$Z_L = j\omega L \quad Y_C = j\omega C$$

Dr. J. E. Rayas-Sánchez

<sub>14</sub>

## 2-Coupled Lossless Symmetrical TLs

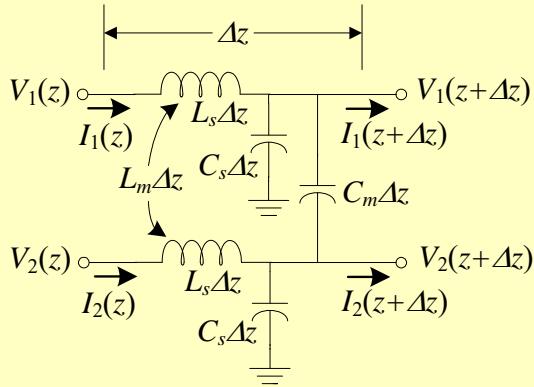

$$\frac{dV_1}{dz} = -j\omega L_s I_1 - j\omega L_m I_2 \quad \frac{dI_1}{dz} = -j\omega(C_s + C_m)V_1 + j\omega C_m V_2$$

$$\frac{dV_2}{dz} = -j\omega L_m I_1 - j\omega L_s I_2 \quad \frac{dI_2}{dz} = +j\omega C_m V_1 - j\omega(C_s + C_m)V_2$$

Dr. J. E. Rayas-Sánchez

15

## 2-Coupled Lossless Symmetrical TLs (cont.)

$$\frac{dV_1}{dz} = -j\omega L_s I_1 - j\omega L_m I_2$$

$$\frac{dV_2}{dz} = -j\omega L_m I_1 - j\omega L_s I_2$$

$$\frac{dI_1}{dz} = -j\omega(C_s + C_m)V_1 + j\omega C_m V_2$$

$$\frac{dI_2}{dz} = +j\omega C_m V_1 - j\omega(C_s + C_m)V_2$$

$$\mathbf{V} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \mathbf{I} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\mathbf{Y}_c = j\omega \begin{bmatrix} (C_s + C_m) & -C_m \\ -C_m & (C_s + C_m) \end{bmatrix}$$

$$\mathbf{Z}_L = j\omega \begin{bmatrix} L_s & L_m \\ L_m & L_s \end{bmatrix}$$

$$-\frac{d}{dz} \begin{bmatrix} \mathbf{V} \\ \mathbf{I} \end{bmatrix} = \begin{bmatrix} \mathbf{0} & \mathbf{Z}_L \\ \mathbf{Y}_c & \mathbf{0} \end{bmatrix} \begin{bmatrix} \mathbf{V} \\ \mathbf{I} \end{bmatrix}$$

Dr. J. E. Rayas-Sánchez

16

## LC Matrices of 2-Coupled TLs

$$\mathbf{C} = \begin{bmatrix} C_{11} & C_{12} \\ C_{21} & C_{22} \end{bmatrix} = \begin{bmatrix} (C_s + C_m) & -C_m \\ -C_m & (C_s + C_m) \end{bmatrix}$$

$$\mathbf{L} = \begin{bmatrix} L_{11} & L_{12} \\ L_{21} & L_{22} \end{bmatrix} = \begin{bmatrix} L_s & L_m \\ L_m & L_s \end{bmatrix}$$

$$Z_0 = ?$$

$$v_p = ?$$

## Even Mode in 2-Coupled Symmetrical TLs

$$\frac{dV_1}{dz} = -j\omega L_s I_1 - j\omega L_m I_2 \quad \frac{dV_2}{dz} = -j\omega L_m I_1 - j\omega L_s I_2$$

$$\frac{dI_1}{dz} = -j\omega(C_s + C_m)V_1 + j\omega C_m V_2 \quad \frac{dI_2}{dz} = j\omega C_m V_1 - j\omega(C_s + C_m)V_2$$

Since  $V_1 = V_2$  and  $I_1 = I_2$

$$\frac{dV_1}{dz} = -j\omega(L_s + L_m)I_1 \quad \frac{dI_1}{dz} = -j\omega C_s V_1$$



The effective  $L$  and  $C$  are

$$L_{\text{eff}} = L_s + L_m \quad C_{\text{eff}} = C_s$$

Hence  $Z_{0\text{-even}} = \sqrt{\frac{L_s + L_m}{C_s}}$   $v_{p\text{-even}} = \frac{1}{\sqrt{(L_s + L_m)C_s}}$

## Even Mode in 2-Coupled Symmetrical TLs (cont.)

$$V_1 = V_2 ; I_1 = I_2$$

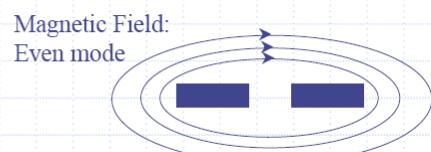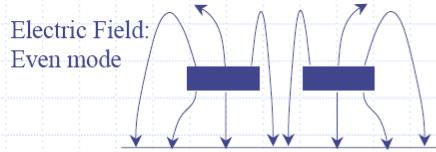

(R. Mellitz 2003)

$$Z_{0\text{-even}} = \sqrt{\frac{L_s + L_m}{C_s}} \quad v_{p\text{-even}} = \frac{1}{\sqrt{(L_s + L_m)C_s}}$$

$Z_{0\text{-even}}$  is the characteristic impedance of one of the conductors when the coupled line is operated in even mode

## Odd Mode in 2-Coupled Symmetrical TLs

$$\frac{dV_1}{dz} = -j\omega L_s I_1 - j\omega L_m I_2 \quad \frac{dV_2}{dz} = -j\omega L_m I_1 - j\omega L_s I_2$$

$$\frac{dI_1}{dz} = -j\omega(C_s + C_m)V_1 + j\omega C_m V_2 \quad \frac{dI_2}{dz} = j\omega C_m V_1 - j\omega(C_s + C_m)V_2$$

Since  $V_1 = -V_2$  and  $I_1 = -I_2$

$$\frac{dV_1}{dz} = -j\omega(L_s - L_m)I_1 \quad \frac{dI_1}{dz} = -j\omega(C_s + 2C_m)V_1$$

The effective  $L$  and  $C$  are

$$L_{\text{eff}} = L_s - L_m \quad C_{\text{eff}} = C_s + 2C_m$$

Hence  $Z_{0\text{-odd}} = \sqrt{\frac{L_s - L_m}{C_s + 2C_m}}$   $v_{p\text{-odd}} = \frac{1}{\sqrt{(L_s - L_m)(C_s + 2C_m)}}$

### Odd Mode in 2-Coupled Symmetrical TLs (cont.)

$$V_1 = -V_2 ; I_1 = -I_2$$





(R. Mellitz 2003)


$$Z_{0\text{-odd}} = \sqrt{\frac{L_s - L_m}{C_s + 2C_m}} \quad v_{p\text{-odd}} = \frac{1}{\sqrt{(L_s - L_m)(C_s + 2C_m)}}$$

$Z_{0\text{-odd}}$  is the characteristic impedance of one of the conductors when the coupled line is operated in odd mode
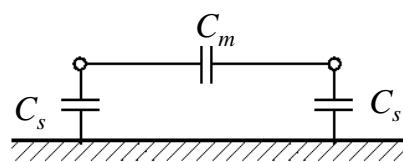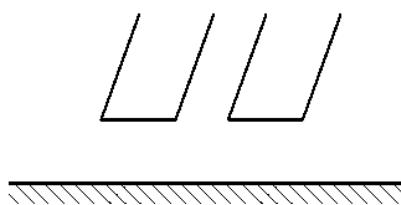
### Distributed Capacitances in Coupled Lines


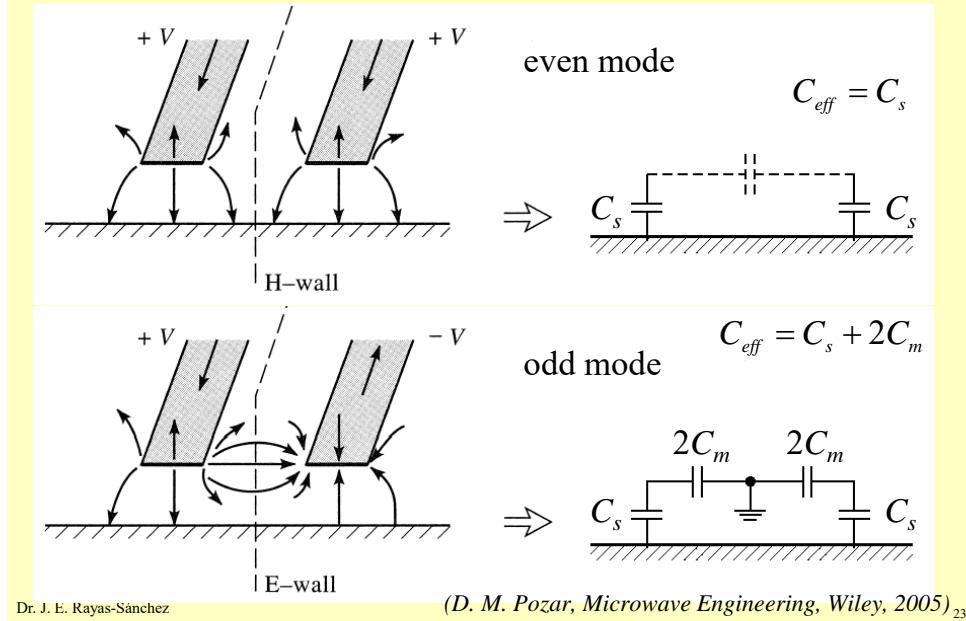
## Distributed Capacitances in Coupled Lines (cont.)



## $Z_0$ and $v_p$ for Even and Odd Modes

- If  $Z_0$  is the characteristic impedance of each isolated conductor, and  $v_p$  is the propagation velocity or wave speed in each isolated conductor

$$Z_0 = \sqrt{\frac{L_s}{C_s}} \quad v_p = \frac{1}{\sqrt{L_s C_s}}$$

- Since

$$Z_{0\text{-even}} = \sqrt{\frac{L_s + L_m}{C_s}} \quad v_{p\text{-even}} = \frac{1}{\sqrt{(L_s + L_m)C_s}}$$

$$Z_{0\text{-odd}} = \sqrt{\frac{L_s - L_m}{C_s + 2C_m}} \quad v_{p\text{-odd}} = \frac{1}{\sqrt{(L_s - L_m)(C_s + 2C_m)}}$$

- then


$$Z_{0\text{-odd}} < Z_0 < Z_{0\text{-even}}$$

$$v_{p\text{-even}} < v_{p\text{-odd}} < v_p$$


## Termination Techniques

- A single-resistor termination for each conductor is not enough for coupled lines
- Proper terminations are needed to avoid reflections in both even and odd modes
- The most common termination networks are the T and Pi configurations


## T-Termination

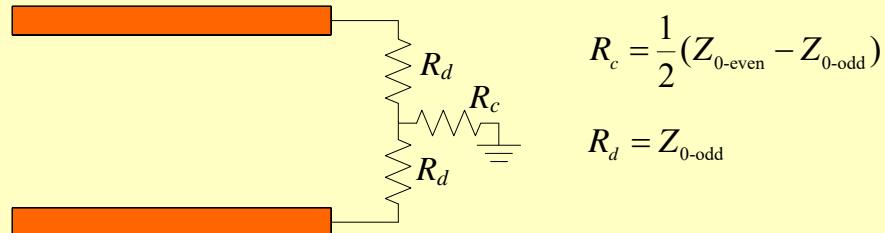

## Pi-Termination

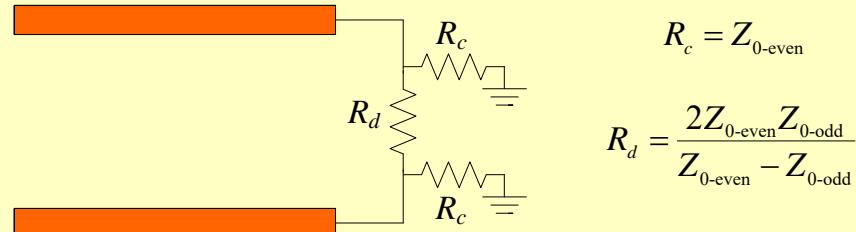
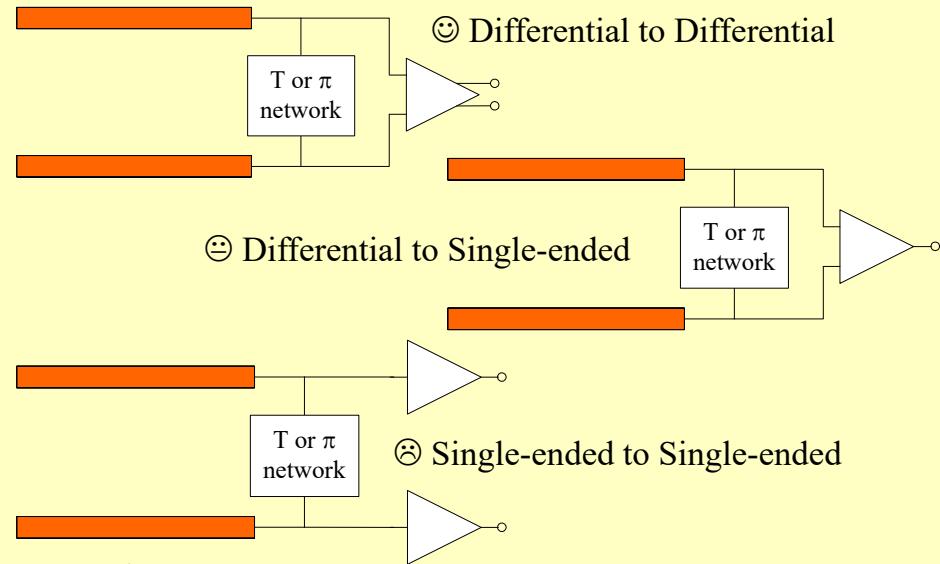
## Adding Buffers for Differential Signaling




## Frequency-Domain Analysis of Transmission Line Circuits (Part 3)


Dr. José Ernesto Rayas-Sánchez

March 6, 2020

### S-Parameters for Two-Coupled Lines

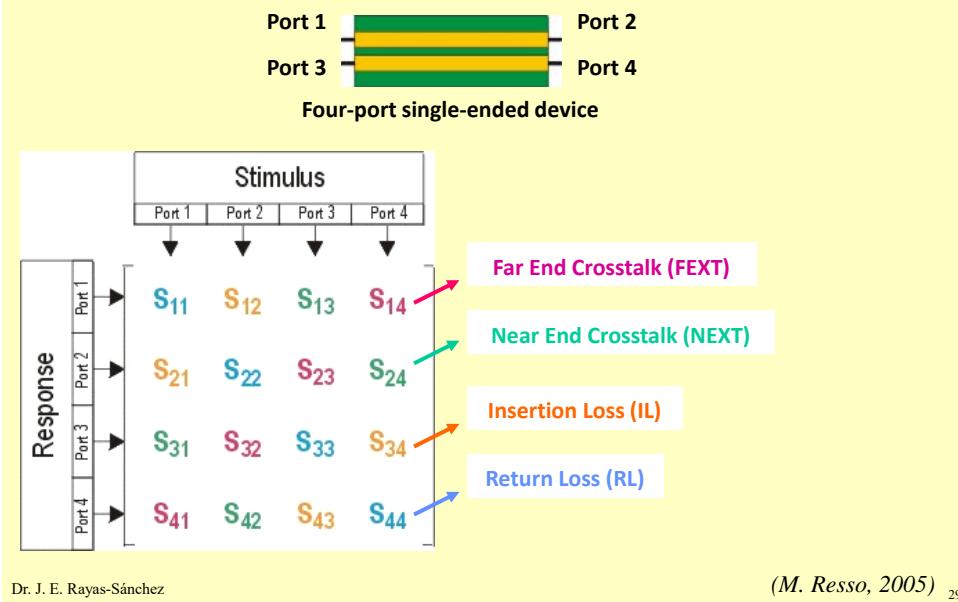
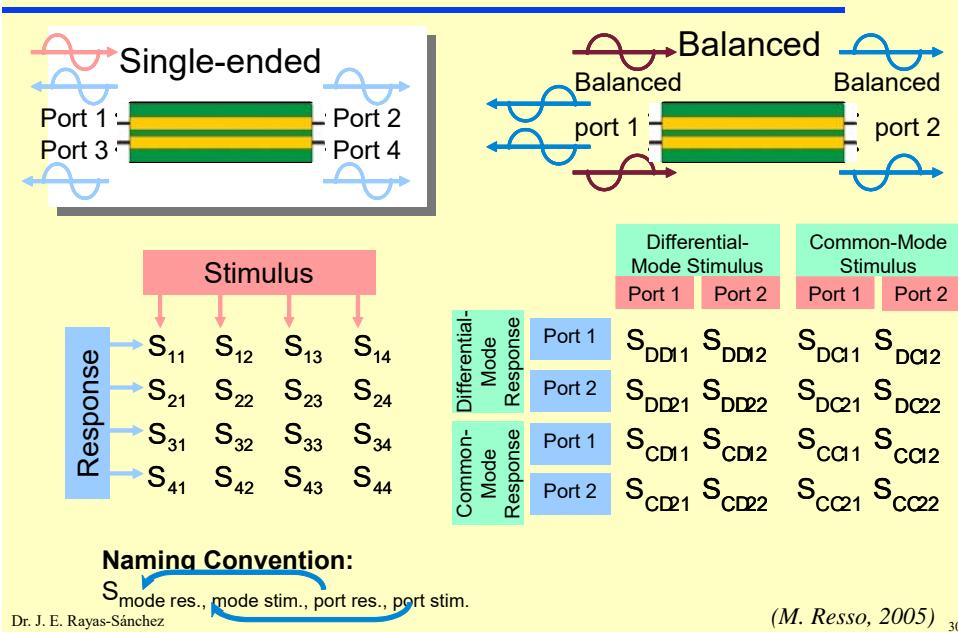
### Single-ended to Balanced S-Parameters



## Balanced, Differential or Mixed-Mode S-Param.

