

Transient-Domain Analysis of Transmission Line Circuits

(Part 1)


Dr. José Ernesto Rayas-Sánchez

1

Outline

- Quarter-wave transformer – steady state response
- Quarter-wave transformer – transient response
- Reflection coefficient revised
- Concept of “transient impedance”
- Applying DC to transmission lines
- Lattice (or bouncing or reflection) diagrams
- Building transient signals from bouncing diagrams

Quarter-Wave Transformer

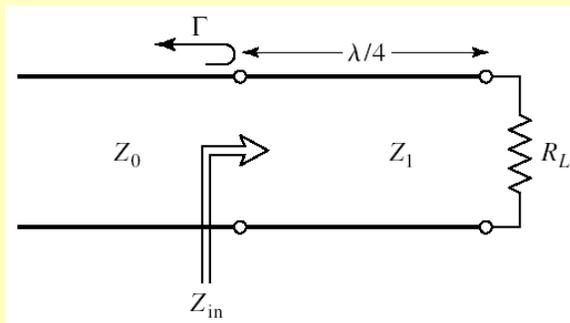

$$Z_{in} = \frac{Z_1^2}{R_L}$$

To make $\Gamma = 0$,

$$Z_1 = \sqrt{R_L Z_o}$$


Z_1 must be the geometric mean of Z_o and R_L

Γ is the steady-state reflection coefficient

Dr. J. E. Rayas-Sánchez

3

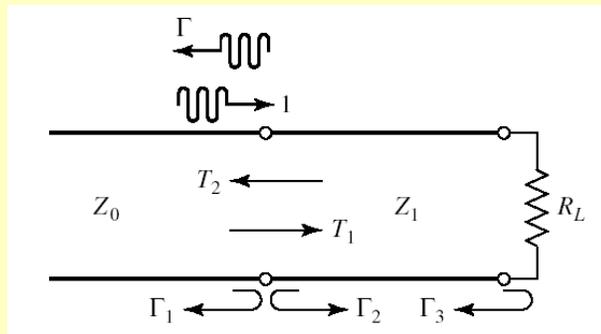Quarter-Wave Transformer – Transient Response



$$\Gamma_1 = \frac{Z_1 - Z_o}{Z_1 + Z_o}$$

$$\Gamma_2 = \frac{Z_o - Z_1}{Z_o + Z_1} = -\Gamma_1$$

$$\Gamma_3 = \frac{R_L - Z_1}{R_L + Z_1}$$

$$T_1 = 1 + \Gamma_1 = \frac{2Z_1}{Z_1 + Z_o}$$


$$T_2 = 1 + \Gamma_2 = \frac{2Z_o}{Z_o + Z_1}$$

Dr. J. E. Rayas-Sánchez

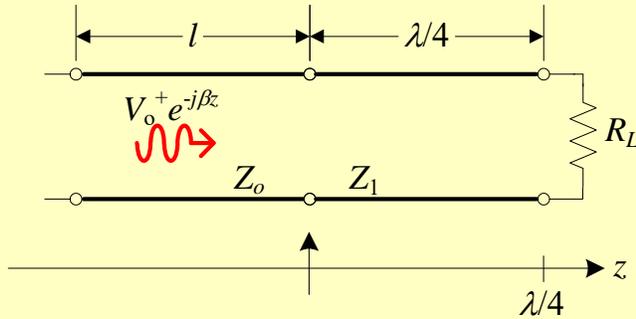(D. M. Pozar, *Microwave Engineering*, Wiley, 2005)

4


Quarter-Wave Transformer – Transient Response




Initially, the incoming wave has only the incident component:

$$V(z) = V_0^+ e^{-j\beta z}$$

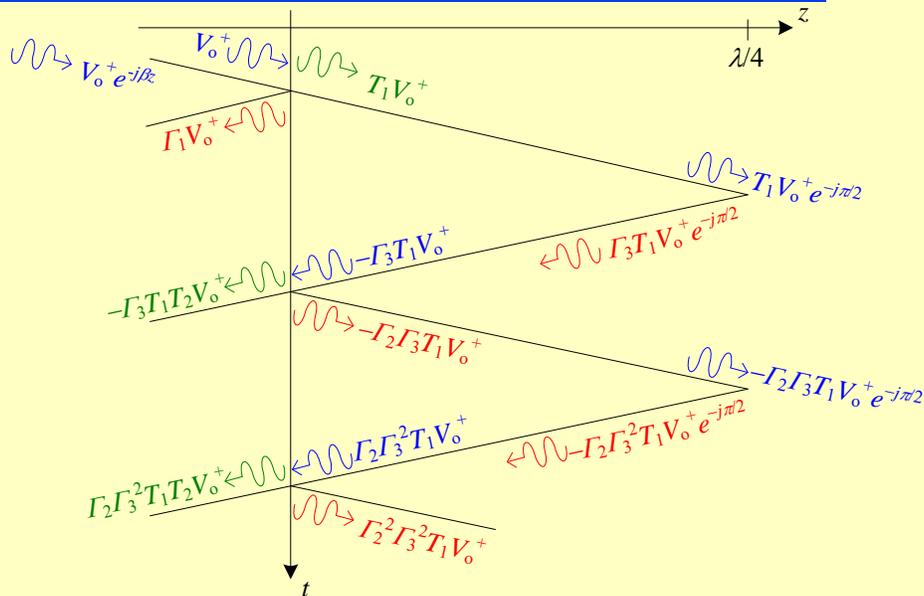Quarter-Wave Transformer – Transient Response



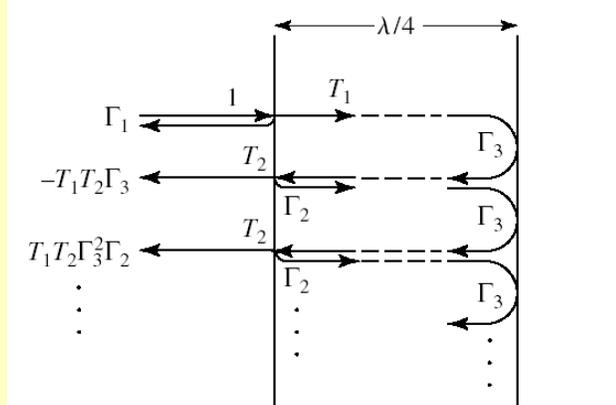Quarter-Wave Transformer – Transient Response



$$\Gamma = \Gamma_1 - T_1 T_2 \Gamma_3 + T_1 T_2 \Gamma_2 \Gamma_3^2 - T_1 T_2 \Gamma_2^2 \Gamma_3^3 + \dots$$

$$\Gamma = \Gamma_1 - T_1 T_2 \Gamma_3 \sum_{n=0}^{\infty} (-\Gamma_2 \Gamma_3)^n$$

Dr. J. E. Rayas-Sánchez

7

Quarter-Wave Transformer – Transient Response

$$\Gamma = \Gamma_1 - T_1 T_2 \Gamma_3 \sum_{n=0}^{\infty} (-\Gamma_2 \Gamma_3)^n$$

Since $\sum_{n=0}^{\infty} x^n = \frac{1}{1-x}$, for $|x| < 1$

$$\Gamma = \Gamma_1 - \frac{T_1 T_2 \Gamma_3}{1 + \Gamma_2 \Gamma_3} = \frac{\Gamma_1 + \Gamma_1 \Gamma_2 \Gamma_3 - T_1 T_2 \Gamma_3}{1 + \Gamma_2 \Gamma_3}$$

using


$$\Gamma_1 = \frac{Z_1 - Z_o}{Z_1 + Z_o} \quad \Gamma_2 = -\Gamma_1 \quad \Gamma_3 = \frac{R_L - Z_1}{R_L + Z_1} \quad T_1 = \frac{2Z_1}{Z_1 + Z_o} \quad T_2 = \frac{2Z_o}{Z_o + Z_1}$$

$$\Gamma_1 + \Gamma_1 \Gamma_2 \Gamma_3 - T_1 T_2 \Gamma_3 = \frac{2(Z_1^2 - Z_o R_L)}{(Z_1 + Z_o)(R_L + Z_1)} = 0 \text{ if } Z_1 = \sqrt{Z_o R_L}$$

Dr. J. E. Rayas-Sánchez

8


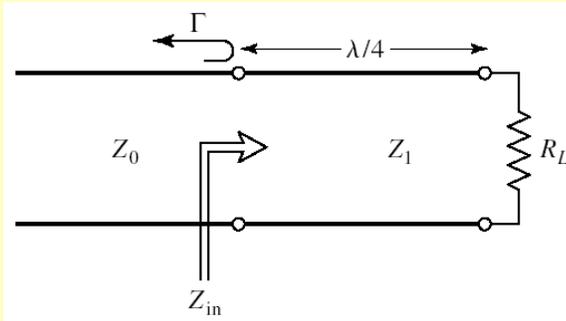
Quarter-Wave Transformer – Transient Response



$$\Gamma = \Gamma_1 - T_1 T_2 \Gamma_3 \sum_{n=0}^{\infty} (-\Gamma_2 \Gamma_3)^n = 0 \quad \text{if } Z_1 = \sqrt{Z_0 R_L}$$

If Z_1 is the geometric mean of Z_0 and R_L , the sum of the infinite number of partial reflections is zero


Applying DC to Transmission Lines

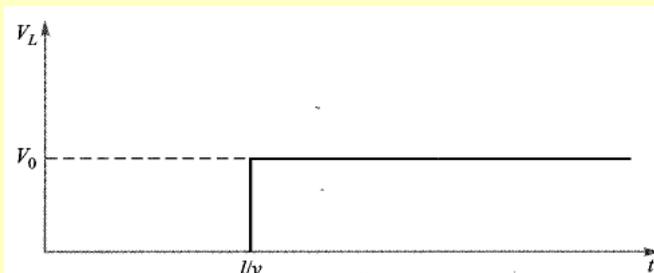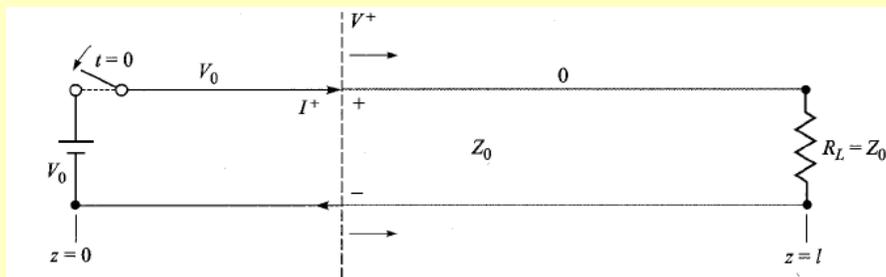

$$I^+ = \frac{V^+}{Z_0}$$

$$v = \frac{c}{\sqrt{\epsilon_e}}$$

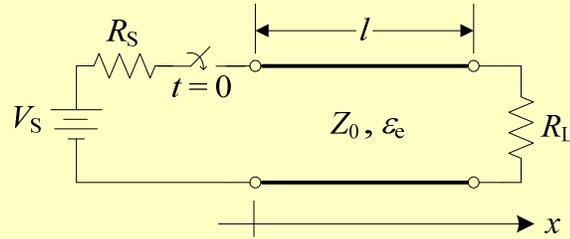Applying DC to Transmission Lines (cont.)



$$\Gamma_S = \frac{R_S - Z_o}{R_S + Z_o} \quad \Gamma_L = \frac{R_L - Z_o}{R_L + Z_o} \quad v_p = \frac{c}{\sqrt{\epsilon_e}}$$


$$V_o^+ = \frac{V_S Z_o}{R_S + Z_o} \quad I_o^+ = \frac{V_o^+}{Z_o}$$

Dr. J. E. Rayas-Sánchez

11

Lattice (or Bouncing or Reflection) Diagrams


Voltage Diagrams

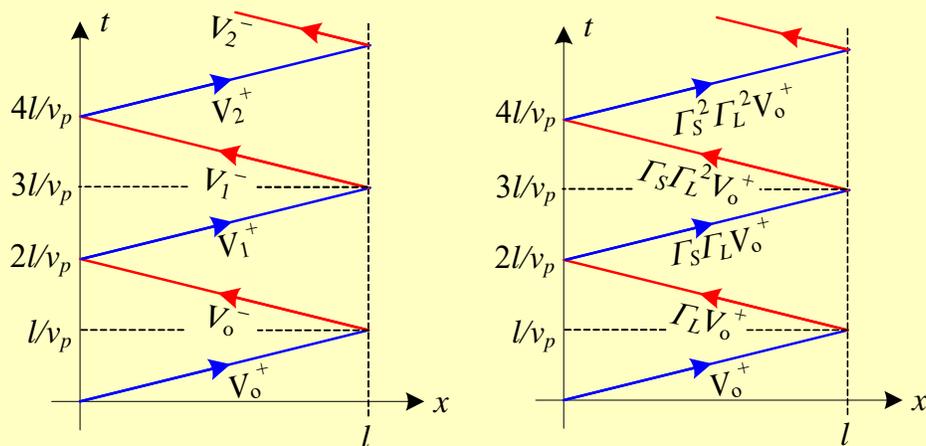

Dr. J. E. Rayas-Sánchez

12


Bouncing Diagrams for Currents

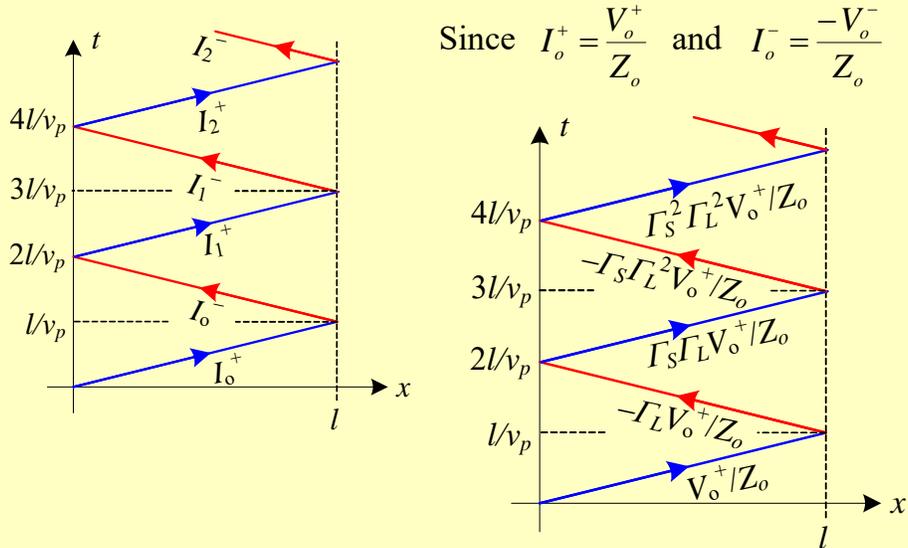

Dr. J. E. Rayas-Sánchez

13


Transient Signals from Bouncing Diagrams

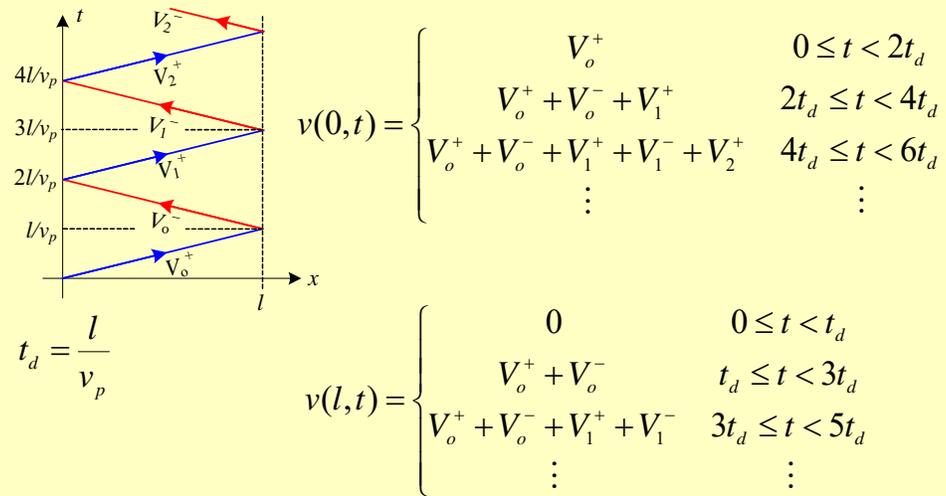


Dr. J. E. Rayas-Sánchez

14

Bouncing Diagrams – Other Representation

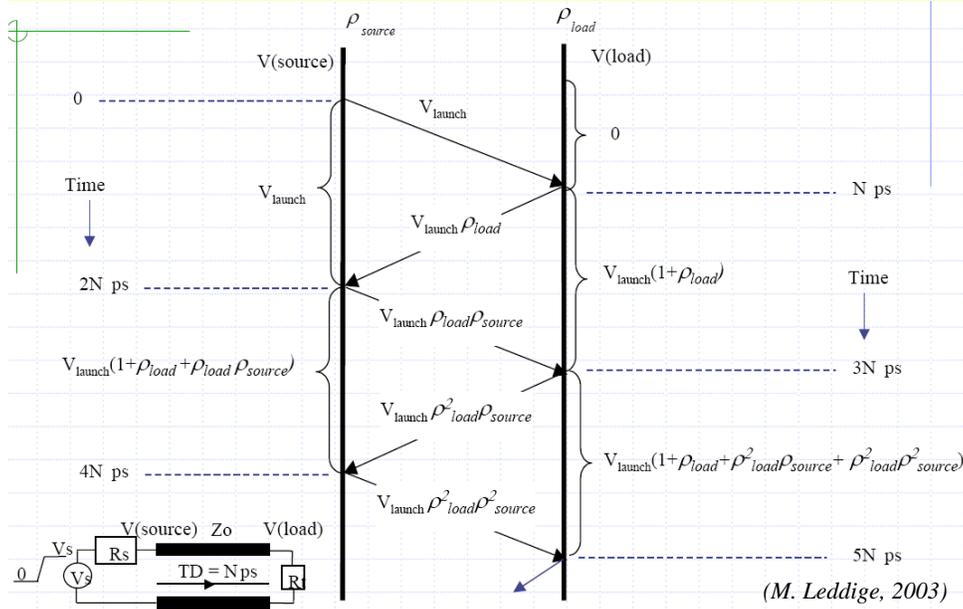

Example – Underdriven Transmission Line

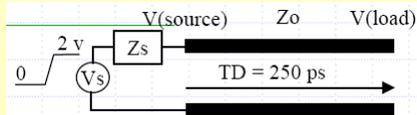


Assume $Z_s = 75$ ohms
 $Z_o = 50$ ohms
 $V_s = 0-2$ volts

$$V_{initial} = V_s \frac{Z_o}{Z_s + Z_o} = (2) \left(\frac{50}{75 + 50} \right) = 0.8$$

$$\rho_{source} = \frac{Z_s - Z_o}{Z_s + Z_o} = \frac{75 - 50}{75 + 50} = 0.2$$
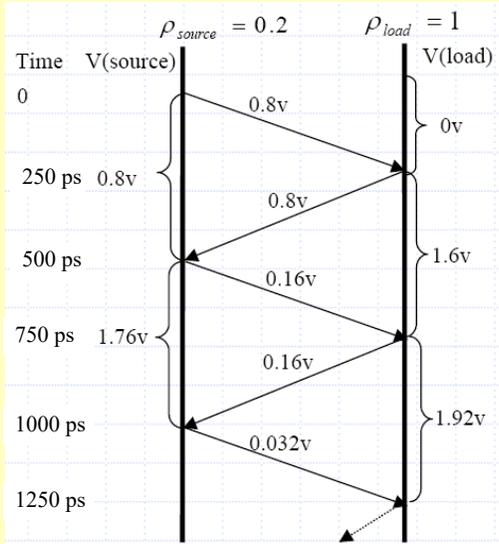
$$\rho_{load} = \frac{Z_l - Z_o}{Z_l + Z_o} = \frac{\infty - 50}{\infty + 50} = 1$$





Transient-Domain Analysis of Transmission Line Circuits (Part 1)

Dr. José Ernesto Rayas-Sánchez

March 28, 2020

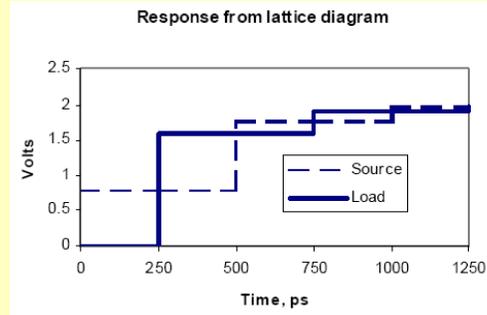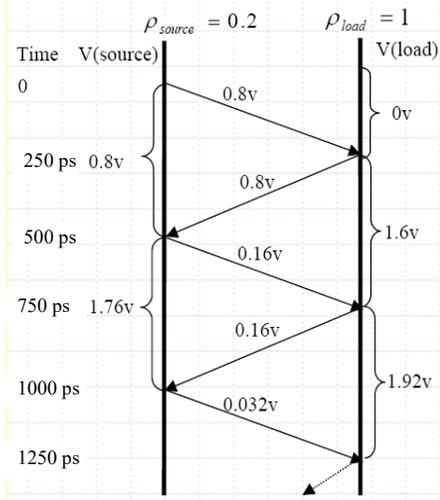Example – Underdriven Transmission Line (cont.)




Dr. J. E. Rayas-Sánchez

(S.H. Hall, G.W. Hall and J.A. McCall, High-Speed Digital System Design, Wiley, 2000)

17

Example – Overdriven Transmission Line

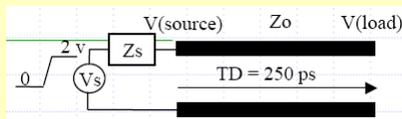

Assume $Z_s = 25$ ohms


$Z_o = 50$ ohms

$V_s = 0-2$ volts

$$V_{initial} = V_s \frac{Z_o}{Z_s + Z_o} = (2) \left(\frac{50}{25 + 50} \right) = 1.3333$$

$$\rho_{source} = \frac{Z_s - Z_o}{Z_s + Z_o} = \frac{25 - 50}{25 + 50} = -0.33333$$
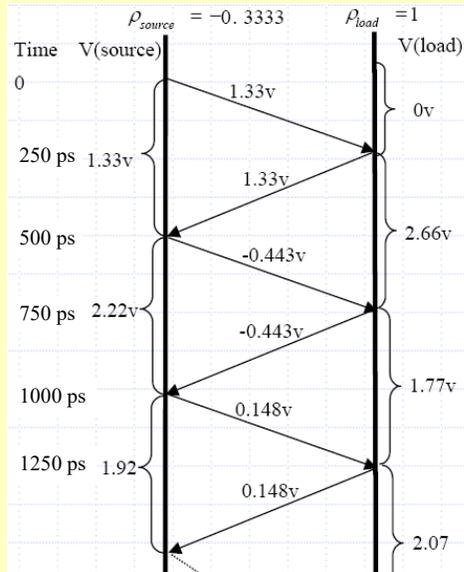
$$\rho_{load} = \frac{Z_l - Z_o}{Z_l + Z_o} = \frac{\infty - 50}{\infty + 50} = 1$$





Dr. J. E. Rayas-Sánchez

(S.H. Hall, G.W. Hall and J.A. McCall, High-Speed Digital System Design, Wiley, 2000)


18

Example – Overdriven Transmission Line

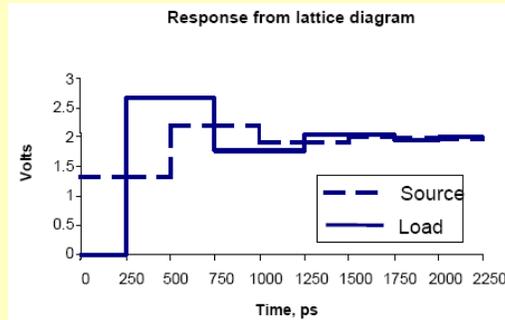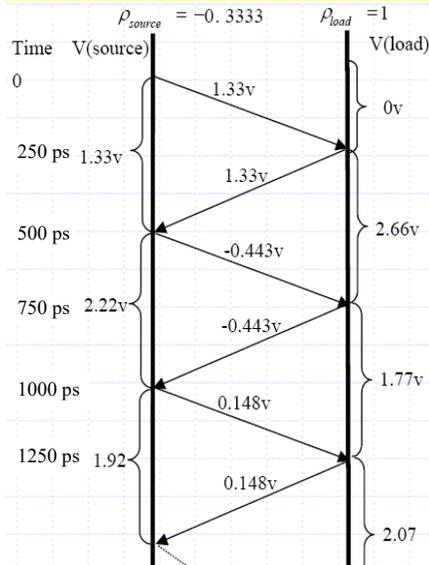

Dr. J. E. Rayas-Sánchez (S.H. Hall, G.W. Hall and J.A. McCall, High-Speed Digital System Design, Wiley, 2000) 19

Using the Bouncing Diagrams – Example

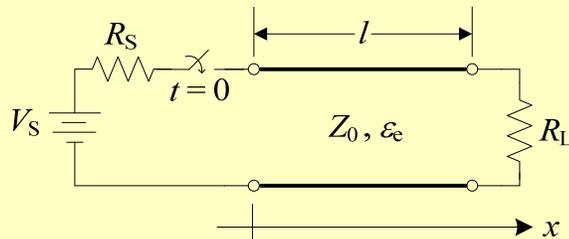

$$R_S = 25\Omega; R_L = 150\Omega;$$

$$V_S = 3V; Z_0 = 50\Omega;$$

$$\epsilon_e = 3; l = 15\text{cm}$$

$$v(x=0,t) = ?; v(x=l,t) = ?; v(x=\frac{3}{4}l,t) = ?$$


$$i(x=0,t) = ?; i(x=l,t) = ?; i(x=\frac{3}{4}l,t) = ?$$

Transient-Domain Analysis of Transmission Line Circuits (Part 1)

Dr. José Ernesto Rayas-Sánchez

March 28, 2020

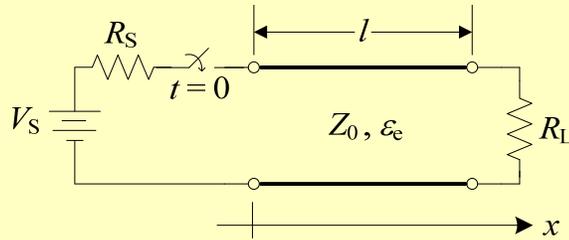Using the Bouncing Diagrams – Example (cont.)



$$R_S = 25\Omega; R_L = 150\Omega;$$

$$V_S = 3V; Z_0 = 50\Omega;$$

$$\epsilon_e = 3; l = 15\text{cm}$$


$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0} = \frac{1}{2} \quad \Gamma_S = \frac{R_S - Z_0}{R_S + Z_0} = -\frac{1}{3} \quad V_o^+ = \frac{V_S Z_0}{R_S + Z_0} = 2V$$

$$v_p = \frac{c}{\sqrt{\epsilon_e}} = 173.2\text{Mm/s} \quad t_d = \frac{l}{v_p} = 866.02\text{ps}$$

Dr. J. E. Rayas-Sánchez

21

Example Simulated with ADS

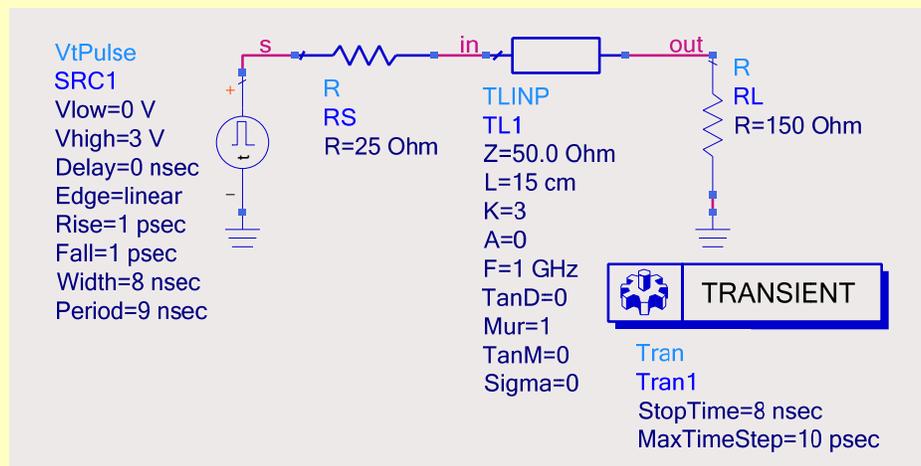

Dr. J. E. Rayas-Sánchez


22

Transient-Domain Analysis of Transmission Line Circuits (Part 1)

Dr. José Ernesto Rayas-Sánchez

March 28, 2020


Example Simulated with ADS (cont.)

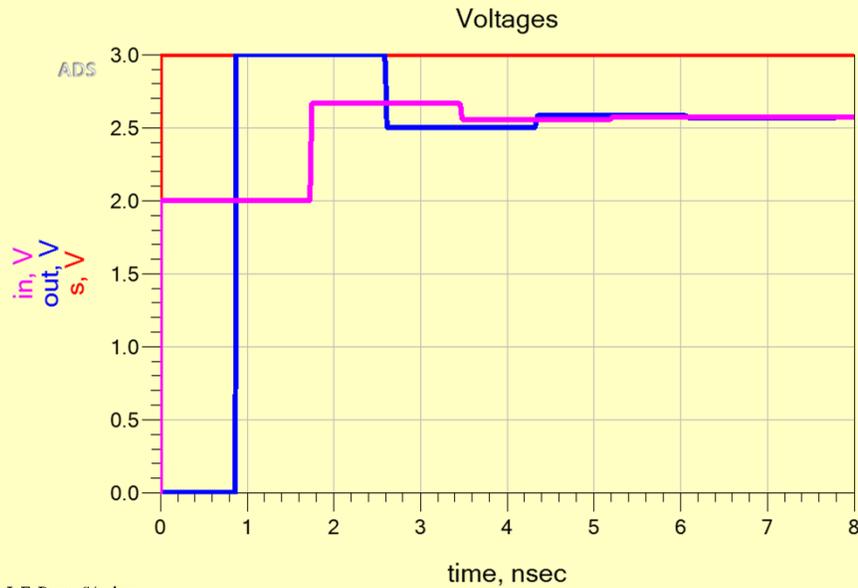

Dr. J. E. Rayas-Sánchez

23

Example Simulated with ADS (Currents)

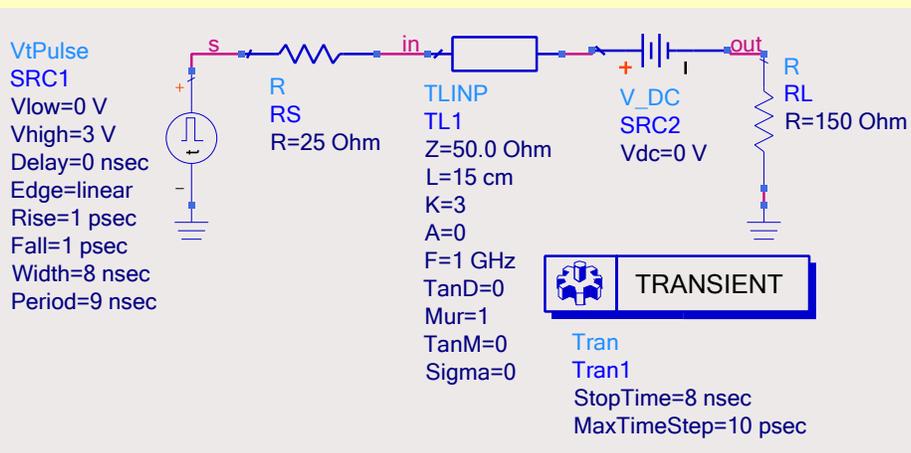

Dr. J. E. Rayas-Sánchez


24

Transient-Domain Analysis of Transmission Line Circuits (Part 1)


Dr. José Ernesto Rayas-Sánchez

March 28, 2020


Example Simulated with ADS (cont.)

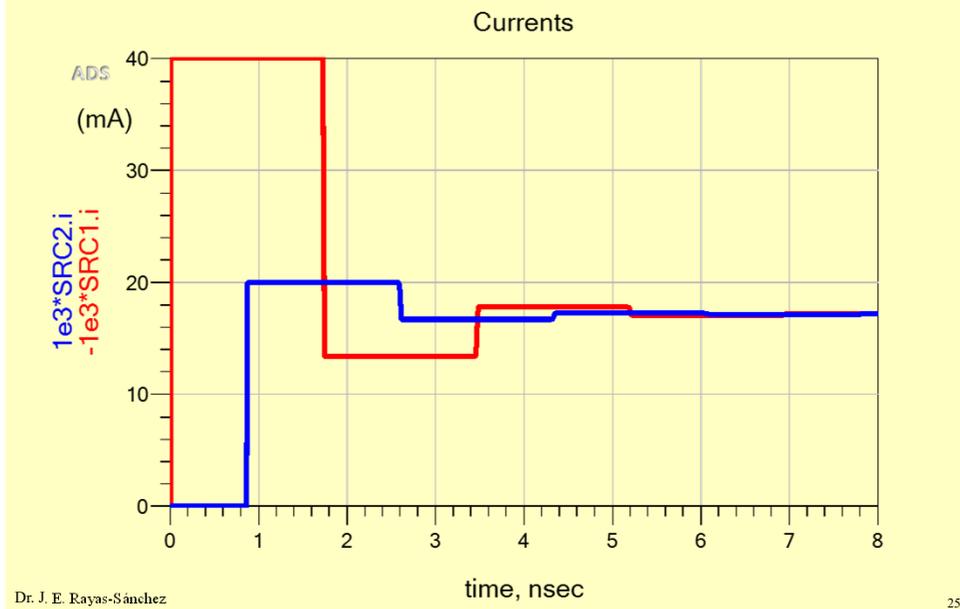

Ideal Case: Matched Source and Load

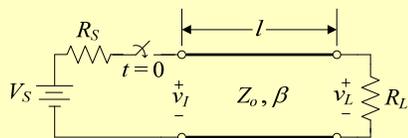
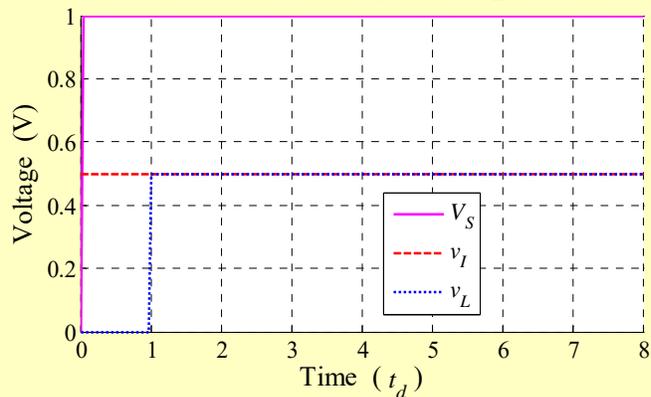
$$V_S = 1\text{V}, Z_o = 50\Omega, R_S = 50\Omega, R_L = 50\Omega$$




Transient-Domain Analysis of Transmission Line Circuits (Part 1)


Dr. José Ernesto Rayas-Sánchez

March 28, 2020

Matched Source, Open Load

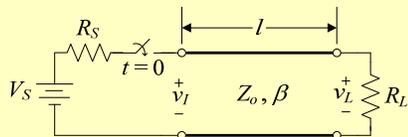

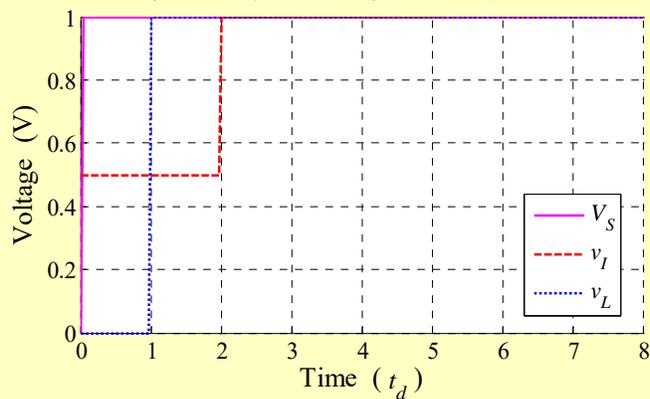
$$V_S = 1\text{V}, Z_o = 50\Omega, R_S = 50\Omega, R_L = 1\text{M}\Omega$$




Dr. J. E. Rayas-Sánchez

27

Matched Load, Short-Circuited Source

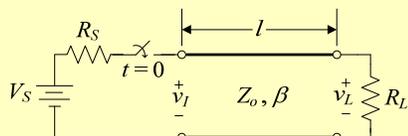
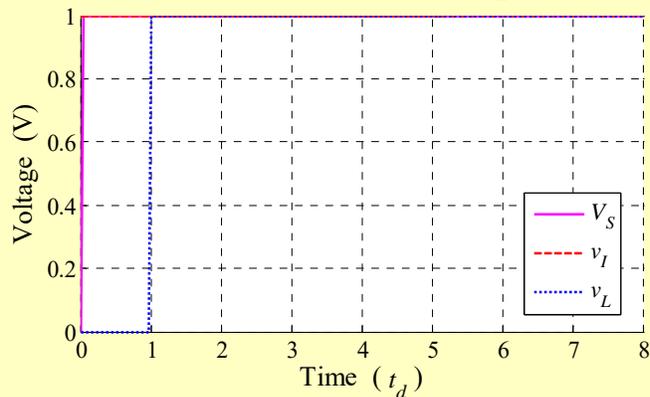
$$V_S = 1\text{V}, Z_o = 50\Omega, R_S = 0.1\Omega, R_L = 50\Omega$$



Dr. J. E. Rayas-Sánchez


28

Transient-Domain Analysis of Transmission Line Circuits (Part 1)


Dr. José Ernesto Rayas-Sánchez

March 28, 2020

Short-Circuited Source, Open Load

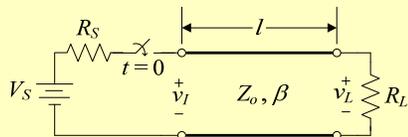

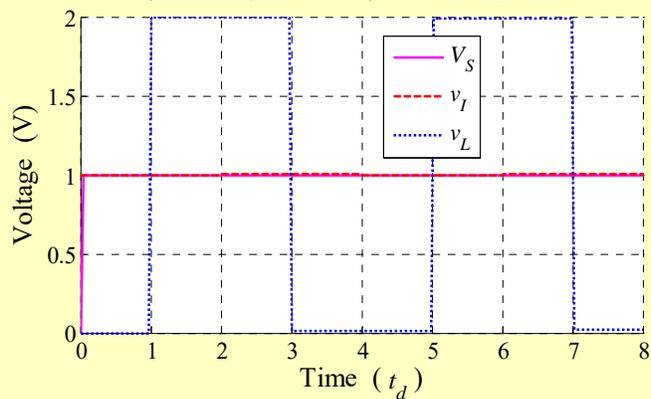
$$V_S = 1\text{V}, Z_o = 50\Omega, R_S = 0.1\Omega, R_L = 1\text{M}\Omega$$




Dr. J. E. Rayas-Sánchez

29

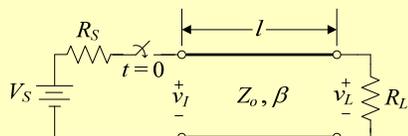Short-Circuited Source, Open Load (cont.)


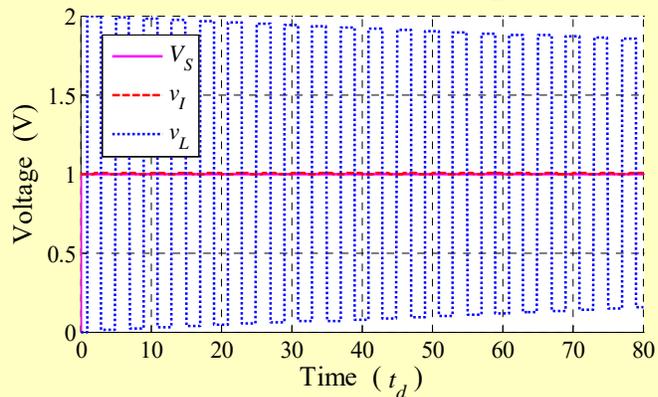
$$V_S = 1\text{V}, Z_o = 50\Omega, R_S = 0.1\Omega, R_L = 1\text{M}\Omega$$



Dr. J. E. Rayas-Sánchez

30