

Transient-Domain Analysis of Transmission Line Circuits (Part 2)

Dr. José Ernesto Rayas-Sánchez

March 30, 2020

Transient-Domain Analysis of Transmission Line Circuits

(Part 2)

Dr. José Ernesto Rayas-Sánchez

1

Outline


- Bouncing diagrams for one section of transmission line
- Bouncing diagrams for multiple sections of transmission lines
- Example of transient response in two sections of transmission lines

Transient-Domain Analysis of Transmission Line Circuits (Part 2)

Dr. José Ernesto Rayas-Sánchez

March 30, 2020


Lattice Diagrams for One TL Section

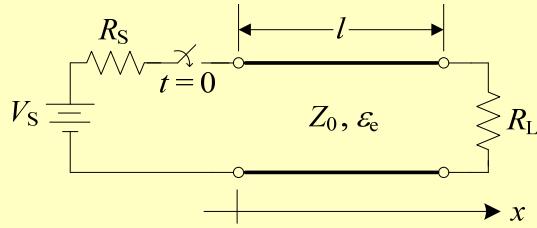

$$\Gamma_s = \frac{R_s - Z_o}{R_s + Z_o} \quad \Gamma_L = \frac{R_L - Z_o}{R_L + Z_o}$$

$$V_o^+ = \frac{V_s Z_o}{R_s + Z_o} \quad v_p = \frac{c}{\sqrt{\epsilon_e}}$$


$$t_d = \frac{l}{v_p}$$

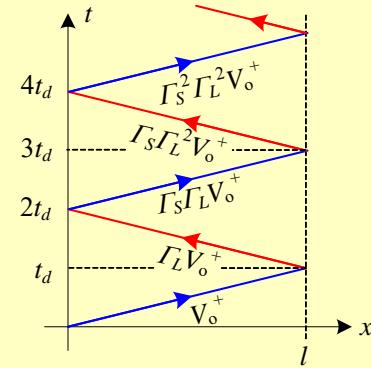

Dr. J. E. Rayas-Sánchez

3

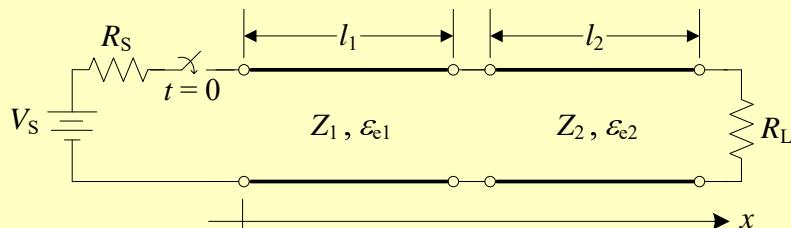Lattice Diagrams for Multiple TL Sections



$$\Gamma_s = \frac{R_s - Z_1}{R_s + Z_1} \quad \Gamma_L = \frac{R_L - Z_2}{R_L + Z_2} \quad \Gamma_p = \frac{Z_2 - Z_1}{Z_2 + Z_1} \quad \Gamma_N = \frac{Z_1 - Z_2}{Z_1 + Z_2} = -\Gamma_p$$

$$V_o^+ = \frac{V_s Z_1}{R_s + Z_1} \quad v_{p1} = \frac{c}{\sqrt{\epsilon_{e1}}} \quad v_{p2} = \frac{c}{\sqrt{\epsilon_{e2}}} \quad T_p = 1 + \Gamma_p$$


$$T_N = 1 + \Gamma_N$$

$$t_{d1} = \frac{l_1}{v_{p1}} \quad t_{d2} = \frac{l_2}{v_{p2}}$$

Dr. J. E. Rayas-Sánchez

4

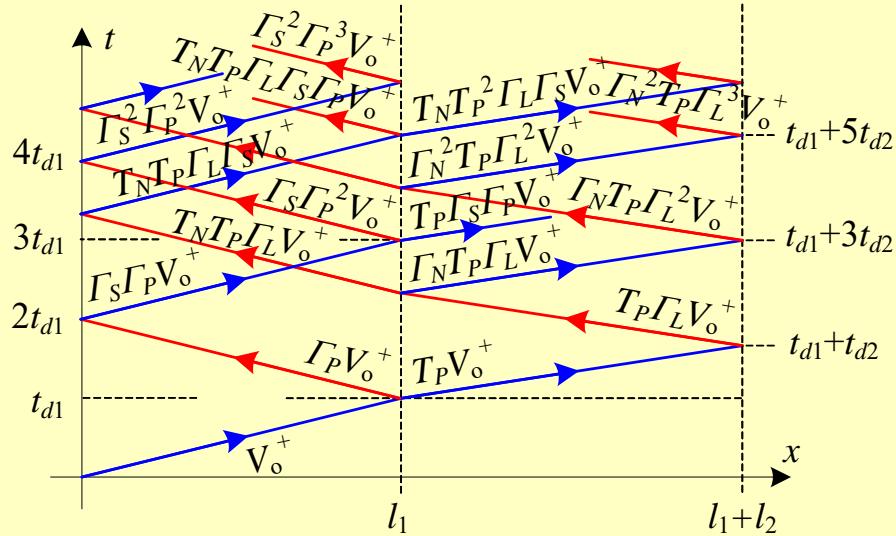
Lattice Diagrams for Multiple TL Sections (cont.)



Dr. J. E. Rayas-Sánchez

5

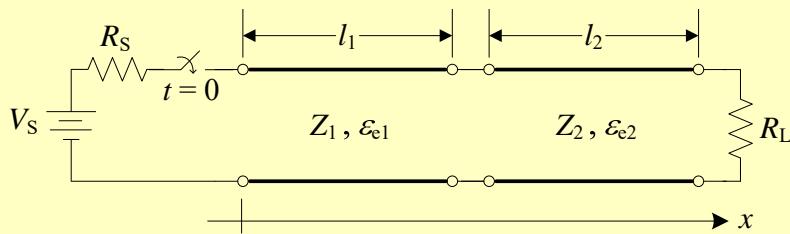Example of Transient Response in 2-TL Sections



$$R_S = 25\Omega; R_L = 150\Omega; V_S = 3V;$$

$$Z_1 = 50\Omega; Z_2 = 40\Omega;$$

$$\epsilon_{e1} = 3; \epsilon_{e2} = 3.5;$$

$$l_1 = 15\text{cm}; l_2 = 10\text{cm}$$

Dr. J. E. Rayas-Sánchez


6

Transient-Domain Analysis of Transmission Line Circuits (Part 2)

Dr. José Ernesto Rayas-Sánchez

March 30, 2020


Example Simulated with ADS

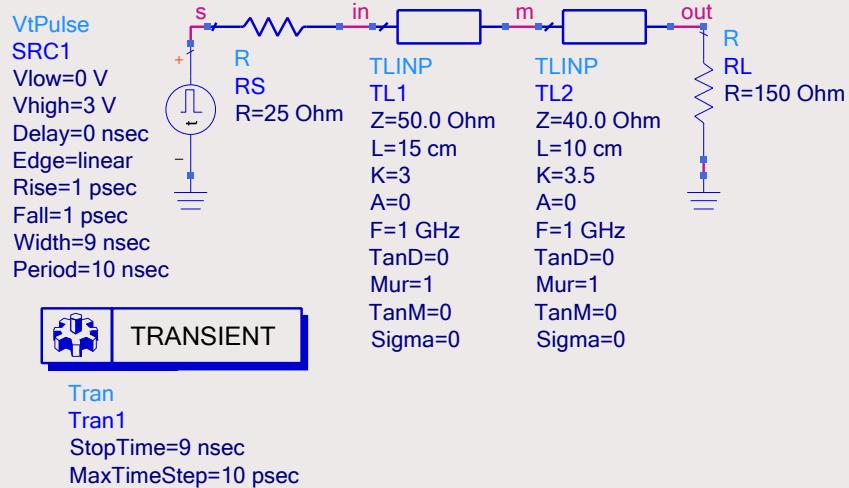

Dr. J. E. Rayas-Sánchez

7

Example Simulated with ADS (cont.)

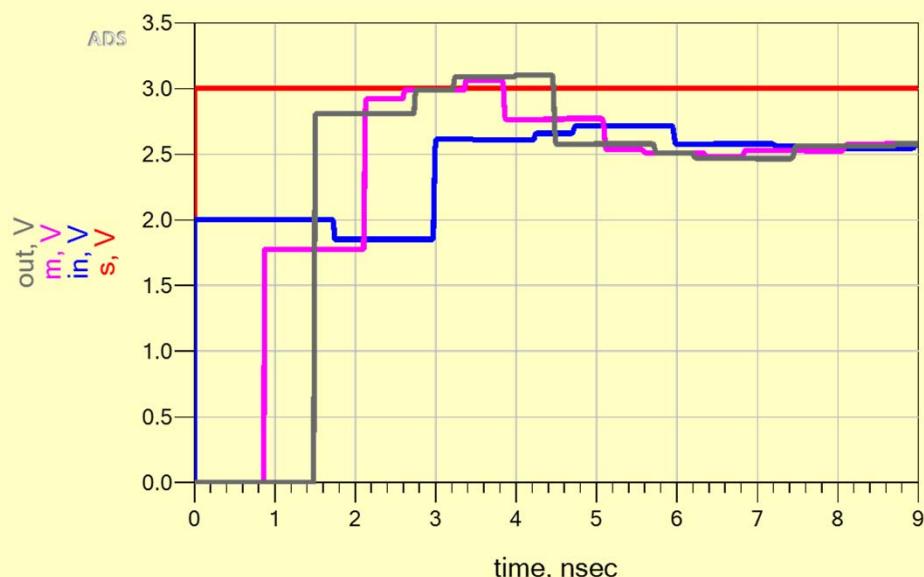

Dr. J. E. Rayas-Sánchez

8