TRANSMISSION LINE INPUT IMPEDANCE

Dr. J. E. Rayas-Sánchez Feb. 3, 2017

VARIATION OF THE TRANSMISSION LINE INPUT IMPEDANCE WITH FREQUENCY AND LENGTH

The input impedance is given by

Consider the following lossless transmission line circuit.



 $Z_{in}(l) = Z_0 \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)}$ where Z_0 is the characteristic impedance of the transmission line, Z_L is the load impedance, β is the propagation constant, and l is the physical length. The effective permittivity is ε_e . Let $Z_0 = 50 \Omega$, and $\varepsilon_e = 4$.

Fixed frequency, f = 2 GHz, varying length:



Notice that, in this case, $\frac{\lambda}{4} = \frac{v_p}{4f} = \frac{c}{4f\sqrt{\varepsilon_e}} = \frac{0.3 \text{Gm/s}}{4(2\text{GHz})\sqrt{4}} = 1.875 \text{ cm}.$

Dr. J. E. Rayas-Sánchez



Fixed length, l = 2.5 cm, varying frequency:

Since $\frac{\lambda}{4} = \frac{v_{\rm p}}{4f} = \frac{c}{4f\sqrt{\varepsilon_{\rm e}}}$, then the frequency at which $l = \lambda/4$ is $f = \frac{c}{4l\sqrt{\varepsilon_{\rm e}}} = \frac{0.3 \text{Gm/s}}{4(2.5 \text{cm})\sqrt{4}} = 1.5 \text{ GHz}.$