

Frequency-Domain Analysis of Transmission Line Circuits

(Part 1)


Dr. José Ernesto Rayas Sánchez

1

Outline

- N -port networks
- Impedance matrix representation
- Admittance matrix representation
- Scattering matrix representation
- Meaning of the S-parameters
- Generalized S-parameters


An N-port High-Speed Network

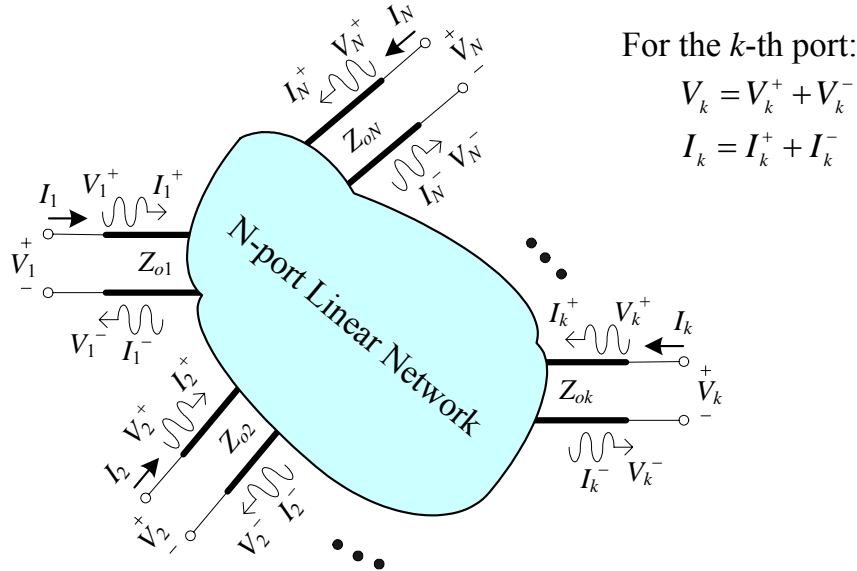

Dr. J.E. Rayas Sánchez

3

Examples of N-port Networks

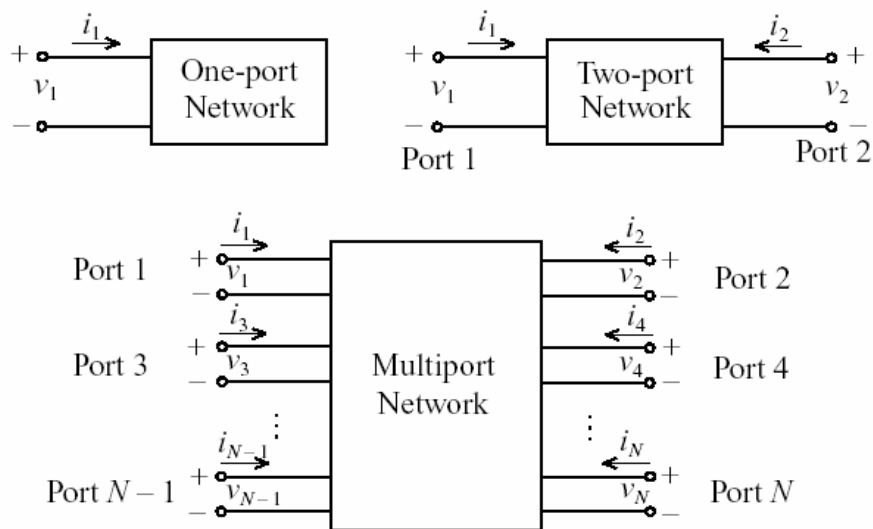

Dr. J.E. Rayas Sánchez

(R. Ludwig and P. Bretchko, *RF Circuit Design*, Prentice Hall, 2000) 4

Impedance Matrix Representation (\mathbf{Z})

$$\mathbf{V} = \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix} \quad \mathbf{I} = \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix} \quad \mathbf{V} = \mathbf{Z}\mathbf{I}$$
$$\mathbf{Z} = \begin{bmatrix} Z_{11} & Z_{12} & \dots & Z_{1N} \\ Z_{21} & Z_{22} & \dots & Z_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ Z_{N1} & Z_{N2} & \dots & Z_{NN} \end{bmatrix}$$

Each element of matrix \mathbf{Z} is given by

$$Z_{ij} = \left. \frac{V_i}{I_j} \right|_{I_k=0 \text{ for } k \neq j}$$

Admittance Matrix Representation (\mathbf{Y})

$$\mathbf{V} = \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix} \quad \mathbf{I} = \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix} \quad \mathbf{I} = \mathbf{Y}\mathbf{V}$$
$$\mathbf{Y} = \begin{bmatrix} Y_{11} & Y_{12} & \dots & Y_{1N} \\ Y_{21} & Y_{22} & \dots & Y_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ Y_{N1} & Y_{N2} & \dots & Y_{NN} \end{bmatrix}$$

Each element of matrix \mathbf{Y} is given by

$$Y_{ij} = \left. \frac{I_i}{V_j} \right|_{V_k=0 \text{ for } k \neq j}$$

Some Properties of the Z and Y Matrices

- If the network is reciprocal (not containing any nonreciprocal media such as ferrites or plasmas), then Z and Y are symmetric,

$$Z_{ij} = Z_{ji} \quad Y_{ij} = Y_{ji}$$


- If the network is lossless, all the elements in Z and Y are purely imaginary
- In most practical cases, high-speed interconnects can be considered as reciprocal networks, and in many cases, lossless networks

Dr. J.E. Rayas Sánchez

7

The Scattering Matrix Representation (S)

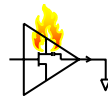- They can be more easily obtained at high frequencies:
 - Incident and reflected waves can be measured using a Vector Network Analyzer (VNA)
 - They do not require “shorts” or “opens” (active devices might oscillate or self-destroy)




- They are more directly related to high-frequency effects (Γ , T , IL , RL , SWR , etc.)
- We can convert back and forth between S , Y and Z parameters

Dr. J.E. Rayas Sánchez

8

The Scattering Matrix (S)

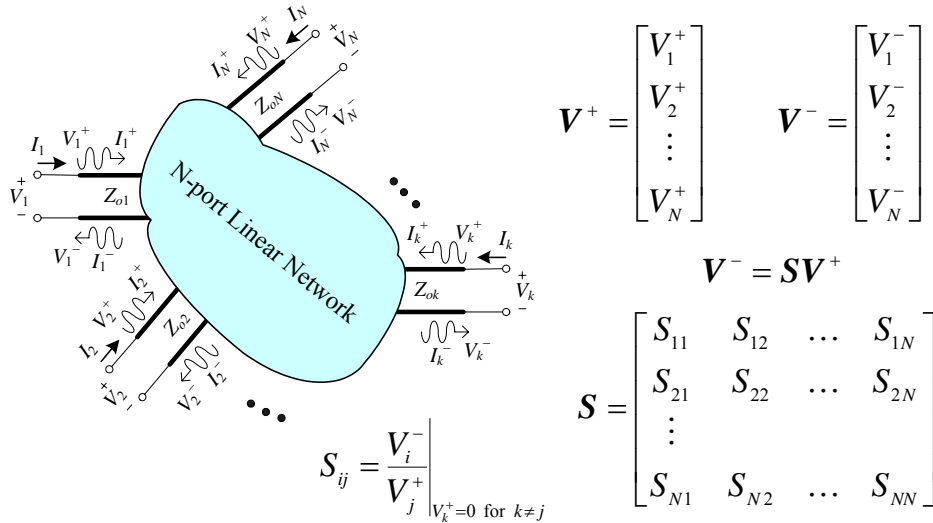

$V_k^+ = 0$ if we terminate port k with a matched load ($Z_{LK} = Z_{ok}$)

Dr. J.E. Rayas Sánchez

9

Meaning of the S-parameters

- S_{ii} represents the reflection coefficient at port i when all the remaining ports are terminated with matched loads
- S_{ij} represents the transmission coefficient from port j to port i when all the other ports are terminated with matched loads

Dr. J.E. Rayas Sánchez

10

Meaning of the S-parameters (cont)

- S11 = forward reflection coefficient (**input match**)
 S22 = reverse reflection coefficient (**output match**)
 S21 = forward transmission coefficient (**gain or loss**)
 S12 = reverse transmission coefficient (**isolation**)

$$S_{ii} \neq \Gamma_i \quad S_{ii} = \left. \frac{V_i^-}{V_i^+} \right|_{V_k^+ = 0 \text{ for } k \neq i} = \Gamma_i \Big|_{V_k^+ = 0 \text{ for } k \neq i}$$

$$S_{ij} \neq T_{ji} \quad S_{ij} = \left. \frac{V_i^-}{V_j^+} \right|_{V_k^+ = 0 \text{ for } k \neq j} = T_{ji} \Big|_{V_k^+ = 0 \text{ for } k \neq j}$$

Conversion between S and Y and Z Matrices

$$\left. \begin{aligned} S &= (\mathbf{Z} + \mathbf{I})^{-1}(\mathbf{Z} - \mathbf{I}) \\ \mathbf{Z} &= (\mathbf{I} - \mathbf{S})^{-1}(\mathbf{I} + \mathbf{S}) \end{aligned} \right\} \begin{array}{l} \text{(normalized } \mathbf{Z}, \\ \text{assuming all ports} \\ \text{have the same } Z_o) \end{array}$$

where \mathbf{I} is the identity matrix (N by N)

$$\mathbf{Z} = \mathbf{Y}^{-1}$$

$$\mathbf{Y} = \mathbf{Z}^{-1}$$

Conversion between S and Y and Z (cont)

$$\mathbf{S} = (\mathbf{Z}\mathbf{Y}_o + \mathbf{I})^{-1}(\mathbf{Z}\mathbf{Y}_o - \mathbf{I})$$

$$\mathbf{Z} = \mathbf{Y}_o^{-1}(\mathbf{I} - \mathbf{S})^{-1}(\mathbf{I} + \mathbf{S})$$

where \mathbf{I} is the identity matrix (N by N) and

$$\mathbf{Y}_o = \text{diag}(1/Z_{o1} \quad 1/Z_{o2} \quad \dots \quad 1/Z_{oN})$$

$$\mathbf{Z} = \mathbf{Y}^{-1}$$

$$\mathbf{Y} = \mathbf{Z}^{-1}$$

Some Properties of the S Matrix

- If the network is reciprocal (not containing any nonreciprocal media such as ferrites or plasmas), then S is symmetric,

$$S_{ij} = S_{ji}$$

- If the network is lossless, matrix S is unitary (orthonormal complex)

$$\sum_{k=1}^N S_{ki} S_{ki}^* = 1 \quad \sum_{k=1}^N S_{ki} S_{kj}^* = 0$$

- In most practical cases, high-speed interconnects can be considered as reciprocal networks, and in some cases, lossless networks

Generalized Scattering Parameters

- In many practical cases,

$$Z_{o1} = Z_{o2} = \dots = Z_{oN} = Z_o = 50\Omega$$

- If Z_o is different for each port, we define the incident and reflected waves at the k -th port as

$$a_k = \frac{V_k^+}{\sqrt{Z_{ok}}} \quad b_k = \frac{V_k^-}{\sqrt{Z_{ok}}}$$

- The total voltage and current at port k -th are

$$V_k = V_k^+ + V_k^- = (a_k + b_k)\sqrt{Z_{ok}}$$
$$I_k = I_k^+ + I_k^- = \frac{V_k^+}{Z_{ok}} - \frac{V_k^-}{Z_{ok}} = (a_k - b_k)/\sqrt{Z_{ok}}$$

Dr. J.E. Rayas Sánchez

15

Generalized Scattering Parameters (cont)

$$V_k = (a_k + b_k)\sqrt{Z_{ok}} \quad I_k = (a_k - b_k)/\sqrt{Z_{ok}}$$

- The average power delivered to the k -th port is

$$P_k = \frac{1}{2} \operatorname{Re}\{V_k I_k^*\}$$
$$P_k = \frac{1}{2} \operatorname{Re}\{|a_k|^2 - |b_k|^2 + (b_k a_k^* - a_k b_k^*)\} = \frac{1}{2} |a_k|^2 - \frac{1}{2} |b_k|^2$$

(incident power minus reflected power)

Dr. J.E. Rayas Sánchez

16

Generalized Scattering Parameters - Summary

- The Generalized Scattering Matrix relates the incident and reflected waves

$$\mathbf{b} = \mathbf{S}\mathbf{a}$$
$$\mathbf{a} = \begin{bmatrix} a_1 \\ \vdots \\ a_N \end{bmatrix} \quad \mathbf{b} = \begin{bmatrix} b_1 \\ \vdots \\ b_N \end{bmatrix} \quad S_{ij} = \left. \frac{b_i}{a_j} \right|_{V_k^+ = 0 \text{ for } k \neq j}$$
$$a_j = \frac{V_j^+}{\sqrt{Z_{oj}}} \quad b_i = \frac{V_i^-}{\sqrt{Z_{oi}}}$$

- To convert from the original S-parameters to generalized S-parameters

$$S_{ij} = \left. \frac{V_i^- \sqrt{Z_{oj}}}{V_j^+ \sqrt{Z_{oi}}} \right|_{V_k^+ = 0 \text{ for } k \neq j}$$