

Frequency-Domain Analysis of Transmission Line Circuits

(Part 2)

Dr. José Ernesto Rayas Sánchez

1

Outline


- The transmission or ABCD matrix
- ABCD parameters
- Cascaded connections of 2-port networks
- Conversion between ABCD, Z, Y, and S parameters
- Analyzing interconnects with discontinuities
- Microstrip discontinuities
- Waveguide discontinuities

The Transmission Matrix (ABCD Parameters)

- Many practical high-frequency circuits consists of cascaded connections of two or more two-port networks
- The Transmission Matrix, or ABCD Parameters, or Chain Parameters, are very convenient for analyzing cascaded two-port circuits

Definition of ABCD Parameters

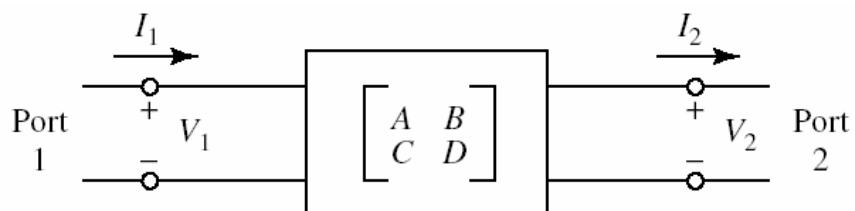- The ABCD matrix is defined for two-port networks, as follows:




$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} \quad A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad B = \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} \quad D = \left. \frac{I_1}{I_2} \right|_{V_2=0}$$

Cascaded Connections of Two-Port Networks

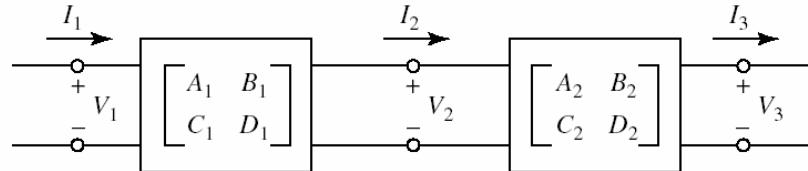- The ABCD matrix of a cascaded connection is the multiplication of the corresponding ABCD matrices:




$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} \quad \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

Dr. J.E. Rayas Sánchez

5

Converting ABCD to other Parameters

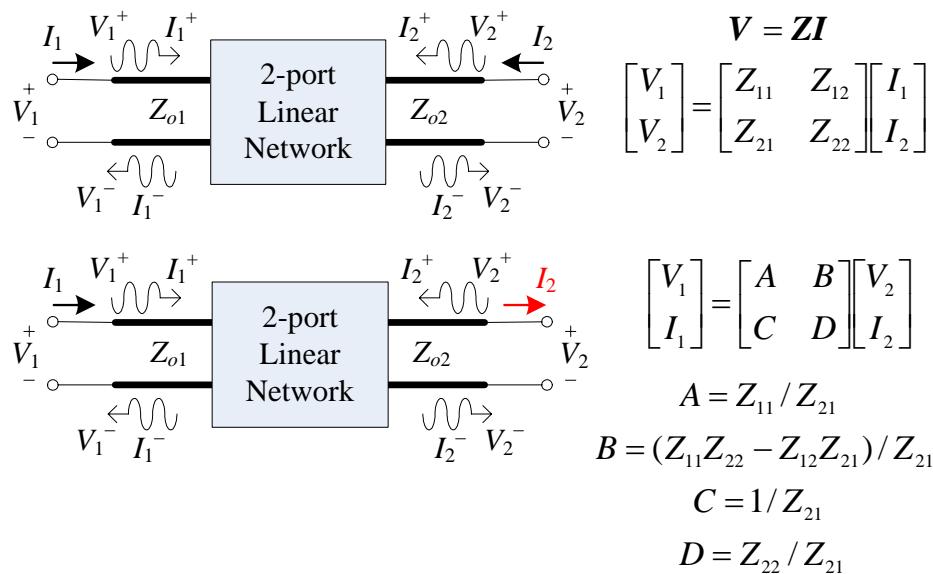

Dr. J.E. Rayas Sánchez

6

Properties of the ABCD Matrix



- If the 2-port network is lossless, A and D are real, B and C are imaginary
- If the 2-port network is reciprocal, the determinant of the ABCD matrix is one

$$AD - BC = 1$$



Converting Between Different Parameters

	[Z]	[Y]	[h]	[ABCD]
[Z]	$Z_{11} Z_{12}$ $Z_{21} Z_{22}$	$\frac{Z_{22}}{\Delta Z} - \frac{Z_{12}}{\Delta Z}$ $\frac{Z_{21}}{\Delta Z} \frac{Z_{11}}{\Delta Z}$	$\frac{\Delta Z}{Z_{22}} \frac{Z_{12}}{Z_{22}}$ $\frac{Z_{21}}{Z_{22}} \frac{1}{Z_{22}}$	$\frac{Z_{11}}{Z_{21}} \frac{\Delta Z}{Z_{21}}$ $\frac{1}{Z_{21}} \frac{Z_{22}}{Z_{21}}$
[Y]	$\frac{Y_{22}}{\Delta Y} - \frac{Y_{12}}{\Delta Y}$ $\frac{Y_{21}}{\Delta Y} \frac{Y_{11}}{\Delta Y}$	$Y_{11} Y_{12}$ $Y_{21} Y_{22}$	$\frac{1}{Y_{11}} - \frac{Y_{12}}{Y_{11}}$ $\frac{Y_{21}}{Y_{11}} \frac{\Delta Y}{Y_{11}}$	$\frac{Y_{22}}{Y_{21}} - \frac{1}{Y_{21}}$ $\frac{\Delta Y}{Y_{21}} \frac{Y_{11}}{Y_{21}}$
[h]	$\frac{\Delta h}{h_{22}} \frac{h_{12}}{h_{22}}$ $\frac{h_{21}}{h_{22}} \frac{1}{h_{22}}$	$\frac{1}{h_{11}} \frac{h_{12}}{h_{11}}$ $\frac{h_{21}}{h_{11}} \frac{\Delta h}{h_{11}}$	$h_{11} h_{12}$ $h_{21} h_{22}$	$\frac{\Delta h}{h_{21}} \frac{h_{11}}{h_{21}}$ $\frac{h_{22}}{h_{21}} - \frac{1}{h_{21}}$
[ABCD]	$\frac{A}{C} \frac{\Delta ABCD}{C}$ $\frac{1}{C} \frac{D}{C}$	$\frac{D}{B} - \frac{\Delta ABCD}{B}$ $-\frac{1}{B} \frac{A}{B}$	$\frac{B}{D} \frac{\Delta ABCD}{D}$ $-\frac{1}{D} \frac{C}{D}$	$\Delta Z = \text{Det}(Z)$ $\Delta Y = \text{Det}(Y)$ $\Delta h = \text{Det}(H)$


ABCD Parameters for Useful Circuits

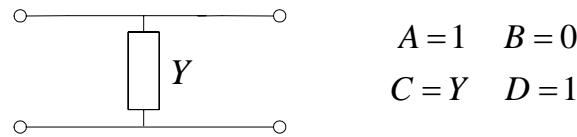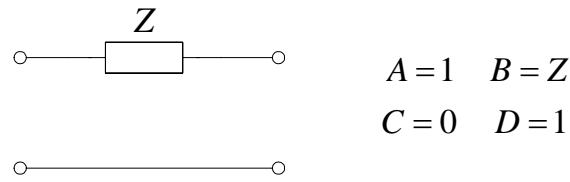

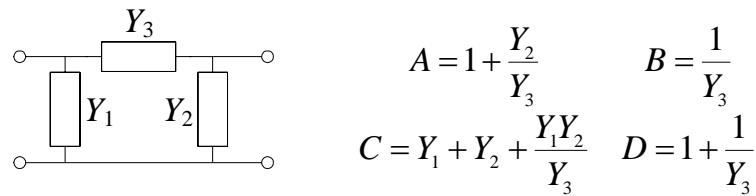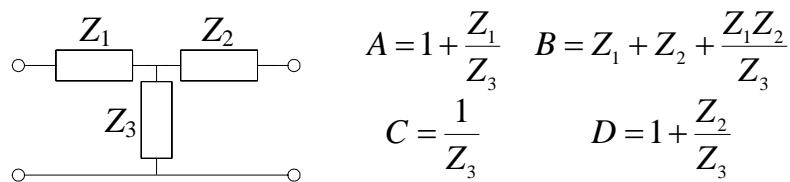
ABCD Parameters for Useful Circuits (cont)



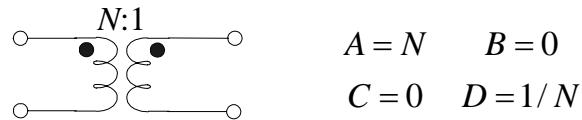ABCD Parameters for Useful Circuits (cont)


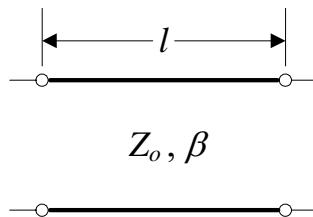
$$A = N \quad B = 0 \\ C = 0 \quad D = 1/N$$




$$A = \cos \beta l \quad B = jZ_o \sin \beta l \\ C = jY_o \sin \beta l \quad D = \cos \beta l$$

Analyzing Interconnects

As a first-order approximation (“hand” calculations),

- Uniform interconnects can be modeled by transmission lines (usually lossless)
- Transitions or discontinuities can be modeled by equivalent lumped circuits (estimating their values by formulae or by curve-fitting), or directly by Z, Y, or ABCD matrices obtained from measured S parameters
- Each section is represented by its ABCD matrix, Z matrix or Y matrix
- Calculations are performed by combining the corresponding matrices

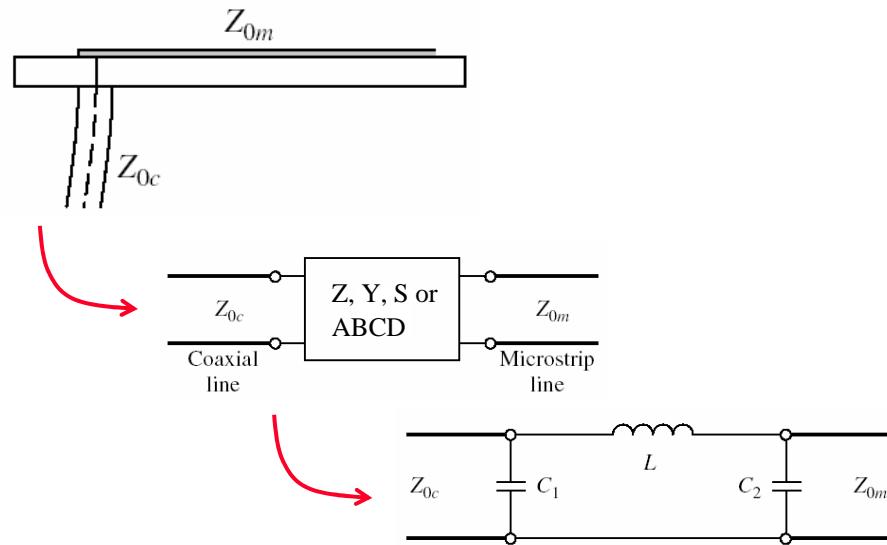
Modeling Interconnects with Transitions – Ex. 1



Dr. J.E. Rayas Sánchez

13


Microstrip Discontinuities

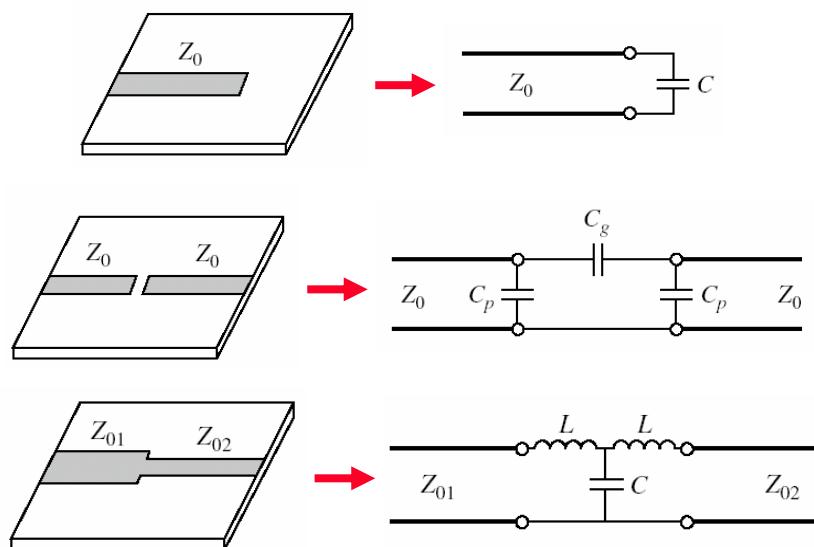

Dr. J.E. Rayas Sánchez

(D. M. Pozar, *Microwave Engineering*, Wiley, 2005) 14


Microstrip Discontinuities (cont)

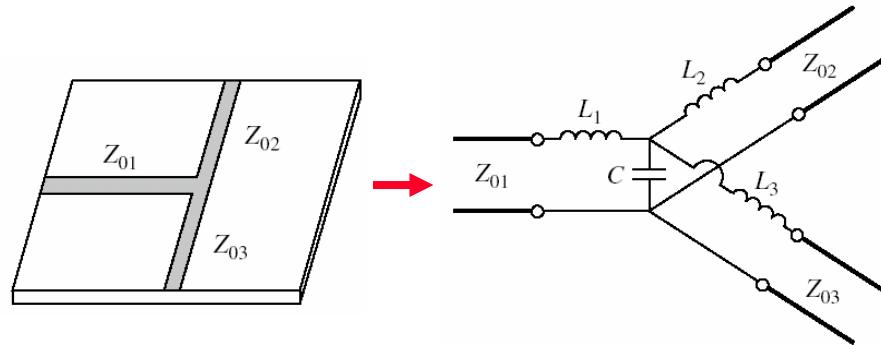

Dr. J.E. Rayas Sánchez

(D. M. Pozar, *Microwave Engineering*, Wiley, 2005) ₁₅


Rectangular Waveguide Discontinuities

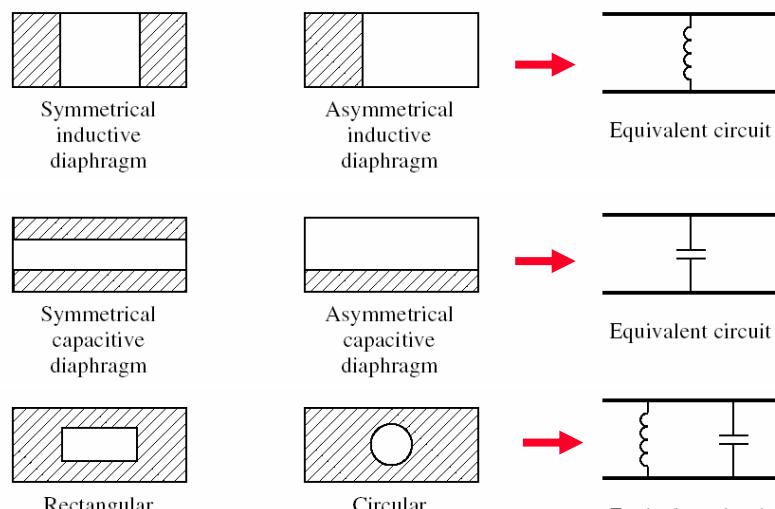


Dr. J.E. Rayas Sánchez

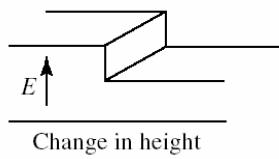(D. M. Pozar, *Microwave Engineering*, Wiley, 2005) ₁₆


Rectangular Waveguide Discontinuities (cont)




Change in height

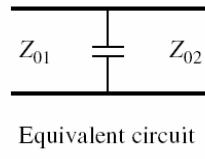

Equivalent circuit

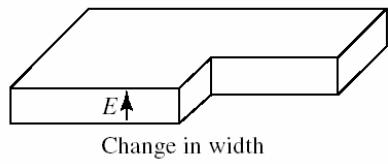

Change in width

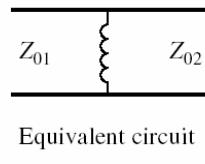

Equivalent circuit