

Frequency-Domain Analysis of Transmission Line Circuits

(Part 3)

Dr. José Ernesto Rayas Sánchez

1


Outline

- Differential transmission lines
- Common mode signaling
- Differential mode signaling
- Mode conversion
- Even and odd modes
- 2-coupled lossless transmission line theory
- Termination techniques
- Differential or Mixed-Mode S-parameters

Differential Transmission Lines

For high data rates, differential signaling is more used due to:

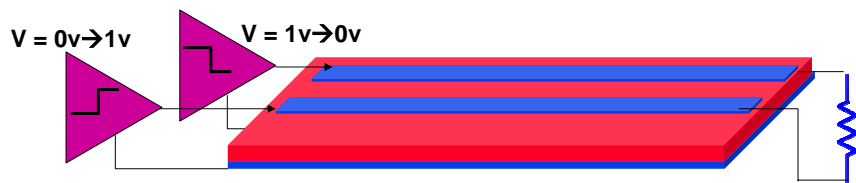
- Radiation is reduced (cancellation of fields)
- Receiver rejects signals that are common to both lines (high CMRR at the receiver)
- Signal voltage amplitudes can be smaller



Dr. J.E. Rayas Sánchez

(M. Resso, 2005) ₃

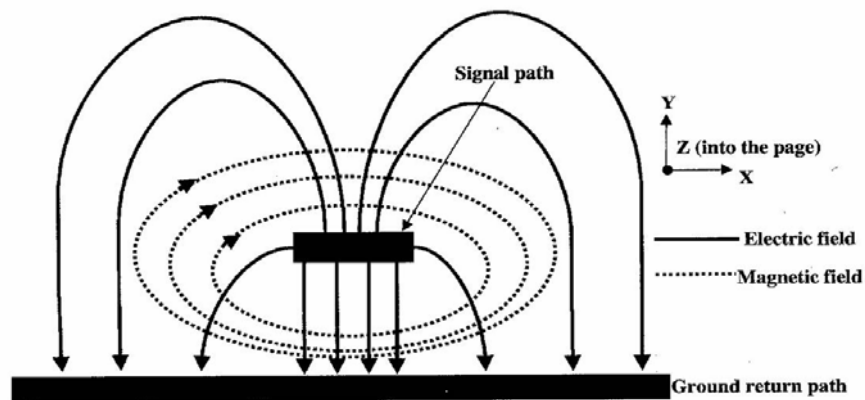Electromagnetic Fields in a Microstrip Line




Dr. J.E. Rayas Sánchez

4

Common Mode Signaling

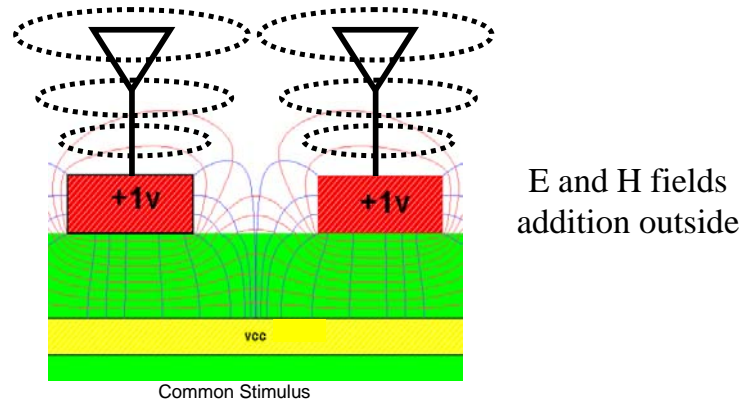As data rates go up, frequencies increase, lines become antennas (both send and receive) and corrupt the communication (BER, crosstalk, etc)




Dr. J.E. Rayas Sánchez

(M. Resso, 2005) ₅

Differential Mode Signaling

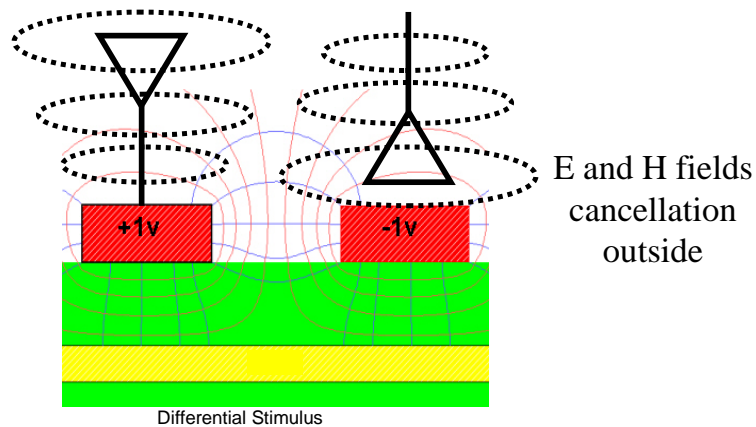Using differential excitations (differential transmission lines), most of the outside electromagnetic field cancels




Dr. J.E. Rayas Sánchez

(M. Resso, 2005) ₆

Mode Conversion

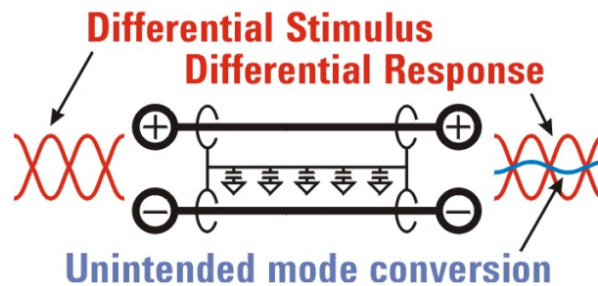- Is produced by asymmetries in the differential pairs
- Can cause a differential signal to be converted to a common mode signal (radiation, crosstalk, etc.)




Dr. J.E. Rayas Sánchez

(M. Resso, 2005) ₇

Even Mode and Odd Mode

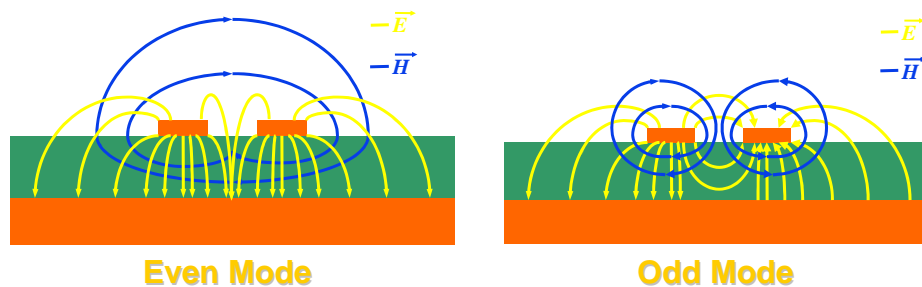- Practical differential pairs operate at even and odd modes simultaneously
- Even mode – excited in phase with equal amplitudes
- Odd mode – driven 180° out of phase with equal amplitudes




Dr. J.E. Rayas Sánchez

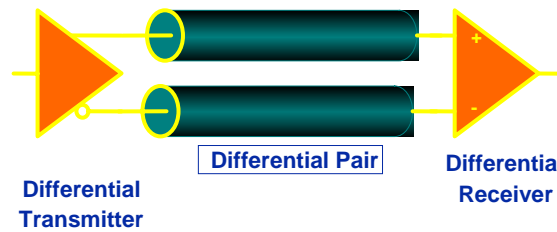(H. Heck 2002) ₈

Differential Signaling for High-Speed Links


- Differential signaling can operate at much higher data rates
- High speed links operating in excess of ~1 Gb/s use differential signaling (e.g. Infiniband, PCI-Express).
- In fact, differential signals are already used for high speed clocks in desktop



Dr. J.E. Rayas Sánchez

(H. Heck 2002) 9

Lossless Transmission Lines

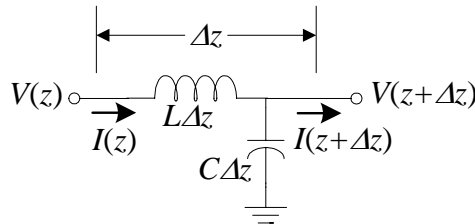

$$\frac{dV(z)}{dz} = -(j\omega L)I(z)$$

$$\frac{dI(z)}{dz} = -(j\omega C)V(z)$$

$$\frac{dV}{dz} = -j\omega LI$$

$$\frac{dI}{dz} = -j\omega CV$$

$$V(z) = V_o^+ e^{-j\beta z} + V_o^- e^{+j\beta z}$$

$$I(z) = I_o^+ e^{-j\beta z} + I_o^- e^{+j\beta z}$$

$$\beta = \omega\sqrt{LC}$$

$$Z_o = \sqrt{\frac{L}{C}} \quad v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$


$$-\frac{d}{dz} \begin{bmatrix} V \\ I \end{bmatrix} = \begin{bmatrix} 0 & Z_L \\ Y_C & 0 \end{bmatrix} \begin{bmatrix} V \\ I \end{bmatrix}$$

$$Z_L = j\omega L \quad Y_C = j\omega C$$

Dr. J.E. Rayas Sánchez

10

2-Coupled Lossless Symmetrical TLs

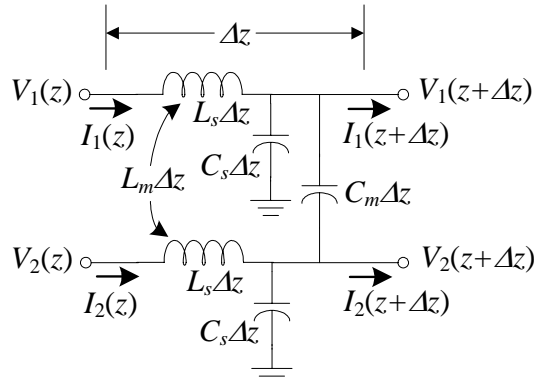

$$\frac{dV_1}{dz} = -j\omega L_s I_1 - j\omega L_m I_2$$

$$\frac{dI_1}{dz} = -j\omega(C_s + C_m)V_1 + j\omega C_m V_2$$

$$\frac{dV_2}{dz} = -j\omega L_m I_1 - j\omega L_s I_2$$

$$\frac{dI_2}{dz} = +j\omega C_m V_1 - j\omega(C_s + C_m)V_2$$

Dr. J.E. Rayas Sánchez

11

2-Coupled Lossless Symmetrical TLs (cont)

$$\frac{dV_1}{dz} = -j\omega L_s I_1 - j\omega L_m I_2$$

$$\frac{dV_2}{dz} = -j\omega L_m I_1 - j\omega L_s I_2$$

$$\frac{dI_1}{dz} = -j\omega(C_s + C_m)V_1 + j\omega C_m V_2$$

$$\frac{dI_2}{dz} = +j\omega C_m V_1 - j\omega(C_s + C_m)V_2$$

$$\mathbf{V} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \mathbf{I} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\mathbf{Y}_C = j\omega \begin{bmatrix} (C_s + C_m) & -C_m \\ -C_m & (C_s + C_m) \end{bmatrix}$$

$$\mathbf{Z}_L = j\omega \begin{bmatrix} L_s & L_m \\ L_m & L_s \end{bmatrix}$$

$$-\frac{d}{dz} \begin{bmatrix} \mathbf{V} \\ \mathbf{I} \end{bmatrix} = \begin{bmatrix} \mathbf{0} & \mathbf{Z}_L \\ \mathbf{Y}_C & \mathbf{0} \end{bmatrix} \begin{bmatrix} \mathbf{V} \\ \mathbf{I} \end{bmatrix}$$

Dr. J.E. Rayas Sánchez

12

LC Matrices of 2-Coupled TLs

$$\mathbf{C} = \begin{bmatrix} C_{11} & C_{12} \\ C_{21} & C_{22} \end{bmatrix} = \begin{bmatrix} (C_s + C_m) & -C_m \\ -C_m & (C_s + C_m) \end{bmatrix}$$

$$\mathbf{L} = \begin{bmatrix} L_{11} & L_{12} \\ L_{21} & L_{22} \end{bmatrix} = \begin{bmatrix} L_s & L_m \\ L_m & L_s \end{bmatrix}$$

$$Z_o = ?$$

$$v_p = ?$$

Dr. J.E. Rayas Sánchez

13

Even Mode in 2-Coupled Symmetrical TLs

$$\frac{dV_1}{dz} = -j\omega L_s I_1 - j\omega L_m I_2$$

$$\frac{dV_2}{dz} = -j\omega L_m I_1 - j\omega L_s I_2$$

$$\frac{dI_1}{dz} = -j\omega(C_s + C_m)V_1 + j\omega C_m V_2$$

$$\frac{dI_2}{dz} = j\omega C_m V_1 - j\omega(C_s + C_m)V_2$$

Since $V_1 = V_2$ and $I_1 = I_2$

$$\frac{dV_1}{dz} = -j\omega(L_s + L_m)I_1$$

$$\frac{dI_1}{dz} = -j\omega C_s V_1$$

The effective L and C are

$$L_{eff} = L_s + L_m$$

$$C_{eff} = C_s$$

Hence


$$Z_{o-even} = \sqrt{\frac{L_s + L_m}{C_s}}$$

$$v_{p-even} = \frac{1}{\sqrt{(L_s + L_m)C_s}}$$

Dr. J.E. Rayas Sánchez

14

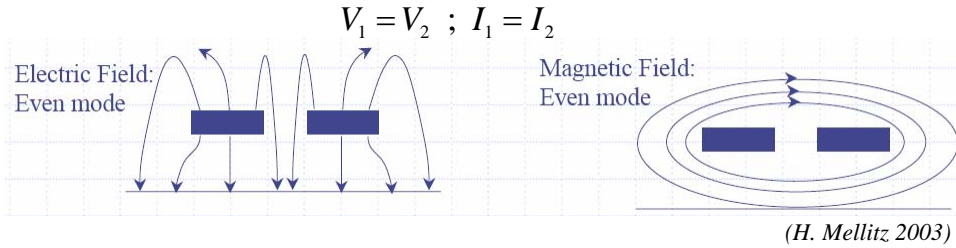Even Mode in 2-Coupled Symmetrical TLs (cont)



$$Z_{o-even} = \sqrt{\frac{L_s + L_m}{C_s}} \quad v_{p-even} = \frac{1}{\sqrt{(L_s + L_m)C_s}}$$

Z_{o-even} is the characteristic impedance of one of the conductors when the coupled line is operated in even mode

Odd Mode in 2-Coupled Symmetrical TLs

$$\begin{aligned} \frac{dV_1}{dz} &= -j\omega L_s I_1 - j\omega L_m I_2 & \frac{dV_2}{dz} &= -j\omega L_m I_1 - j\omega L_s I_2 \\ \frac{dI_1}{dz} &= -j\omega(C_s + C_m)V_1 + j\omega C_m V_2 & \frac{dI_2}{dz} &= j\omega C_m V_1 - j\omega(C_s + C_m)V_2 \end{aligned}$$

Since $V_1 = -V_2$ and $I_1 = -I_2$

$$\begin{aligned} \frac{dV_1}{dz} &= -j\omega(L_s - L_m)I_1 & \frac{dI_1}{dz} &= -j\omega(C_s + 2C_m)V_1 \end{aligned}$$


The effective L and C are

$$L_{eff} = L_s - L_m \quad C_{eff} = C_s + 2C_m$$

Hence

$$Z_{o-odd} = \sqrt{\frac{L_s - L_m}{C_s + 2C_m}} \quad v_{p-odd} = \frac{1}{\sqrt{(L_s - L_m)(C_s + 2C_m)}}$$

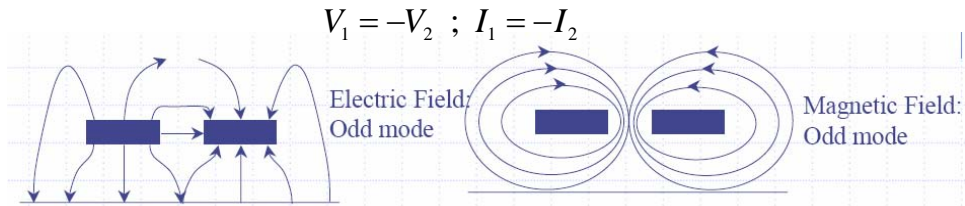Odd Mode in 2-Coupled Symmetrical TLs (cont)




(H. Mellitz 2003)


$$Z_{o-odd} = \sqrt{\frac{L_s - L_m}{C_s + 2C_m}} \quad v_{p-odd} = \frac{1}{\sqrt{(L_s - L_m)(C_s + 2C_m)}}$$

Z_{o-odd} is the characteristic impedance of one of the conductors when the coupled line is operated in odd mode

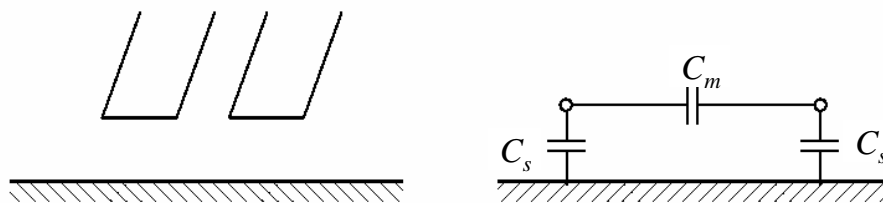Distributed Capacitances in Coupled Lines



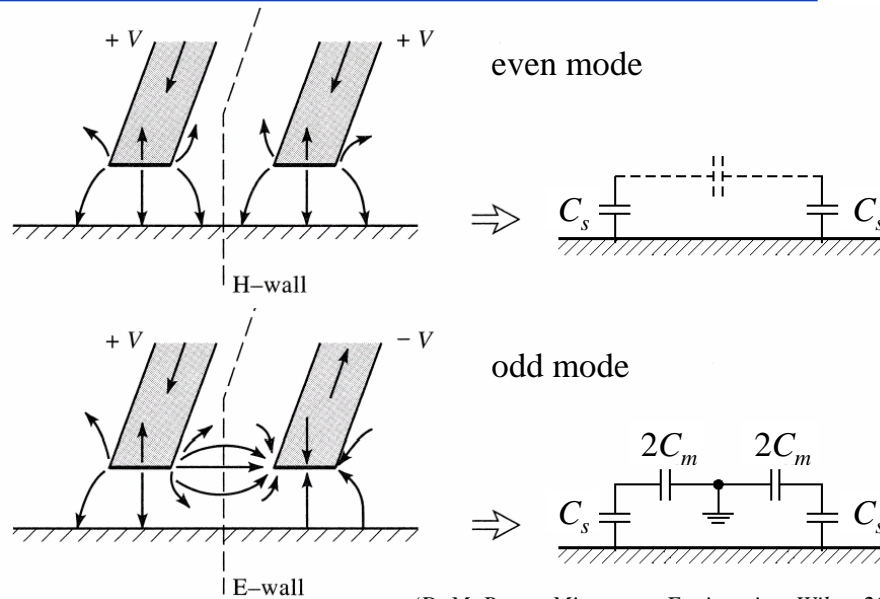Distributed Capacitances in Coupled Lines (cont)



Dr. J.E. Rayas Sánchez

(D. M. Pozar, *Microwave Engineering*, Wiley, 2005)₁₉

Z_o and v_p for Even and Odd Modes

- If Z_o is the characteristic impedance of each isolated conductor, and v_p is the propagation velocity or wave speed in each isolated conductor

$$Z_o = \sqrt{\frac{L_s}{C_s}} \quad v_p = \frac{1}{\sqrt{L_s C_s}}$$

- Since

$$Z_{o-even} = \sqrt{\frac{L_s + L_m}{C_s}} \quad v_{p-even} = \frac{1}{\sqrt{(L_s + L_m)C_s}}$$

$$Z_{o-odd} = \sqrt{\frac{L_s - L_m}{C_s + 2C_m}} \quad v_{p-odd} = \frac{1}{\sqrt{(L_s - L_m)(C_s + 2C_m)}}$$

- then

$$Z_{o-odd} < Z_o < Z_{o-even} \quad v_{p-even} < v_p$$

Dr. J.E. Rayas Sánchez

20


Termination Techniques

- A single-resistor termination for each conductor is not enough for coupled lines
- Proper terminations are needed to avoid reflections in both even and odd modes
- The most common termination networks are the T and Pi configurations

Dr. J.E. Rayas Sánchez

21


T-Termination

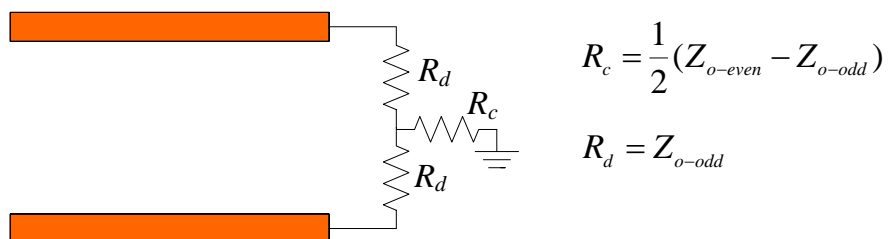

Dr. J.E. Rayas Sánchez

22


Pi-Termination

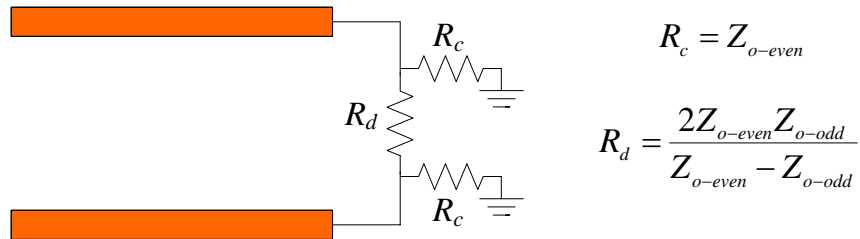

Dr. J.E. Rayas Sánchez

23

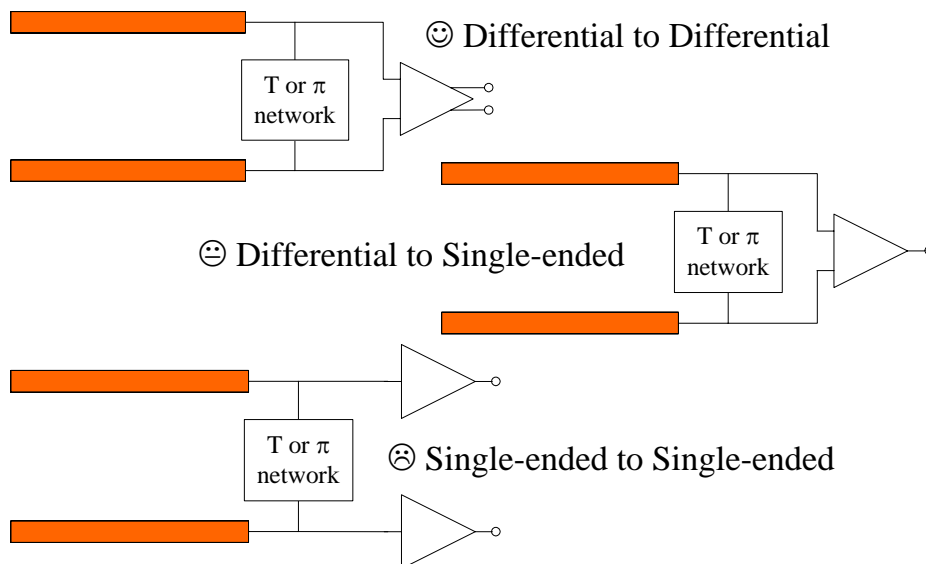
Adding Buffers for Differential Signaling



Dr. J.E. Rayas Sánchez

24


S-Parameters for Two-Coupled Lines

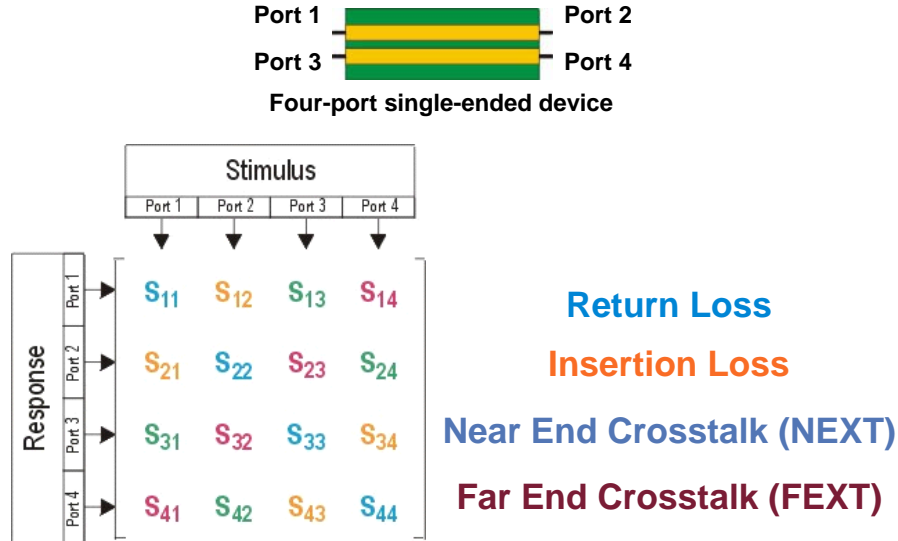

Dr. J.E. Rayas Sánchez

(M. Resso, 2005) 25

Single-ended to Balanced S-Parameters

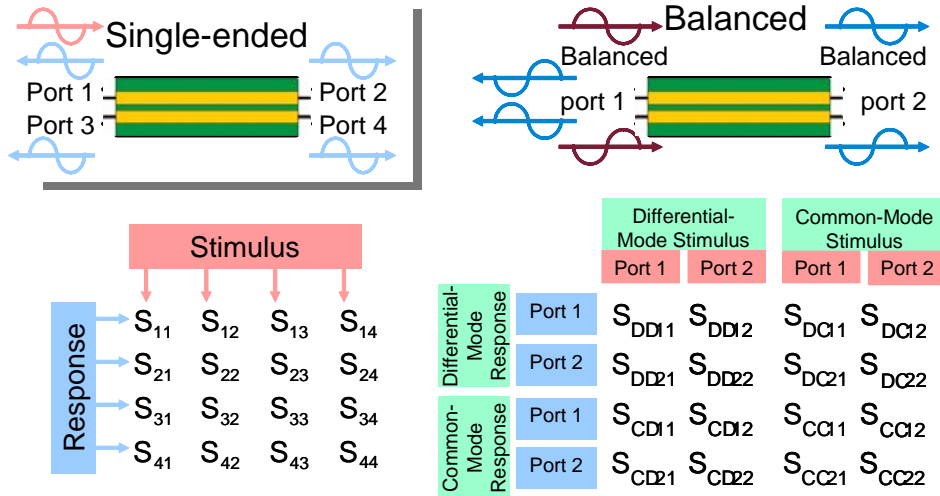


Naming Convention:

$S_{\text{mode res.}, \text{mode stim.}, \text{port res.}, \text{port stim.}}$

Dr. J.E. Rayas Sánchez

(M. Resso, 2005) 26

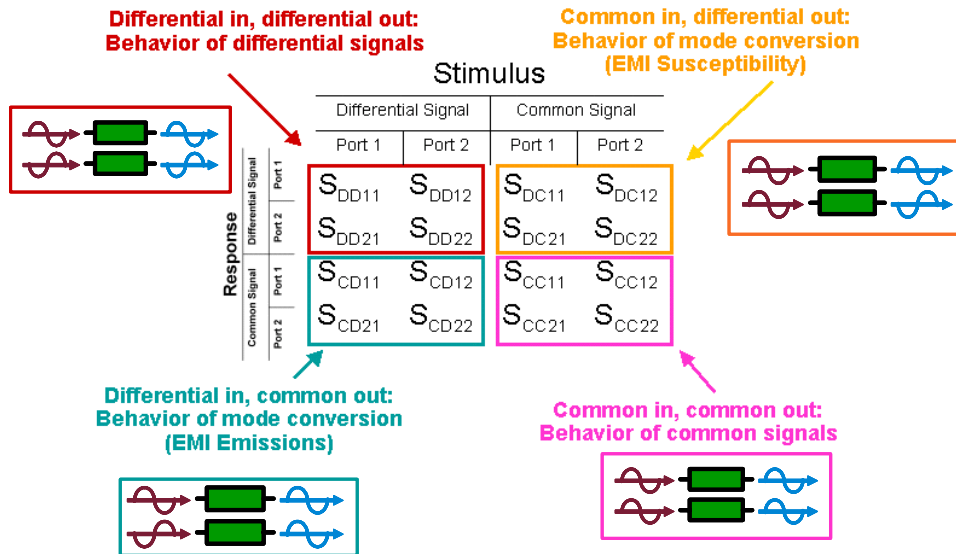Balanced, Differential or Mixed-Mode S-Param.



Dr. J.E. Rayas Sánchez

(M. Resso, 2005) 27