

# Frequency-Domain Analysis of Transmission Line Circuits

(Part 4)

**Dr. José Ernesto Rayas Sánchez**


1

## Outline

---

- Walker's formulae for 2-coupled microstrip lines
- Variation of the LC-parameters with the separation of the lines
- Variation of  $Z_o$  with the separation of the lines
- Variation of  $v_p$  with the separation of the lines
- Conclusions

## Two-Coupled Microstrip Lines

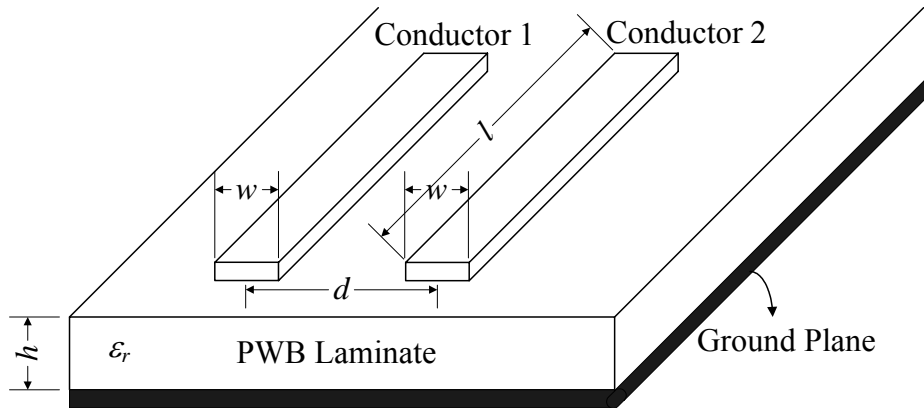


In the following analysis, we neglect the thickness of each conductor and losses

Dr. J.E. Rayas Sánchez

3

## Lossless Transmission Line Model

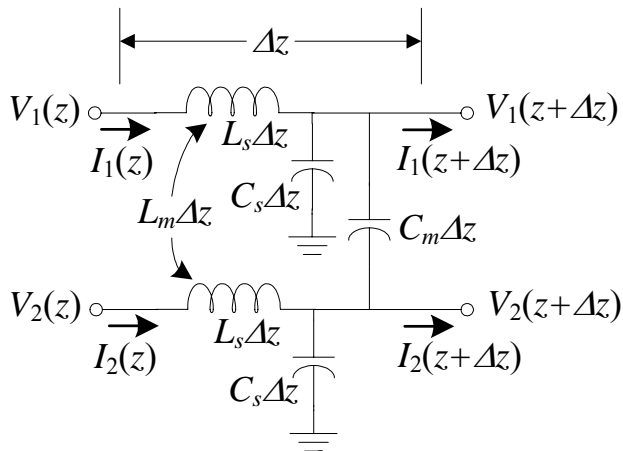

Dr. J.E. Rayas Sánchez

4

## Walker's Formulae for Cs

---

$$C_s = \varepsilon_r \varepsilon_o K_C \left( \frac{w}{h} \right) \text{ F/m} \quad \begin{array}{l} \varepsilon_o = 8.854 \times 10^{-12} \text{ (F/m)} \\ \mu_o = 4\pi \times 10^{-7} \text{ (H/m)} \end{array}$$

$$L_s = \frac{\mu_r \mu_o}{K_L} \left( \frac{h}{w} \right) \text{ H/m}$$

$$C_m = \frac{\varepsilon_r \varepsilon_o}{4\pi} K_C K_L \left( \frac{w}{h} \right)^2 \ln \left[ 1 + \left( \frac{2h}{d} \right)^2 \right] \text{ F/m}$$

$$L_m = \frac{\mu_r \mu_o}{4\pi} \ln \left[ 1 + \left( \frac{2h}{d} \right)^2 \right] \text{ H/m}$$

where  $K_C$  and  $K_L$  are the fringing factors given by ...

Dr. J.E. Rayas Sánchez C.S. Walker, *Capacitance, Inductance and Crosstalk Analysis*. Norwood, MA: Artech House, 1990. 5

## Walker's Formulae (cont)

---

$$K_C = \left[ \frac{120\pi}{Z_{o(\varepsilon_r=1)}} \left( \frac{h}{w} \right) \sqrt{\frac{\varepsilon_e}{K_L \varepsilon_r}} \right]^2 \quad K_L = \frac{120\pi}{Z_{o(\varepsilon_r=1)}} \left( \frac{h}{w} \right)$$

where


$$\varepsilon_e = \frac{\varepsilon_r + 1}{2} + \frac{\varepsilon_r - 1}{2} \frac{1}{\sqrt{1 + 10h/w}}$$

$$\text{if } \frac{w}{h} \leq 1, \quad Z_{o(\varepsilon_r=1)} = 60 \ln \left( \frac{8h}{w} + \frac{w}{4h} \right) \Omega$$

$$\text{if } \frac{w}{h} \geq 1, \quad Z_{o(\varepsilon_r=1)} = \frac{120\pi}{\left( \frac{w}{h} \right) + 2.42 - 0.44 \left( \frac{h}{w} \right) + \left( 1 - \frac{h}{w} \right)^6} \Omega$$

Dr. J.E. Rayas Sánchez C.S. Walker, *Capacitance, Inductance and Crosstalk Analysis*. Norwood, MA: Artech House, 1990. 6

## Variation of Capacitances – Example

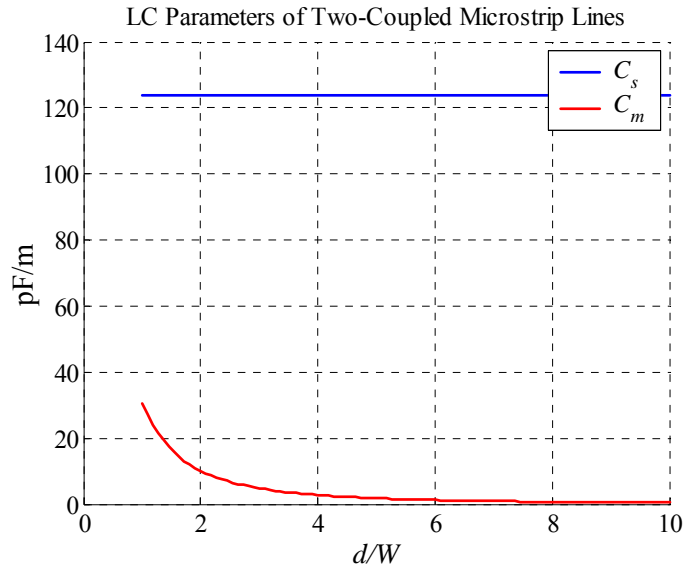


Dr. J.E. Rayas Sánchez

$W = 74.65\text{mil}; H = 40\text{mil}; \epsilon_r = 4.5$

7

## Variation of Inductances – Example

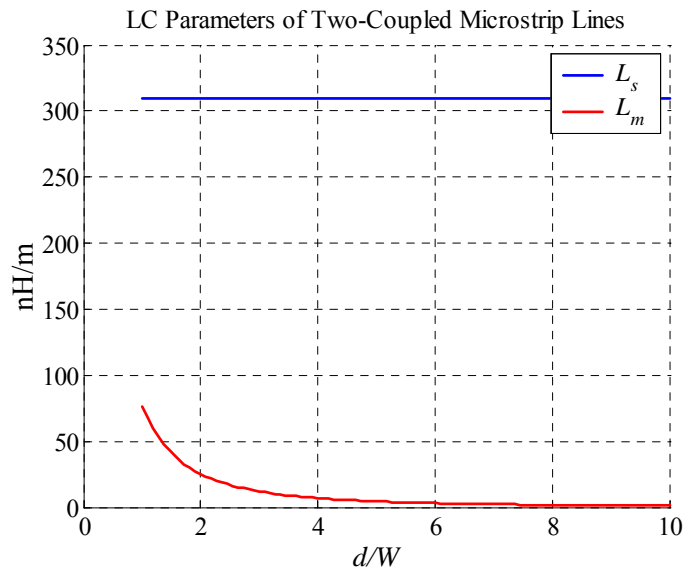

Dr. J.E. Rayas Sánchez

$W = 74.65\text{mil}; H = 40\text{mil}; \epsilon_r = 4.5$

8

## $Z_o$ and $v_p$ for Even and Odd Modes

- If  $Z_o$  is the characteristic impedance of each isolated conductor, and  $v_p$  is the propagation velocity or wave speed in each isolated conductor

$$Z_o = \sqrt{\frac{L_s}{C_s}} \quad v_p = \frac{1}{\sqrt{L_s C_s}}$$

- Since

$$Z_{o-even} = \sqrt{\frac{L_s + L_m}{C_s}} \quad v_{p-even} = \frac{1}{\sqrt{(L_s + L_m)C_s}}$$

$$Z_{o-odd} = \sqrt{\frac{L_s - L_m}{C_s + 2C_m}} \quad v_{p-odd} = \frac{1}{\sqrt{(L_s - L_m)(C_s + 2C_m)}}$$


- then

$$Z_{o-odd} < Z_o < Z_{o-even} \quad v_{p-even} < v_p$$

Dr. J.E. Rayas Sánchez

9
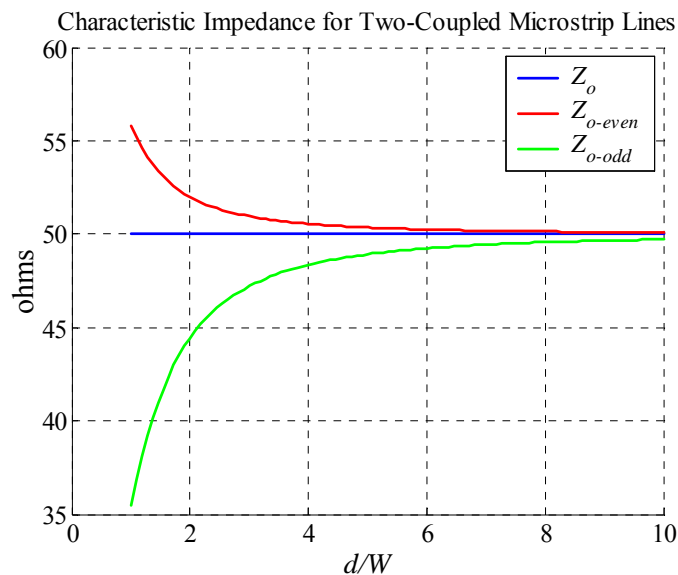
## Variation of $Z_o$ for Even and Odd Modes




Dr. J.E. Rayas Sánchez

$W = 74.65\text{mil}; H = 40\text{mil}; \epsilon_r = 4.5$

10
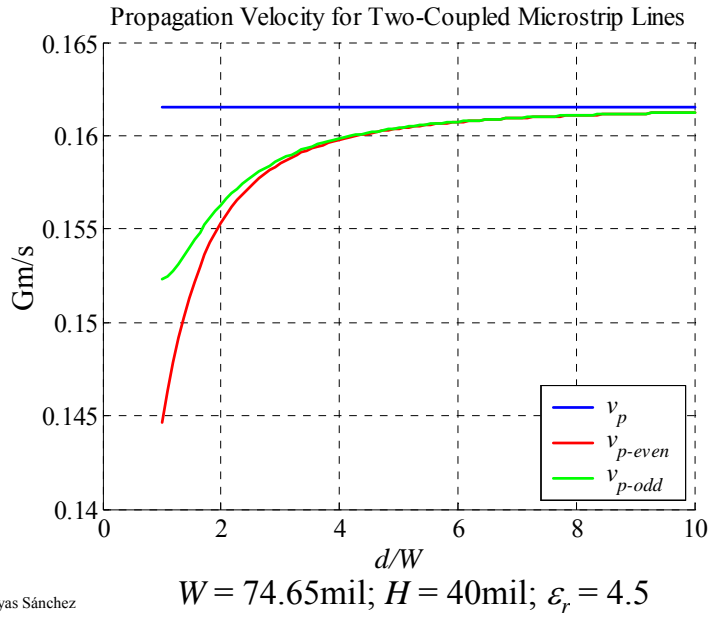
## Variation of $v_p$ for Even and Odd Modes



Dr. J.E. Rayas Sánchez

11

## Conclusions

- It has been verified that

$$Z_{o-odd} < Z_o < Z_{o-even} \quad v_{p-even} < v_{p-odd} < v_p$$

- If the coupled lines are very separated (large  $d$ )

$$C_m, L_m \rightarrow 0 \quad Z_{o-odd}, Z_{o-even} \rightarrow Z_o \quad v_{p-odd}, v_{p-even} \rightarrow v_p$$

Dr. J.E. Rayas Sánchez

12