

# Modeling I/O Buffers

(Part 1)

**Dr. José Ernesto Rayas Sánchez**

1


## Outline

---

- Buffers driving transmission lines
- Types of buffer models
- Transistor-level models
- Transistor-level models: ECL techniques
- Transistor-level models: GTL techniques

## Buffers Driving Transmission Lines

Example of a multiprocessor system

 


Dr. J.E. Rayas Sánchez

(Kudoh, 1995) <sub>3</sub>

## Buffers Driving Transmission Lines (cont)

Bus model of the multiprocessor system

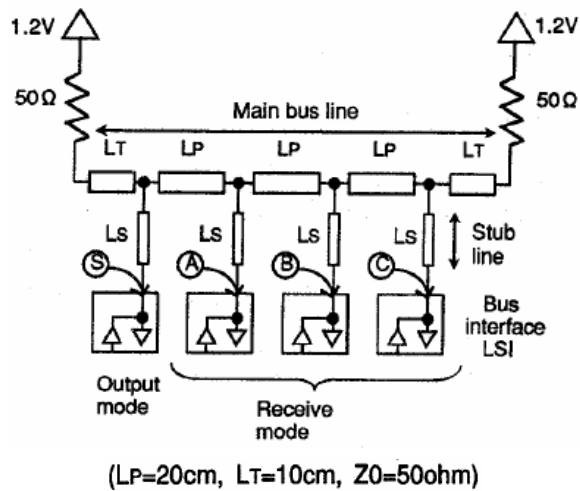

Dr. J.E. Rayas Sánchez

(Kudoh, 1995) <sub>4</sub>

## Types of Buffer Models for Digital Design

---

- Linear models
- Nonlinear behavioral models
- Detailed electrical models (transistor level)

Dr. J.E. Rayas Sánchez

5

## Transistor Level Models

---

- ☺ Advantages
  - Accuracy
- ☹ Drawbacks
  - Relatively high computational cost during simulation
  - Detailed models are difficult to find (proprietary info)
- Requirements
  - I/O circuit schematic or netlist (text file)
  - Technology process files (foundry)
  - Device dimensions
- Sources of information
  - Component suppliers (databooks, SPICE models)
  - Model libraries from CAD tools

Dr. J.E. Rayas Sánchez

6

## Transistor Level Models – ECL Drivers

- ECL technology allows very high-speed switching
- As oppose to TTL, ECL transistors are not allow to saturate
- ECL buffering techniques are enjoying renewed popularity due to the availability of BiCMOS IC process technology

ECL 10K AND 100K LOGIC

	MECL 10K	Fairchild 100K
$V_{OH(max)}$ (V)	-0.81	-0.88
$V_{OH(min)}$ (V)	-0.96	-1.03
$V_{OL(max)}$ (V)	-1.65	-1.62
$V_{OL(min)}$ (V)	-1.85	-1.81


Dr. J.E. Rayas Sánchez

(Lefebvre, 1997)

7

## Transistor Level Models – ECL Drivers (cont)

### ECL Output Driver

 


( $D_1$ ,  $D_2$  and  $R_3$  are used for temperature compensation)

Dr. J.E. Rayas Sánchez

(Lefebvre, 1997) 8

## Transistor Level Models – ECL Drivers (cont)

### ECL Input Driver

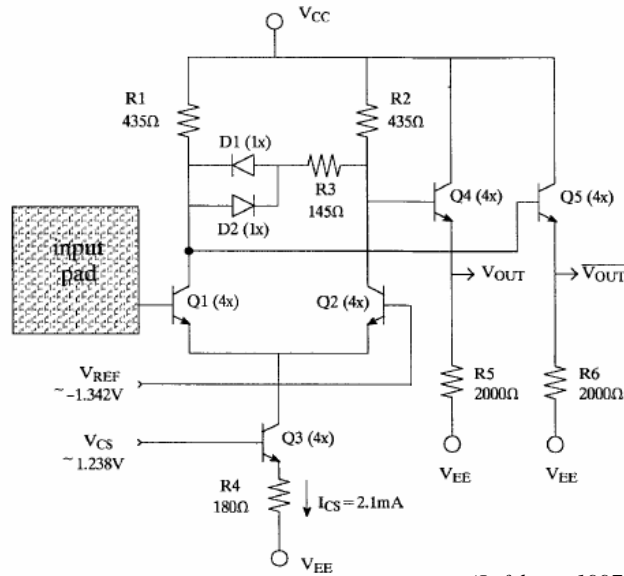

Dr. J.E. Rayas Sánchez

(Lefebvre, 1997)

## Transistor Level Models – ECL Drivers (cont)

Major drawback of ECL techniques: power consumption

Logic level	Power (Watts)	Termination (both ends)
ECL	20	50Ω to 3.0V
BTL	11	50Ω to 2.0V
GTL	1.5	50Ω to 1.2V

**Table 1: Estimated nominal power for 160 active I/O drivers.**

(Gunning, 1992)

Dr. J.E. Rayas Sánchez

10

## Transistor Level Models – GTL Drivers

---

- GTL uses CMOS process technology (low power consumption and low fabrication cost)
- Essentially, the drivers are open drain NMOS common source stages, and the receivers are NMOS differential amplifiers


Dr. J.E. Rayas Sánchez

11
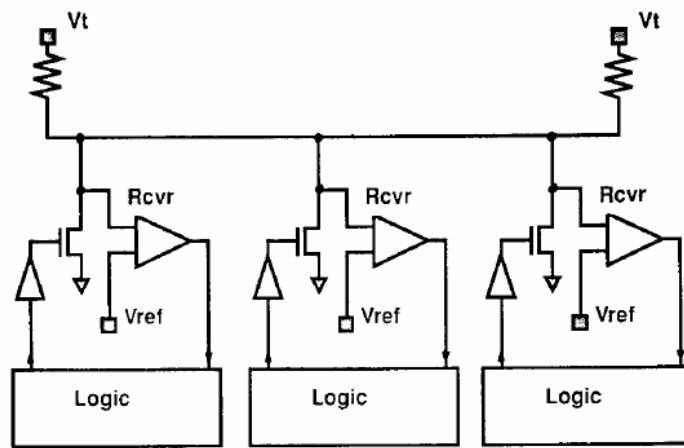
## Transistor Level Models – GTL Drivers (cont)

---

I/O Transceivers in a bidirectional transmission line bus



(the transmission line is terminated at both ends)


Dr. J.E. Rayas Sánchez

(Gunning, 1992) 12

## Transistor Level Models – GTL Drivers (cont)

---

### Output driver (transmitter)

 


Dr. J.E. Rayas Sánchez

(Gunning, 1992) 13

## Transistor Level Models – GTL Drivers (cont)

---

### Input buffer (receiver)


 


Dr. J.E. Rayas Sánchez

(Gunning, 1992) 14



## Transistor Level Models – GTL Drivers (cont)

### Open drain MOS output driver

  

Vref = 0.80V  
Undershoot = 0.72V

### Push-pull MOS output driver

  



Undershoot = 0.96V  
Vref = 0.80V

Dr. J.E. Rayas Sánchez

(Kudoh, 1995)<sub>15</sub>

## Transistor Level Models – GTL Drivers (cont)
  
### Push-pull MOS output driver with dynamic termination



Undershoot = 1.05V  
Vref = 0.80V

(In receive mode, the pull-up NMOS transistor acts as a dynamic resistance to compensate the undershoot)

Dr. J.E. Rayas Sánchez

(Kudoh, 1995)<sub>16</sub>