

Transmission Line Theory

(Part 1)

Dr. José Ernesto Rayas Sánchez


1

Outline

- Common transmission media
- Modeling uniform interconnects
- Interconnect parasitics and their physical significance
- From lumped circuits to distributed circuits
- Fundamental transmission line equations

Common Transmission Media

- Uniform Interconnects

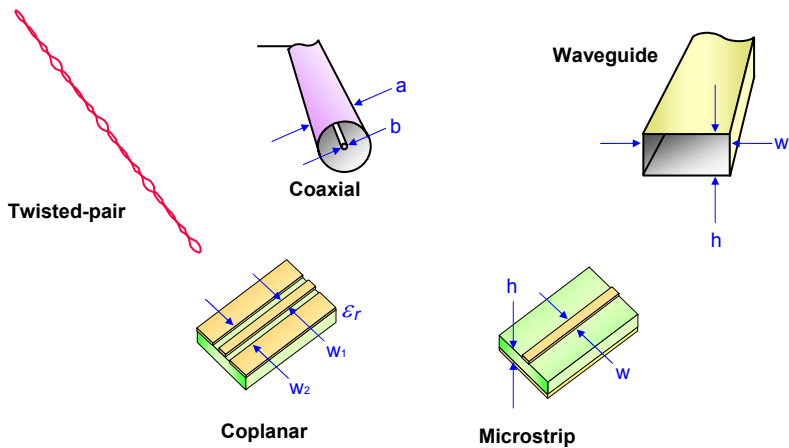


Dr. J.E. Rayas Sánchez

(Hewlett-Packard's RF Design and Measurement Seminar, 2000) ₃

Common Transmission Media (cont)

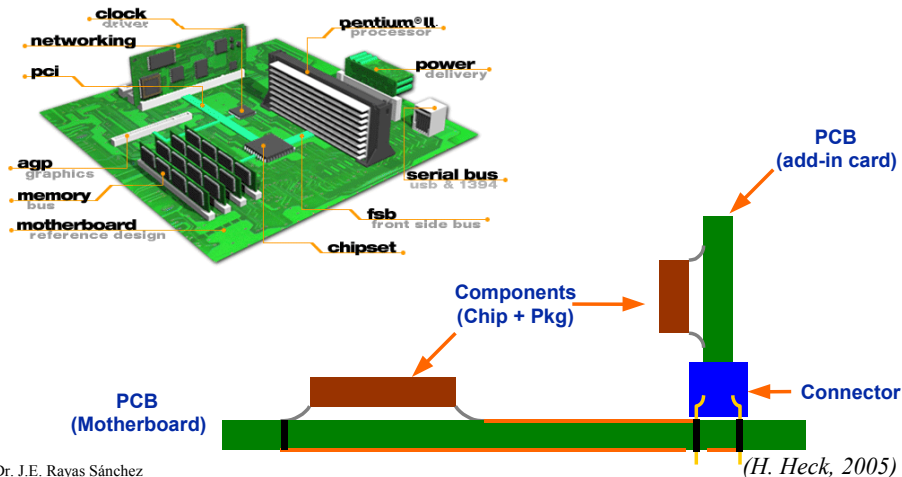- Practical interconnects can be decomposed in segments of uniform interconnects (if necessary)




Dr. J.E. Rayas Sánchez

(H. Heck, 2005)

4

Modeling Uniform Interconnects

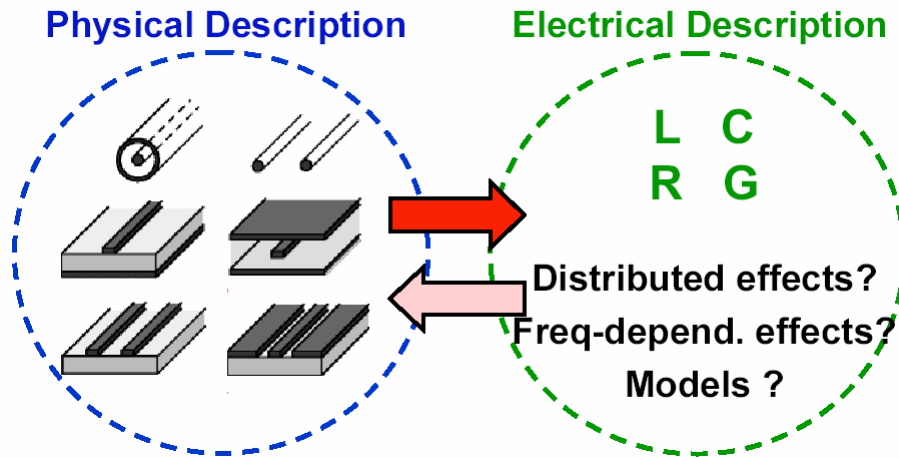

(A. Weisshaar, Tutorial on High-Speed Interconnects, IMS June 2004, Fort Worth, TX)

Dr. J.E. Rayas Sánchez

5

Modeling Uniform Interconnects (cont)

Cross-sectional view of typical **uniform** interconnects:



- Parasitic effects associated to each transmission media
 - Capacitance between conductors, C
 - Resistance of conductors (conductor losses), R
 - Inductance of conductor loops, L
 - Dielectric conductivity (dielectric losses), G
- R , C , L , and G must be determined per unit length


Dr. J.E. Rayas Sánchez

6

Interconnect Shunt Capacitance


- capacitance

$$C = Q/V$$

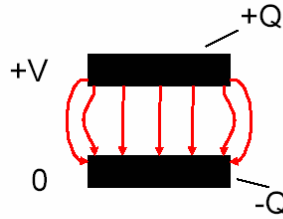

- parallel-plate capacitor and field-fringing effect
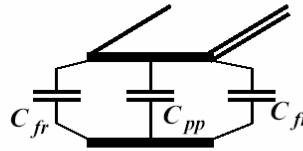
$$C_{pp}/l = \epsilon_0 \epsilon_r \frac{w}{d}$$




- Actual capacitance is **larger** than parallel-plate capacitance due to fringing fields

(A. Weisshaar, Tutorial on High-Speed Interconnects, IMS June 2004, Fort Worth, TX)

Dr. J.E. Rayas Sánchez

7

Fringing Capacitance Effect

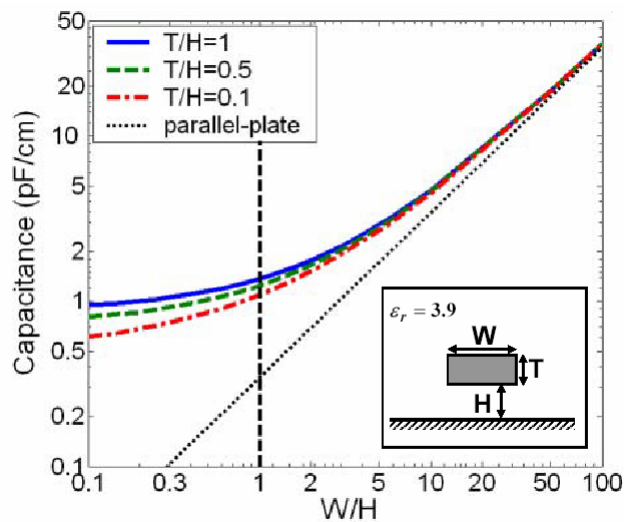

(A. Weisshaar, Tutorial on High-Speed Interconnects, IMS June 2004, Fort Worth, TX)


Dr. J.E. Rayas Sánchez

8

Interconnect Series Inductance

- **External Inductance**

$$\frac{L}{l} = \frac{\psi}{I}$$

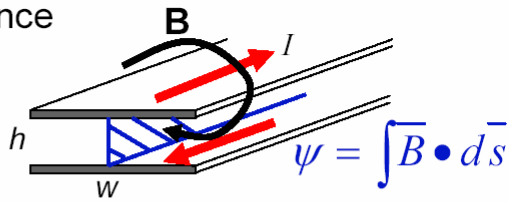

- parallel-plate inductance $\frac{L_{pp}}{l} = \mu_0 \frac{h}{w}$
- closely spaced return path means smaller inductance
- **Internal Inductance**
 - associated with flux inside conductors

(A. Weisshaar, Tutorial on High-Speed Interconnects, IMS June 2004, Fort Worth, TX)


Dr. J.E. Rayas Sánchez

9

Interconnect Series DC Resistance

- DC resistance

$$\frac{R}{l} = \frac{\rho}{A}$$

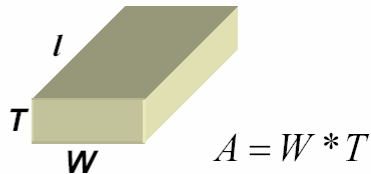

- Sheet resistance

$$R = \rho l / A = \rho \frac{W}{W T} = \rho / T$$

$$\boxed{R_s = \rho / T} \text{ (ohms per square)}$$



(A. Weisshaar, Tutorial on High-Speed Interconnects, IMS June 2004, Fort Worth, TX)


Dr. J.E. Rayas Sánchez

10

Skin Effect


- Skin depth in conductor
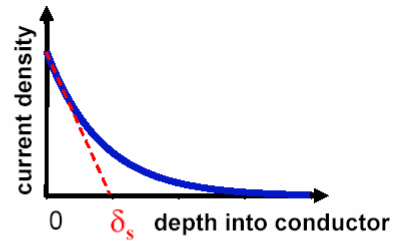
$$\delta_s = \sqrt{\frac{\rho}{\pi f \mu_0}} = \frac{1}{\sqrt{\pi f \sigma \mu_0}}$$



→ for copper at 1 GHz: $\delta_s \cong 2.1 \mu\text{m}$; at 10 GHz: $\delta_s \cong 0.7 \mu\text{m}$

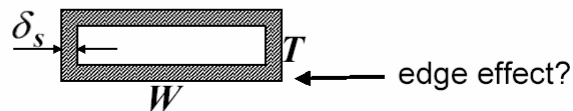- High-frequency approximation ($W, T \gg \delta_s$)




(A. Weisshaar, Tutorial on High-Speed Interconnects, IMS June 2004, Fort Worth, TX)

Dr. J.E. Rayas Sánchez

11

EM-Simulation of Conductor Current Distribution

(with currents in same direction)

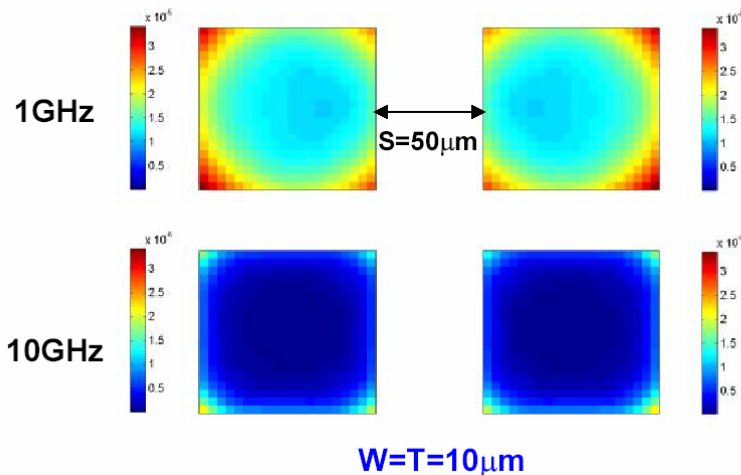


(A. Weisshaar, Tutorial on High-Speed Interconnects, IMS June 2004, Fort Worth, TX)

Dr. J.E. Rayas Sánchez

12

Proximity Effect

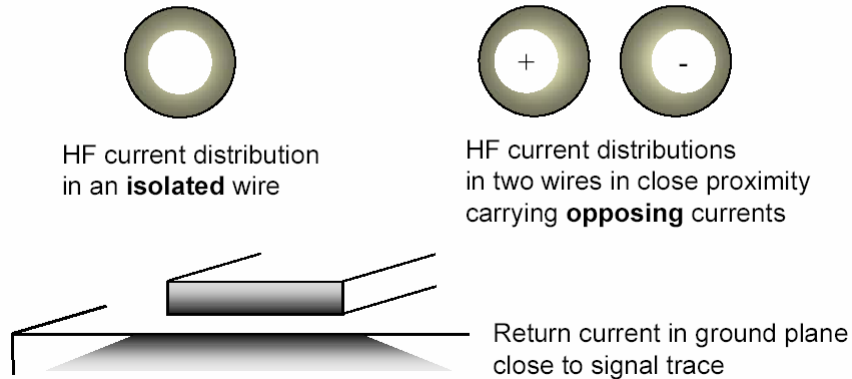- Opposing high frequency (HF) currents in close proximity are drawn to each other




(A. Weisshaar, *Tutorial on High-Speed Interconnects*, IMS June 2004, Fort Worth, TX)

Dr. J.E. Rayas Sánchez

13

Edge and Indy Effects – Example

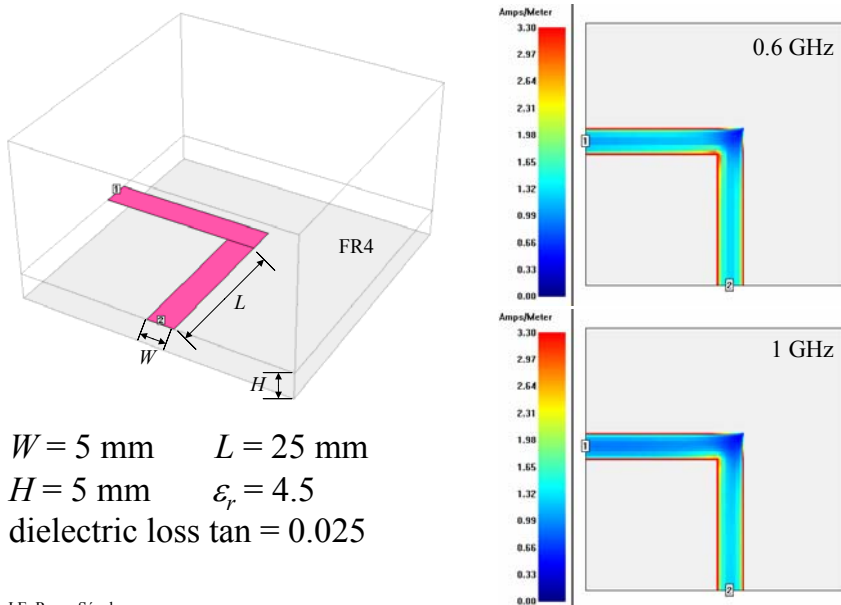



Dr. J.E. Rayas Sánchez

14

Interconnect Shunt Conductance

- shunt loss due to
 - ohmic losses (free charge carriers)
 - out-of-phase polarization (power loss due to frictional damping forces)

- simple model

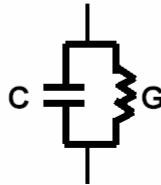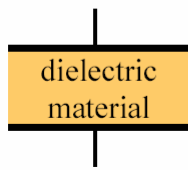

loss tangent:

$$\tan \delta_d = G / \omega C$$

$$= \epsilon'' / \epsilon'$$

where $\epsilon = \epsilon' - j\epsilon''$

(A. Weisshaar, Tutorial on High-Speed Interconnects, IMS June 2004, Fort Worth, TX)

Dr. J.E. Rayas Sánchez

15

Loss Tangent of Typical Materials

Dielectric Material	Loss Tangent	Dielectric Constant
Ceramic (Alumina)	0.001	9.4
Glass-epoxy	0.03	4.0
Glass (Quartz)	0.00006	3.8
Polyimide	0.01	3.5
Silicon (100 Ω-cm)	0.51	11.8
Silicon (10 Ω-cm)	5.1	11.8
Teflon	0.00015	2.1

at 3GHz

(A. Weisshaar, Tutorial on High-Speed Interconnects, IMS June 2004, Fort Worth, TX)

Dr. J.E. Rayas Sánchez

16


Equivalent **Circuit** Models for Interconnects

- On-chip Interconnects
 - lumped C if very short
 - lumped RC if very short and R significant
 - cascaded lumped RC if short
 - distributed RC if long
 - RLC distributed line (high performance VLSI circuits and microwave ICs)
- Off-chip Interconnects (→ usually distributed models)
 - LC line if losses can be ignored
 - RLC line on low dielectric loss PCBs
 - RLGC line (if dielectric loss is significant)

Dr. J.E. Rayas Sánchez

17


Lumped Equivalent Circuit Models

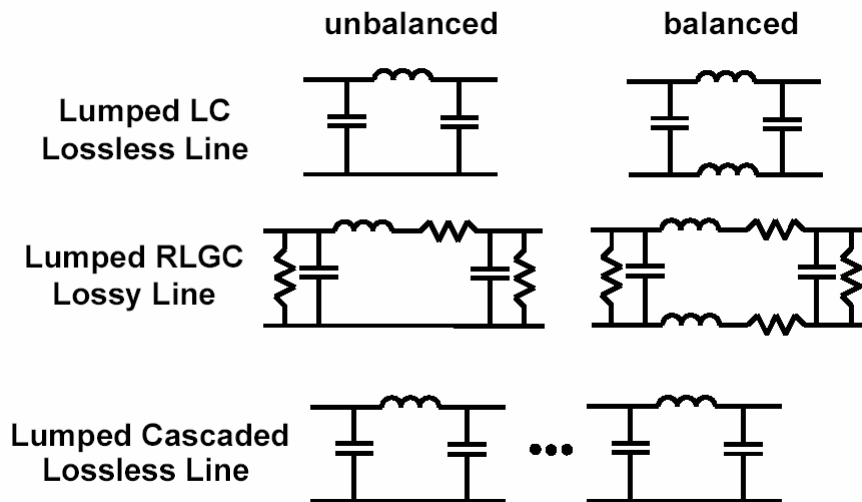

Dr. J.E. Rayas Sánchez

18

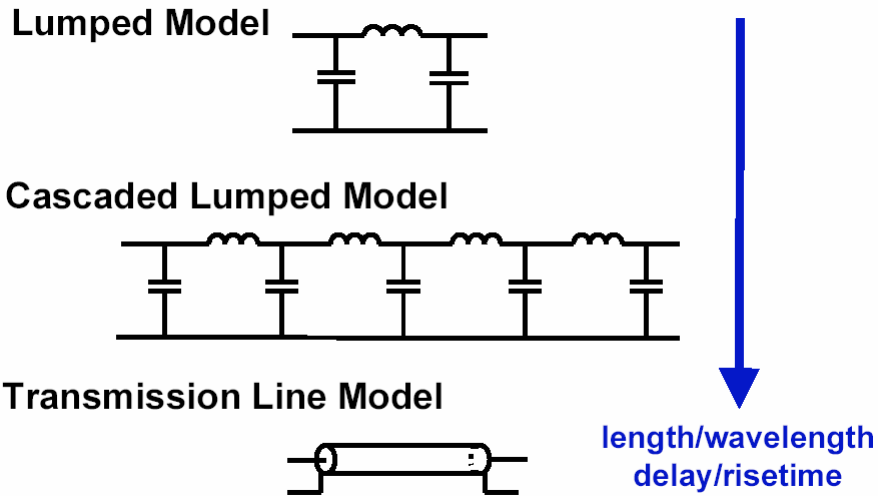From Lumped Circuits to Distributed Circuits




(A. Weisshaar, Tutorial on High-Speed Interconnects, IMS June 2004, Fort Worth, TX)

Dr. J.E. Rayas Sánchez

19

Transmission Line Model

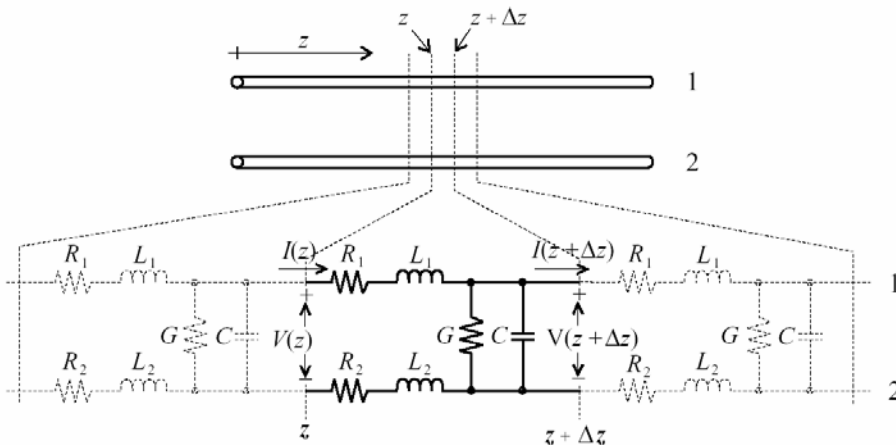


The interconnect is modeled using an infinite number of RLCG sections

Dr. J.E. Rayas Sánchez

(R. Ludwig and P. Bretchko, RF Circuit Design, Prentice Hall, 2000)

20

Transmission Line Model

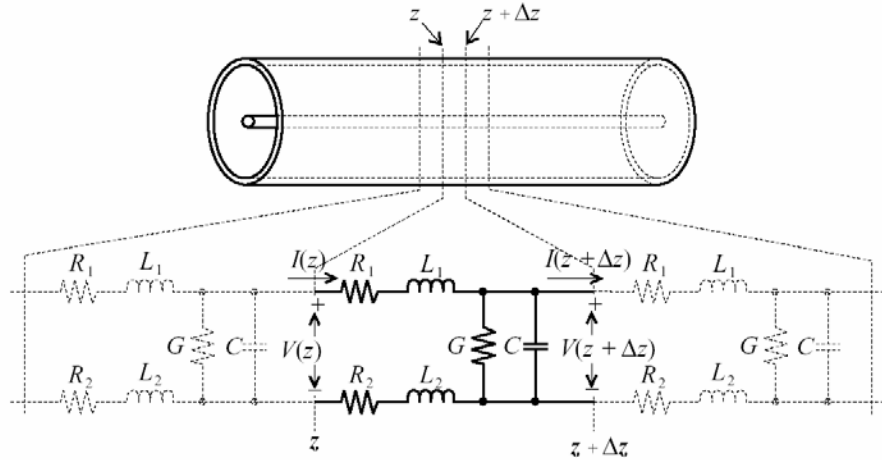


The interconnect is modeled using an infinite number of RLCG sections

Dr. J.E. Rayas Sánchez

(R. Ludwig and P. Bretchko, *RF Circuit Design*, Prentice Hall, 2000) 21

Transmission Line Model

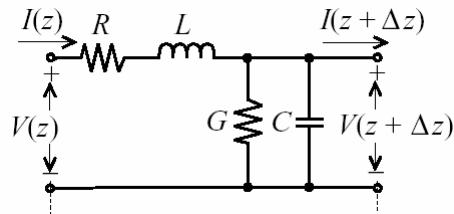

- Generic equivalent circuit for each section (R, L, C and G are per unit length)
- The interconnect is modeled using an infinite number of these sections, making $\Delta z \rightarrow 0$

Dr. J.E. Rayas Sánchez

(R. Ludwig and P. Bretchko, *RF Circuit Design*, Prentice Hall, 2000) 22

Transmission Line Equations

- Time-Domain (Telegrapher Equations)

$$\frac{\partial v(z,t)}{\partial z} = -Ri(z,t) - L \frac{\partial i(z,t)}{\partial t}$$

$$\frac{\partial i(z,t)}{\partial z} = -Gv(z,t) - C \frac{\partial v(z,t)}{\partial t}$$

- Telegrapher Equations in Frequency-Domain

$$\frac{dV(z)}{dz} = -(R + j\omega L)I(z)$$

$$\frac{dI(z)}{dz} = -(G + j\omega C)V(z)$$

Dr. J.E. Rayas Sánchez

23

Transmission Line Equations (cont)

- Wave Equation (frequency domain)

$$\frac{d^2V(z)}{dz^2} - \gamma^2 V(z) = 0 \qquad \frac{d^2I(z)}{dz^2} - \gamma^2 I(z) = 0$$

where $\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} \equiv \alpha + j\beta$
is the complex propagation constant

- Solutions to the wave equation are

$$V(z) = V_o^+ e^{-\gamma z} + V_o^- e^{+\gamma z} \qquad I(z) = I_o^+ e^{-\gamma z} + I_o^- e^{+\gamma z}$$

incident waves reflected waves

Dr. J.E. Rayas Sánchez

24

Transmission Line Equations (cont)

- Characteristic Impedance of the TL

$$Z_o \equiv \frac{V_o^+}{I_o^+} = \frac{V_o^-}{-I_o^-}$$

then

$$Z_o = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

- Reflection Coefficient along the line, Γ_z

$$V(z) = V_o^+ e^{-\gamma z} + V_o^- e^{+\gamma z}$$

$$\Gamma_z(z) = \frac{V_o^- e^{+\gamma z}}{V_o^+ e^{-\gamma z}} = \frac{V_o^-}{V_o^+} e^{+2\gamma z}$$

Dr. J.E. Rayas Sánchez

25

Transmission Line Equations (cont)

- Solutions in the frequency domain

$$V(z) = V_o^+ e^{-\gamma z} + V_o^- e^{+\gamma z} \quad I(z) = I_o^+ e^{-\gamma z} + I_o^- e^{+\gamma z}$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} \equiv \alpha + j\beta$$

- Solutions in the time domain

$$v(z, t) = |V_o^+| \cos(\omega t - \beta z + \phi^+) e^{-\alpha z} + |V_o^-| \cos(\omega t + \beta z + \phi^-) e^{+\alpha z}$$

- Wavelength
- Phase velocity, wave velocity or propagation speed

$$\lambda = \frac{v_p}{f} = \frac{2\pi}{\beta}$$

$$v_p = \frac{dz}{dt} = \frac{\omega}{\beta}$$


(speed at which a constant phase point travels down the line)

Dr. J.E. Rayas Sánchez


26

Transmission Line Symbol

- (Lossy) Transmission Line

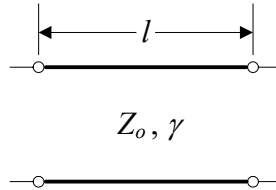

- Length along the line

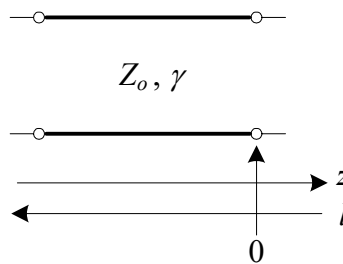


Dr. J.E. Rayas Sánchez

27

Reflection Coefficient

- Reflection coefficient along the line

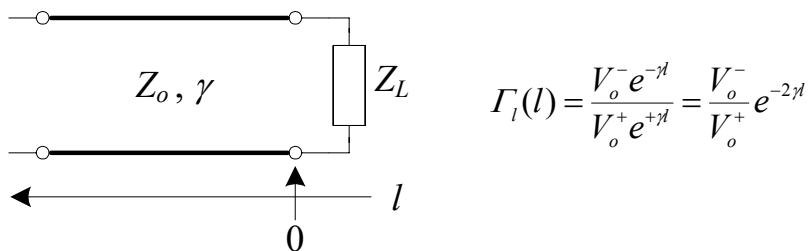

- Reflection coefficient at the load


$$\Gamma = \Gamma_l(l=0) = \frac{V_o^-}{V_o^+} = \frac{Z_L - Z_o}{Z_L + Z_o}$$

Dr. J.E. Rayas Sánchez

28

Input Impedance

- Input Impedance along the line

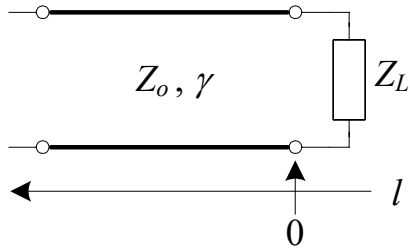

$$Z_{in}(l) = \frac{V(l)}{I(l)} = Z_o \frac{Z_L + Z_o \tanh(\gamma l)}{Z_o + Z_L \tanh(\gamma l)}$$