

Transmission Line Theory

(Part 3)


Dr. José Ernesto Rayas Sánchez

1

Outline

- Input impedance in lossless transmission lines (TL)
- Special cases of lossless terminated TL
- Insertion loss
- Transmission coefficient
- Smith Chart interpretation
- Basic Smith Chart applications

Input Impedance in Lossless TL

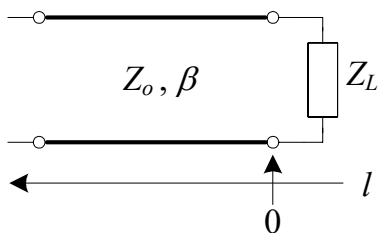

$$V(z) = V_o^+ (e^{-j\beta z} + \Gamma e^{+j\beta z})$$

$$I(z) = \frac{V_o^+}{Z_o} (e^{-j\beta z} - \Gamma e^{+j\beta z})$$

$$Z_{in}(l) = \frac{V(l)}{I(l)} = Z_o \frac{e^{j\beta l} + \Gamma e^{-j\beta l}}{e^{j\beta l} - \Gamma e^{-j\beta l}} = Z_o \frac{1 + \Gamma e^{-j2\beta l}}{1 - \Gamma e^{-j2\beta l}}$$


$$Z_{in}(l) = Z_o \frac{1 + \Gamma_l}{1 - \Gamma_l}$$

$$\Gamma_l = \frac{Z_{in}(l) - Z_o}{Z_{in}(l) + Z_o}$$

Dr. J.E. Rayas Sánchez

3

Input Impedance in Lossless TL

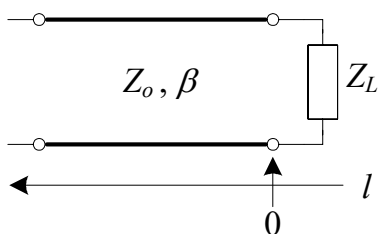

$$V(z) = V_o^+ (e^{-j\beta z} + \Gamma e^{+j\beta z})$$

$$I(z) = \frac{V_o^+}{Z_o} (e^{-j\beta z} - \Gamma e^{+j\beta z})$$

$$Z_{in}(l) = \frac{V(l)}{I(l)} = Z_o \frac{Z_L + jZ_o \tan(\beta l)}{Z_o + jZ_L \tan(\beta l)}$$

Since $\beta = \frac{2\pi}{\lambda}$

βl is the electrical length


$$Z_{in}(l = 0, \frac{\lambda}{2}, \lambda, \frac{3\lambda}{2}, \dots) = Z_L \quad Z_{in}(l = \frac{\lambda}{4}, \frac{3\lambda}{4}, \frac{5\lambda}{4}, \dots) = \frac{Z_o^2}{Z_L}$$

(Period = $\lambda/2$)

Dr. J.E. Rayas Sánchez

4

Short-Circuited Lossless TL

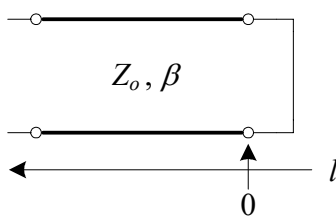



$$\Gamma = \frac{Z_L - Z_o}{Z_L + Z_o} = -1$$

$$V(z) = V_o^+ (e^{-j\beta z} + \Gamma e^{+j\beta z}) = V_o^+ (e^{-j\beta z} - e^{+j\beta z})$$

$$I(z) = \frac{V_o^+}{Z_o} (e^{-j\beta z} - \Gamma e^{+j\beta z}) = \frac{V_o^+}{Z_o} (e^{-j\beta z} + e^{+j\beta z})$$

$$V(z) = -2jV_o^+ \sin \beta z$$

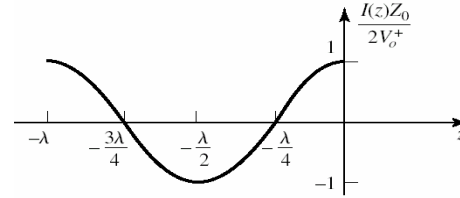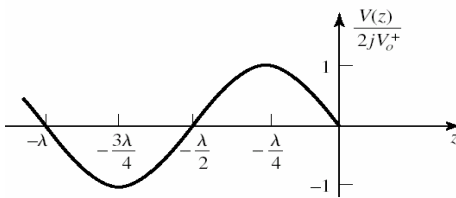
$$I(z) = \frac{2V_o^+}{Z_o} \cos \beta z$$



Dr. J.E. Rayas Sánchez

5


Short-Circuited Lossless TL (cont)

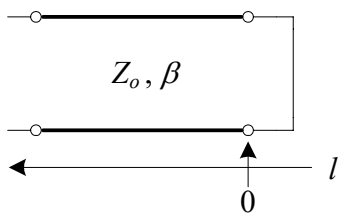

$$Z_{in}(l) = Z_o \frac{Z_L + jZ_o \tan(\beta l)}{Z_o + jZ_L \tan(\beta l)}$$

$$Z_{in}(l) = jZ_o \tan(\beta l)$$


Z_{in} is purely reactive

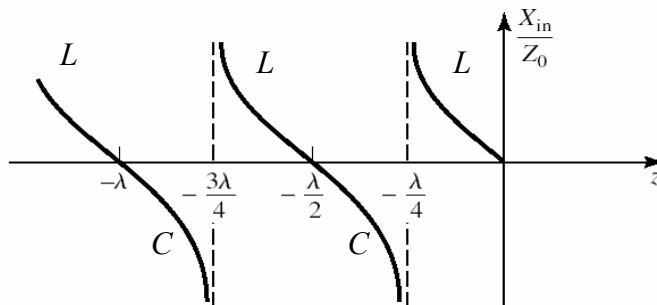

Dr. J.E. Rayas Sánchez

6

Open-Circuited Lossless TL

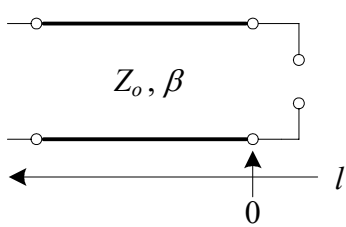



$$\Gamma = \frac{Z_L - Z_o}{Z_L + Z_o} = +1$$

$$V(z) = V_o^+ (e^{-j\beta z} + e^{+j\beta z})$$

$$I(z) = \frac{V_o^+}{Z_o} (e^{-j\beta z} - e^{+j\beta z})$$

$$V(z) = 2V_o^+ \cos \beta z$$

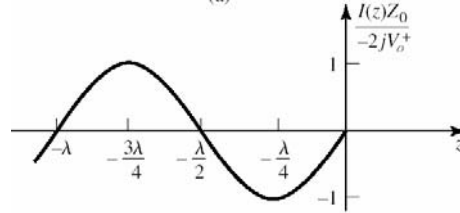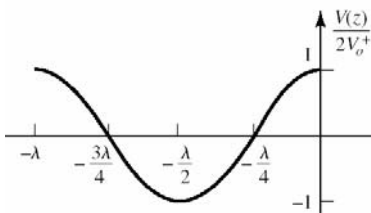
$$I(z) = \frac{j2V_o^+}{Z_o} \sin \beta z$$



Dr. J.E. Rayas Sánchez

7


Open-Circuited Lossless TL (cont)

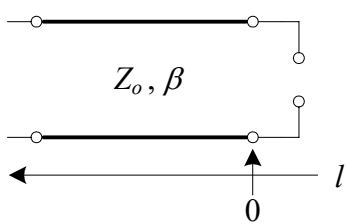

$$Z_{in}(l) = Z_o \frac{Z_L + jZ_o \tan(\beta l)}{Z_o + jZ_L \tan(\beta l)}$$

$$Z_{in}(l) = \frac{Z_o}{j \tan(\beta l)} = -jZ_o \cot(\beta l)$$

Z_{in} is purely reactive

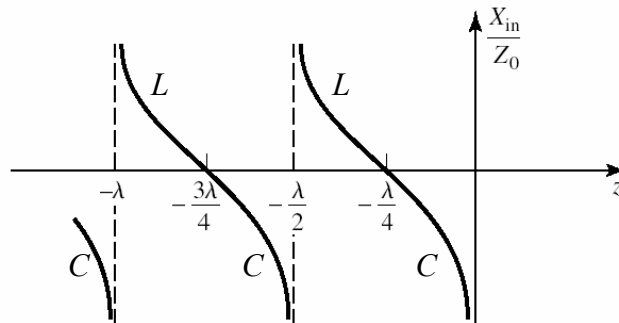


Dr. J.E. Rayas Sánchez

8

Transmission Coefficient, T

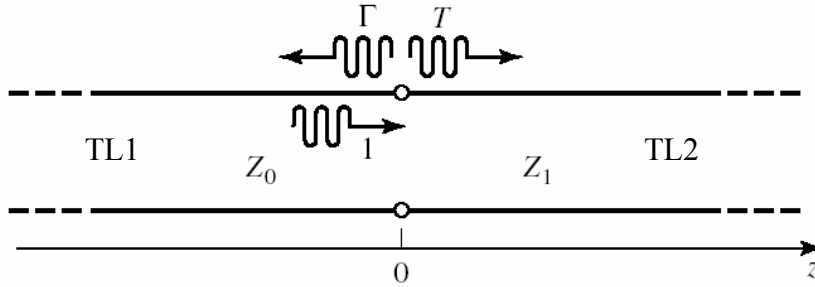- It is a measure of the capacity of a TL to transmit an incoming wave



$$\Gamma = \frac{Z_1 - Z_0}{Z_1 + Z_0}$$

$$V(z) = V_o^+ (e^{-j\beta z} + \Gamma e^{+j\beta z}) \quad \text{for } z \leq 0$$

$$V(z) = V_o^+ T e^{-j\beta z} \quad \text{for } z \geq 0 \text{ (assuming TL2 infinite)}$$


$$V(0) = V_o^+ [1 + \Gamma] = T V_o^+ \quad T = 1 + \Gamma$$

Dr. J.E. Rayas Sánchez

9

Insertion Loss, IL

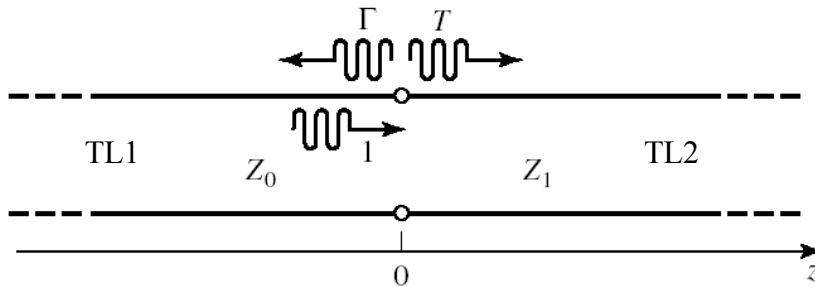- It is a measure of the reflections caused by an inserted TL




$$IL = -20 \log |T| \quad (\text{dB})$$

$$IL(|T| = 0) = \infty \text{ dB} \quad IL(|T| = 1) = 0 \text{ dB}$$

Dr. J.E. Rayas Sánchez

10

Lightwave Analogy to RF Energy

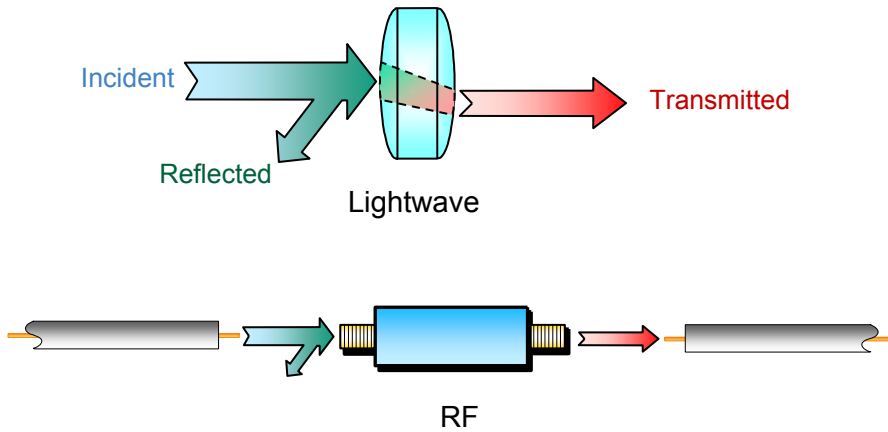


Dr. J.E. Rayas Sánchez

(Hewlett-Packard's RF Design and Measurement Seminar, 2000)₁₁

Reflection Parameters

Reflection Coefficient $\Gamma = \frac{V_{\text{reflected}}}{V_{\text{incident}}} = \rho \angle \Phi = \frac{Z_L - Z_0}{Z_L + Z_0}$

Return loss = $-20 \log(\rho)$, $\rho = |\Gamma|$

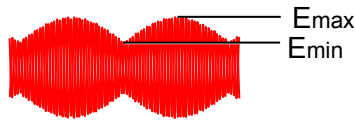

Voltage Standing Wave Ratio

$$\text{VSWR} = \frac{E_{\text{max}}}{E_{\text{min}}} = \frac{1 + \rho}{1 - \rho}$$

No reflection
($Z_L = Z_0$)

Full reflection
($Z_L = \text{open, short}$)

0	ρ	1
∞ dB	RL	0 dB
1	VSWR	∞

Dr. J.E. Rayas Sánchez

(Hewlett-Packard's RF Design and Measurement Seminar, 2000)₁₂

Transmission Parameters



$$\text{Transmission Coefficient} = T = \frac{V_{\text{Transmitted}}}{V_{\text{Incident}}} = \tau \angle \phi$$

$$\text{Insertion Loss (dB)} = -20 \text{ Log} \left| \frac{V_{\text{Trans}}}{V_{\text{Inc}}} \right| = -20 \log \tau$$

$$\text{Gain (dB)} = 20 \text{ Log} \left| \frac{V_{\text{Trans}}}{V_{\text{Inc}}} \right| = 20 \log \tau$$

$$\text{Insertion Phase (deg)} = \angle \frac{V_{\text{Trans}}}{V_{\text{Inc}}} = \phi$$

Dr. J.E. Rayas Sánchez

(Hewlett-Packard's RF Design and Measurement Seminar, 2000)₁₃


The Smith Chart

- Developed in 1939 by P. H. Smith at Bell Labs
- Very useful for visualizing transmission line phenomena and impedance matching problems
- It is part of most current CAD tools and modern measurement equipments
- It is essentially a plot of Γ in polar coordinates
- Any impedance can be mapped in the Γ plane

Dr. J.E. Rayas Sánchez

14

The Smith Chart (cont)

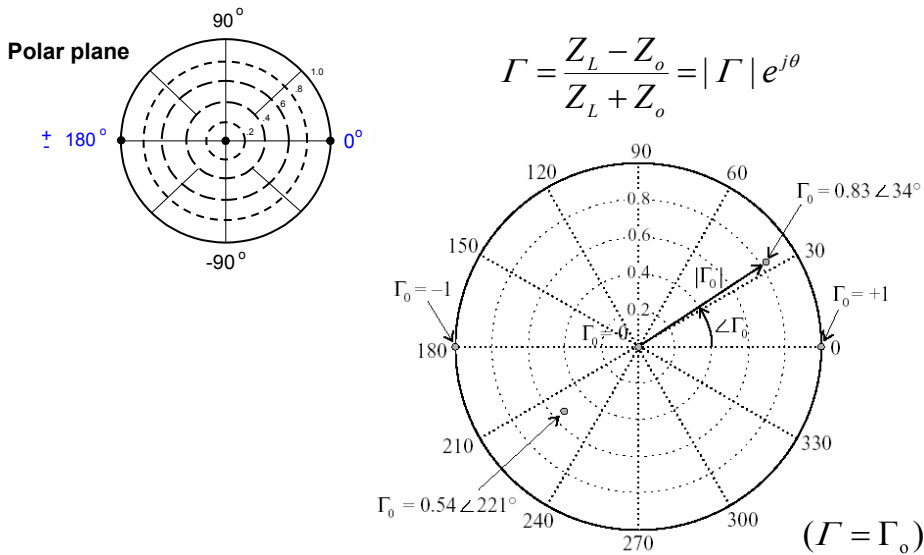

Dr. J.E. Rayas Sánchez

(R. Ludwig and P. Bretchko, *RF Circuit Design*, Prentice Hall, 2000) 15

The Smith Chart (cont)

$$\Gamma = \frac{Z - Z_o}{Z + Z_o} = |\Gamma| e^{j\theta}$$

Normalizing Z w.r.t Z_o

$$\frac{z-1}{z+1} = |\Gamma| e^{j\theta} \quad \text{where} \quad z = \frac{Z}{Z_o}$$

$$z = \frac{1 + |\Gamma| e^{j\theta}}{1 - |\Gamma| e^{j\theta}}$$

$$r + jx = \frac{(1 + \Gamma_r) + j\Gamma_i}{(1 - \Gamma_r) - j\Gamma_i}$$

Solving for r and x

$$r = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

$$x = \frac{2\Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

Rearranging

$$\left(\Gamma_r - \frac{r}{1+r}\right)^2 + \Gamma_i^2 = \left(\frac{1}{1+r}\right)^2$$


$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2$$

Dr. J.E. Rayas Sánchez

16

The Smith Chart – Circles of Constant r
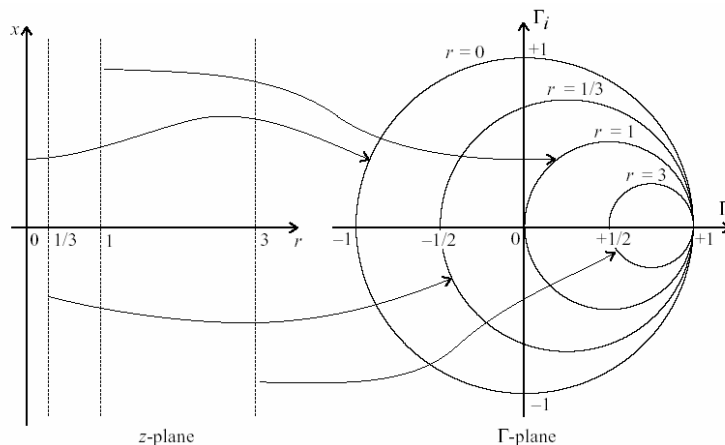
$$\left(\Gamma_r - \frac{r}{1+r}\right)^2 + \Gamma_i^2 = \left(\frac{1}{1+r}\right)^2$$




Constant resistance lines ($r = \text{const}$)

Dr. J.E. Rayas Sánchez

(R. Ludwig and P. Bretchko, *RF Circuit Design*, Prentice Hall, 2000) 17

The Smith Chart – Circles of Constant x

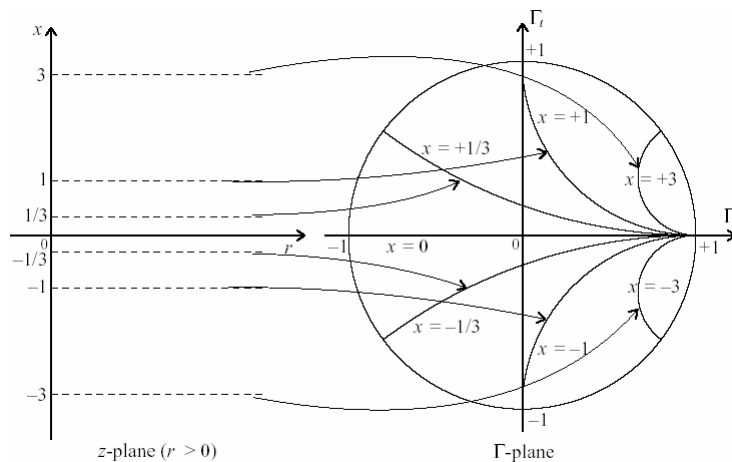
$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2$$



Dr. J.E. Rayas Sánchez

(R. Ludwig and P. Bretchko, *RF Circuit Design*, Prentice Hall, 2000) 18


The Smith Chart – Combining both Circles

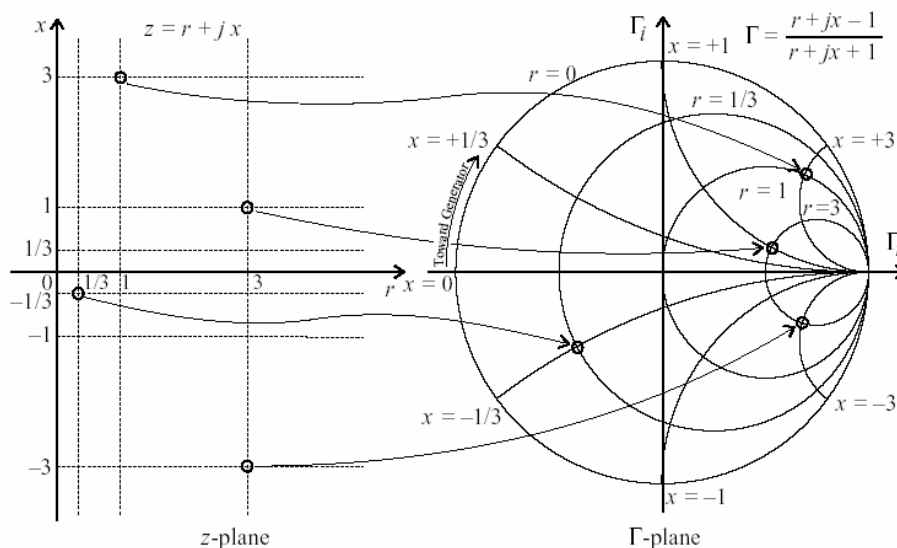

Dr. J.E. Rayas Sánchez

(R. Ludwig and P. Bretchko, *RF Circuit Design*, Prentice Hall, 2000) 19

The Smith Chart – Interpretation

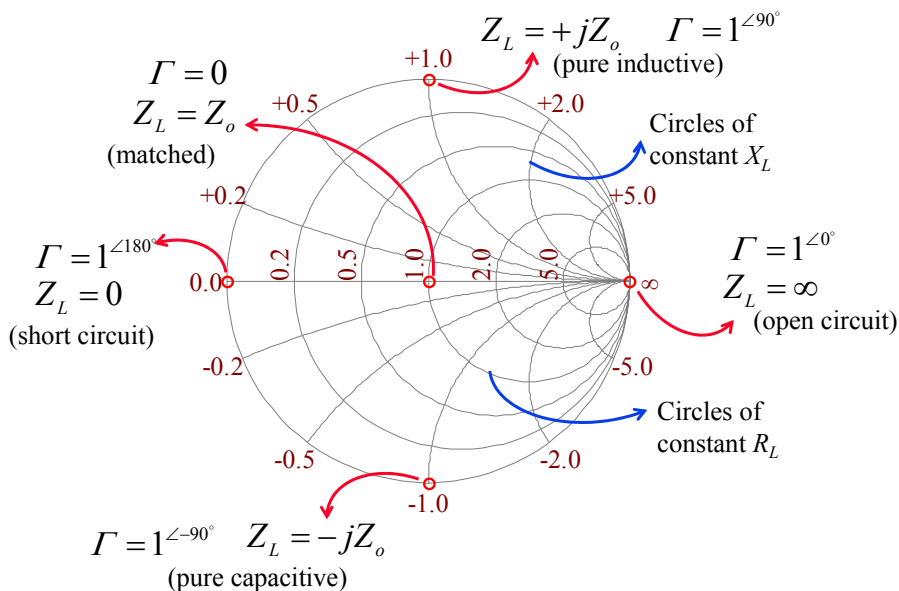

Dr. J.E. Rayas Sánchez

20

Smith Chart – Calculating Γ , RL , SWR

Example:

$$Z_o = 50\Omega$$


$$Z_L = 25 + j75 \Omega$$

$$\Gamma = ?$$

$$RL = ?$$

$$SWR = ?$$

$$z_L = 0.5 + j1.5$$

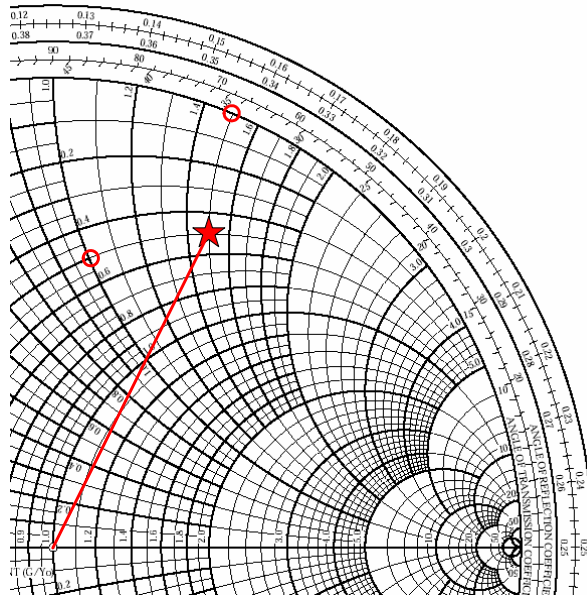

Dr. J.E. Rayas Sánchez

23

Smith Chart – Calculating Γ , RL , SWR (cont)


Example:

$$Z_o = 50\Omega$$

$$Z_L = 25 + j75 \Omega$$

$$z_L = 0.5 + j1.5$$

$$\Gamma = |\Gamma| \angle 63.4^\circ$$

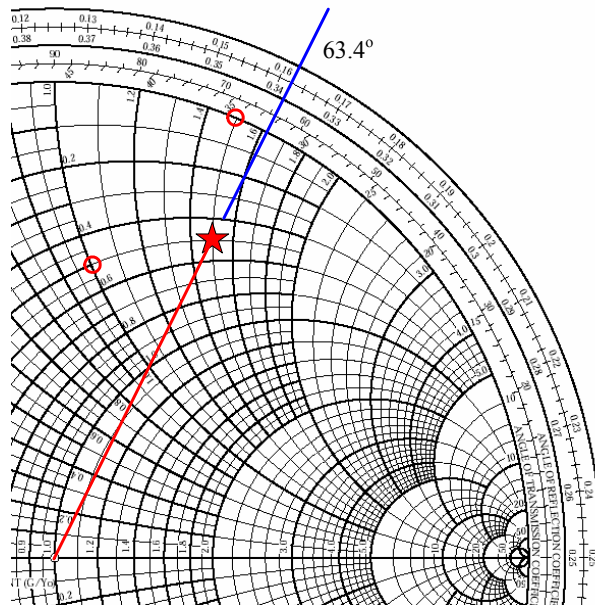

Dr. J.E. Rayas Sánchez

24

Smith Chart – Calculating Γ , RL , SWR (cont)


Example:

$$Z_o = 50\Omega$$

$$Z_L = 25 + j75 \Omega$$

$$z_L = 0.5 + j1.5$$

$$\Gamma = |\Gamma| \angle 63.4^\circ$$

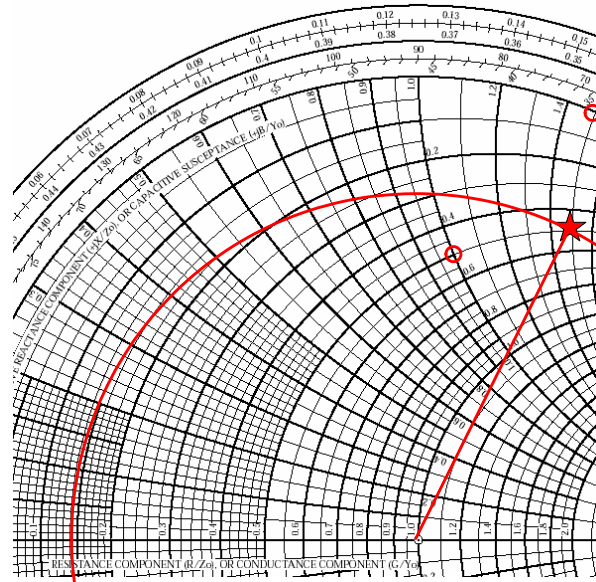

Dr. J.E. Rayas Sánchez

25

Smith Chart – Calculating Γ , RL , SWR (cont)

Example:

$$Z_o = 50\Omega$$


$$Z_L = 25 + j75 \Omega$$

$$z_L = 0.5 + j1.5$$

$$\Gamma \approx 0.75 \angle 63.4^\circ$$

$$SWR \approx 7$$

$$RL \approx 2.5 \text{ dB}$$

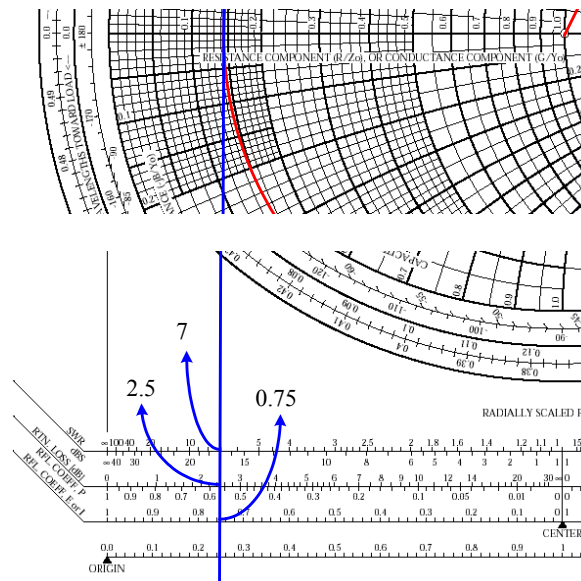

Dr. J.E. Rayas Sánchez

26

Smith Chart – Circles of *SWR*

Example:

$$Z_o = 50\Omega$$


$$Z_L = 25 + j75 \Omega$$

$$z_L = 0.5 + j1.5$$

$$\Gamma \approx 0.75 \angle 63.4^\circ$$

$$SWR \approx 7$$

$$RL \approx 2.5 \text{ dB}$$

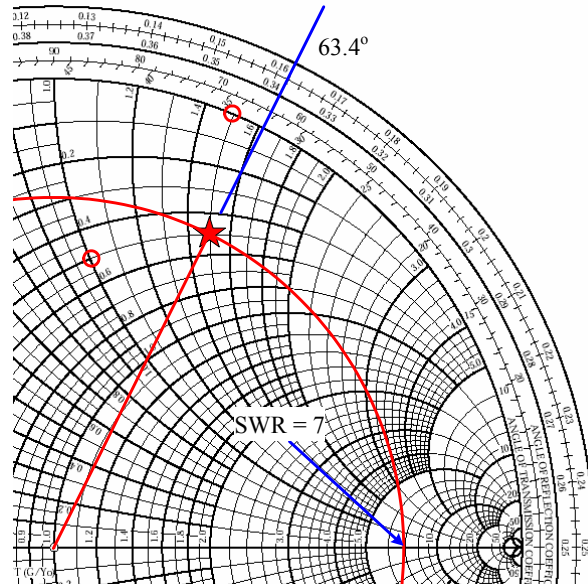

Dr. J.E. Rayas Sánchez

27

Smith Chart – Circles of *SWR* (cont)

Examples:


$$Z_o = 50\Omega$$

a) $Z_L = 50 \Omega$

b) $Z_L = 48.5 \Omega$

c) $Z_L = 75 + j25 \Omega$



d) $Z_L = 10 - j5 \Omega$

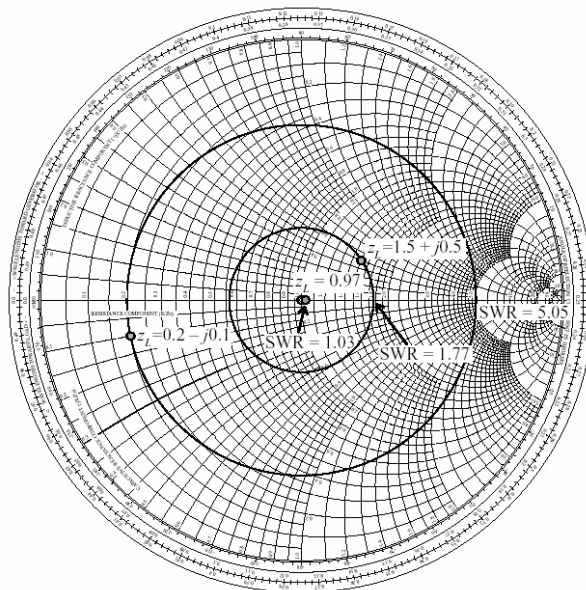

Dr. J.E. Rayas Sánchez

28

Smith Chart – Calculating Γ_l

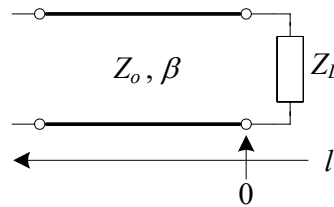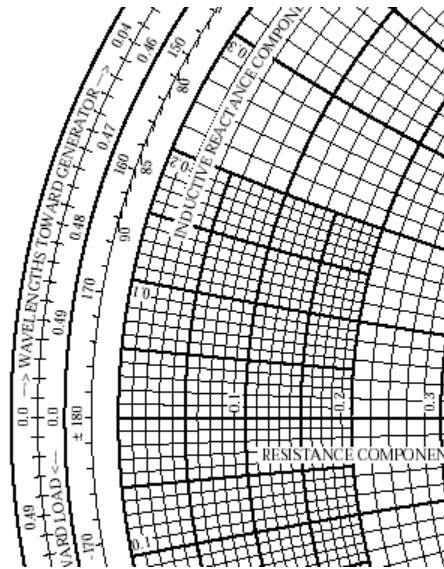

$$\Gamma_l(l) = \frac{V_o^- e^{-j\beta l}}{V_o^+ e^{j\beta l}} = \frac{V_o^-}{V_o^+} e^{-2j\beta l} = \Gamma e^{-2j\beta l}$$

$$\text{Since } \beta = \frac{2\pi}{\lambda}$$



$$\Gamma_l(l) = \Gamma e^{-2j\frac{2\pi}{\lambda}l} \quad (\text{Period} = \lambda/2)$$

$\frac{l}{\lambda}$ is the length in wavelengths

Dr. J.E. Rayas Sánchez

29

Smith Chart – Calculating Z_{in}

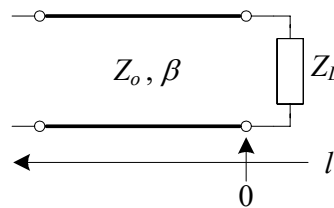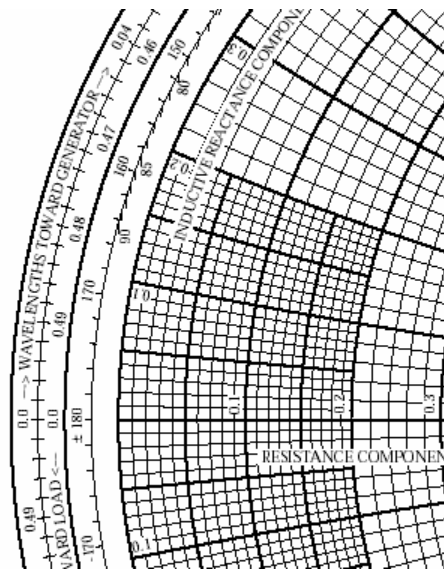

$$\Gamma_l(l) = \Gamma e^{-2j\frac{2\pi}{\lambda}l}$$

$\frac{l}{\lambda}$ is the length in wavelengths

$$\Gamma_l = \frac{Z_{in}(l) - Z_o}{Z_{in}(l) + Z_o}$$

Dr. J.E. Rayas Sánchez

30

Smith Chart – Calculating Γ_l and Z_{in}

Example:

$$Z_o = 50\Omega$$

$$Z_L = 25 + j75 \Omega$$

$$l = 1\text{cm}$$

$$f = 1\text{GHz}$$


$$\epsilon_r = 4$$

$$\Gamma_l = ?$$

$$Z_{in} = ?$$

$$z_L = 0.5 + j1.5$$
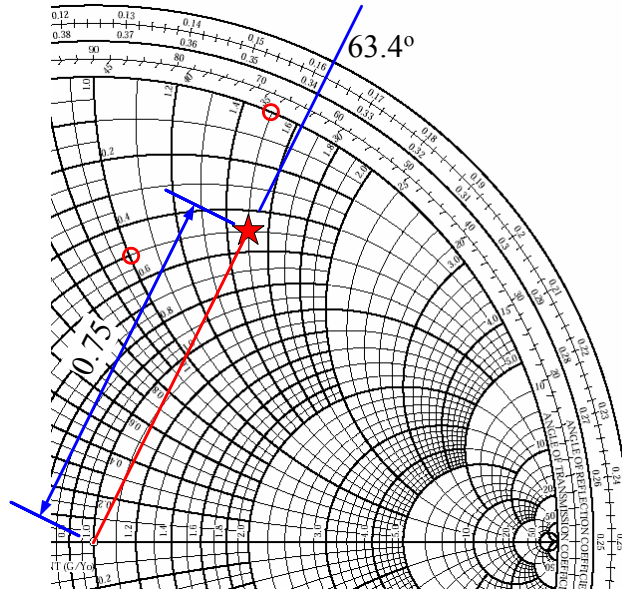
$$\Gamma \approx 0.75 \angle 63.4^\circ$$



Dr. J.E. Rayas Sánchez

31

Smith Chart – Calculating Γ_l and Z_{in} (cont)

Example:

$$Z_o = 50\Omega$$

$$Z_L = 25 + j75 \Omega$$

$$l = 1\text{cm}$$

$$f = 1\text{GHz}$$


$$\epsilon_r = 4$$

$$\Gamma_l = ?$$

$$Z_{in} = ?$$

$$\lambda = \frac{v_p}{f} = \frac{c}{f\sqrt{\epsilon_r}}$$
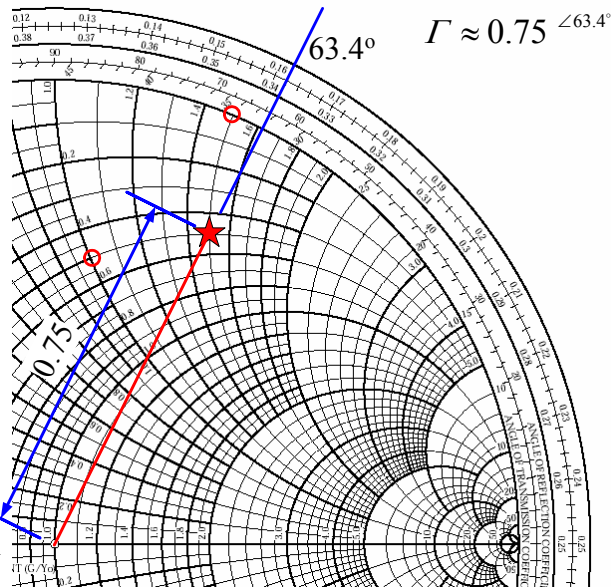
$$\lambda = \frac{0.3\text{Gm/s}}{1\text{GHz}\sqrt{4}} = 15\text{cm}$$



Dr. J.E. Rayas Sánchez

32

Smith Chart – Calculating Γ_l and Z_{in} (cont)

Example:

$$Z_o = 50\Omega$$

$$Z_L = 25 + j75 \Omega$$

$$l = 1\text{cm}$$

$$f = 1\text{GHz}$$

$$\epsilon_r = 4$$


$$\Gamma_l = ?$$

$$Z_{in} = ?$$

$$\frac{l}{\lambda} = \frac{1\text{cm}}{15\text{cm}} = 0.067$$

$$0.162 + 0.067 = 0.229$$

Dr. J.E. Rayas Sánchez

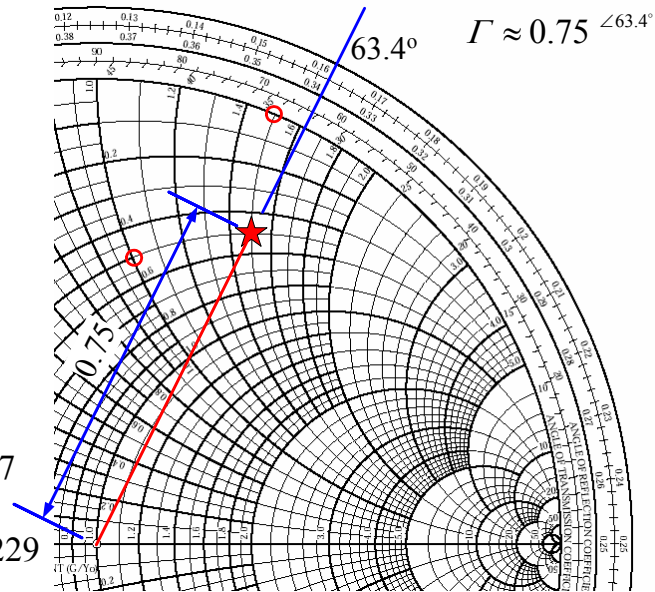

33

Smith Chart – Calculating Γ_l and Z_{in} (cont)

Example:

$$Z_o = 50\Omega$$

$$Z_L = 25 + j75 \Omega$$

$$l = 1\text{cm}$$

$$f = 1\text{GHz}$$

$$\epsilon_r = 4$$


$$\Gamma_l = ?$$

$$Z_{in} = ?$$

$$\frac{l}{\lambda} = \frac{1\text{cm}}{15\text{cm}} = 0.0667$$

$$0.162 + 0.067 = 0.229$$

Dr. J.E. Rayas Sánchez

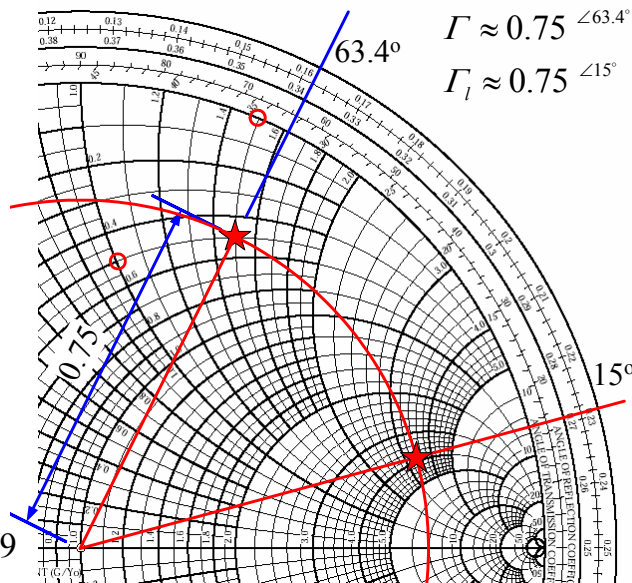

34

Smith Chart – Calculating Γ_l and Z_{in} (cont)

Example:

$$Z_o = 50\Omega$$

$$Z_L = 25 + j75 \Omega$$

$$l = 1\text{cm}$$

$$f = 1\text{GHz}$$

$$\epsilon_r = 4$$

$$\Gamma_l = ?$$


$$Z_{in} = ?$$

$$z_{in} = 3.8 + j3.4$$

$$Z_{in} = 50(3.8 + j3.4) \Omega$$

$$Z_{in} \approx 190 + j170 \Omega$$

Dr. J.E. Rayas Sánchez

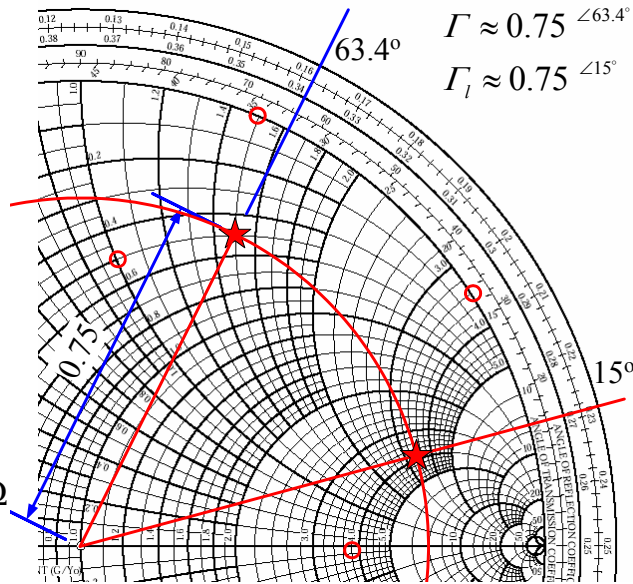

35

Smith Chart – Circles of SWR , V_{max} and V_{min}

Since $|V(l)| = |V_o^+| |1 + |\Gamma| e^{+j(\theta - 2\beta l)}|$

where $\Gamma = |\Gamma| e^{j\theta}$

We can locate the positions of V_{max} and V_{min} along the line

Example:

$$Z_o = 50\Omega$$

$$Z_L = 60 + j40 \Omega$$


$$z_L = 1.2 + j0.8 \Omega$$

$$SWR \approx 2.1$$

$$WL_{max} = 0.25 - 0.172$$

$$WL_{max} = 0.078$$

Dr. J.E. Rayas Sánchez

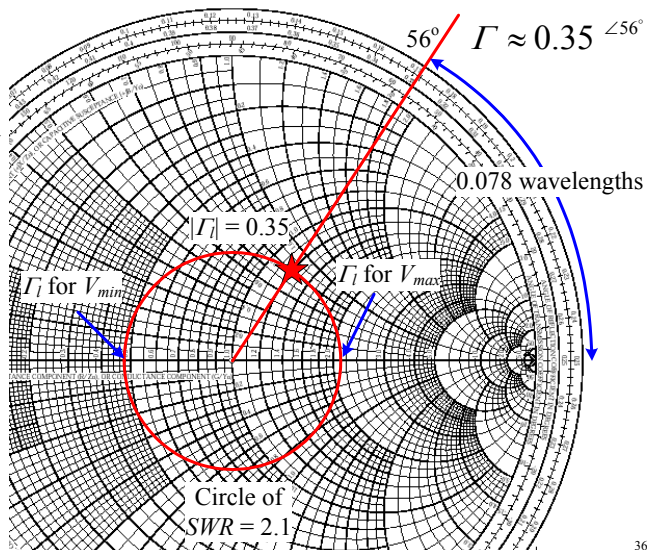

36