

Transmission Line Theory

(Part 4)


Dr. José Ernesto Rayas Sánchez

1

Outline



- Open circuit transformations
- Short circuit transformations
- Impedance-admittance transformations
- The quarter-wave transformer
- Lossy vs lossless transmission lines
- The low-loss TL
- The lossy distortionless TL

Open Circuit Transformations

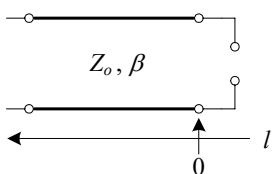

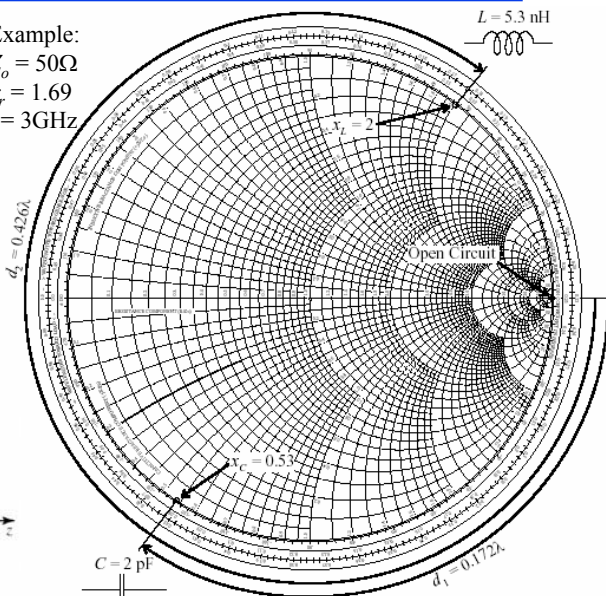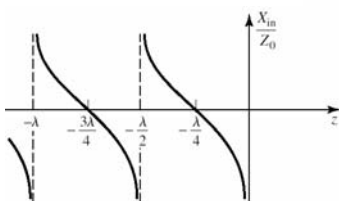
Example:
 $Z_o = 50\Omega$
 $\epsilon_r = 1.69$
 $f = 3\text{GHz}$

Given Z_o , ϵ_r and f ,
 we can calculate the
 lengths for a desired
 C or L





3

Short Circuit Transformations

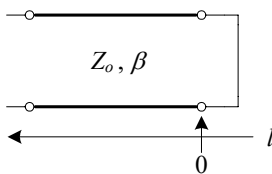

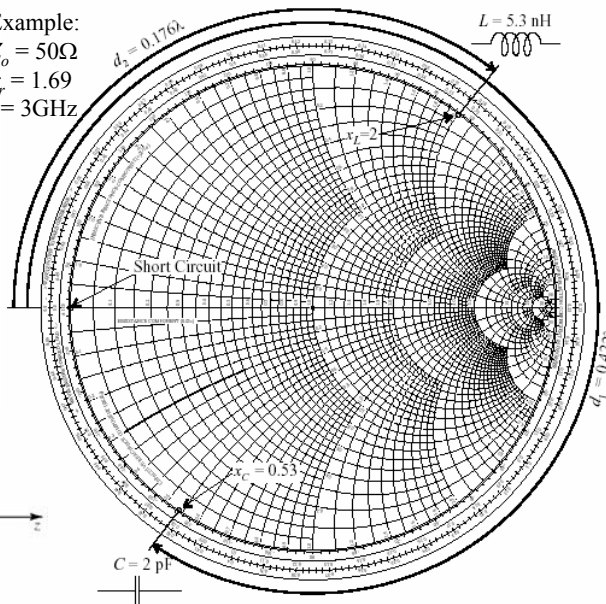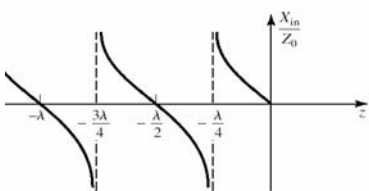
Example:
 $Z_o = 50\Omega$
 $\epsilon_r = 1.69$
 $f = 3\text{GHz}$

Given Z_o , ϵ_r and f ,
 we can calculate the
 lengths for a desired
 L or C



4


Impedance–Admittance Transformations

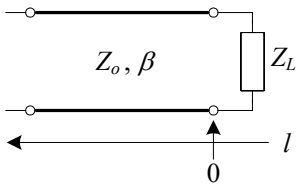

$$Z_{in}(l) = Z_o \frac{Z_L + jZ_o \tan(\beta l)}{Z_o + jZ_L \tan(\beta l)}$$

$$Z_{in}(l = \frac{\lambda}{4}, \frac{3\lambda}{4}, \frac{5\lambda}{4}, \dots) = \frac{Z_o^2}{Z_L}$$
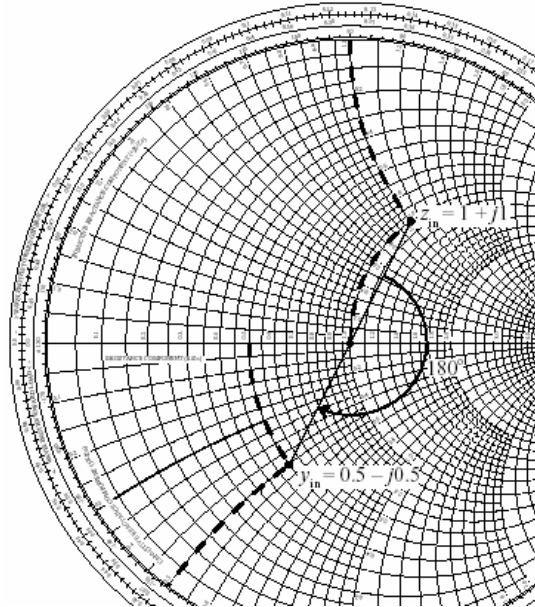
$$z_{in}(l = \frac{\lambda}{4}) = \frac{1}{z_L} = y_{in}$$




Dr. J.E. Rayas Sánchez

5

Quarter-Wave Transformer

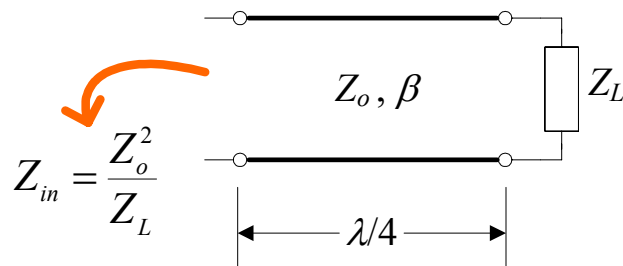
- Simple technique for impedance matching
- It can achieve perfect match at a single frequency



Dr. J.E. Rayas Sánchez

6

Quarter-Wave Transformer (cont)

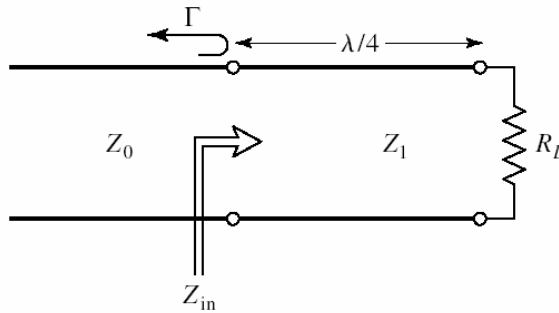

$$Z_{in} = \frac{Z_1^2}{R_L}$$

To make $\Gamma = 0$,


$$Z_1 = \sqrt{R_L Z_0}$$

Z_1 must be the geometric mean of Z_0 and R_L

Dr. J.E. Rayas Sánchez

7

Quarter-Wave Transformer - Example

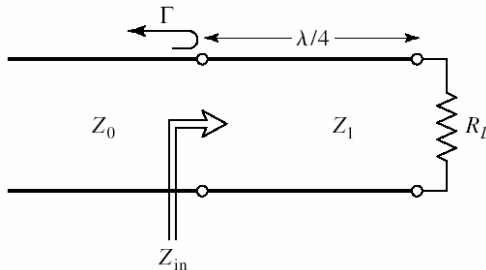

$$Z_0 = 50\Omega$$

$$R_L = 100\Omega$$

$$Z_1 = ?$$

$$\Gamma(f) = ?$$

$$Z_1 = \sqrt{(50)(100)} = 70.71\Omega$$

$\Gamma = 0$ only at the frequencies at which the electrical length of the matching section is 90° , 270° , ...


$$\text{Since } \Gamma_l = \frac{Z_{in}(l) - Z_0}{Z_{in}(l) + Z_0} \quad \text{and} \quad Z_{in}(l) = Z_0 \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)}$$

$$\beta l = \left(\frac{2\pi}{\lambda} \right) \left(\frac{\lambda_0}{4} \right) = \left(\frac{2\pi f}{v_p} \right) \left(\frac{v_p}{4f_0} \right) = \frac{\pi f}{2 f_0}$$

Dr. J.E. Rayas Sánchez

8

Quarter-Wave Transformer - Example

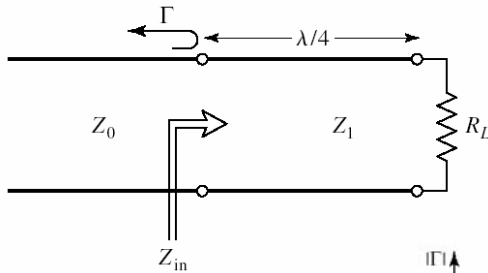

$$Z_o = 50\Omega$$


$$R_L = 100\Omega$$

$$Z_1 = ?$$

$$\Gamma(f) = ?$$

$$Z_1 = \sqrt{(50)(100)} = 70.71\Omega$$

$$\beta l = \frac{\pi f}{2 f_o}$$

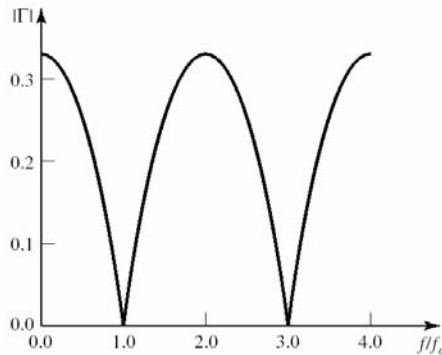

Dr. J.E. Rayas Sánchez

9

Lossy Transmission Lines

- In practice, all transmission lines have losses due to some finite conductivity and/or lossy dielectric
- These losses are usually small
- For analysis purposes (first-order approximations), these losses may be neglected
- There are two special cases of interest:
 - The low-loss line
 - The lossy distortionless line

Dr. J.E. Rayas Sánchez

10

Lossy vs Lossless Transmission Lines

$$V(z) = V_o^+ [e^{-\gamma z} + \Gamma e^{+\gamma z}]$$

$$I(z) = \frac{V_o^+}{Z_o} [e^{-\gamma z} - \Gamma e^{+\gamma z}]$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\gamma \equiv \alpha + j\beta$$

$$Z_o = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\Gamma_z(z) = \Gamma e^{+2\gamma z}$$

$$V(z) = V_o^+ [e^{-j\beta z} + \Gamma e^{+j\beta z}]$$

$$I(z) = \frac{V_o^+}{Z_o} [e^{-j\beta z} - \Gamma e^{+j\beta z}]$$

$$\beta = \omega\sqrt{LC} \quad Z_o = \sqrt{\frac{L}{C}}$$

$$\Gamma_z(z) = \Gamma e^{+2j\beta z}$$

$$Z_o \equiv \frac{V_o^+}{I_o^+} = \frac{V_o^-}{-I_o^-} \quad \Gamma = \frac{V_o^-}{V_o^+} = \frac{Z_L - Z_o}{Z_L + Z_o} \quad \lambda = \frac{v_p}{f} = \frac{2\pi}{\beta} \quad v_p = \frac{\omega}{\beta}$$

Dr. J.E. Rayas Sánchez

11

The Low-Loss Transmission Line

- It is a line where $R \ll \omega L$ and $G \ll \omega C$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\gamma = \sqrt{(j\omega L)(j\omega C) \left(1 + \frac{R}{j\omega L}\right) \left(1 + \frac{G}{j\omega C}\right)}$$

$$\gamma = j\omega\sqrt{LC} \sqrt{1 - j\left(\frac{R}{\omega L} + \frac{G}{\omega C}\right) - \frac{RG}{\omega^2 LC}}$$

$$\gamma \approx j\omega\sqrt{LC} \sqrt{1 - j\left(\frac{R}{\omega L} + \frac{G}{\omega C}\right)}$$

$$\text{Using } \sqrt{1+x} = 1 + \frac{1}{2}x - \frac{1}{2 \cdot 4}x^2 + \frac{1 \cdot 3}{2 \cdot 4 \cdot 6}x^3 - \dots$$

Dr. J.E. Rayas Sánchez

12

The Low-Loss Transmission Line (cont)

- It is a line where $R \ll \omega L$ and $G \ll \omega C$

$$\gamma \approx j\omega\sqrt{LC} \left[1 - \frac{j}{2} \left(\frac{R}{\omega L} + \frac{G}{\omega C} \right) \right]$$

$$\gamma \equiv \alpha + j\beta$$

$$\beta \approx \omega\sqrt{LC} \quad \beta \text{ is almost a linear function of } \omega$$

(no dispersion)

$$\alpha \approx \frac{1}{2} \left(R\sqrt{\frac{C}{L}} + G\sqrt{\frac{L}{C}} \right) \quad Z_o = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \approx \sqrt{\frac{L}{C}}$$

$$\alpha \approx \frac{1}{2} \left(\frac{R}{Z_o} + GZ_o \right)$$

Dr. J.E. Rayas Sánchez

13

The Lossy Distorsionless Transmission Line

- It is a line where $R/L = G/C$

$$\text{Since } \gamma = j\omega\sqrt{LC} \sqrt{1 - j \left(\frac{R}{\omega L} + \frac{G}{\omega C} \right) - \frac{RG}{\omega^2 LC}}$$

$$\gamma = j\omega\sqrt{LC} \sqrt{1 - 2j \frac{R}{\omega L} - \frac{R^2}{\omega^2 L^2}}$$

$$\gamma = j\omega\sqrt{LC} \left(1 - j \frac{R}{\omega L} \right)$$

$$\gamma \equiv \alpha + j\beta$$

$$\beta = \omega\sqrt{LC} \quad \alpha = R\sqrt{\frac{C}{L}}$$

β is a linear function of ω (non dispersive TL)

Dr. J.E. Rayas Sánchez

14