

Time-Domain Analysis of Transmission Line Circuits

(Part 1)


Dr. José Ernesto Rayas Sánchez

1

Outline

- Quarter-wave transformer – steady state response
- Quarter-wave transformer – transient response
- Reflection coefficient revised
- Concept of “transient impedance”
- Applying DC to transmission lines
- Lattice (or bouncing or reflection) diagrams
- Building transient signals from bouncing diagrams

Quarter-Wave Transformer

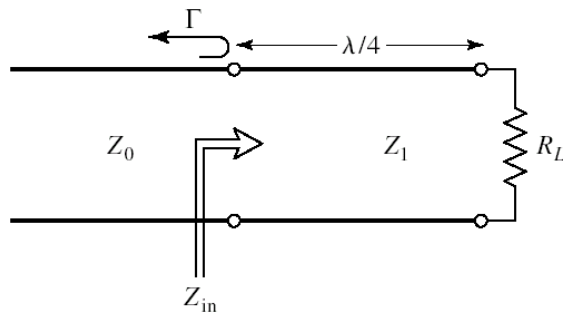

$$Z_{in} = \frac{Z_1^2}{R_L}$$

To make $\Gamma = 0$,

$$Z_1 = \sqrt{R_L Z_0}$$


Z_1 must be the geometric mean of Z_0 and R_L

Γ is the steady-state reflection coefficient

Dr. J.E. Rayas Sánchez

3

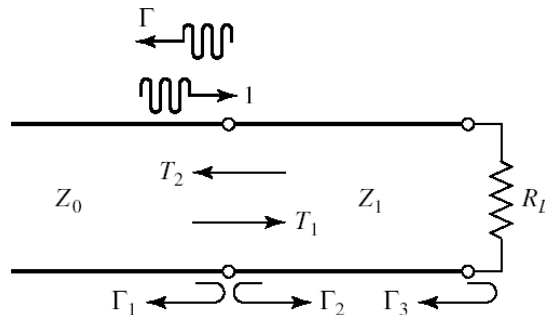Quarter-Wave Transformer – Transient Response



$$\Gamma_1 = \frac{Z_1 - Z_0}{Z_1 + Z_0}$$

$$\Gamma_2 = \frac{Z_0 - Z_1}{Z_0 + Z_1} = -\Gamma_1$$

$$\Gamma_3 = \frac{R_L - Z_1}{R_L + Z_1}$$


$$T_1 = 1 + \Gamma_1 = \frac{2Z_1}{Z_1 + Z_0}$$

$$T_2 = 1 + \Gamma_2 = \frac{2Z_0}{Z_0 + Z_1}$$

Dr. J.E. Rayas Sánchez

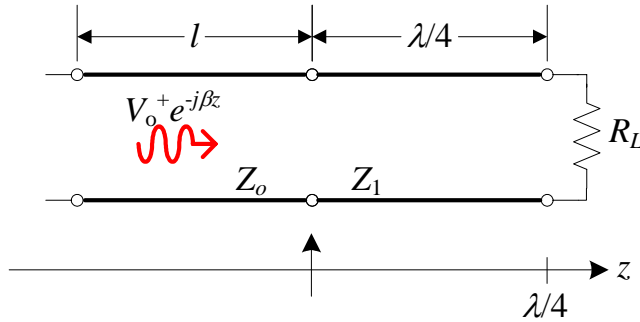(D. M. Pozar, *Microwave Engineering*, Wiley, 2005) 4

Quarter-Wave Transformer – Transient Response




Initially, the incoming wave has only the incident component:

$$V(z) = V_o^+ e^{-j\beta z}$$

Dr. J.E. Rayas Sánchez

5

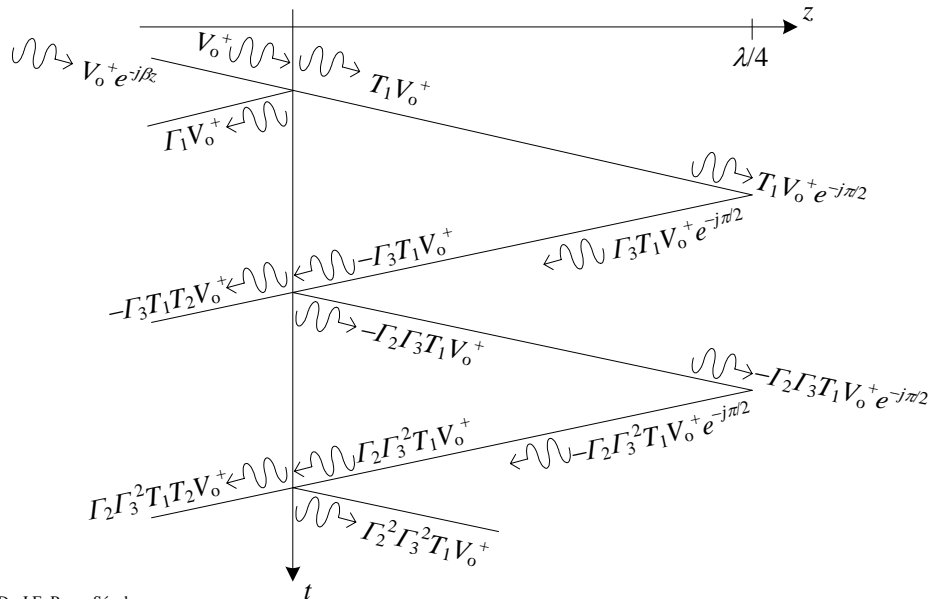
Quarter-Wave Transformer – Transient Response



Dr. J.E. Rayas Sánchez

6

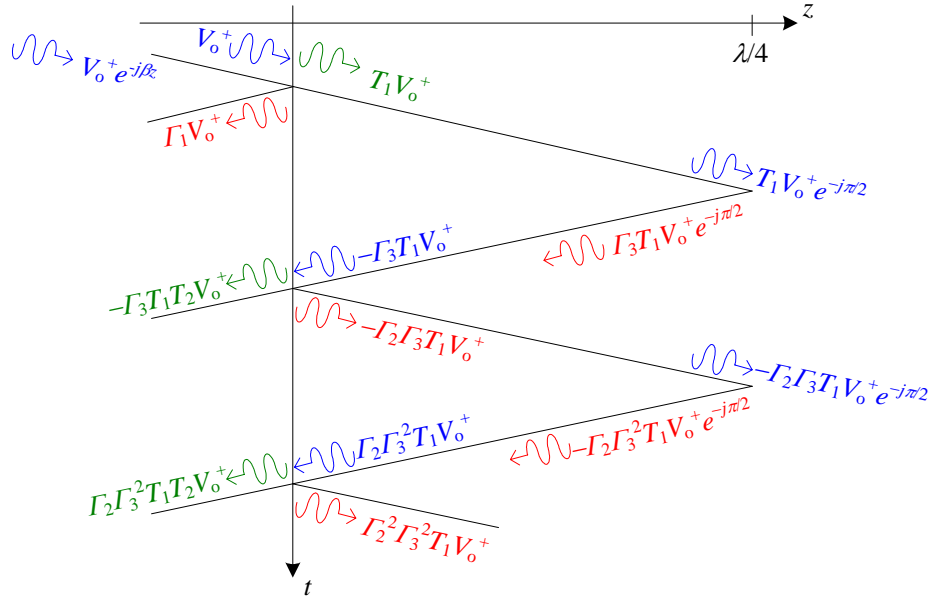
Quarter-Wave Transformer – Transient Response



Dr. J.E. Rayas Sánchez

7

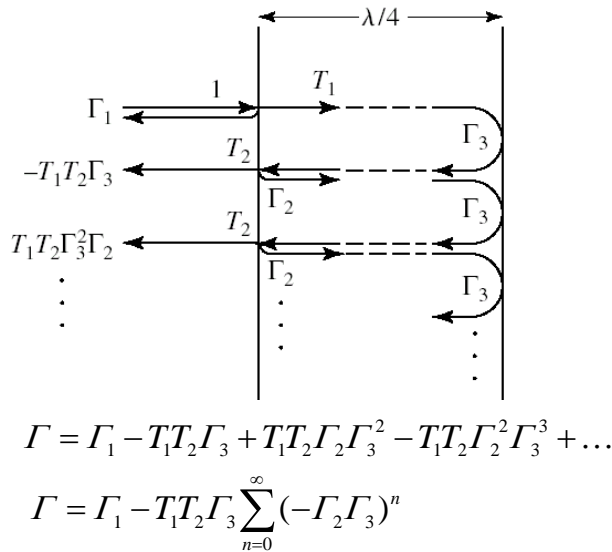Quarter-Wave Transformer – Transient Response



Dr. J.E. Rayas Sánchez

8

Quarter-Wave Transformer – Transient Response

$$\Gamma = \Gamma_1 - T_1 T_2 \Gamma_3 \sum_{n=0}^{\infty} (-\Gamma_2 \Gamma_3)^n$$

Since $\sum_{n=0}^{\infty} x^n = \frac{1}{1-x}$, for $|x| < 1$

$$\Gamma = \Gamma_1 - \frac{T_1 T_2 \Gamma_3}{1 + \Gamma_2 \Gamma_3} = \frac{\Gamma_1 + \Gamma_1 \Gamma_2 \Gamma_3 - T_1 T_2 \Gamma_3}{1 + \Gamma_2 \Gamma_3}$$

using


$$\Gamma_1 = \frac{Z_1 - Z_o}{Z_1 + Z_o} \quad \Gamma_2 = -\Gamma_1 \quad \Gamma_3 = \frac{R_L - Z_1}{R_L + Z_1} \quad T_1 = \frac{2Z_1}{Z_1 + Z_o} \quad T_2 = \frac{2Z_o}{Z_o + Z_1}$$

$$\Gamma_1 + \Gamma_1 \Gamma_2 \Gamma_3 - T_1 T_2 \Gamma_3 = \frac{2(Z_1^2 - Z_o R_L)}{(Z_1 + Z_o)(R_L + Z_1)} = 0 \quad \text{if } Z_1 = \sqrt{Z_o R_L}$$

Dr. J.E. Rayas Sánchez

9

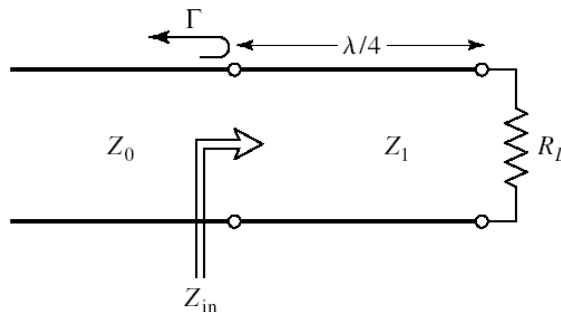Quarter-Wave Transformer – Transient Response




$$\Gamma = \Gamma_1 - T_1 T_2 \Gamma_3 \sum_{n=0}^{\infty} (-\Gamma_2 \Gamma_3)^n = 0 \quad \text{if } Z_1 = \sqrt{Z_o R_L}$$

If Z_1 is the geometric mean of Z_o and R_L , the sum of the infinite number of partial reflections is zero

Dr. J.E. Rayas Sánchez

10


Applying DC to Transmission Lines

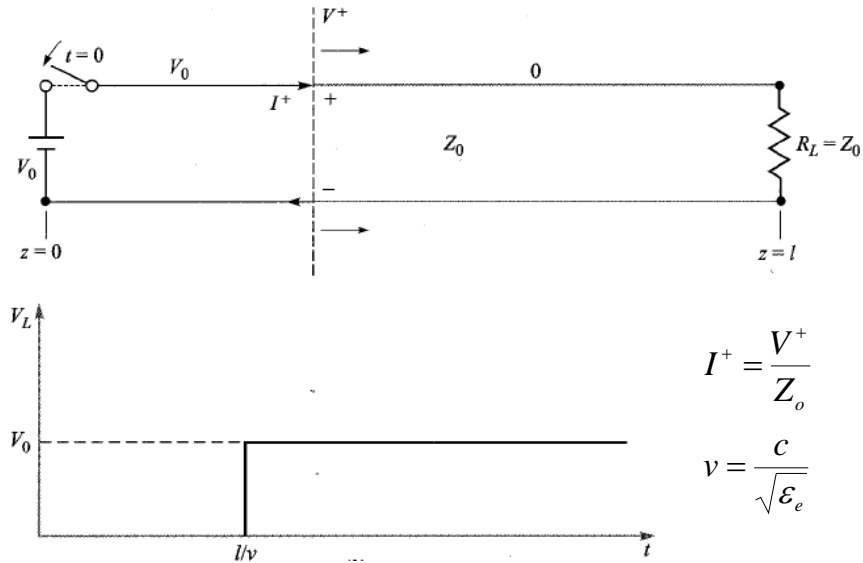

Dr. J.E. Rayas Sánchez

11

Applying DC to Transmission Lines (cont)

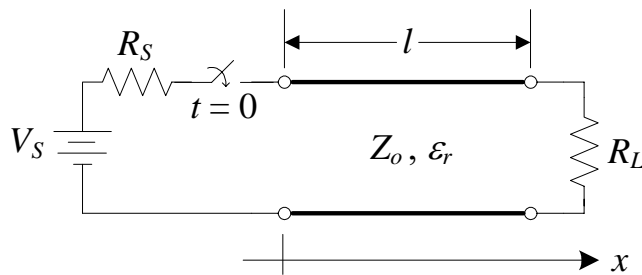

$$\Gamma_S = \frac{R_S - Z_0}{R_S + Z_0} \quad \Gamma_L = \frac{R_L - Z_0}{R_L + Z_0} \quad v_p = \frac{c}{\sqrt{\epsilon_e}}$$


$$V_o^+ = \frac{V_S Z_0}{R_S + Z_0} \quad I_o^+ = \frac{V_o^+}{Z_0}$$

Dr. J.E. Rayas Sánchez

12

Lattice (or Bouncing or Reflection) Diagrams


- Voltage Diagrams

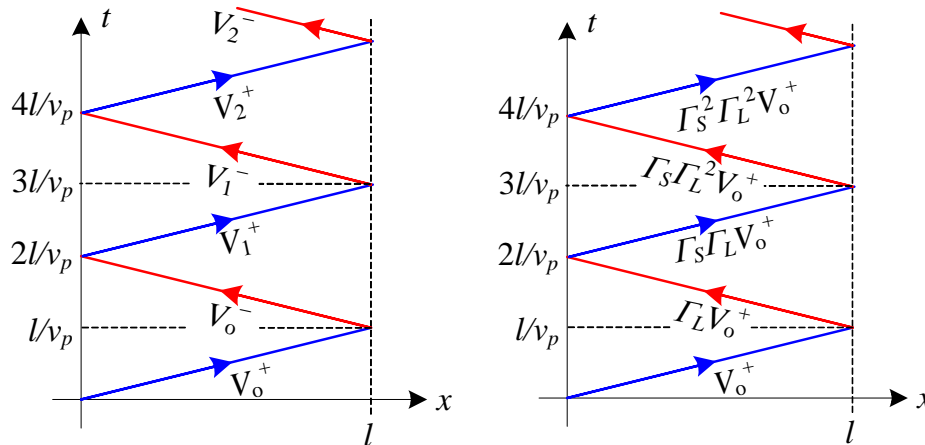

Dr. J.E. Rayas Sánchez

13


Bouncing Diagrams for Currents

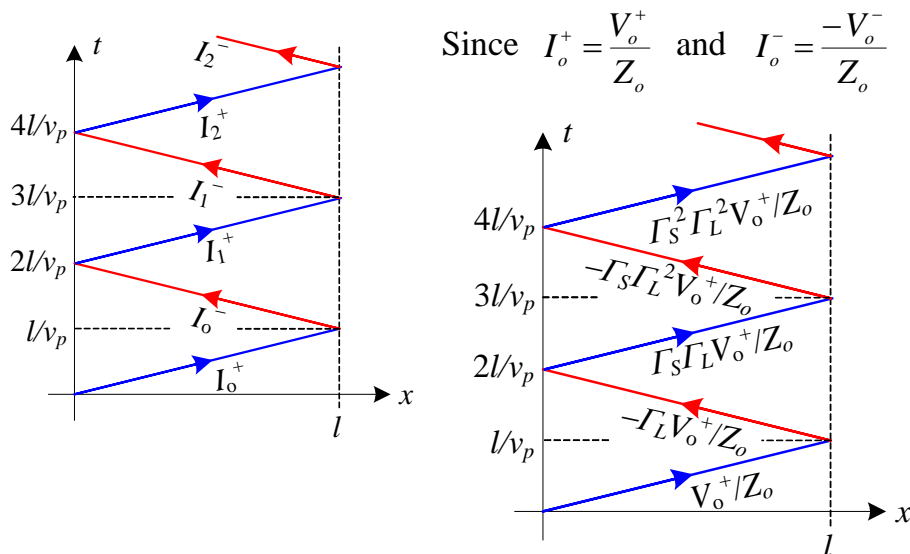

Dr. J.E. Rayas Sánchez

14


Transient Signals from Bouncing Diagrams

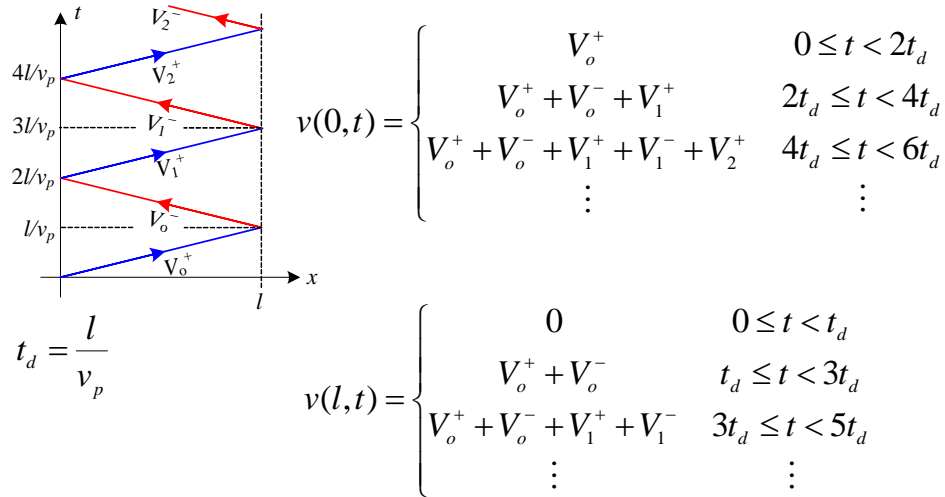


Dr. J.E. Rayas Sánchez

15

Bouncing Diagrams – Other Representation

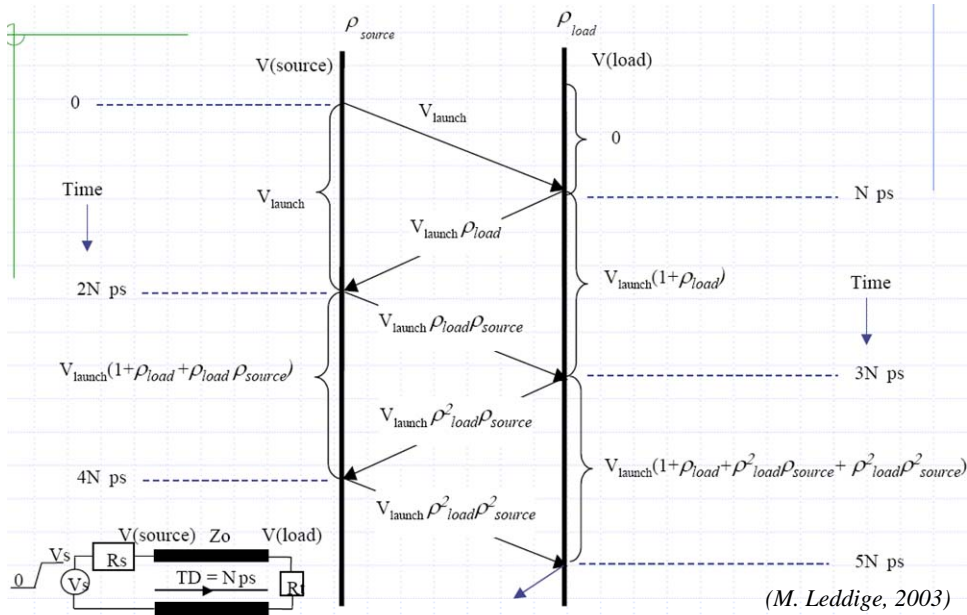

Example – Underdriven Transmission Line

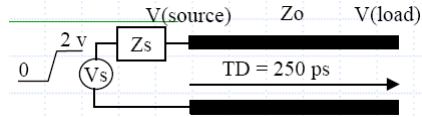


Assume $Z_s = 75$ ohms
 $Z_o = 50$ ohms
 $V_s = 0-2$ volts

$$V_{initial} = V_s \frac{Z_o}{Z_s + Z_o} = (2) \left(\frac{50}{75 + 50} \right) = 0.8$$



$$\rho_{source} = \frac{Z_s - Z_o}{Z_s + Z_o} = \frac{75 - 50}{75 + 50} = 0.2$$
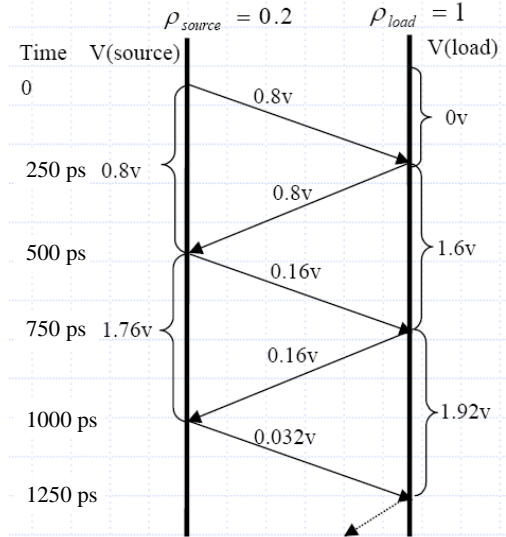
$$\rho_{load} = \frac{Z_l - Z_o}{Z_l + Z_o} = \frac{\infty - 50}{\infty + 50} = 1$$




Dr. J.E. Rayas Sánchez (S.H. Hall, G.W. Hall and J.A. McCall, *High-Speed Digital System Design*, Wiley, 2000) ¹⁷

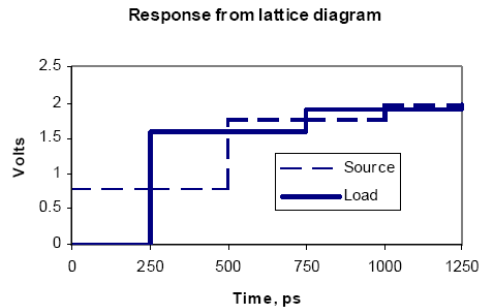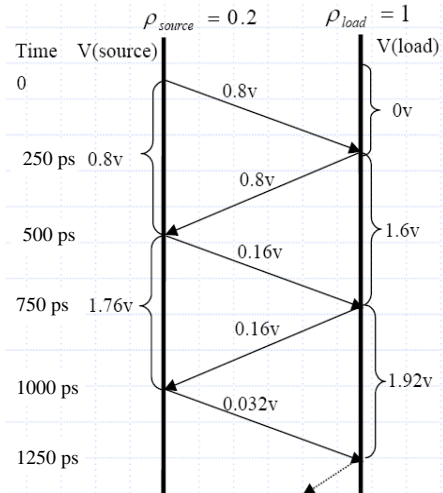Example – Underdriven Transmission Line (cont)



Dr. J.E. Rayas Sánchez (S.H. Hall, G.W. Hall and J.A. McCall, *High-Speed Digital System Design*, Wiley, 2000) ¹⁸

Example – Overdriven Transmission Line

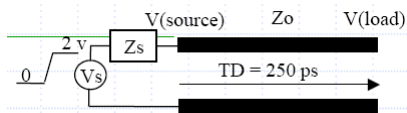


Assume $Z_s=25$ ohms
 $Z_o=50$ ohms
 $V_s=0-2$ volts

$$V_{initial} = V_s \frac{Z_o}{Z_s + Z_o} = (2) \left(\frac{50}{25 + 50} \right) = 1.3333$$


$$\rho_{source} = \frac{Z_s - Z_o}{Z_s + Z_o} = \frac{25 - 50}{25 + 50} = -0.333333$$
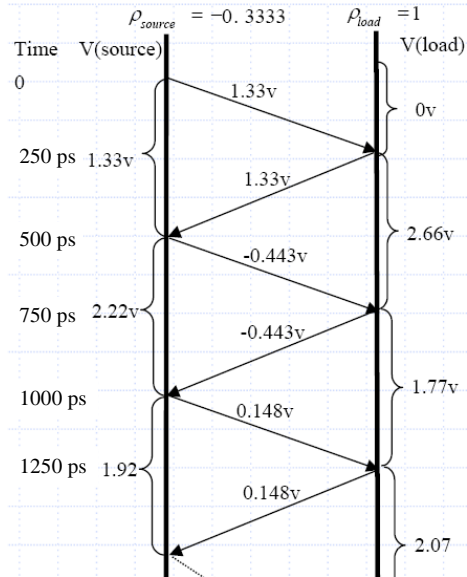
$$\rho_{load} = \frac{Z_l - Z_o}{Z_l + Z_o} = \frac{\infty - 50}{\infty + 50} = 1$$




Dr. J.E. Rayas Sánchez (S.H. Hall, G.W. Hall and J.A. McCall, *High-Speed Digital System Design*, Wiley, 2000) ¹⁹

Example – Overdriven Transmission Line

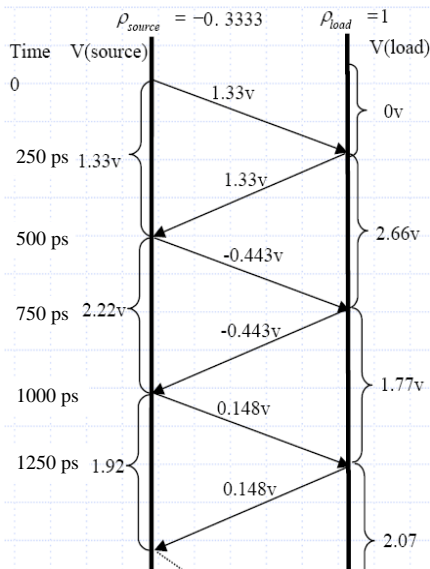


Response from lattice diagram

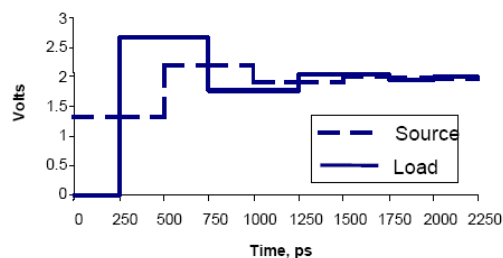

Dr. J.E. Rayas Sánchez (S.H. Hall, G.W. Hall and J.A. McCall, *High-Speed Digital System Design*, Wiley, 2000) ²⁰

Using the Bouncing Diagrams – Example

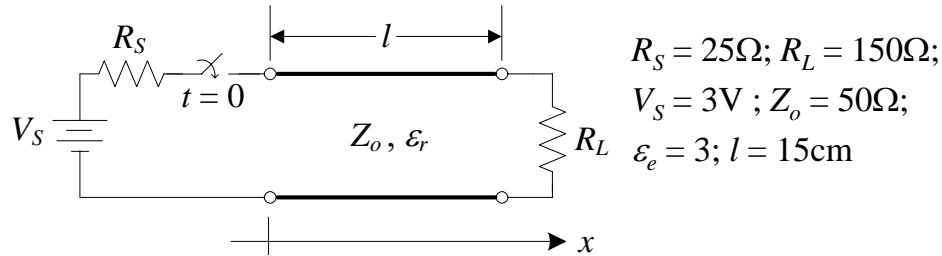


$$v(x=0,t) = ?; \quad v(x=l,t) = ?; \quad v(x=\frac{3}{4}l,t) = ?$$

$$i(x=0,t) = ?; \quad i(x=l,t) = ?; \quad i(x=\frac{3}{4}l,t) = ?$$

Dr. J.E. Rayas Sánchez

21

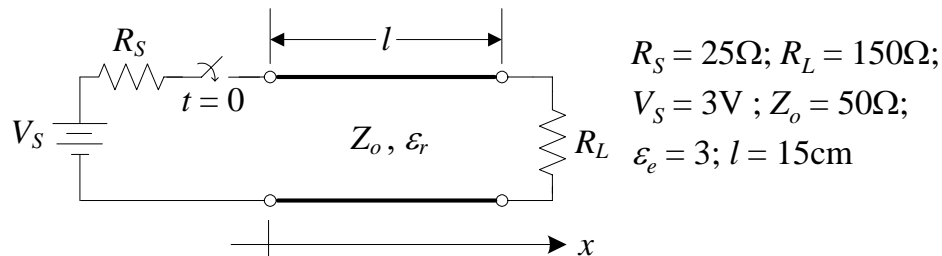Using the Bouncing Diagrams – Example (cont)




$$\Gamma_L = \frac{R_L - Z_o}{R_L + Z_o} = \frac{1}{2} \quad \Gamma_S = \frac{R_S - Z_o}{R_S + Z_o} = -\frac{1}{3} \quad V_o^+ = \frac{V_S Z_o}{R_S + Z_o} = 2\text{V}$$

$$v_p = \frac{c}{\sqrt{\epsilon_e}} = 173.2\text{Mm/s} \quad t_d = \frac{l}{v_p} = 866.02\text{ps}$$

Dr. J.E. Rayas Sánchez

22


Example Simulated with APLAC

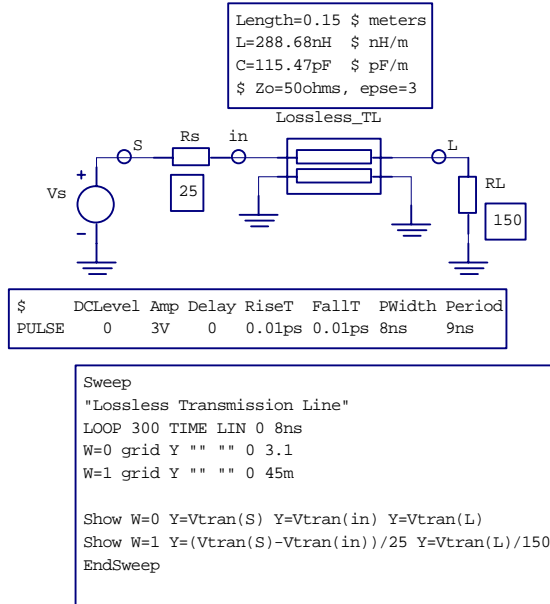

Dr. J.E. Rayas Sánchez

23

Example Simulated with APLAC (cont)

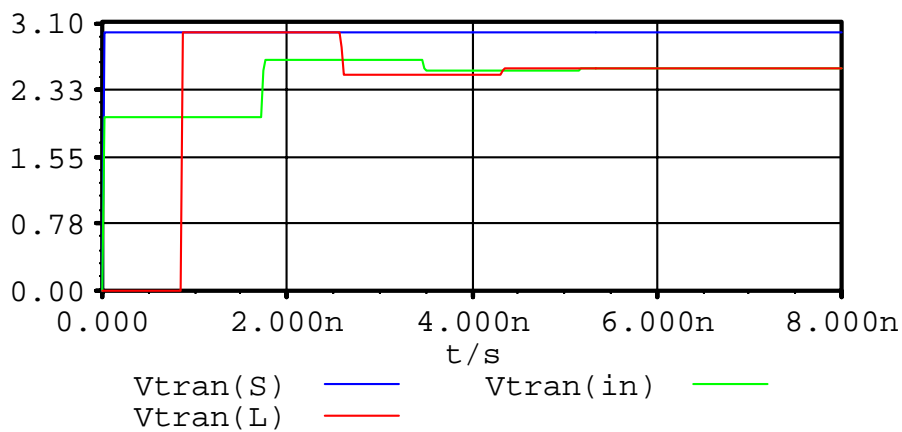

Dr. J.E. Rayas Sánchez

24

Example Simulated with APLAC (cont)

