

Time-Domain Analysis of Transmission Line Circuits

(Part 2)


Dr. José Ernesto Rayas Sánchez

1

Outline

- Usual definition of under-driven and over-driven lines
- Conditions for under-driven lines
- Conditions for over-driven lines
- Examples of under-driven and over-driven lines
- Bouncing diagrams for multiple sections of transmission lines
- Example of transient response in two sections of transmission lines

Example – Underdriven Transmission Line

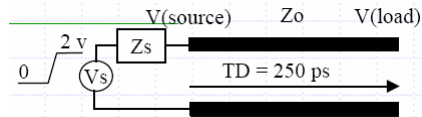


Assume $Z_s = 75$ ohms
 $Z_o = 50$ ohms
 $V_s = 0-2$ volts

$$V_{initial} = V_s \frac{Z_o}{Z_s + Z_o} = (2) \left(\frac{50}{75 + 50} \right) = 0.8$$

$$\rho_{source} = \frac{Z_s - Z_o}{Z_s + Z_o} = \frac{75 - 50}{75 + 50} = 0.2$$



$$\rho_{load} = \frac{Z_l - Z_o}{Z_l + Z_o} = \frac{\infty - 50}{\infty + 50} = 1$$

($\Gamma_S > 0$)

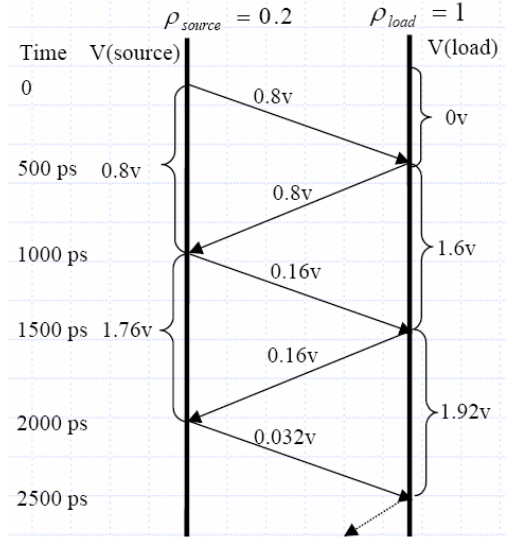

Dr. J.E. Rayas Sánchez (S.H. Hall, G.W. Hall and J.A. McCall, *High-Speed Digital System Design*, Wiley, 2000) 3

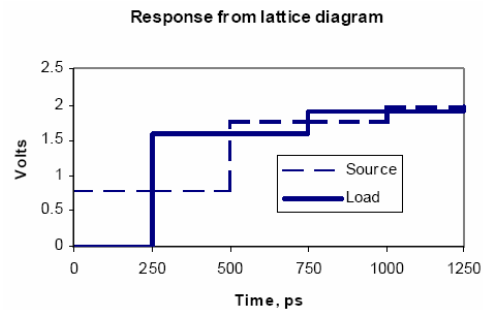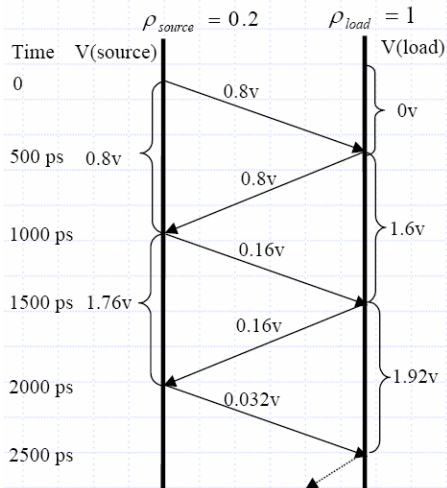
Example – Underdriven Transmission Line (cont)



($\Gamma_S > 0$)

Dr. J.E. Rayas Sánchez (S.H. Hall, G.W. Hall and J.A. McCall, *High-Speed Digital System Design*, Wiley, 2000) 4

Example – Overdriven Transmission Line

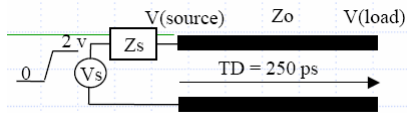


Assume $Z_s=25$ ohms
 $Z_o=50$ ohms
 $V_s=0-2$ volts

$$V_{initial} = V_s \frac{Z_o}{Z_s + Z_o} = (2) \left(\frac{50}{25 + 50} \right) = 1.3333$$

$$\rho_{source} = \frac{Z_s - Z_o}{Z_s + Z_o} = \frac{25 - 50}{25 + 50} = -0.33333$$


$$\rho_{load} = \frac{Z_l - Z_o}{Z_l + Z_o} = \frac{\infty - 50}{\infty + 50} = 1$$

($\Gamma_S < 0$)

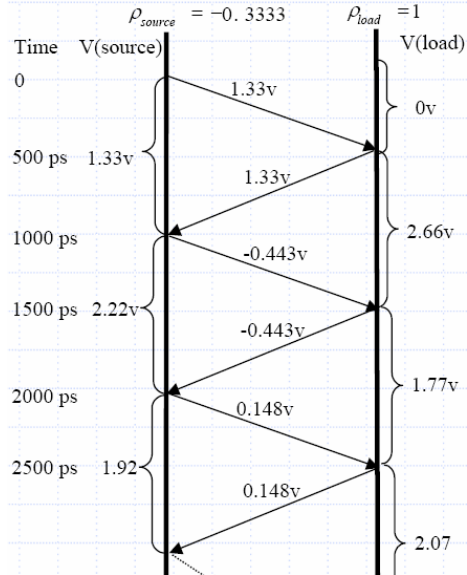


Dr. J.E. Rayas Sánchez (S.H. Hall, G.W. Hall and J.A. McCall, *High-Speed Digital System Design*, Wiley, 2000) 5

Example – Overdriven Transmission Line

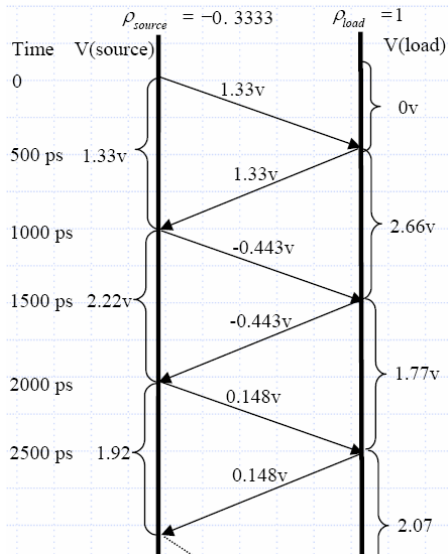


Response from lattice diagram

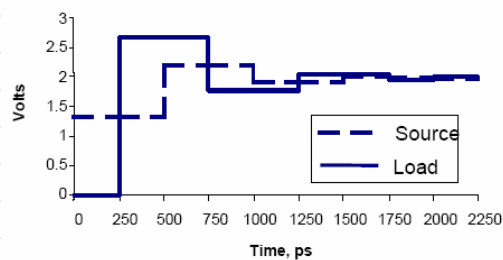

($\Gamma_S < 0$)

Dr. J.E. Rayas Sánchez (S.H. Hall, G.W. Hall and J.A. McCall, *High-Speed Digital System Design*, Wiley, 2000) 6

Underdriven and Overdriven Lines Revised

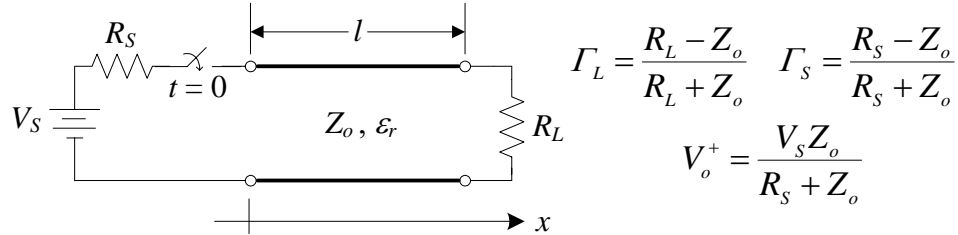

Let $v(x=l, t=t_d) = v_d$ } A line is underdriven if $v_d < v_\infty$
 $v(x=l, t \rightarrow \infty) = v_\infty$ } A line is overdriven if $v_d > v_\infty$


$$v_\infty = \frac{V_S R_L}{R_S + R_L} \quad v_d = V_o^+ (1 + \Gamma_L)$$

$$v_d = \frac{V_S Z_o}{R_S + Z_o} \left(1 + \frac{R_L - Z_o}{R_L + Z_o} \right) = \frac{V_S Z_o}{R_S + Z_o} \left(\frac{2R_L}{R_L + Z_o} \right)$$

Dr. J.E. Rayas Sánchez

7

Conditions for Underdriven Lines

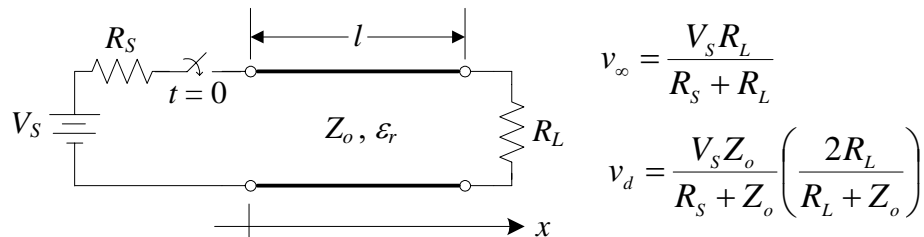

$v_d < v_\infty$ if

$$\frac{2Z_o}{R_S + Z_o} < \frac{R_L + Z_o}{R_L + R_S}$$


if $R_S > Z_o$, let $R_S = aZ_o$, $a > 1$ if $R_S < Z_o$, let $R_S = aZ_o$, $0 < a < 1$
 $(R_L - Z_o) < a(R_L - Z_o)$ $(R_L - Z_o) < a(R_L - Z_o)$
→ $R_L > Z_o$ **→** $R_L < Z_o$

Hence, $\Gamma_S \Gamma_L > 0$ **↔** underdriven line

Dr. J.E. Rayas Sánchez

8

Conditions for Overdriven Lines

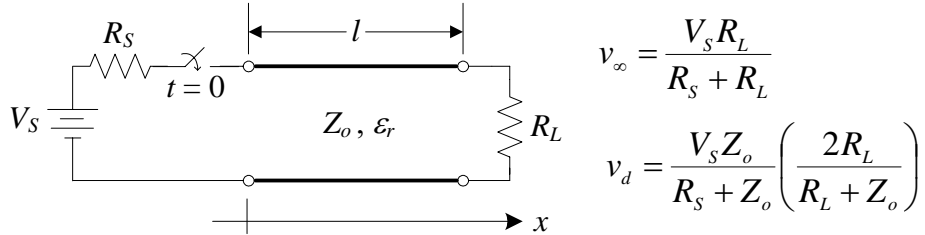

$v_d > v_\infty$ if

$$\frac{2Z_o}{R_S + Z_o} > \frac{R_L + Z_o}{R_L + R_S}$$

if $R_S > Z_o$, let $R_S = aZ_o$, $a > 1$ if $R_S < Z_o$, let $R_S = aZ_o$, $0 < a < 1$

$$(R_L - Z_o) > a(R_L - Z_o)$$

$$(R_L - Z_o) > a(R_L - Z_o)$$

→ $R_L < Z_o$



→ $R_L > Z_o$

Hence, $\Gamma_S \Gamma_L < 0 \iff$ overdriven line

Dr. J.E. Rayas Sánchez

9

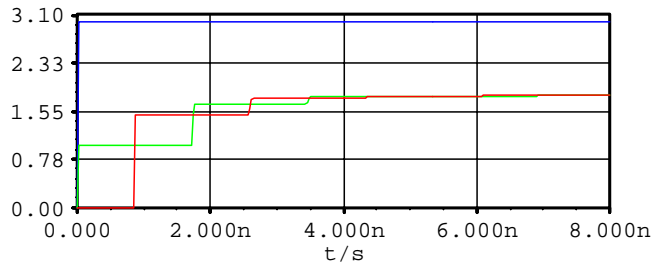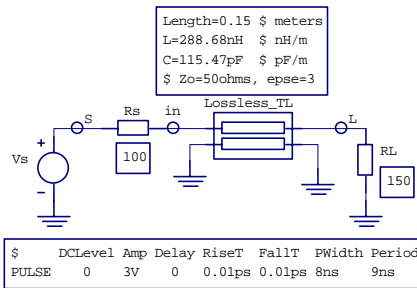
Example 1: $\Gamma_S > 0$ and $\Gamma_L > 0$



Dr. J.E. Rayas Sánchez

10

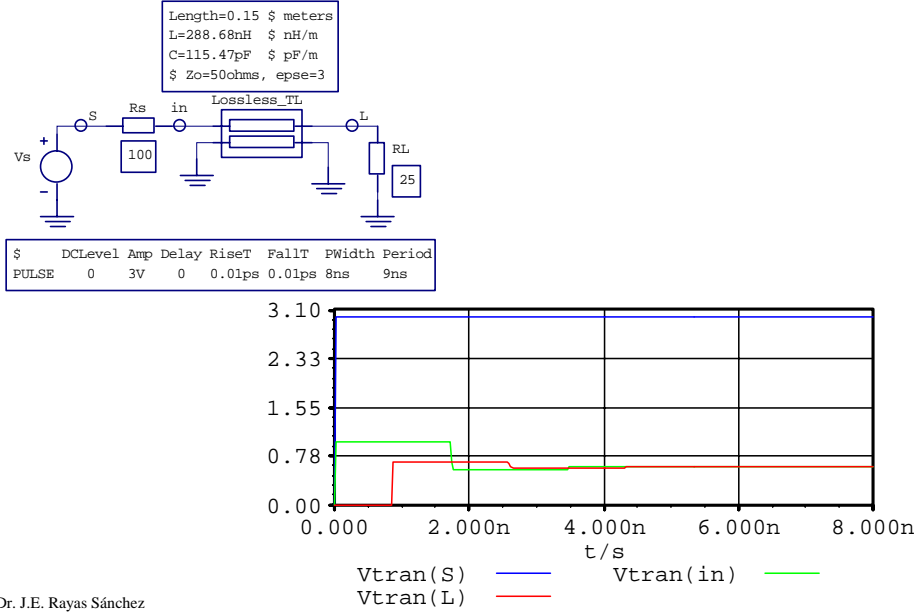
Example 2: $\Gamma_S > 0$ and $\Gamma_L < 0$



Dr. J.E. Rayas Sánchez

11

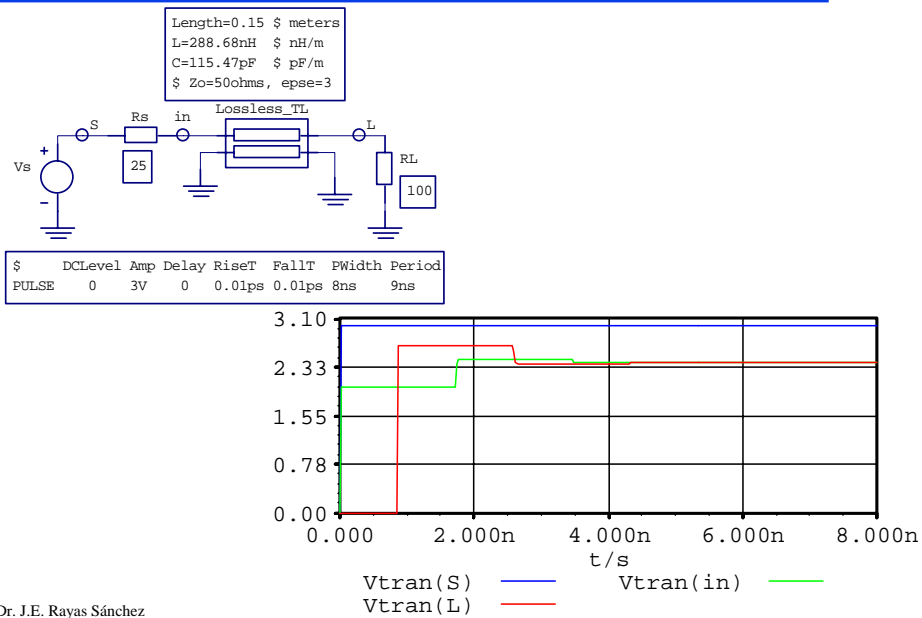
Example 3: $\Gamma_S < 0$ and $\Gamma_L > 0$



Dr. J.E. Rayas Sánchez

12

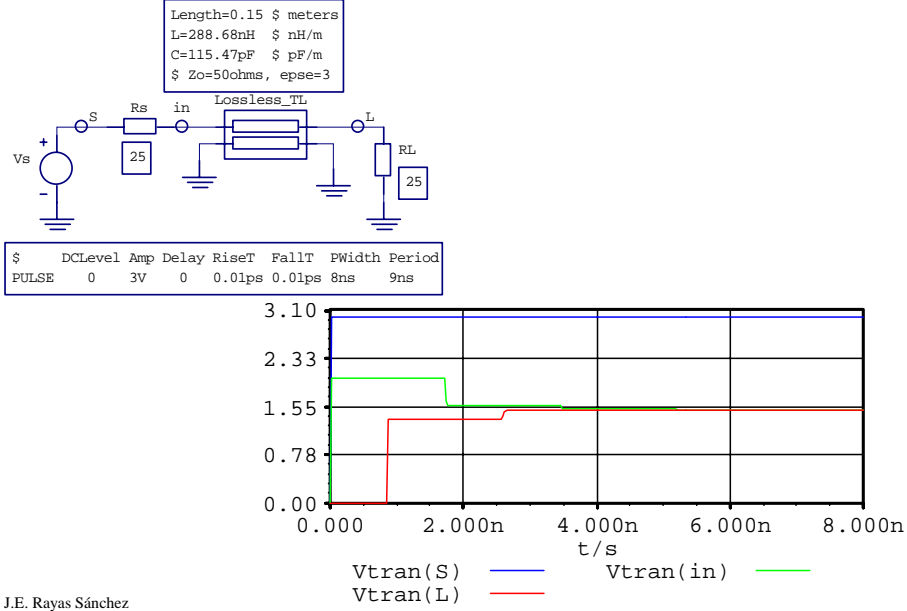
Example 4: $\Gamma_S < 0$ and $\Gamma_L < 0$



Dr. J.E. Rayas Sánchez

13


Lattice Diagrams for One TL Section

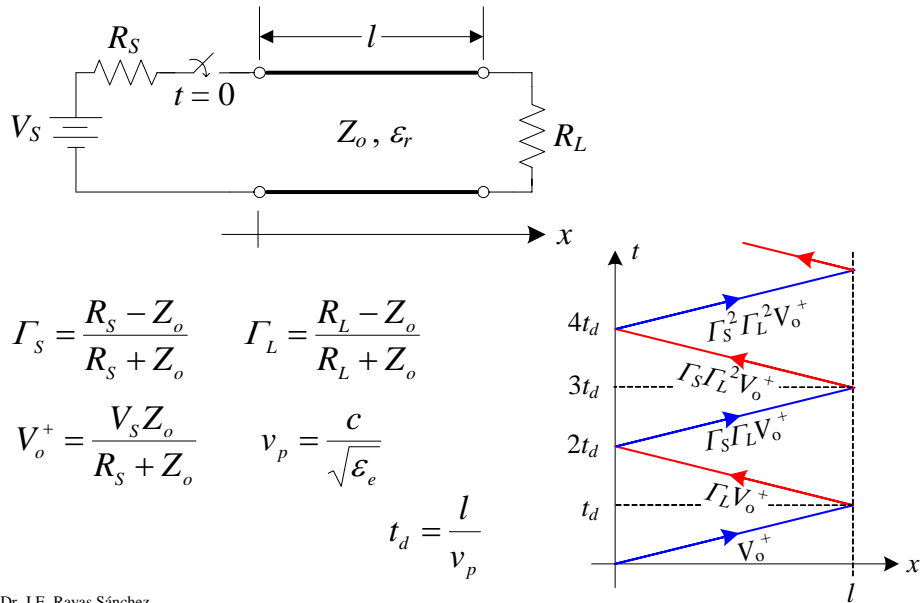

Dr. J.E. Rayas Sánchez

14

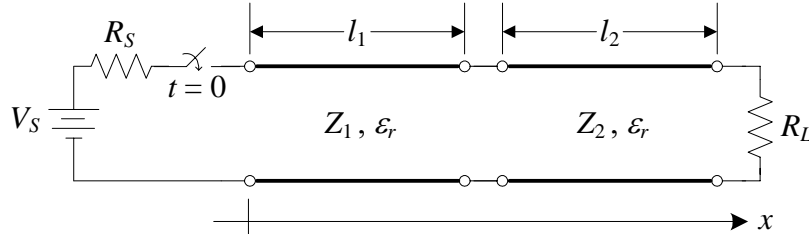Lattice Diagrams for Multiple TL Sections



$$\Gamma_S = \frac{R_S - Z_1}{R_S + Z_1} \quad \Gamma_L = \frac{R_L - Z_2}{R_L + Z_2} \quad \Gamma_P = \frac{Z_2 - Z_1}{Z_2 + Z_1} \quad \Gamma_N = \frac{Z_1 - Z_2}{Z_1 + Z_2} = -\Gamma_P$$

$$V_o^+ = \frac{V_S Z_1}{R_S + Z_1} \quad v_{p1} = \frac{c}{\sqrt{\epsilon_{e1}}} \quad v_{p2} = \frac{c}{\sqrt{\epsilon_{e2}}} \quad T_P = 1 + \Gamma_P$$


$$T_N = 1 + \Gamma_N$$

$$t_{d1} = \frac{l_1}{v_{p1}} \quad t_{d2} = \frac{l_2}{v_{p2}}$$

Dr. J.E. Rayas Sánchez

15

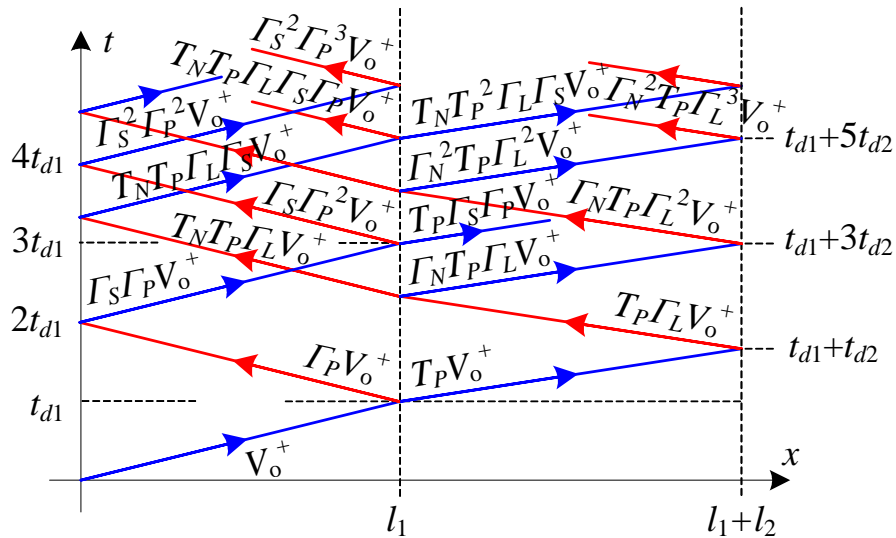
Lattice Diagrams for Multiple TL Sections (cont)



Dr. J.E. Rayas Sánchez

16

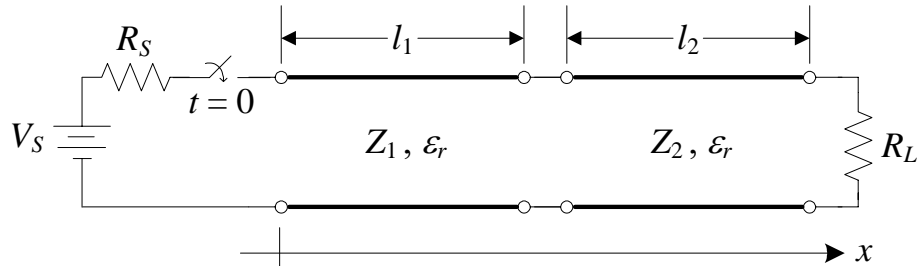Example of Transient Response in 2-TL Sections



$$R_S = 25\Omega; R_L = 150\Omega; V_S = 3V;$$

$$Z_1 = 50\Omega; Z_2 = 40\Omega;$$


$$\epsilon_{e1} = 3; \epsilon_{e2} = 3.5;$$

$$l_1 = 15\text{cm}; l_2 = 10\text{cm}$$

Dr. J.E. Rayas Sánchez

17

Example Simulated with AplaC

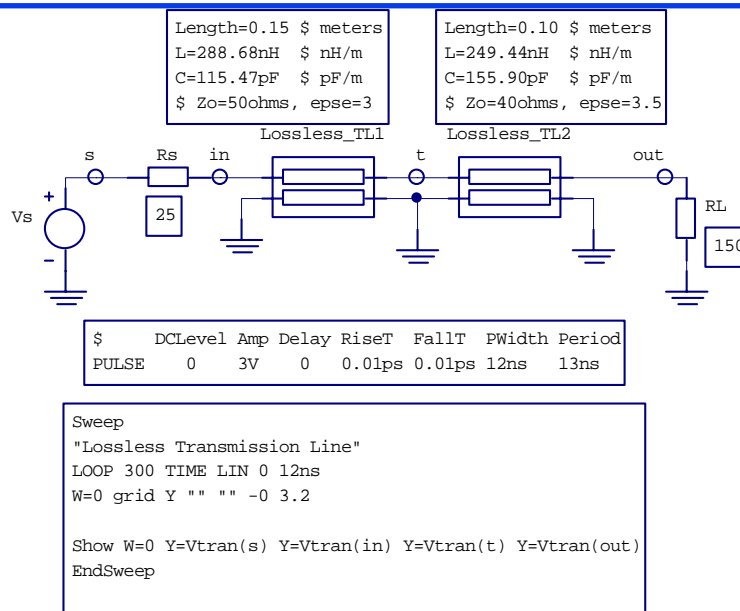

Dr. J.E. Rayas Sánchez

18

Example Simulated with Aplac (cont)

