

Time-Domain Analysis of Transmission Line Circuits

(Part 3)


Dr. José Ernesto Rayas Sánchez

1

Outline

- Bouncing diagrams for TLs with ideal excitation pulses and resistive terminations
- Example of a TL with resistive terminations and ideal pulse excitation
- Transients in TLs with capacitive loads
- Examples of TLs with capacitive load (over-driven and under-driven cases)
- Conclusions on TLs with capacitive loads


Lattice Diagrams for a DC Excitation

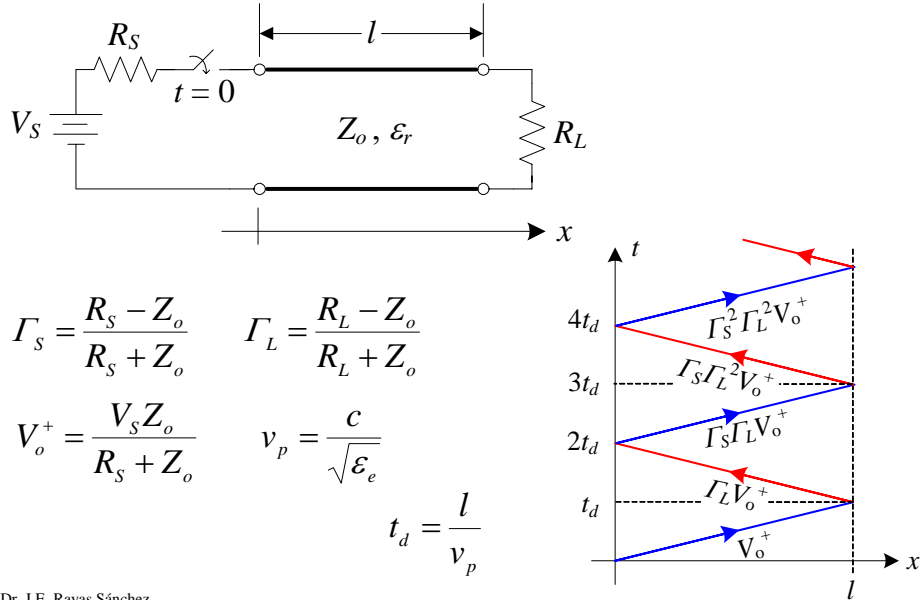

Dr. J.E. Rayas Sánchez

3

Lattice Diagrams for Pulses

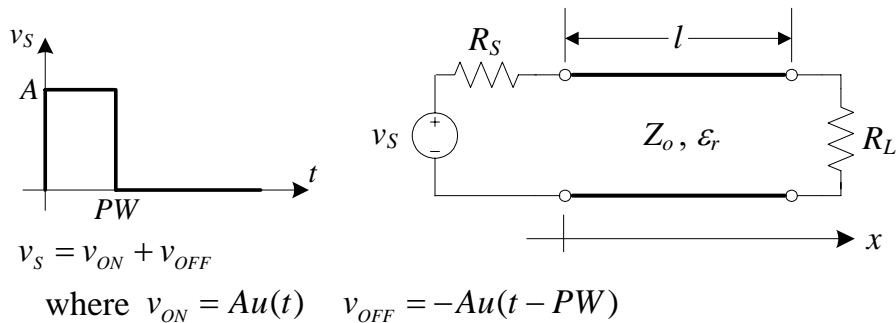


- We built two lattice diagrams, one for v_{ON} and one for v_{OFF}
- The lattice diagram for v_{OFF} is a negative and delayed version of that one for v_{ON}
- The resultant signals are obtained by adding both lattice diagrams

Dr. J.E. Rayas Sánchez


4

Lattice Diagrams for Pulses (cont)

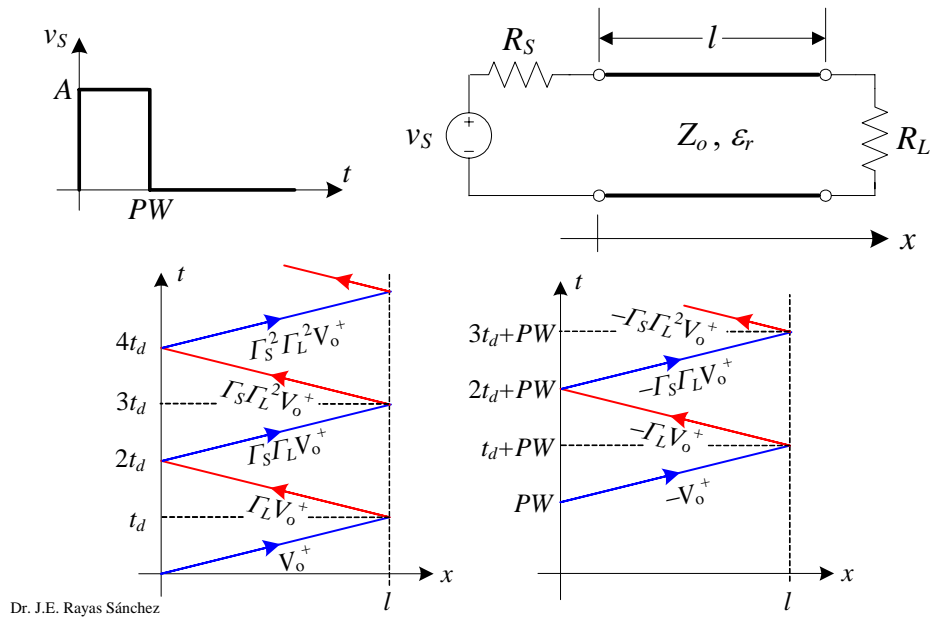

5

Example of TL with a Pulse Excitation

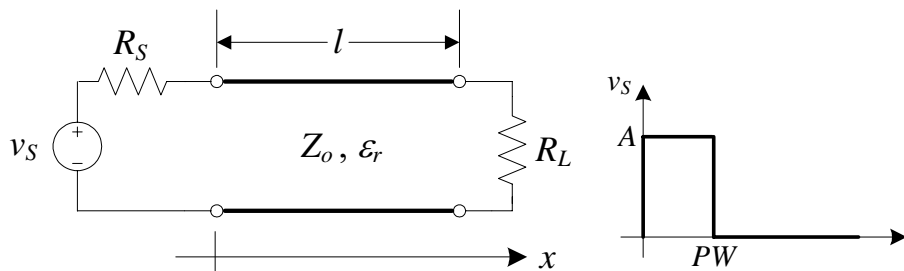


$$R_S = 75\Omega; R_L = 30\Omega; A = 3V; PW = 2.5\text{ns}$$

$$Z_0 = 50\Omega; \epsilon_r = 3; l = 17.321\text{cm}$$

Dr. J.E. Rayas Sánchez

6


Example Simulated with AplaC

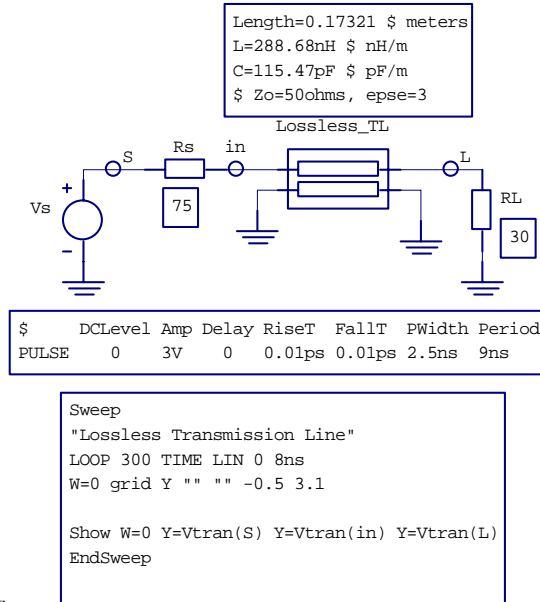

Dr. J.E. Rayas Sánchez

7


Example Simulated with AplaC

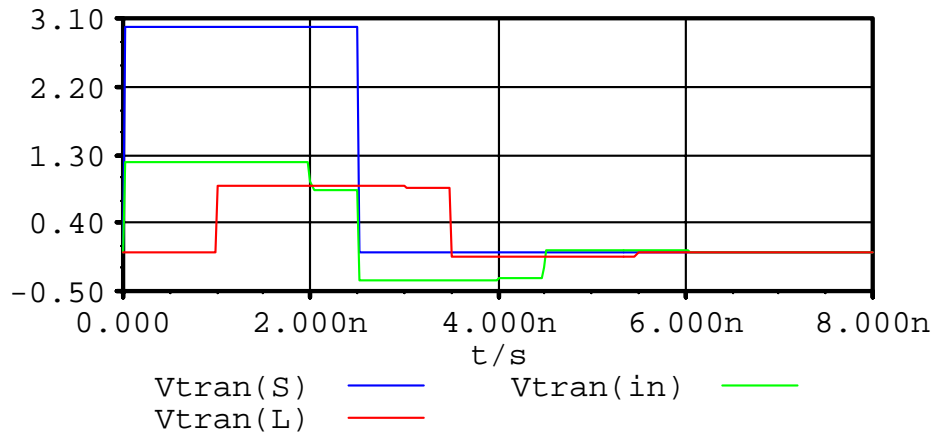

Dr. J.E. Rayas Sánchez

8

Transients in TLs with Capacitive Loads

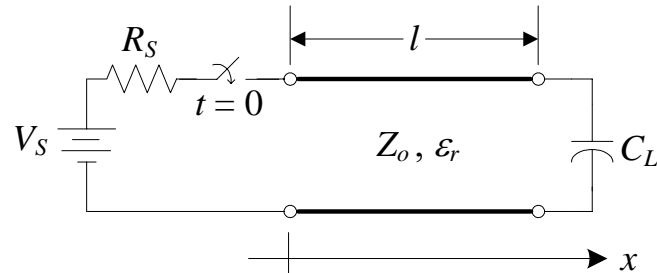


- C_L can be treated as a time-dependent impedance
- Initially, C_L is discharged, hence $\Gamma_L = -1$
- At the steady state, C_L is fully charged, hence $\Gamma_L = +1$
- At any other time, Γ_L can not be calculated

Dr. J.E. Rayas Sánchez

9

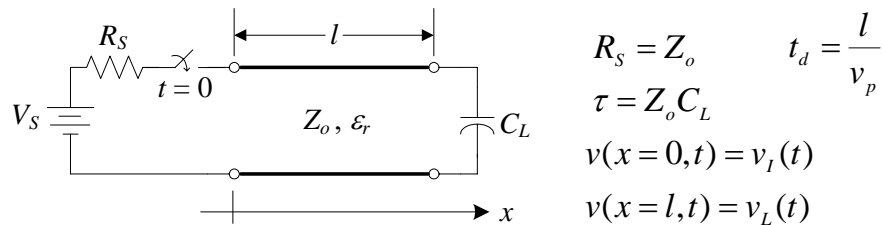Transients in TLs with Capacitive Load ($R_S = Z_o$)



$$R_S = Z_o \quad t_d = \frac{l}{v_p}$$

$$\tau = Z_o C_L$$

$$v(x=0, t) = v_I(t)$$

$$v(x=l, t) = v_L(t)$$

time	$v_I(t)$	$v_L(t)$
$0 \leq t \leq t_d$	$V_o^+ = \frac{V_S Z_o}{R_S + Z_o} = \frac{V_S}{2}$	0
$t_d \leq t < 2t_d$	$V_S / 2$	$V_S [1 - e^{-(t-t_d)/\tau}]$
$t = 2t_d$	0	$V_S [1 - e^{-t_d/\tau}]$
$t \geq 2t_d$	$V_S [1 - e^{-(t-2t_d)/\tau}]$	$V_S [1 - e^{-(t-t_d)/\tau}]$

Dr. J.E. Rayas Sánchez

10


Transients in TLs with Capacitive Load ($R_S = Z_0$)

time	$v_I(t)$	$v_L(t)$
$0 \leq t \leq t_d$		
$t_d \leq t < 2t_d$		
$t = 2t_d$	0	$V_S [1 - e^{-t_d/\tau}]$
$t \geq 2t_d$		

Dr. J.E. Rayas Sánchez

11

TL with Capacitive Load – Example 1

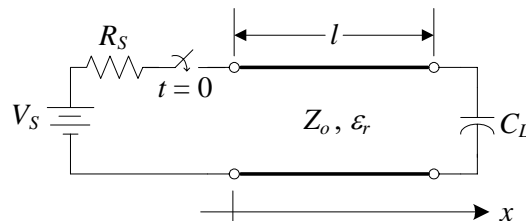

$$V_S = 3\text{V}; R_S = 50\Omega$$

$$Z_0 = 50\Omega; \epsilon_r = 3$$

$$l = 17.321\text{cm}$$


$$C_L = 30\text{pF}$$

$$V_o^+ = \frac{V_S}{2} = 1.5\text{V}$$

$$v_I(2t_d) = 0$$

$$2V_o^+ [1 - e^{-t_d/\tau}] = 1.46\text{V}$$

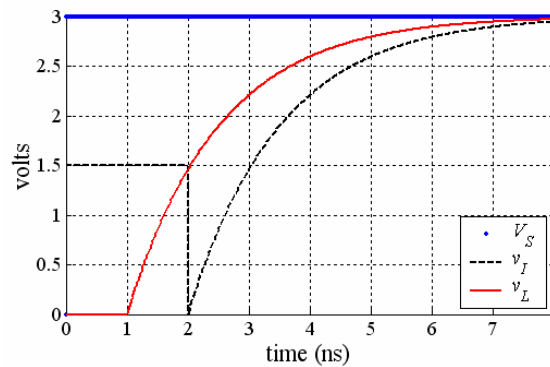
$$2V_o^+ [1 - e^{-2t_d/\tau}] = 2.21\text{V}$$



Dr. J.E. Rayas Sánchez

12


TL with Capacitive Load – Example 2

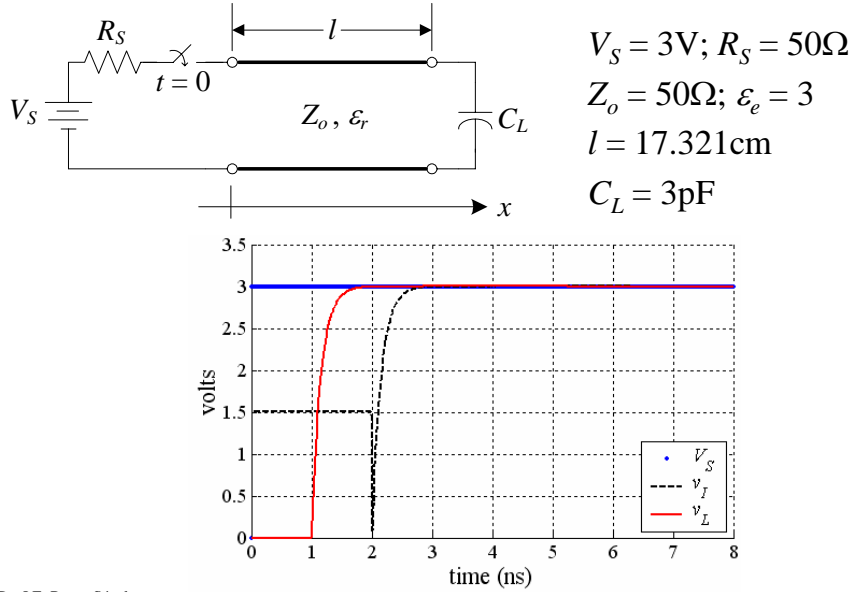

Dr. J.E. Rayas Sánchez

13

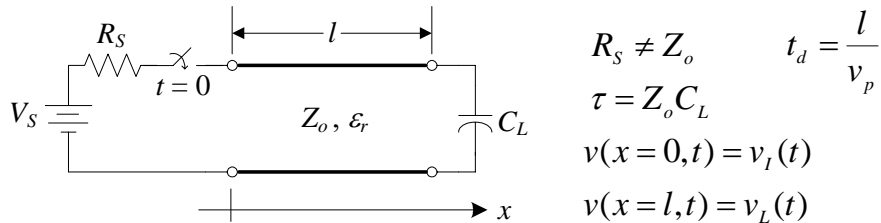TLs with Capacitive Load and Unmatched Source



time	$v_i(t)$	$v_L(t)$
$0 \leq t \leq t_d$	$V_o^+ = \frac{V_S Z_o}{R_S + Z_o}$	0
$t_d \leq t < 2t_d$	V_o^+	$2V_o^+ [1 - e^{-(t-t_d)/\tau}]$
$t = 2t_d$	$V_o^+ - V_o^+ - \Gamma_S V_o^+ = -\Gamma_S V_o^+$	$2V_o^+ [1 - e^{-t_d/\tau}]$
$2t_d \leq t < 3t_d$	$[2V_o^+ + 2\Gamma_S V_o^+] [1 - e^{-(t-2t_d)/\tau}] - \Gamma_S V_o^+$	$2V_o^+ [1 - e^{-(t-t_d)/\tau}]$
$t = 3t_d$	$[2V_o^+ + 2\Gamma_S V_o^+] [1 - e^{-t_d/\tau}] - \Gamma_S V_o^+$	$2V_o^+ [1 - e^{-2t_d/\tau}]$
$t > 3t_d$?	?

Dr. J.E. Rayas S

14

TLs with Capacitive Load and Unmatched Source

time	$v_i(t)$	$v_L(t)$
$0 \leq t \leq t_d$		
$t_d \leq t < 2t_d$		
$t = 2t_d$	$-\Gamma_S V_o^+$	$2V_o^+[1 - e^{-t_d/\tau}]$
$2t_d \leq t < 3t_d$		
$t = 3t_d$	$[2V_o^+ + 2\Gamma_S V_o^+][1 - e^{-t_d/\tau}] - \Gamma_S V_o^+$	$2V_o^+[1 - e^{-2t_d/\tau}]$
$t > 3t_d$?	?


Dr. J.E. Rayas Sánchez

15

TLs with Capacitive Load and Unmatched Source

$$v_i(2t_d) = -\Gamma_S V_o^+$$

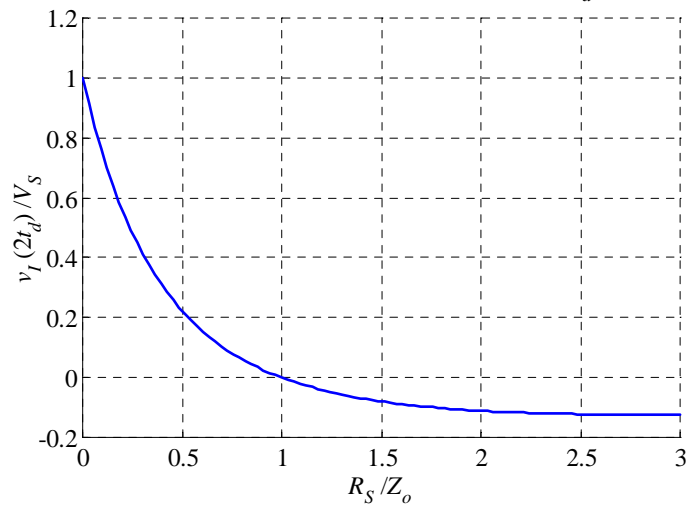
Normalized Input Voltage Amplitude at $2t_d$



Dr. J.E. Rayas Sánchez

16

TL with Capacitive Load – Example 3

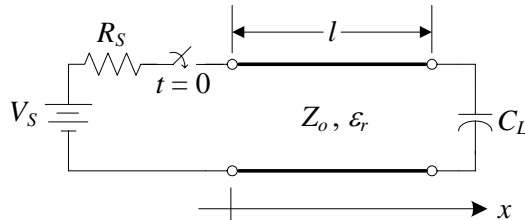

$V_S = 3\text{V}; R_S = 25\Omega$
 $Z_o = 50\Omega; \epsilon_r = 3$
 $l = 17.321\text{cm}$
 $C_L = 30\text{pF}$

$$V_o^+ = V_S Z_o / (R_S + Z_o) = 2\text{V}$$


$$\Gamma_S = \frac{R_S - Z_o}{R_S + Z_o} = -0.333$$

$$v_I(2t_d) = -\Gamma_S V_o^+ = 0.667\text{V}$$

$$2V_o^+ [1 - e^{-t_d/\tau}] = 1.946\text{V}$$

$$2V_o^+ [1 - e^{-2t_d/\tau}] = 2.946\text{V}$$

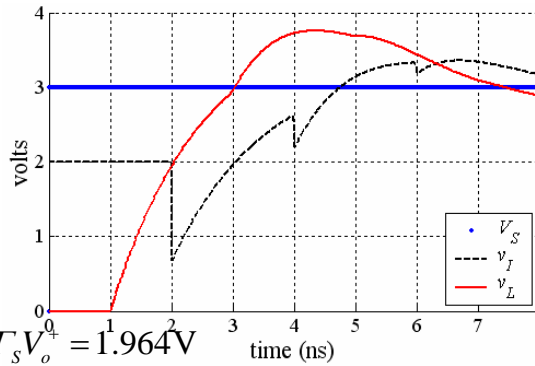
$$[2V_o^+ + 2\Gamma_S V_o^+] [1 - e^{-t_d/\tau}] - \Gamma_S V_o^+ = 1.964\text{V}$$




Dr. J.E. Rayas Sánchez

17

TL with Capacitive Load – Example 3b

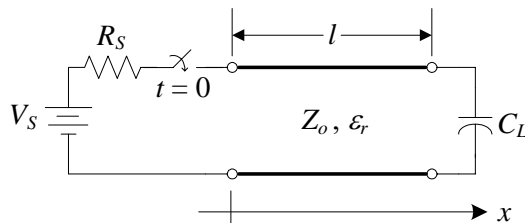

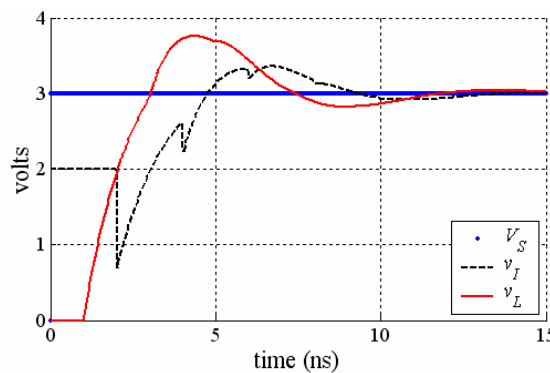
$V_S = 3\text{V}; R_S = 25\Omega$
 $Z_o = 50\Omega; \epsilon_r = 3$
 $l = 17.321\text{cm}$
 $C_L = 30\text{pF}$



Dr. J.E. Rayas Sánchez

18

TL with Capacitive Load – Example 4

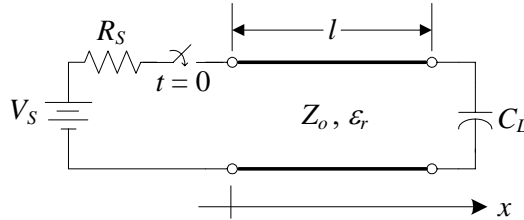

$$V_S = 3\text{V}; R_S = 25\Omega$$

$$Z_o = 50\Omega; \epsilon_r = 3$$


$$l = 17.321\text{cm}$$

$$C_L = 3\text{pF}$$

$$2V_o^+[1 - e^{-\infty/\tau}] = 2V_o^+ = 4\text{V}$$

$$[2V_o^+ + 2\Gamma_S V_o^+][1 - e^{-\infty/\tau}] - \Gamma_S V_o^+ =$$

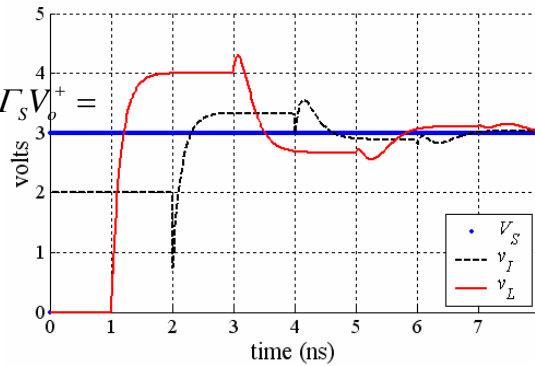
$$2V_o^+ + \Gamma_S V_o^+ = 3.333\text{V}$$



Dr. J.E. Rayas Sánchez

19

TL with Capacitive Load – Example 5

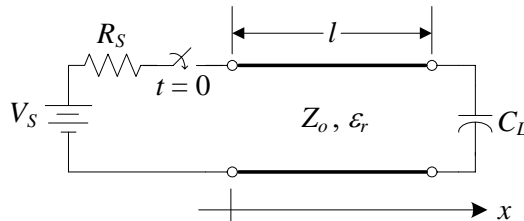

$$V_S = 3\text{V}; R_S = 10\Omega$$

$$Z_o = 50\Omega; \epsilon_r = 3$$

$$l = 17.321\text{cm}$$

$$C_L = 3\text{pF}$$


$$V_o^+ = V_S Z_o / (R_S + Z_o) = 2.5\text{V}$$

$$\Gamma_S = \frac{R_S - Z_o}{R_S + Z_o} = -0.6667$$

$$v_I(2t_d) = -\Gamma_S V_o^+ = 1.667\text{V}$$

$$2V_o^+[1 - e^{-\infty/\tau}] = 2V_o^+ = 5\text{V}$$

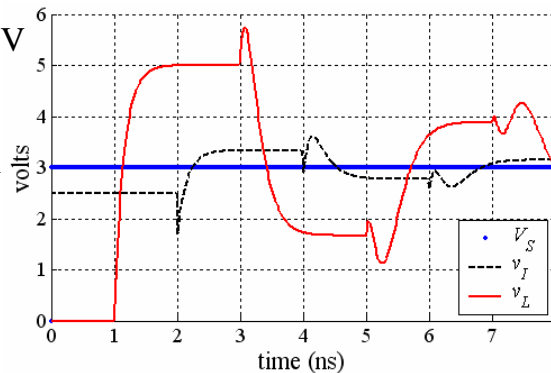
$$2V_o^+ + \Gamma_S V_o^+ = 3.331\text{V}$$



Dr. J.E. Rayas Sánchez


20

TL with Capacitive Load – Example 5b

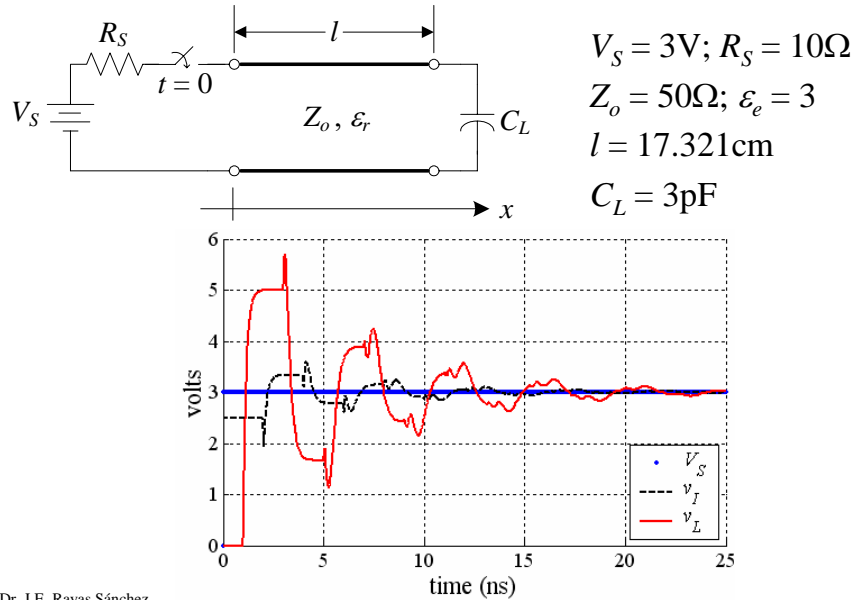


21

TL with Capacitive Load – Example 6

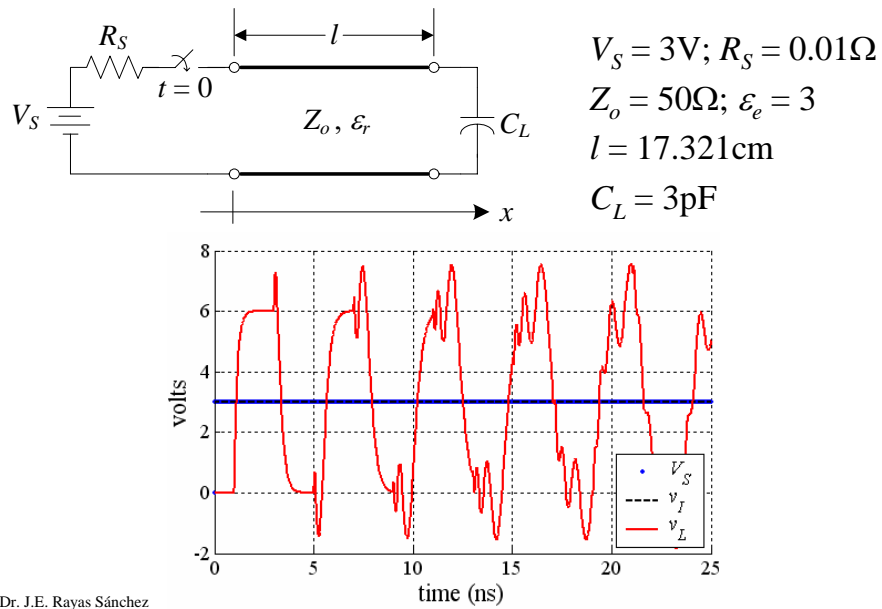


22

TL with Capacitive Load – Example 6b

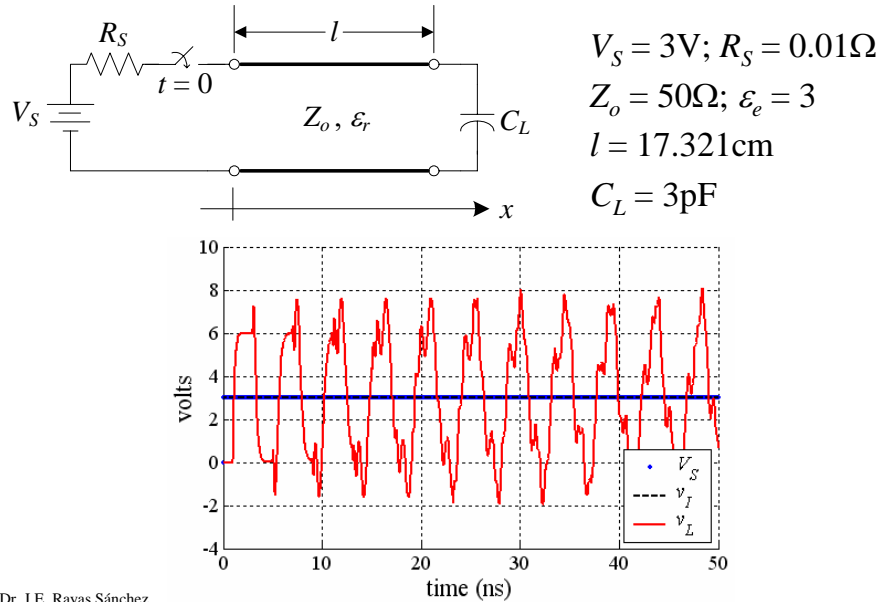



23

TL with Capacitive Load – Example 6c

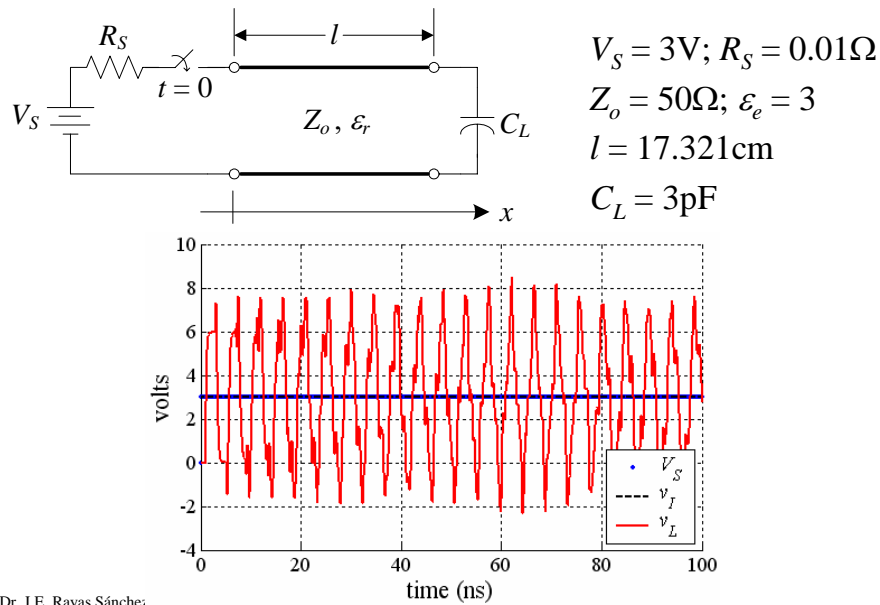

24



TL with Capacitive Load – Example 6d

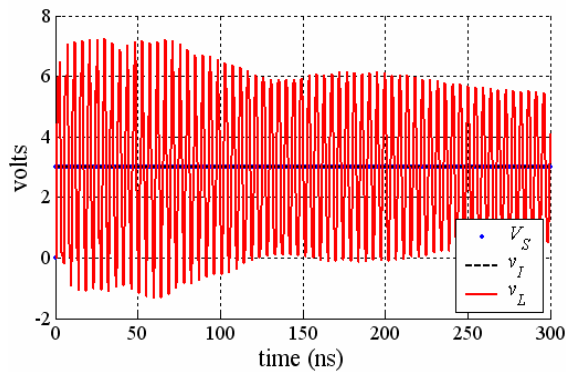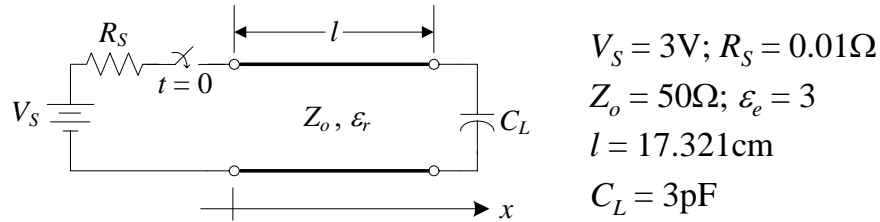

Dr. J.E. Rayas Sánchez

25


TL with Capacitive Load – Example 6e

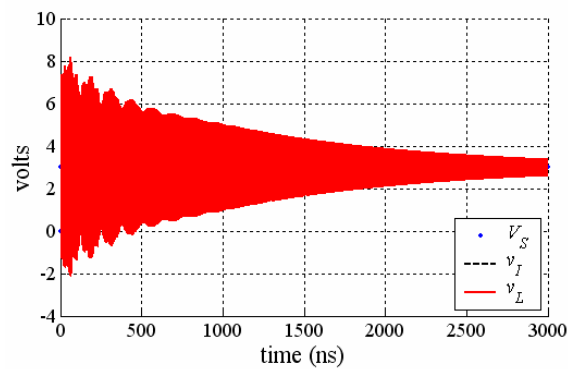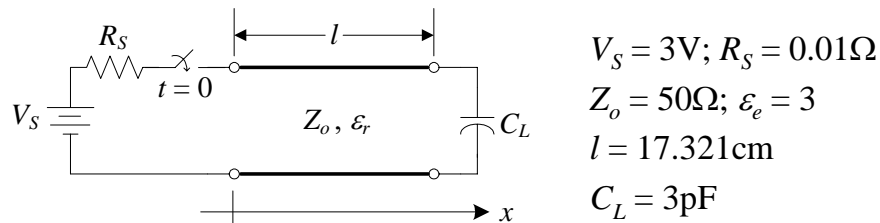


Dr. J.E. Rayas Sánchez

26

TL with Capacitive Load – Example 7

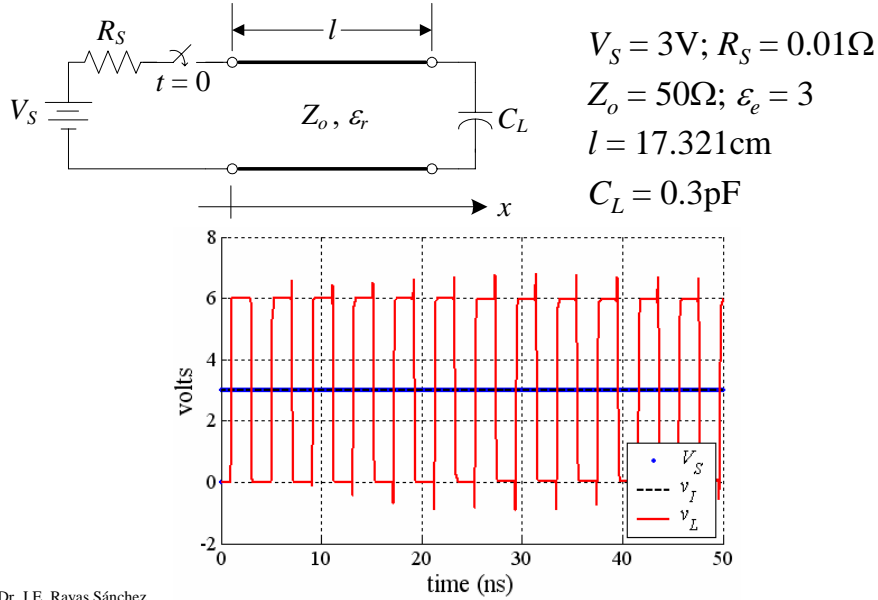

TL with Capacitive Load – Example 8

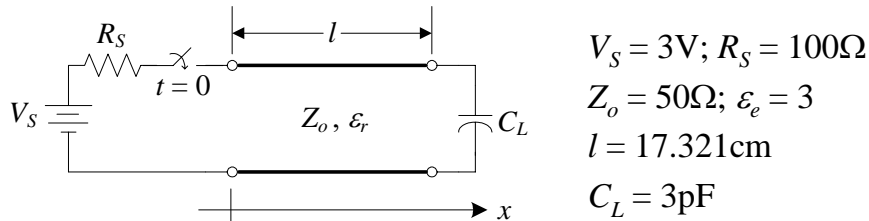


$$V_o^+ = V_S Z_o / (R_S + Z_o) = 1\text{V}$$

$$\Gamma_S = \frac{R_S - Z_o}{R_S + Z_o} = 0.333$$


$$v_I(2t_d) = -\Gamma_S V_o^+ = -0.333\text{V}$$

$$2V_o^+ [1 - e^{-\infty/\tau}] = 2V_o^+ = 2\text{V}$$
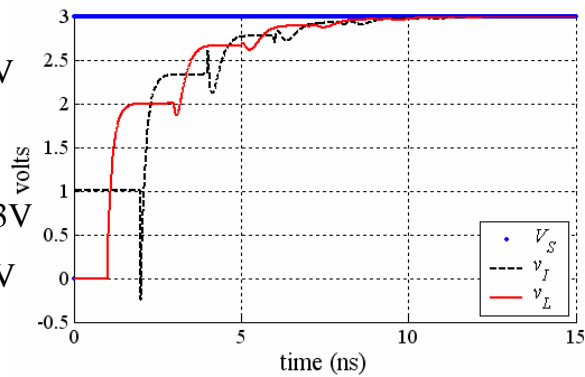
$$2V_o^+ + \Gamma_S V_o^+ = 2.333\text{V}$$




TL with Capacitive Load – Example 9

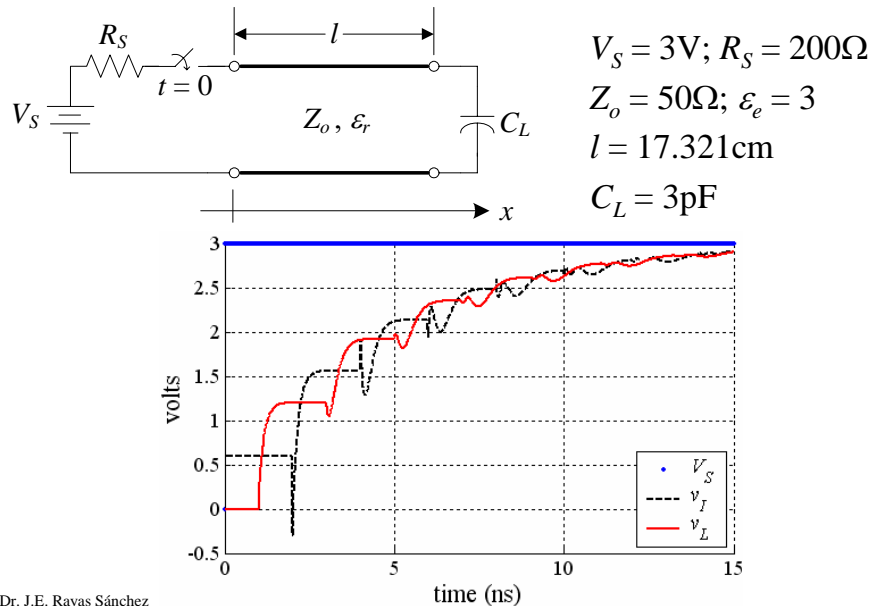

29

Transients in TLs with Capacitive Loads

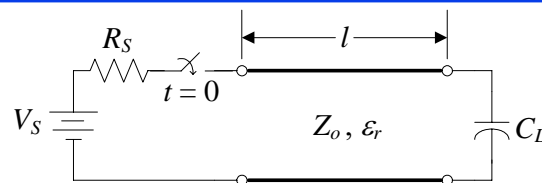

SOME CONCLUSIONS:

- Lattice diagrams can not be directly applied
- If $\Gamma_S = 0$ analytical solutions are easy, otherwise the problem becomes too complex for $t > 3t_d$ (simulation required)
- If $\Gamma_S > 0$, the line behaves as an under-driven line
- If $\Gamma_S < 0$, there will be overshooting voltages at the load (over-driven line)
- If $\Gamma_S \ll 0$, there will be significant oscillations at the load

Dr. J.E. Rayas Sánchez

30